

**CS/ECE 252: INTRODUCTION TO COMPUTER ENGINEERING  
COMPUTER SCIENCES DEPARTMENT  
UNIVERSITY OF WISCONSIN-MADISON**

Prof. David A. Wood  
TAs Spyros Blanas, Priyananda Shenoy, Shengnan Wang  
Midterm Examination 2  
In Class (50 minutes)  
Monday, March 10, 2008  
Weight: 15%

**CLOSED BOOK, NOTE, CALCULATOR, PHONE, & COMPUTER.**

The exam is two-sided and has 12 pages, including two blank pages at the end.

Plan your time carefully, since some problems are longer than others.

NAME: \_\_\_\_\_

SECTION: \_\_\_\_\_

ID# \_\_\_\_\_

**"Blue Version"**

<b>Problem Number</b>	<b>Maximum Points</b>	<b>Actual Points</b>	<b>Grader</b>
1	10		SB
2	9		SB
3	12		SW
4	8		SW
5	11		SB
6	15		SW
7	15		SB/PS
8	20		PS
Total	100		

**Problem 1 (10 points)**

Write the Boolean expression corresponding to the following truth table. You need not simplify the expression.

Inputs			Output
A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Z = (A \text{ AND } B) \text{ OR } (B \text{ AND NOT}(C))$$

**Problem 2 (9 points)**

Suppose a 32-bit instruction takes the following format:

OPCODE	DR	SR1	SR2	UNUSED
--------	----	-----	-----	--------

If there are 313 opcodes and 64 registers:

- a) What is the minimum number of bits required to represent the OPCODE?

**9**

- b) What is the minimum number of bits required to represent the destination register DR, and source registers SR1 and SR2? (Give the total number of bits.)


**18**

- c) What is the maximum number of UNUSED bits in the instruction encoding?

**$32 - 18 - 9 = 5$**

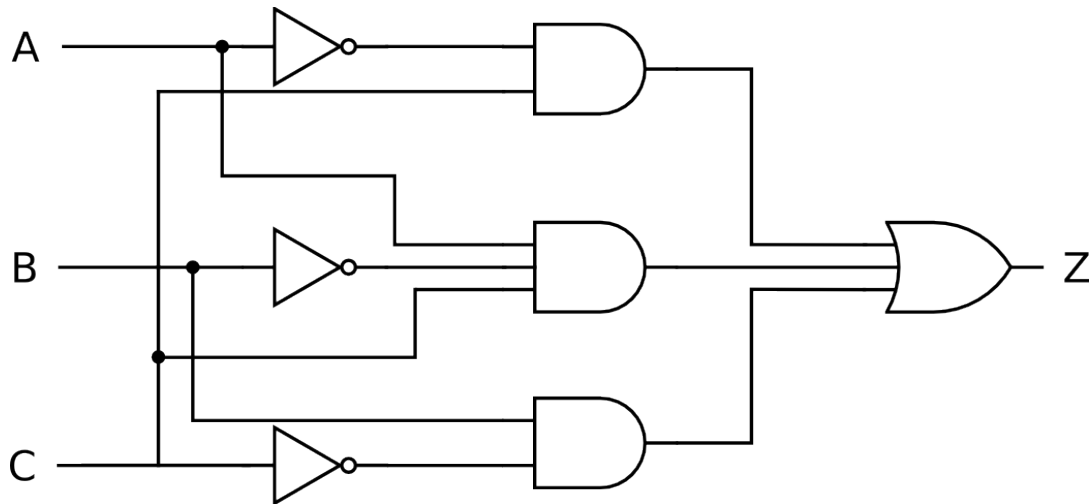**Problem 3 (12 points)**


The figure below shows a combinational logic circuit. Complete the truth table corresponding to this circuit.



Inputs			Output
A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

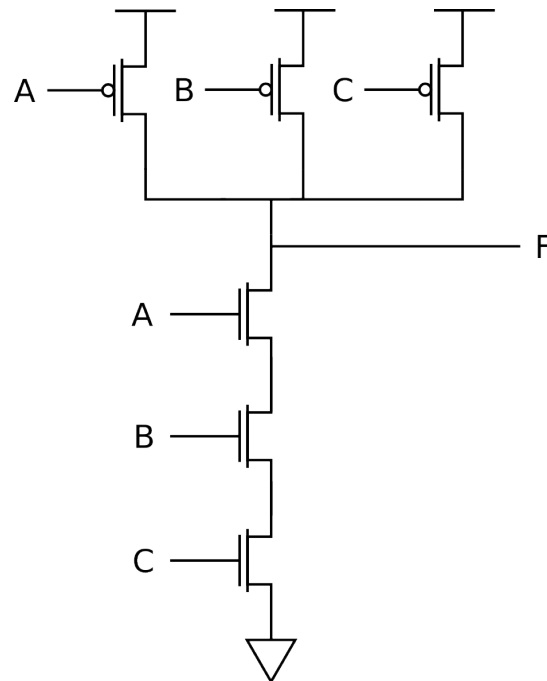**Problem 4 (8 points)**


Fill in the truth table for the following transistor level circuit. Note that two wires with the same name are assumed to be connected to each other.



Inputs			Output
A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

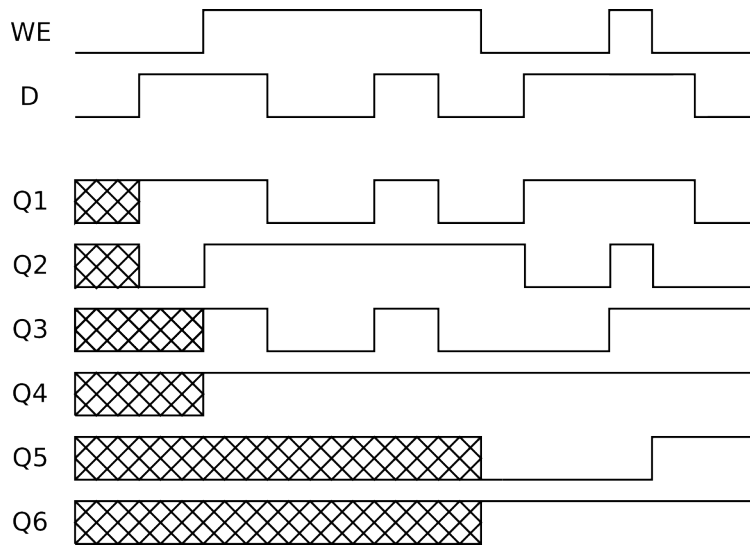**Problem 5 (11 points)**

In the following timing diagram WE and D represent the inputs to a *gated D latch*. Which one of the outputs corresponds to the output of the latch? Circle the correct answer.




- a. Q1
- b. Q2
- c. **Q3**
- d. Q4
- e. Q5
- f. Q6

**Q3**

**Problem 6 (15 points)**

A vending machine delivers a bottle of water after \$1.5 dollars (150 cents) are deposited. It has a single coin slot which accepts only half dollars (50 cents) or \$1 (100 cents). No other types of coins are accepted. The vending machine does not return back any change.

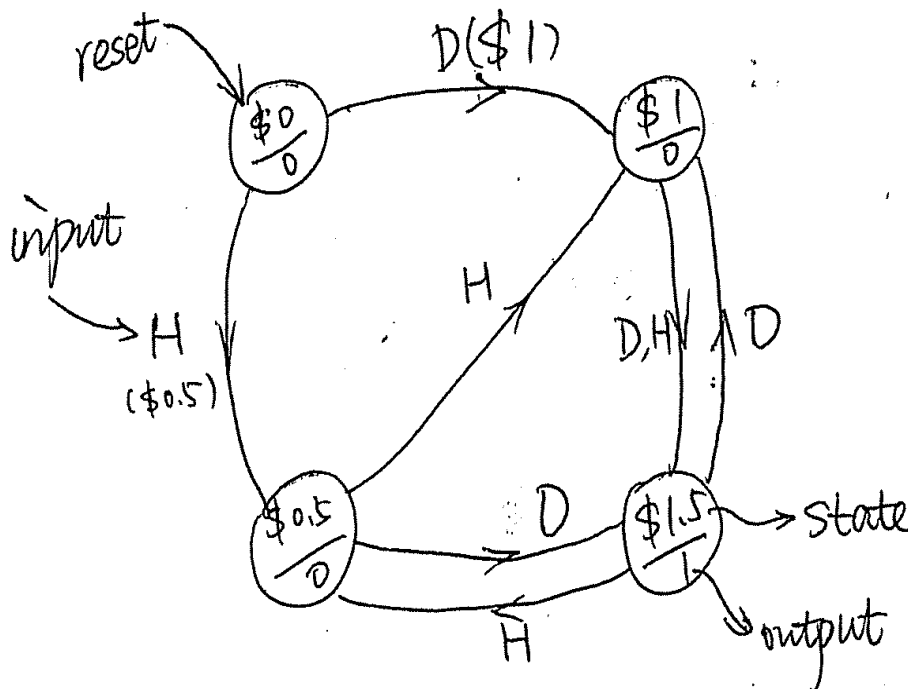- I. Draw the finite state machine diagram for the vending machine. The machine takes one input every clock cycle which can be H(\$0.5), D(\$1) or reset. The machine outputs a 1 when it opens to deliver a bottle of water, otherwise it outputs a 0.



- II. How many flip-flops (storage elements) will be needed to implement this finite state machine designed in your answer to part I?

2 flip-flops.



**Problem 7 (15 points)**


Use the following table to indicate which registers in our von Neumann machine change during different phases of execution. Circle A, L or J if this register is modified during this phase of an add (ADD), load (LDR) or jump (JMP) instruction respectively. Circle all appropriate letters if a register is modified when executing more than one type of instructions.

Instruction	MAR changes	MDR changes	PC changes	IR changes	RegFile is written
Fetch	A L J	A L J	A L J	A L J	
Decode					
Evaluate Address					
Fetch Operands	L	L			
Execute					
Store Result			J		A L

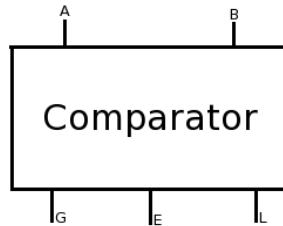
**Problem 8 (20 points)**

A *1-bit comparator* is a unit which takes two 1-bit inputs A and B and gives three 1-bit outputs G,E,L such that:

- G is 1 if A is greater than B, 0 otherwise
- E is 1 if A is equal to B, 0 otherwise
- L is 1 if A is lesser than B, 0 otherwise



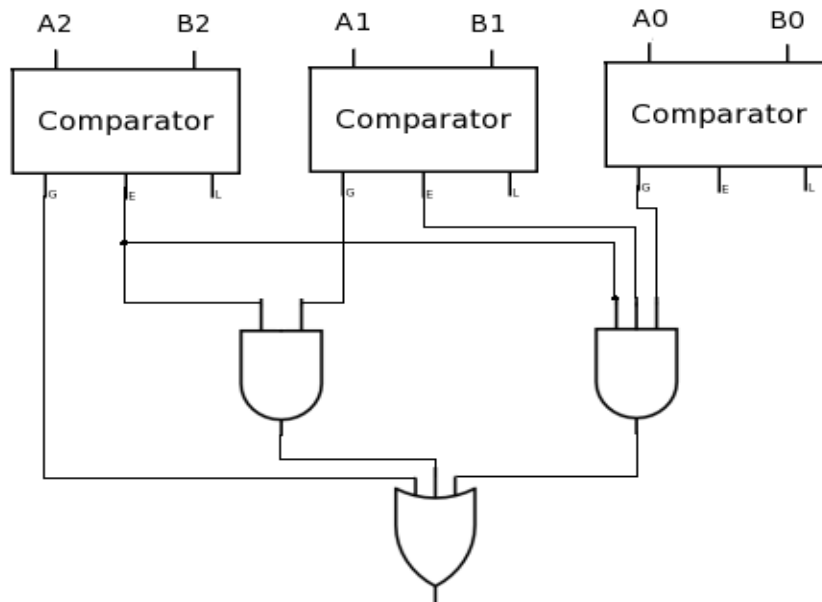Using any number of such 1-bit comparator as a building block, design a unit which takes two 3-bit numbers A and B, in **unsigned integer** representation and gives an output of 1 if **A is greater than B**, 0 otherwise.



$$A > B \Rightarrow (A_2 > B_2) \text{ or } (A_2 = B_2 \text{ and } A_1 > B_1) \text{ or } (A_2 = B_2 \text{ and } A_1 = B_1 \text{ and } A_0 > B_0)$$

**Scratch Sheet 1 (in case you need additional space for some of your answers)**

**Scratch Sheet 2 (in case you need additional space for some of your answers)**