

# Discussion Session 3

CS/ECE 552

Ramkumar Ravi

13 Feb 2012

# GENERAL HW DELIVERABLES


- ELECTRONIC
  - All verilog files including testbench
  - Vcheck.out files
  - Anything else that is mentioned in the assignment
- MANUAL
  - Annotated waveforms
  - Schematic of the design
  - Anything else that is mentioned in the assignment

# Problem 1 – Barrel shifter

- Barrel shifters are often utilized by embedded digital signal processors and general-purpose processors to manipulate data
- In this table, the bit vector for A is denoted as  $a_7a_6a_5a_4a_3a_2a_1a_0$  and the shift/rotate amount is 3 bits. As illustrated in this table

Operation	Y
3-bit shift right logical	0 0 0 $a_7 a_6 a_5 a_4 a_3$
<b>3-bit shift right arithmetic</b>	$a_7 a_7 a_7 a_7 a_6 a_5 a_4 a_3$
<b>3-bit rotate right</b>	$a_2 a_1 a_0 a_7 a_6 a_5 a_4 a_3$
<b>3-bit shift left logical</b>	$a_4 a_3 a_2 a_1 a_0 0 0 0$
3-bit shift left arithmetic	$a_7 a_3 a_2 a_1 a_0 0 0 0$
<b>3-bit rotate left</b>	$a_4 a_3 a_2 a_1 a_0 a_7 a_6 a_5$
 
# 8-bit Right Rotate example implementation



# Points to note

- EXPLORE – Design can be simplified by using a combination of 2:1 MUX and the 4:1 MUX you designed in the last HW (<= 50 lines of code)
- Hint: What do you think about this code below ?

```
wire [15:0] S0;
```

```
wire [15:0] L0;
```

```
// level 1
```

```
mux2_1 inst [13:0] (.InA(In[13:0]), .InB(In[15:2]), .Out(lev0[14:1]), .S(Op[1]));
```

```
mux4_1 inst1 (.out(lev0[0]), .InA(In[15]), .InB(1'd0), .InC(In[1]), .InD(In[1]), .S(Op));
```

```
mux4_1 inst2 (.out(lev0[15]), .InA(In[14]), .InB(In[14]), .InC(In[0]), .InD(In[15]), .S(Op));
```

```
mux2_1 inst [15:0] (.InA(In), .InB(L0), .S(cnt[0]), .out(out));
```

```
/levels 2, 4 and 8
```

```
??
```

# From previous slide – All 1 bit operations

- For rotate left (Op = 00)
  - lev0 [14:1] = In [13:0]
  - lev0 [0] = In [15]
  - lev0 [15] = In [14]
- For shift left (Op = 01)
  - lev0 [14:1] = In [13:0]
  - lev0 [0] = 0
  - lev0 [15] = In [14]
- For rotate right (Op = 10)
  - lev0 [14:1] = In [15:2]
  - lev0 [0] = In [1]
  - lev0 [15] = In [0]
- For shift right arithmetic (Op = 11)
  - lev0 [14:1] = In [15:2]
  - lev0 [0] = In [1]
  - lev0 [15] = In [15]

# WHAT TO SUBMIT

- ELECTRONIC
  - Verilog code of all modules and testbench
- MANUAL
  - Neat Schematic of the design (hand-drawn is fine)
  - Annotated waveforms
  - Explain why you chose a set of inputs for your simulation (in 3 or 4 sentences)

# Problem 2 - ALU

- Carry look ahead adder example (works on carry-generate and carry-propagate)

$$G(A, B) = A \cdot B$$

$$P'(A, B) = A \oplus B$$

$$C_{i+1} = G_i + (P_i \cdot C_i)$$

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + P_1 \cdot C_1$$

$$C_3 = G_2 + P_2 \cdot C_2$$


$$C_4 = G_3 + P_3 \cdot C_3$$

$$C_1 = G_0 + P_0 \cdot C_0$$

$$C_2 = G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1$$

$$C_3 = G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + C_0 \cdot P_0 \cdot P_1 \cdot P_2$$
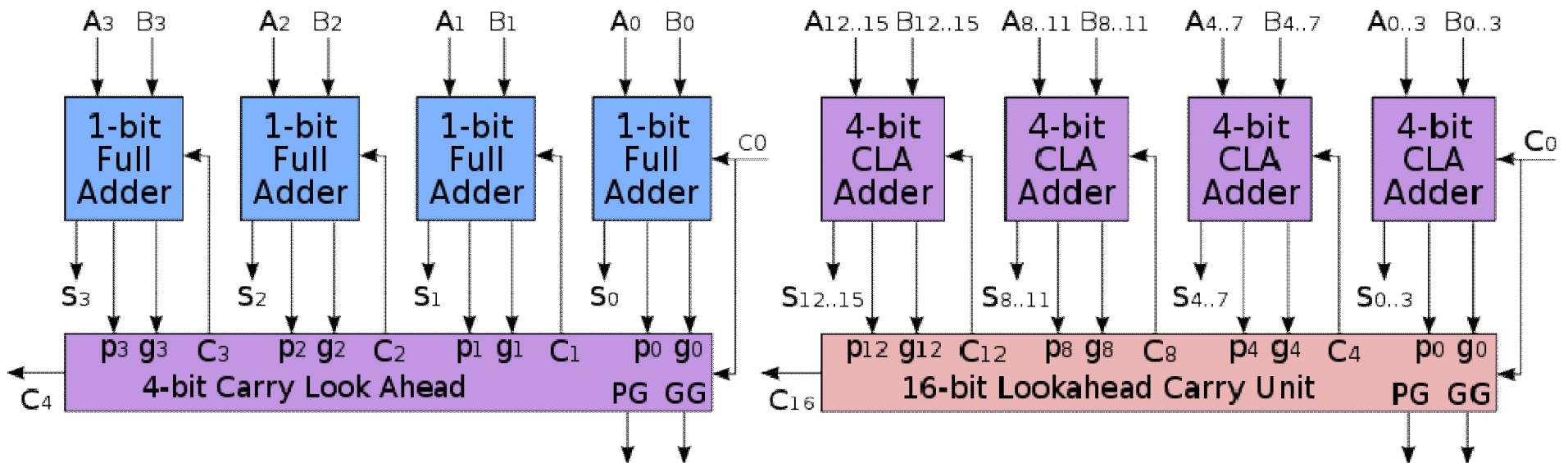
$$C_4 = G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3 + C_0 \cdot P_0 \cdot P_1 \cdot P_2 \cdot P_3$$





# 2's complement representation

- Represent positive 2's complement numbers as simple binary
- Represent negative 2's complement as a binary that when added to a positive number of same magnitude equals 0

Signed	Unsigned	2's complement
3	3	0000 0011
2	2	0000 0010
1	1	0000 0001
0	0	0000 0000
-1	255	1111 1111
-2	254	1111 1110
-3	253	1111 1101

# 2's complement examples

- Addition

$$5 + (-3)$$

$$0000\ 0101 = +5$$

$$+ 1111\ 1101 = -3$$

-----

$$0000\ 0010 = +2$$

## SIGN EXTENSION

Signed -1 in 16-bits is 1111 1111 1111 1111

Signed +1 in 16-bits is 0000 0000 0000 0001

- Subtraction

$$7 - 12 = 7 + (-12)$$

$$0000\ 0111 = +7$$

$$+ 1111\ 0100 = -12$$

-----

$$1111\ 1011 = -5$$

# Other things to note

- Use shifter designed in problem 1
- Shift amount is represented by lower 4 bits of input B  
Input to be shifted is A  
 $a1 = \text{inv}A ? (\sim \text{In}A) : \text{In}A;$   
 $b1 = \text{inv}B ? (\sim \text{In}B) : \text{In}B;$
- Take care of OFL -> Keep track of sign bit and 'cout' bit
- Underflow is don't care

# WHAT TO SUBMIT

- ELECTRONIC
  - Verilog code of all modules and testbench
- MANUAL
  - Neat Schematic of the design (hand-drawn is fine)
  - Annotated waveforms
  - Explain why you chose a set of inputs for your simulation (in 3 or 4 sentences)

# Problem 3 and 4

- Translate to MIPS
- For problem 4, after translating to MIPS, you might have a structure similar to this:

XXX

YYY

Loop: PPP

    QQQ

    RRR

Total = 2 + 3\*(number of times loop is executed)

- Memory references for problem 4?? -> Think 😊

# Problem 5

- Total number of instructions is given
- Also mentioned is the % distribution of each instruction along with the number of cycles an instruction takes to execute
  - Overall CPI =  $(40 \times 2 + \dots + \dots + \dots) / \text{total}$
  - Old number of multiplies = 8% of 200 =  $x$
  - 50% of the old number is replaced by shift-add that takes 3.5 cycles each
  - New number of multiplies =  $x \times 50\% = y$
  - Additional ALU instructions =  $x \times 50\% \times (\text{length})$
  - Calculate new total number of instructions and the new CPI

# Problem 6

- Find the maximum IPC

- $IPS = IPC * \text{clock speed}$

- Average CPI

- $$= (2A+B+C+D+E)/(2+1+1+1+1)$$

- Find results for both P1 and P2

- $$\text{Speedup (P2) / Speedup (P1)} = \text{Avg. time per instruction on P1} / \text{Avg. time per instruction on P2}$$

- For P1, average CPI / 4GHz and for P2, average CPI / 6GHz

- Find out that frequency where ratio above is 1

# Problem 7

- $\text{CPI} = (\text{CPU time} \times \text{clock rate}) / \text{No. instr.}$   
CPU time and clock rate is given  
Number of instructions =  $0.85 * (\text{Data in problem 1.12})$
- $\text{Clock rate ratio} = \text{New clock} / \text{old clock}$   
 $(\text{CPI})_{4\text{GHz}} / (\text{CPI})_{x\text{GHz}}$  for a and b  
Why do you think they are dissimilar ? CPU time ?
- $\text{New execution time} / \text{old execution time}$   
 $\text{CPU time reduction} = [1 - (\text{New exec time} / \text{old exec time})] * 100 = ?? \%$