

# Discussion Session 6


CS/ECE 552  
Ramkumar Ravi  
05 Mar 2012

# Introduction


- Rules for HW are up-> Please follow instructions
  - HW3 is due on **03/07**
- EXPLORING FIFO
- MIDTERM REVIEW
  - **03/06, 7:15 to 9:15 PM, Location: CHEM B371**
- WARNING: Codes here are for demonstration purposes only; Not tested and might have bugs as well
 
# Problem 1

- Expect just 3-4 lines of your opinion for each instruction
  - As an example, consider the “Bit Equal” instruction
  - This instruction does a bit-for-bit compare between two registers. For each bit  $i$ , if bit  $i$  of  $\$rs$  is equal otherwise set bit  $i$  of  $\$rd$  to zero.




A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1

 

- Bit equal is hence equivalent to an XNOR instruction. So to incorporate the XNOR instruction in your data path, what changes/modifications will you need to

# Problem 3 - Register file design

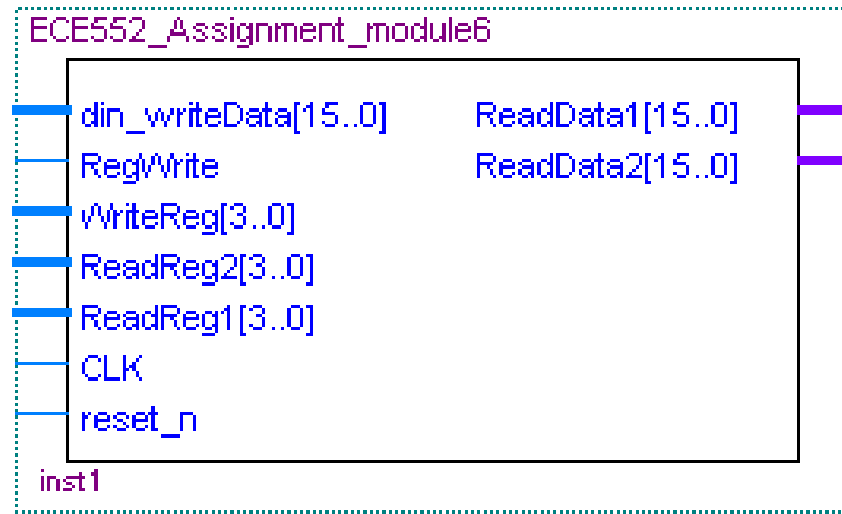


1. `din_writeData [15:0]` Á `writedata [15:0]`
2. `RegWrite` Á `write`
3. `WriteReg [3..0]` Á `writeregsel [2:0]`
4. `ReadReg2[3..0]` Á `read2regsel [2:0]`
5. `ReadReg1 [3..0]` Á `read1regsel [2:0]`
6. `CLK` Á `clk`
7. `Reset_n` Á `rst`
8. `ReadData1 [15..0]` Á `read1data [15:0]`
9. `ReadData2 [15:0]` Á `read2data [15:0]`

# Register File Interface

```
parameter WIDTH = 16;  
input clk, rst;  
input [2:0] read1regsel;  
input [2:0] read2regsel;  
input [2:0] writeregsel;  
input [WIDTH-1:0] writedata;  
input write;  
output [WIDTH-1:0] read1data;  
output [WIDTH-1:0] read2data;  
output err;
```

# Register File design

- Lets start with a 3-8 Decoder

 

- If  $X_0X_1X_2 = 3'b000$ ; select  $z_0$  and so on..

**wire** [7:0] we, awe;

**decode3\_8** decoder (.sel(writeregsel), .Out(we));

**and2** inst[7:0] (.in1(we), .in2({8{write}}), .out(awe));

# Register file – The registers

```
wire [WIDTH-1:0] q0, q1, q2, q3, q4, q5, q6, q7;
```

```
register regs7 (.q(q7), .d(writedata), .clk(clk), .rst(rst), .we(awe[7]));
```

```
register regs6 (.q(q6), .d(writedata), .clk(clk), .rst(rst), .we(awe[6]));
```

and so on..

Now wh

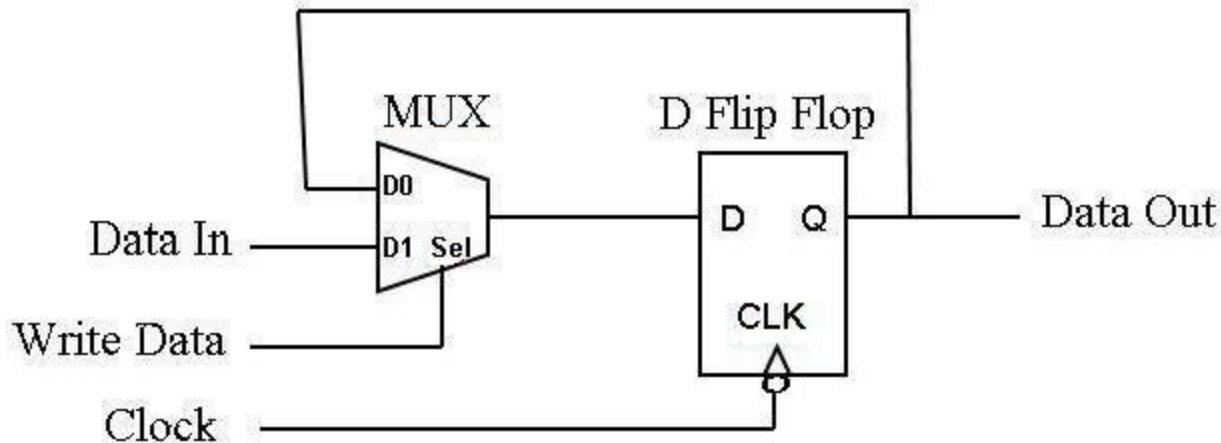


figure below)

# REGISTER module

```
module register (input [15:0] d, input clk, rst, we, output [15:0] q);
```

```
wire [15:0] e_In;
```

```
mux2_1 mux[15:0] (.InA (q), .InB(d), .S({16{we}}), .Out(e_In));
```


```
dff inst[15:0] (.q(q), .d(e_In), .clk({16{clk}}), .rst({16{rst}}));
```

2:1 MUX -> If S is 1'b1; InB is selected else

16 copies of the DFF module

NOTE:

You might also need a 8:1 MUX for

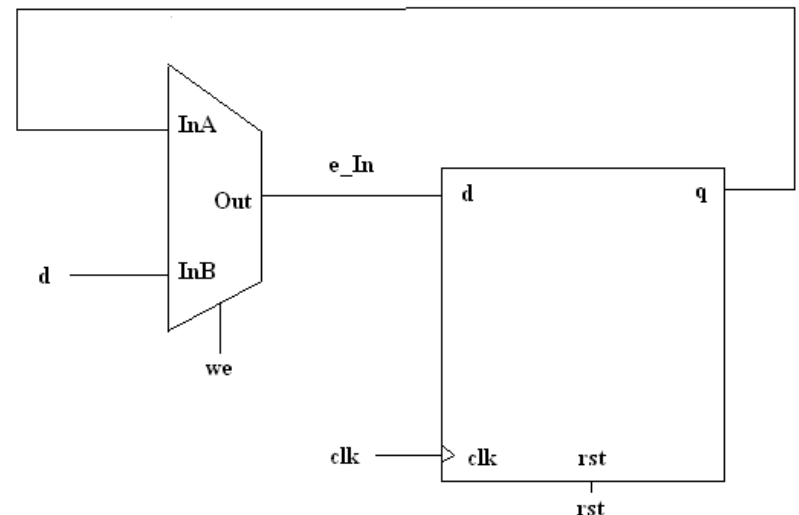



# Problem 4 - Saturating Counter

```
module sc( clk, rst, ctr_rst, out, err);
```

```
    input clk;
```

```
    input rst;
```

```
    input ctr_rst;
```

```
    output [2:0] out;
```

```
    output err;
```

```
endmodule
```

- **rst**: Synchronous reset that sets output to zero at pos clock edge
- **ctr\_rst**: ctr\_rst is different from the global rst signal

# Code Example – One Possible implementation

```
reg [2:0] nextState;  
dff inst [2:0](out, nextState, clk, rst);    /* Out maps to q; nextState maps to d */  
  
always@(out, ctr_rst)  
    begin  
        case(out)                // Every time out changes, keep evaluating by reading  
ctr_rst  
            // If ctr_rst is 0; keep incrementing; if not nextState is 0  
            // Observe that nextState is feeding the D Flip-Flop  
            3'd0: begin  
                nextState=ctr_rst? 3'd0:3'd1;  
                err=1'd0;  
            end
```

# Counter – Sample Output

Shown at the right are the values of **ctr\_rst** and **out** for a sample simulation run

1. **Out** is initially **X** (cycle 0)

2. **Out** is 0 on posedge (**rst=1**). definition, **rst** will be held HIGH in first 2 cycles (Cycle 100)

3. **Out** is 0 (**rst=1**) (Cycle 200)

4. **Out** is being incremented from 0->1->2 (see cycles 300,400 and 500). At 500, **ctr\_rst** is 1

5. So, **Out=0** on next posedge (cycle 600)

```
# time: 0 Cycle
# clk 1 ctr_rst 0 Out x
#
# time: 100 Cycle
# clk 1 ctr_rst 0 Out 0
#
# time: 200 Cycle
# clk 1 ctr_rst 0 Out 0
#
# time: 300 Cycle
# clk 1 ctr_rst 0 Out 0
#
# time: 400 Cycle
# clk 1 ctr_rst 0 Out 1
#
# time: 500 Cycle
# clk 1 ctr_rst 1 Out 2
#
# time: 600 Cycle
# clk 1 ctr_rst 0 Out 0
#
# time: 700 Cycle
# clk 1 ctr_rst 0 Out 1
#
# time: 800 Cycle
# clk 1 ctr_rst 1 Out 2
#
# time: 900 Cycle
# clk 1 ctr_rst 0 Out 0
#
# time: 1000 Cycle
# clk 1 ctr_rst 0 Out 1
#
# time: 1100 Cycle
# clk 1 ctr_rst 0 Out 2
#
# time: 1200 Cycle
# clk 1 ctr_rst 1 Out 3
#
# time: 1300 Cycle
# clk 1 ctr_rst 1 Out 0
```

# Sample Output - Continued

1. **Out** is being continuously increment now from 0->1->2->3->4->5 (see cycles 2000,2100,2200,2300,2400,2500)


```
# time: 2000 Cycle
# clk 1 ctr_rst 0 Out 0
#
# time: 2100 Cycle
# clk 1 ctr_rst 0 Out 1
#
# time: 2200 Cycle
# clk 1 ctr_rst 0 Out 2
```
2. From 2600 onwards, **Out** retains the final value of 5 (see cycles 2600, 2700 and 2800)

```
# time: 2300 Cycle
# clk 1 ctr_rst 0 Out 3
#
# time: 2400 Cycle
# clk 1 ctr_rst 0 Out 4
#
# time: 2500 Cycle
# clk 1 ctr_rst 0 Out 5
#
# time: 2600 Cycle
# clk 1 ctr_rst 0 Out 5
#
# time: 2700 Cycle
# clk 1 ctr_rst 0 Out 5
#
# time: 2800 Cycle
# clk 1 ctr_rst 1 Out 5
#
# time: 2900 Cycle
# clk 1 ctr_rst 0 Out 0
#
```
3. At cycle 2800, **ctr\_rst** goes HIGH
4. At the next clock, **Out** is reset to ZERO

# Sample Output – Special Case (Hold Out at Zero)

1.	Over cycles 1000, 1100 and 1200, Counter is incrementing	# time: 1000 Cycle # clk 1 ctr_rst 0 Out 1 #
2.	At 1200, it saw <b>ctr_rst</b> is 1. So in the next cycle (cycle 1300), <b>Out</b> is ZERO	# time: 1100 Cycle # clk 1 ctr_rst 0 Out 2 #
3.	At 1300, <b>ctr_rst</b> is still 1. So in next cycle (cycle 1400), <b>Out</b> is still ZERO	# time: 1200 Cycle # clk 1 ctr_rst 1 Out 3 #
4.	At 1400, <b>ctr_rst</b> is still 1. So in next cycle (cycle 1500), <b>Out</b> is still ZERO	# time: 1300 Cycle # clk 1 ctr_rst 1 Out 0 #
5.	At 1500, <b>ctr_rst</b> is 0 due to which counter resumes counting (You can see that it incremented from 0 to 1 in cycle 1600)	# time: 1400 Cycle # clk 1 ctr_rst 1 Out 0 # # time: 1500 Cycle # clk 1 ctr_rst 0 Out 0 # # time: 1600 Cycle # clk 1 ctr_rst 0 Out 1 #

# Problem 5 - FIFO

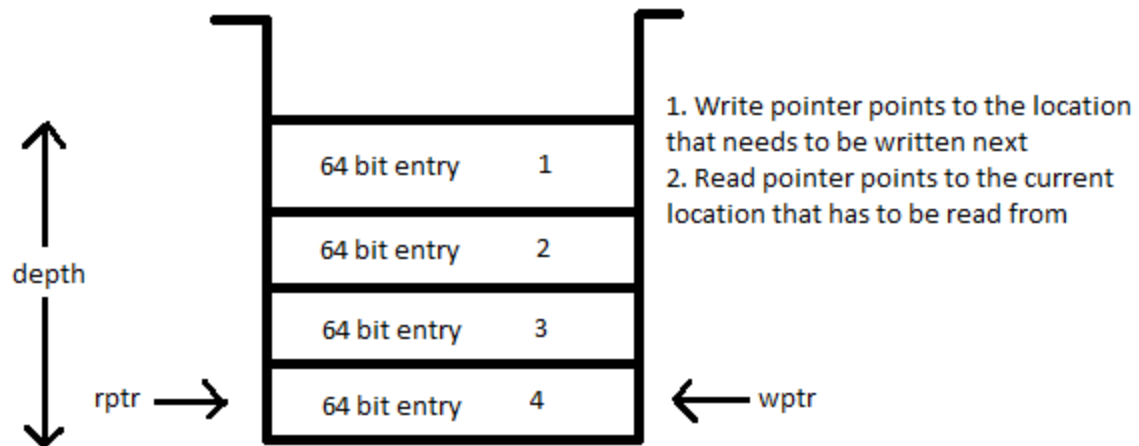

# Sample Code - Instantiation

```
wire [63:0] data[3:0], data_flop[3:0];    // Multi-dimensional array
```

```
wire [1:0] rd_ptr, wr_ptr;
```

```
reg [1:0] rd_nxt, wr_nxt;
```

```
wire [2:0] count;
```

```
reg [2:0] nxt_count;
```

```
// Instantiate DFF for read pointer; similarly for write and count
```

```
dff temp0 [1:0](rd_ptr, rd_nxt, clk, rst);
```

```
dff temp3 [63:0](data_flop[0], data[0], clk, rst);
```

# FIFO SAMPLE CODE (Contd..)

```
assign data[0] =(data_in_valid & (wr_ptr==2'd0) & (~fifo_full)) ? data_in : data_flop[0];
```

```
assign data[1] =(data_in_valid & (wr_ptr==2'd1) & (~fifo_full)) ? data_in : data_flop[1];
```

```
// Similarly for data[2] and data[3]
```

```
// logic for read and write pointers
```

```
always@(*)begin
```

```
    case(rd_ptr)
```

```
        2'd0:rd_nxt=(pop_fifo & (~fifo_empty)) ? 2'd1:2'd0;
```

```
        2'd1:rd_nxt=(pop_fifo & (~fifo_empty)) ? 2'd2:2'd1;
```

```
        comes here
```

```
// logic for 2'd2 and 2'd3
```

```
    endcase
```

```
end
```

```
always@(*)begin
```



# FIFO Sample Code (Contd..)

```
always @(*)begin
```

```
    case(count)
```

```
        3'd0: nxt_count=~(data_in_valid^pop_fifo)?3'd0:data_in_valid?3'd1:3'd0;
```

```
        3'd1: nxt_count=~(data_in_valid^pop_fifo)?3'd1:data_in_valid?3'd2:3'd0;
```

```
        // What happens for other values ?
```

```
    endcase
```

```
end
```

```
assign data_out= data_flop[rd_ptr];
```

```
assign fifo_full=(count==3'??);    // When count reaches ?
```

```
assign fifo_empty=(count==3'??);    // When count is ??
```