

Processor Implementation

Forecast -- heart of course -- key to project

- Sequential logic design review
- Clocking methodology
- Datapath -- 1 CPI
 - single instruction, 2's complement, unsigned
- Control
- Multiple cycle implementation
- Microprogramming
- Exceptions

Review Sequential Logic

Logic is combinational if output is solely function of inputs


e.g., ALU of previous lecture

Logic is sequential or "has state" if output function of

- past and current inputs
- past inputs "remembered" in "state"
- but no magic!

Review Sequential Logic

E.g., D latch

 


Clock high $Q = D$, $\bar{Q} = \bar{D}$ after some min to max propagate delay

clock low Q , \bar{Q} remain unchanged

sensitive to clock level

Review Sequential Logic

E.g., D flip-flop

 


While clock high, D flows into 1st latch, but not 2nd

There Q retains old value

Remember D at falling edges and propagates through 2nd latch

Review Sequential Logic

Can build

 

Why does this fail for latch?

Clocking Methodology

Motivation

- Design datapath/control without thinking about clocks
- Use convention called clocking methodology
 - restricts design freedom
 - hides complexity


Our Methodology

Only Flip-flops

All on same edge (e.g., falling)


All with same clock (omit from pictures)

All logic finishes in one clock cycle

 


Our Methodology, cont.

Do ***NOT*** use qualified clocks:I

 

Correct I

 

Datapath - 1 CPI

Assumption: Get whole instruction done in one long cycle

Instructions: `add`, `sub`, `and`, `or`, `slt`, `lw`, `sw`, & `beq`

To do

- For single instruction
- Put it together


Fetch Instructions

Fetch instruction,
then increment PC

Assumes


- PC updated every cycle
- no branch or jumps

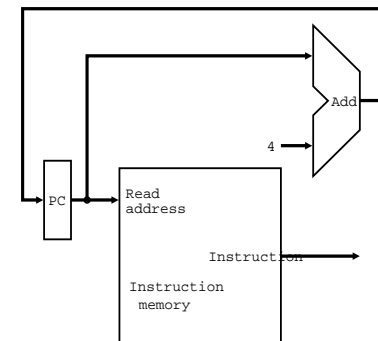after this instruction,
do different things



ALU Instructions

And \$1, \$2, \$3 # \$1 destination

 

Use R-format

opcode rs rt rd shamt funct

6 5 5 5 5 6


Load/Store Instructions

`xw $1, immed($2) # $1 <-> M[SE(immed)+$2]`

Use I-format

opcode rs rt immed

6 5 5 16

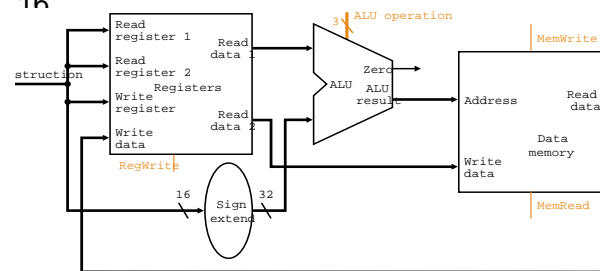


Branch Instructions

beq \$1, \$2, addr # if (\$1 == \$2) PC = PC + addr<<2

Actually

- newPC = PC + 4
- target = newPC + addr<<2 # in MIPS offset from newPC
- if (\$1-\$2 == 0)
- PC = target
- else
- PC = newPC

Branch Instructions

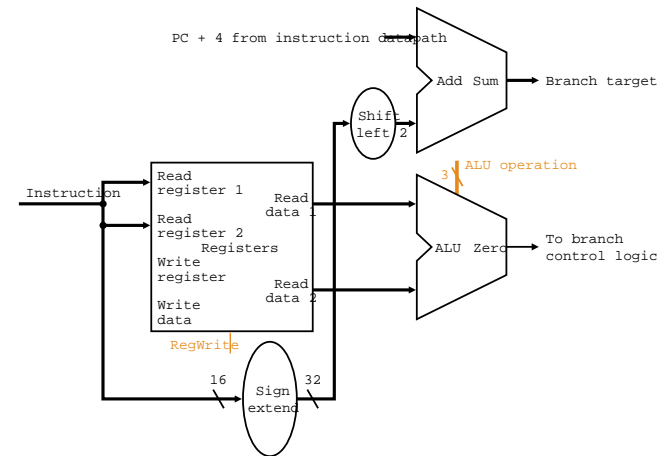

All Together

