

Announcements

Homework 10 (LAST!!) due Wednesday by 5 pm

- Watch TED talk; write essay answering questions

Final Project : Card Game

- Due December 12 – In-class Demos

Intermediate Deadlines

- Wed (11/30): Find project partner
 - Google Doc to find others (email to cs202-tas@cs.wisc.edu)
- Fri (12/2): Project proposal
 - 1 sentence email to cs202-tas@cs.wisc.edu (cc partner)
- Wed (12/7): Project draft to Learn@UW dropbox
 - Whatever you have completed

Instructor Office Hours: None today



Tuesday and Thursday -- 1:30 – 4:30

UNIVERSITY of WISCONSIN-MADISON
Computer Sciences Department

CS 202: Introduction to Computation

Professor Andrea Arpaci-Dusseau

How does a computer... do arithmetic?

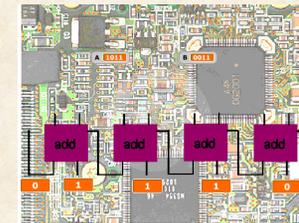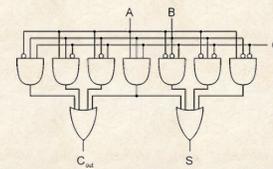

Previous Lecture: Boolean Logic

Boolean logic: Operates on True (1) and False (0)

- Operators: AND, OR, NOT

Boolean expression, truth table, combinational circuit

- All three are equivalent


Truth table: Give output for all input combinations

- 1 input variable → how many rows?
- 2 input variables?
- 3 input variables?
- K inputs variables?

2^k rows

Shorthand in Logic Gates

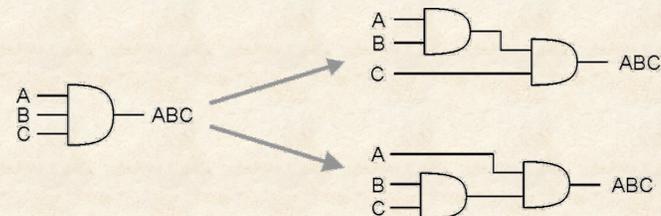Can draw AND and OR gates with more than two inputs



AND gate: Output is 1 if and only if all inputs are 1

OR gate: Output is 1 if one or more inputs are 1


Review: Sum of Products

Can implement ANY truth table with AND, OR, NOT

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0


What is the algorithm? What does circuit look like?

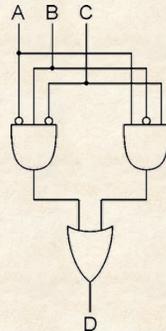1. AND combinations that yield a "1" in the truth table.
2. OR the results of the AND gates.



Today's Challenge

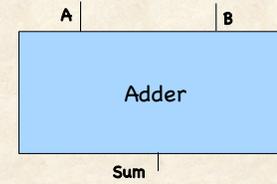Can we perform **addition** using only AND, OR, and NOT gates?



Can compute logic circuit for any function
 "Sum = A plus B" is a function of only inputs
 Therefore, can create circuit for addition!

Approach #1: Sum of Products

Inputs: Two binary numbers A and B
 View each bit of number as an input; 2 bits each

- $A = a_1a_0$
- $B = b_1b_0$

What range of numbers can be added together?

- A can be 00, 01, 10, 11 (0, 1, 2, 3)
- B can be 00, 01, 10, 11 (0, 1, 2, 3)

Output is a three-bit binary number

- $\text{Sum} = s_2s_1s_0$

Are 3 bits enough to represent Sum?

- Largest Sum = 11 + 11 = 3 + 3 = 6 = 100

Approach #1: Sum of Products

View each bit of number as an input; 2 bits each

- $A = a_1a_0$; $B = b_1b_0$

Output is a three-bit binary number

- $\text{Sum} = s_2s_1s_0$

Construct truth table of all input combinations

- How many rows?
- 4 bits of input
- $2^4 = 16$ rows of table

Use sum-of-products algorithm for three outputs

- s_2 , s_1 , and s_0

a ₁	a ₀	b ₁	b ₀	t ₂	t ₁	s ₀
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

How to construct addition circuit?

- 1) Set up Truth Table; Enumerate all 16 input combinations for a₁, a₀, b₁, b₀
- 2) Determine decimal number corresponding to each input
- 3) Calculate decimal sum as output
- 4) Translate decimal number to binary
- 5) Create 3 circuits (Sum-of-products) for s₂, s₁, s₀

Approach #1: Sum of Products

What if 32-bit integers instead of 2-bits??

Number of inputs to circuit?

- $2^{32} = 64$

How many rows in truth table?

- 2^{64}

Implication:
Need a fundamentally different approach for any real architecture!

Approach #2: Modular Design

Modular Design

- Library of small number of basic components
- Combine together to achieve desired functionality
- Basic principle of modern industrial design

Requires some **insight** to design component

What algorithm do you use for decimal addition?

$$\begin{array}{r}
 6925 \\
 + 8729 \\
 \hline
 15654
 \end{array}$$

Informal:

- Memorize facts for adding numbers 0..9 to 0..9 + 1 (carry)
- Apply facts to ones position; record units; carry tens
- Repeat for each position (tens, hundred, thousands) w/ carry
- Record final carry out

Algorithm for binary addition?

19	1 0 0 1 1 10011	16 + 2 + 1 = 19
+27	1 1 0 1 1 11011	16 + 8 + 2 + 1 = 27
46	1 0 1 1 1 0 101110	32 + 8 + 4 + 2 = 46

We know these facts:
 0 + 0 + 0 = 00
 1 + 0 + 0 = 01
 1 + 1 + 0 = 10 (two)
 1 + 1 + 1 = 11 (three)

Modular Design for Addition

Notation:

$$\begin{array}{r}
 c_{N-1} \ c_{N-2} \ \dots \ c_1 \ c_0 \\
 a_{N-1} \ a_{N-2} \ \dots \ a_1 \ a_0 \\
 + \ b_{N-1} \ b_{N-2} \ \dots \ b_1 \ b_0 \\
 \hline
 s_N \ s_{N-1} \ s_{N-2} \ \dots \ s_1 \ s_0
 \end{array}$$

Carry bits

Repeatedly (N times) do **1-bit full add**:
 Take cin, a, b as input
 Compute cout, s as output


Module: 1-bit Full Adder

Implement using just AND, OR, NOT

- Add two bits (A, B) and carry-in (C_{in}), for one-bit sum (S) and carry-out (C_{out})


Truth Table

A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

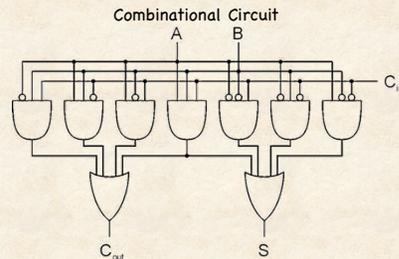


Abstraction: 1-bit Full Adder


Represent this circuit:

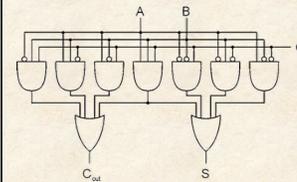

With this diagram:

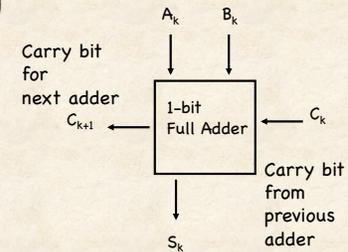


Four-bit Adder

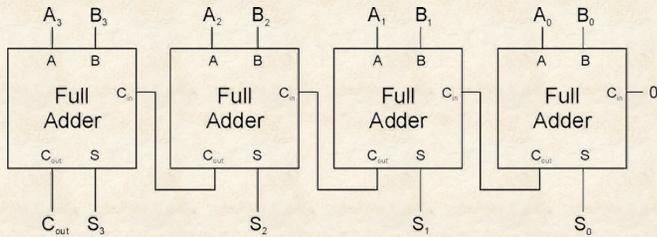


Do you find anything strange or disturbing about this adder?
 To compute sum of higher bits need results from lower bits
 "Ripple-carry" adder

Timing Diagram

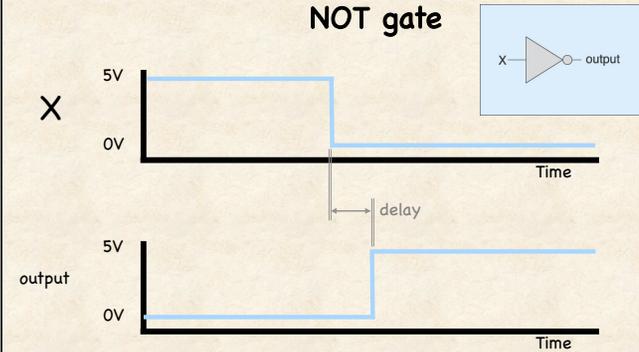

Four-bit Adder

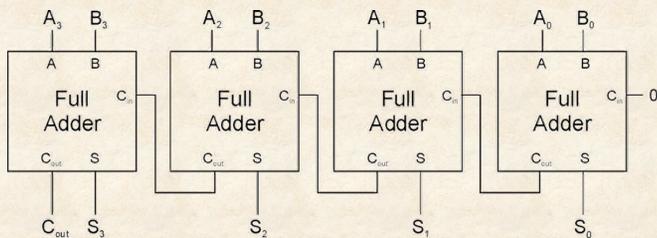

How many gate delays until output settles?
 Each 1-bit adder requires 2 gate delays (AND + OR gates)
 4 adders * 2 gate delays/adder = 8 gate delays
 Influences clock speed of processor

Adder: Example


$$\begin{array}{r}
 25 \quad 110010 \\
 +29 \quad 11001 \\
 \hline
 \end{array}$$

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Create Addition Circuit in Scratch!

Add two 4-bit numbers to produce 1 5-bit number

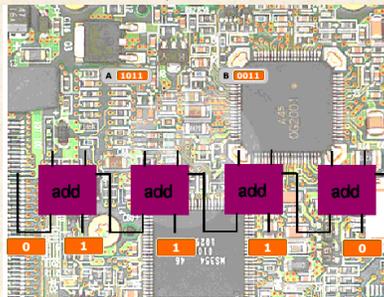- Only use AND, OR, and NOT!
- 4 nearly identical Sprites



Scripts for 1 Full-bit Adder

Scripts identical across 4 Adder Sprites

Each has private variable for a, b, cin, cout, s

```

when clicked
  add to 0
  add to 0

when I receive add
  set a to letter 10 of A
  set b to letter 10 of B
  set cin to add of 10,2
  if
    and a = 0 and cin = 0 or
    and a = 1 and cin = 1
      set s to 0
    else
      set s to 1
  end if
  set cout to 0
  add cout to 0
  
```

To connect adders, simply set cin to cout of "previous" Sprite

Summary

Today's Topics

- We can do addition with just AND, OR, and NOT!

Homework 10 (LAST!!) due Wednesday by 5 pm

- Watch TED talk; write essay answering questions

Final Project : Card Game

- Due December 12 - In-class Demos

Intermediate Deadlines

- Wed (11/30): Find project partner
 - Google Doc to find others (email to cs202-tas@cs.wisc.edu)
- Fri (12/2): Project proposal
 - 1 sentence email to cs202-tas@cs.wisc.edu (cc partner)
- Wed (12/7): Project draft to Learn@UW Dropbox
 - Whatever you have completed

Instructor Office Hours: None today

Tuesday and Thursday -- 1:30 - 4:30