

Today

- Review
 - State machine
 - Circuit blocks
 - LDI computer
- Today
 - Tracing through execution of instructions


Concept

- Every instruction can be processed as 5 stages
 - Fetch, decode, execute, memory write-back
- Each stage maybe multiple “states”
- Each state takes one clock cycle
- State machine represents how the machine transitions to a set of states for each instruction


Implementation

- Datapath
 - Memories
 - Auxiliary registers
 - Circuit blocks
 - Wires connecting these all together
 - Control signals from state-machine controller
- Control-path (State machine controller)
 - Control signals at each cycle (state)
 - Logic for next state

Implementation

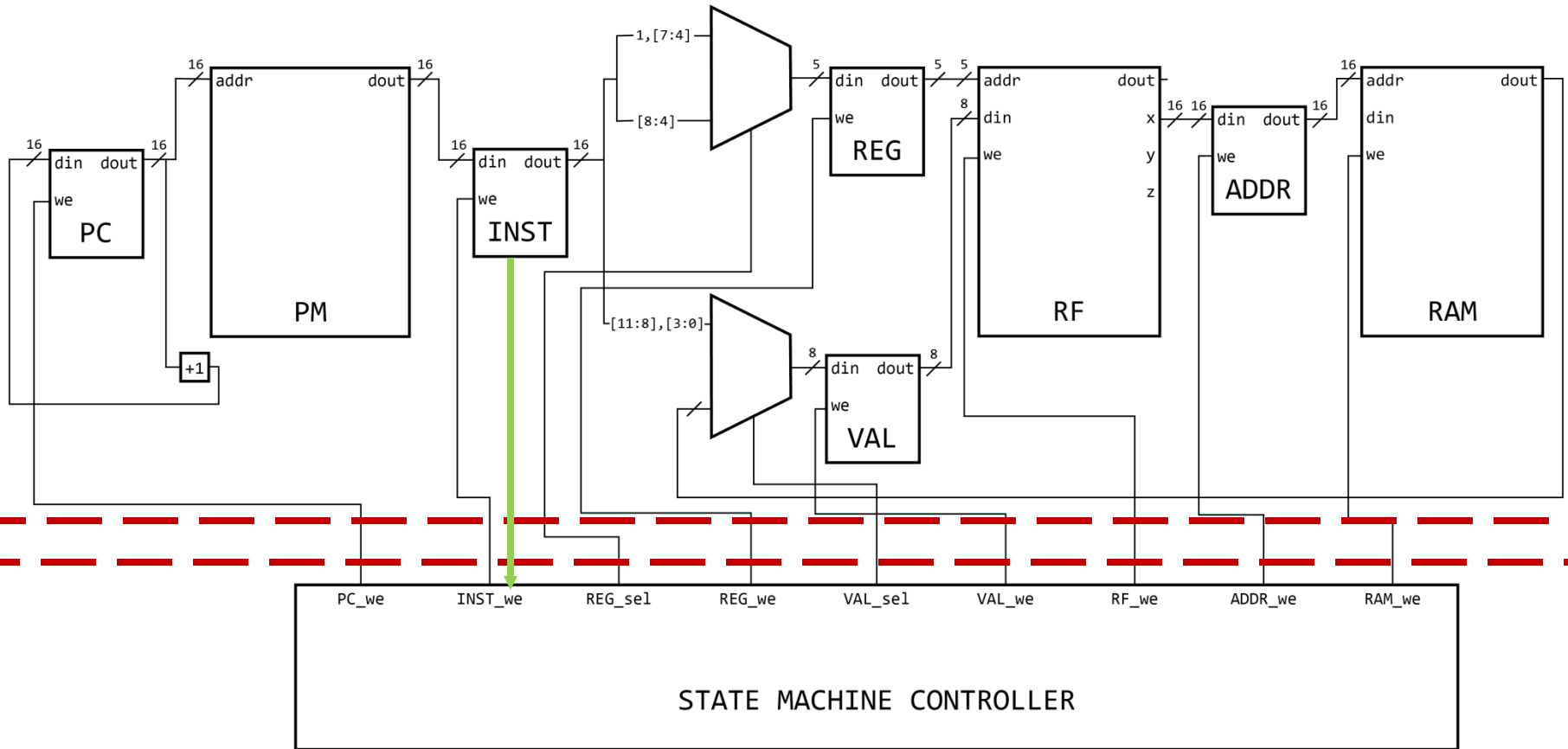

State machine controller

 


State transition table

	PC_we	INST_we	REG_we	REG_sel	VAL_we	VAL_sel	RF_we	ADDR_we	RAM_we
000	INST=PM[PC]	0	1	0		0		0	0
001	REG=1,INST[7:4]	0	0	1	0		0	0	0
010	REG=INST[8:4]	0	0	1	1		0	0	0
011	ADDR=X	0	0	0		0		1	0
100	VAL=INST[11:8],INST[3:0]	0	0	0		1	0	0	0
101	VAL=RAM[ADDR]	0	0	0		1	1	0	0
110	RF[REG]=VAL	0	0	0		0		1	0
111	PC=PC+1	1	0	0		0		0	0

State transition table

		PC_we	INST_we	REG_we	REG_sel	VAL_we	VAL_sel	RF_we	ADDR_we	RAM_we
000	INST=PM[PC]	0	1	0	0	0	0	0	0	0
001	REG=1,INST[7:4]	0	0	0	1	0	0	0	0	0
010	REG=INST[8:4]	0	0	0	0	0	1	0	0	0
011	ADDR=X	0	0	0	0	0	0	1	0	0
100	VAL=INST[11:8],INST[3:0]	0	0	0	0	1	1	0	0	0
101	VAL=RAM[ADDR]	0	0	0	0	0	0	0	1	1
110	RF[REG]=VAL	0	0	1	0	0	0	1	0	0
111	PC=PC+1	1	0	0	0	0	0	0	0	0

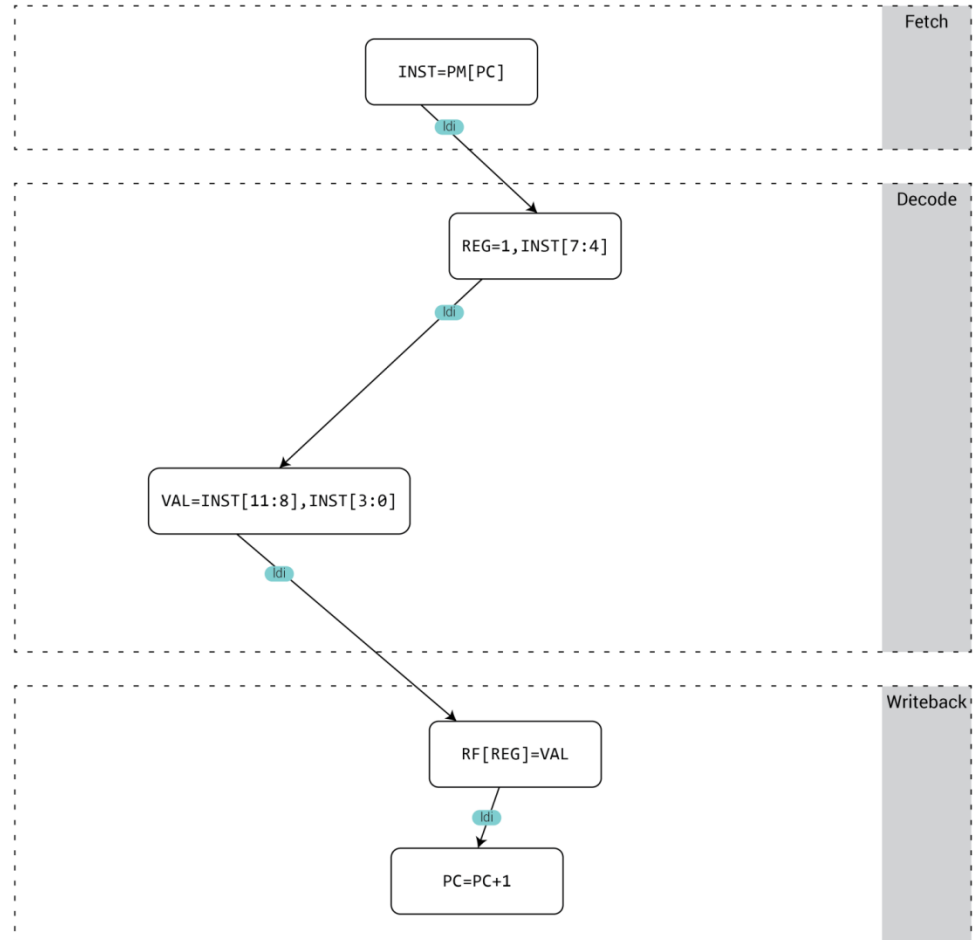

LDI:

ldi <reg>, imm

000 (Fetch)

001 (Decode)

100 (Decode)


110 (Writeback)

111 (Writeback)

State transition table

	PC_we	INST_we	REG_we	REG_sel	VAL_we	VAL_sel	RF_we	ADDR_we	RAM_we
000	INST=PM[PC]	0	1	0					
001	REG=1,INST[7:4]	0	0	1					
010	REG=INST[8:4]	0	0	1					
011	ADDR=X	0	0	0					
100	VAL=INST[11:8],INST[3:0]	0	0	0					
101	VAL=RAM[ADDR]	0	0	0					
110	RF[REG]=VAL	0	0	0					
111	PC=PC+1	1	0	0					

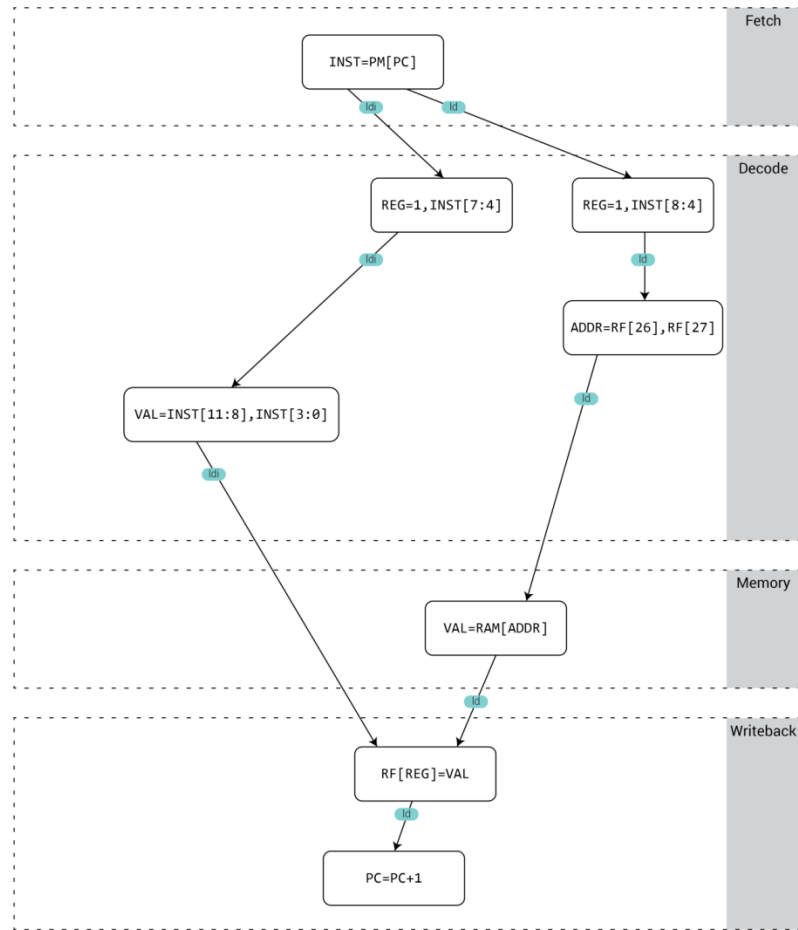LD:
 ld <reg>, X
 000 (Fetch)
 010 (Decode)
 011 (Decode)
 101 (Memory)
 110 (Writeback)
 111 (Writeback)



Next state logic circuit block

From
CH6

Current-state	OPCODE	Next-state
000	1110	001
001	1110	100
100	1110	110
110	1110	111
111	1110	000
000	1010	010
010	1010	011
011	1010	101
101	1010	110
110	1010	111
110	1010	000

Inst.	Opcode
ldi	1110
ld	1010
mov	001011
add	000011
sub	000110
inc	10010100011
dec	10010101010
and	001000
andi	0111
or	001010
ori	0110
com	10010100000
rjmp	1100
breq	111100001
brne	111101001
brsh	111101000
brlo	111100000
cp	000101
cpi	0011

LDI:

ldi <reg>, imm

000 (Fetch)
001 (Decode)
100 (Decode)
110 (Writeback)
111 (Writeback)

LD:

ld <reg>, X

000 (Fetch)
010 (Decode)
011 (Decode)
101 (Memory)
110 (Writeback)
111 (Writeback)

Next state logic circuit block

Current-state	OPCODE	Next-state
000	1110	001
001	1110	100
100	1110	110
110	1110	111
111	1110	000
000	1010	010
010	1010	011
011	1010	101
101	1010	110
110	1010	111
110	1010	000

Inst.	Opcode
ldi	1110
ld	1010
mov	001011
add	000011
sub	000110
inc	10010100011
dec	10010101010
and	001000
andi	0111
or	001010
ori	0110
com	10010100000
rjmp	1100
breq	111100001
brne	111101001
brsh	111101000
brlo	111100000
cp	000101
cpi	0011

LDI:
ldi <reg>, imm

- 000 (Fetch)
- 001 (Decode)
- 100 (Decode)
- 110 (Writeback)
- 111 (Writeback)


LD:
ld <reg>, X

- 000 (Fetch)
- 010 (Decode)
- 011 (Decode)
- 101 (Memory)
- 110 (Writeback)
- 111 (Writeback)

252's Cool Axiom for Ch7


- Given a set of inputs as boolean values and a corresponding set of boolean outputs, one can automatically create a boolean function (circuit block) that will produce that output

State machine controller

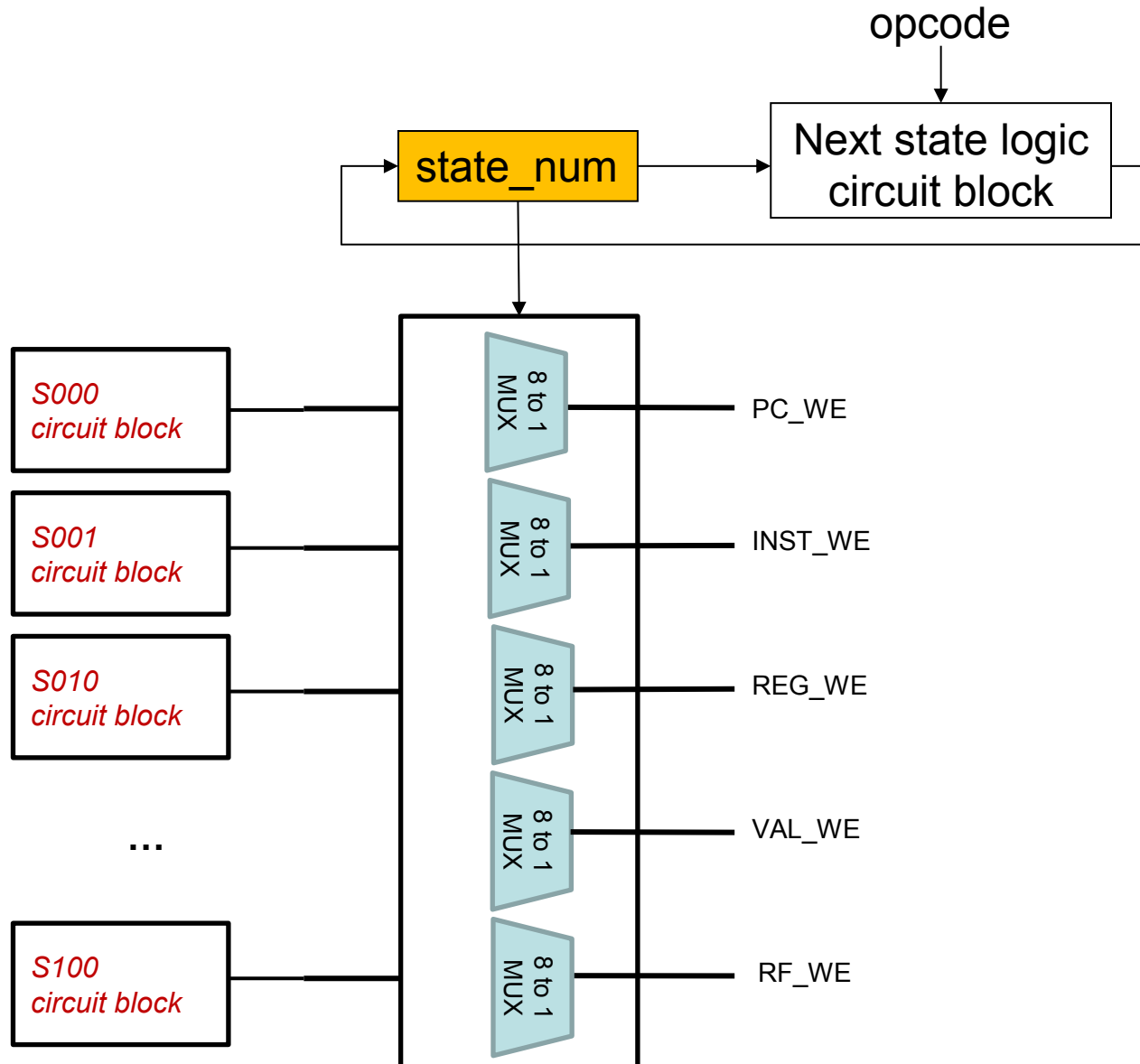


Complete machine

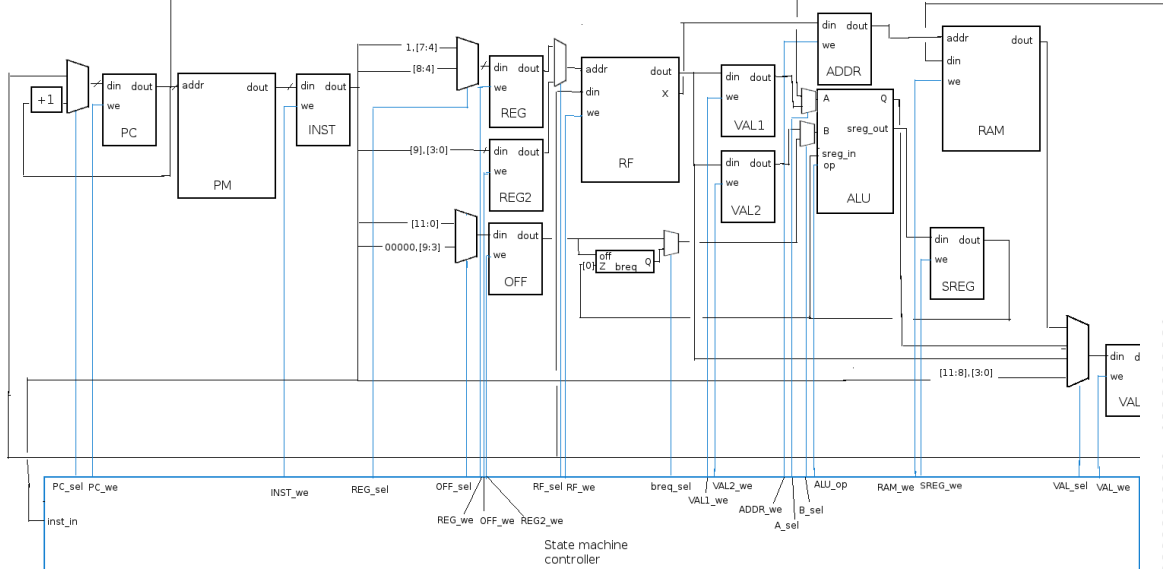- Complete state machine
- State transition table
- Datapath




Inst.	Opcode
ldi	1110
ld	1010
mov	001011
add	000011
sub	000110


	PC_sel	PC_we	INST_we	REG_sel	REG_we	OFF_we	OFF_sel	REG2_we	RF_sel	RF_we	breq_sel	VAL1_we	VAL2_we	ADDR_we	A_sel	B_sel	ALU_op	RAM_we	SREG_we	VAL_sel	VA	
INST=PM[PC]	0	1																				0
REG=1,INST[7:4]	0	0	0	1	0																	0
REG=INST[8:4]	0	0	1																			0
OFF=00000,INST[9:3]	0	0			1	1																0
OFF=INST[11:0]	0	0			1	0																0
VAL=INST[11:8],INST[3:0]	0	0																			3	1
VAL=RF[REG]	0	0																			2	1
VAL1=RF[REG]	0	0										1										0
VAL2=RF[REG2]	0	0										1	0									0
ADDR=X	0	0												1								0
REG2=INST[9],INST[3:0]	0	0						1														0
VAL=VAL1+VAL2	0	0																			1	1
VAL=VAL1-VAL2	0	0																			1	1
Update SREG	0	0																				0
VAL=OFF+PC	0	0													1	1	0					1
OFF=OFF&ZZZZZZZ ~Z	0	0									1											0
VAL=RAM[ADDR]	0	0																			0	1
RAM[ADDR]=VAL	0	0																				0
RF[REG]=VAL	0	0										1										0
PC=PC+1	0	1																				0
PC=VAL	1	1																				0

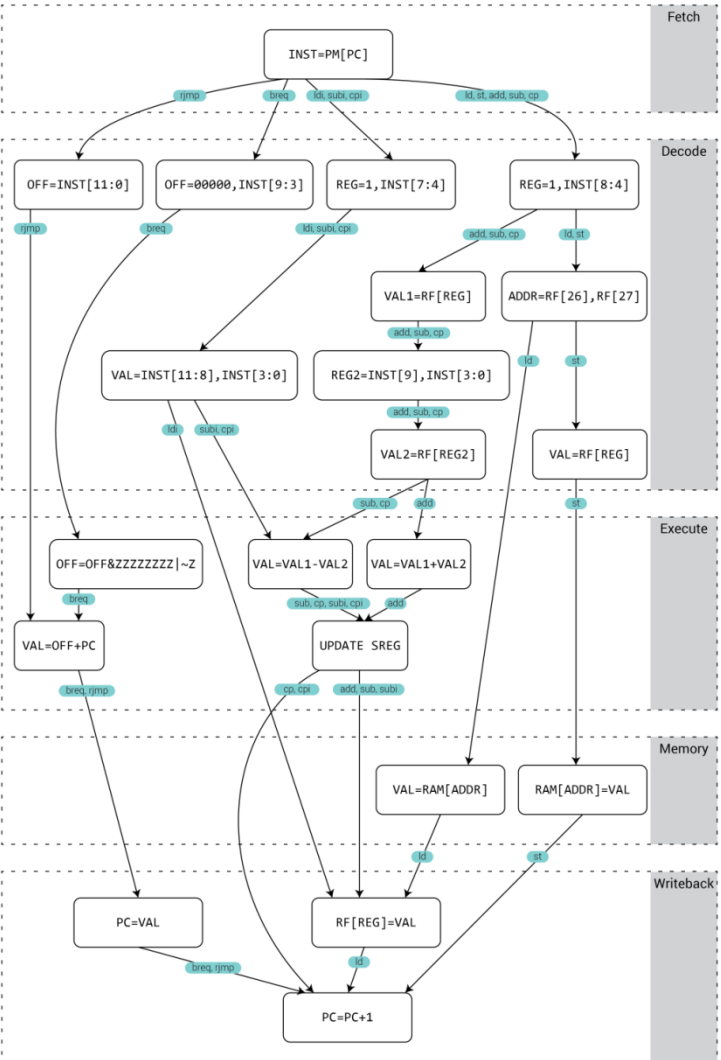

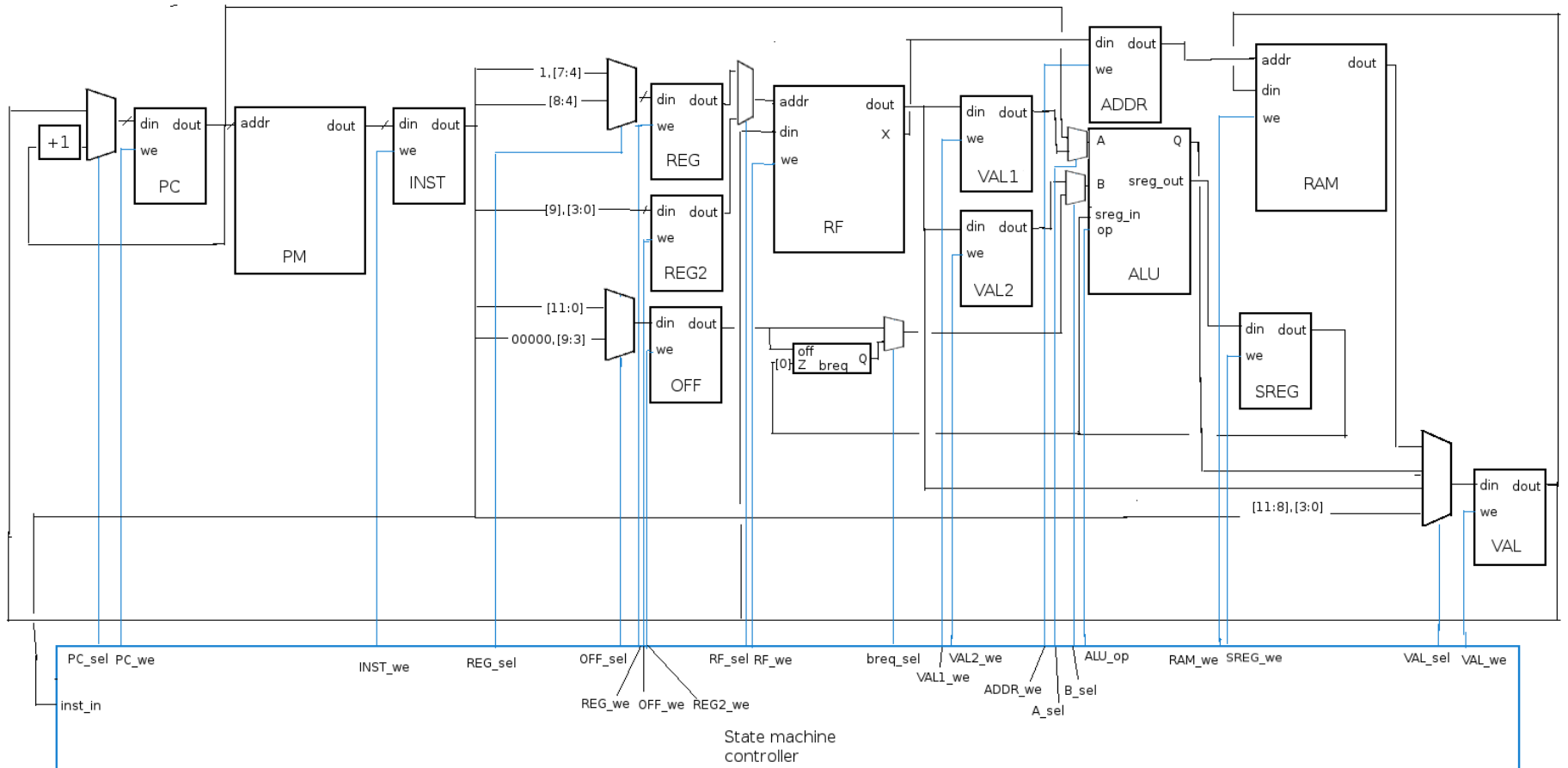Its all numbers and we can
trace the execution of any
instruction and any program!





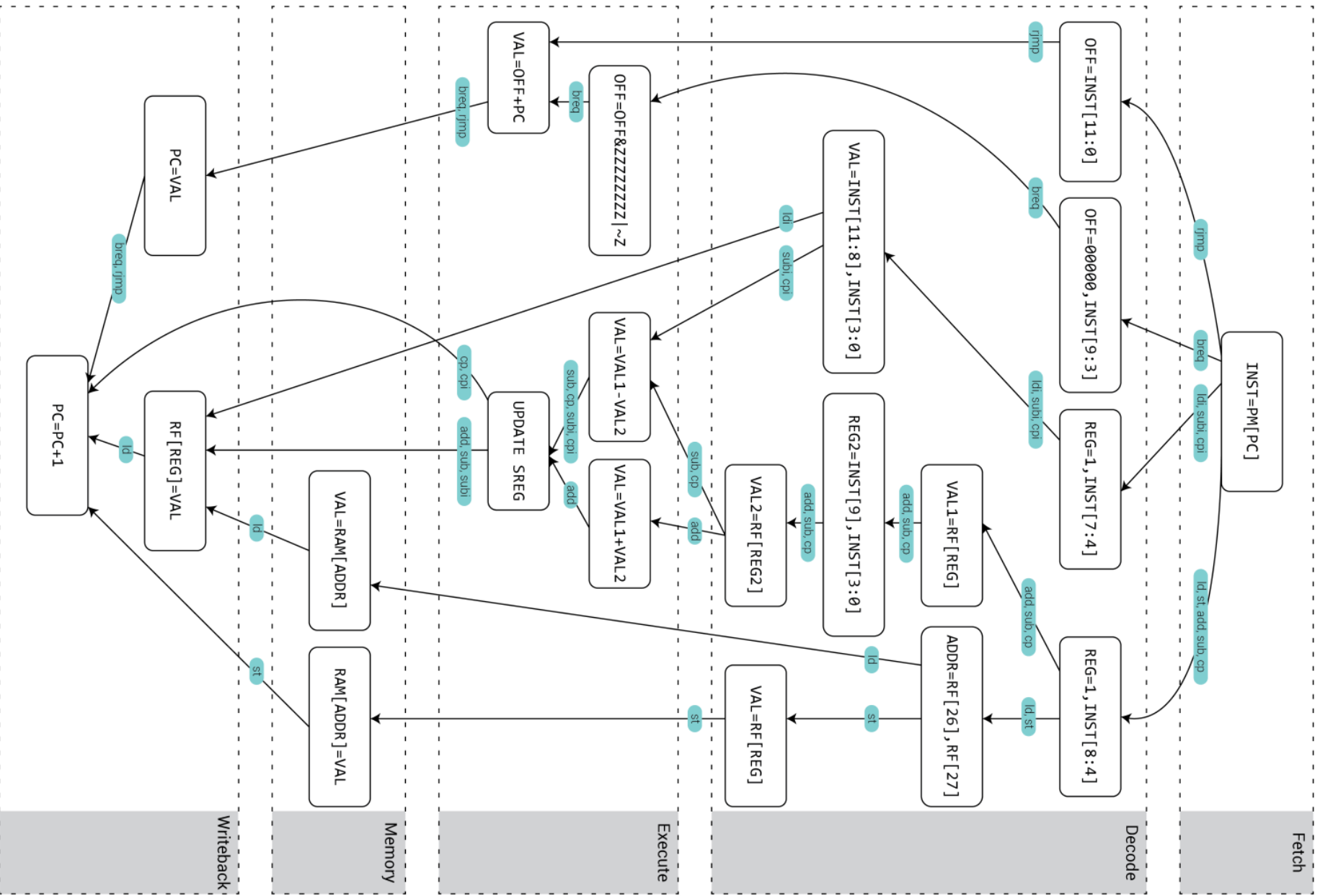

	PC_sel	PC_we	INST_we	REG_sel	REG_we	OFF_we	OFF_sel	REG2_we	RF_sel	RF_we	breg_sel	VAL1_we	VAL2_we	ADDR_we	A_sel	B_sel	ALU_op	RAM_we	SREG_we	VAL_sel	VAL_we	
INST=PM[PC]		0	1		0	0		0		0		0	0	0				0	0			0
REG=1,INST[7:4]		0	0	0	1	0		0		0		0	0	0				0	0			0
REG=INST[8:4]		0	0	1	1	0		0		0		0	0	0				0	0			0
OFF=00000,INST[9:3]		0	0		0	1	1	0		0		0	0	0				0	0			0
OFF=INST[11:0]		0	0		0	1	0	0		0		0	0	0				0	0			0
VAL=INST[11:8],INST[3:0]		0	0		0	0		0		0		0	0	0				0	0		3	1
VAL=RF[REG]		0	0		0	0		0	0	0		0	0	0				0	0		2	1
VAL1=RF[REG]		0	0		0	0		0	0	0		1	0	0				0	0			0
VAL2=RF[REG2]		0	0		0	0		0	1	0		0	1	0				0	0			0
ADDR=X		0	0		0	0		0		0		0	0	1				0	0			0
REG2=INST[9],INST[3:0]		0	0		0	0		1		0		0	0	0				0	0			0
VAL=VAL1+VAL2		0	0		0	0		0		0		0	0	0	0	0	0	0	0		1	1
VAL=VAL1-VAL2		0	0		0	0		0		0		0	0	0	0	0	1	0	0		1	1
Update SREG		0	0		0	0		0		0		0	0	0				0	0			0
VAL=OFF+PC		0	0		0	0		0		0	0	0	0	0	1	1	0	0	0			1
OFF=OFF&ZZZZZZ ~Z		0	0		0	0		0		0	1	0	0	0	1	1	0	0	0			0
VAL=RAM[ADDR]		0	0		0	0		0		0		0	0	0				0	0		0	1
RAM[ADDR] = VAL		0	0		0	0		0		0		0	0	0				0	0			0
RF[REG]=VAL		0	0		0	0		0	0	1		0	0	0				0	0			0
PC=PC+1	0	1	0		0	0		0		0		0	0	0				0	0			0
PC=VAL	1	1	0		0	0		0		0		0	0	0				0	0			0

Summary

- State machine + datapath == computer
- Tracing of instruction execution

CS 252

Lecture 24; 2015 Nov 9th; Transcribed Lecture notes

Outline

Review state machine, circuit blocks, and LDI computer
Tracing through execution of instructions

Review

Every instruction can be processed as 5 stages

- fetch
- decode
- execute
- memory
- write back

Each stage may be multiple “states”

Implementation

Important to know how stuff are implements down the the transistor and semiconductor level.

Control signals select different multiplexers to do different things

Control path has 2 pieces: (1) control signals for each state, and (2) some logic to transition to the next state

State machine controlling implementation: states generate constants. The select lines of the mux depends on the state. There is next state logic block to implement all possible transitions that needs to be done by current state.

Example 1: LDI instruction goes fetch -> decode -> decode -> writeback -> writeback

Example 2: LD instruction goes from fetch -> decode -> decode -> memory -> writeback -> writeback

Machine can be at exactly one state at a given point of time

Next state logic circuit block: opcodes from instructions tell the controller how to transition to the next state.

Given current state and opcode transition, we can create a table to transition to the next state.

Can create a large table with a set of states, set of opcodes, and set of transition next states. This table will provide everything that the machine needs to implement.

252's cool axiom for chapter 7: given a set of inputs as boolean values and corresponding set of boolean outputs, one can create a boolean function that will produce that output.

complete machine: state machine, state transition table, and datapath needs to be implemented for every instruction.

Start with a set of opcodes. Based on the instruction, transition to the next state or perform some sort of computation. Then we can organize all of ours memories

