 



Today

- Transistor behavior
- Logic gates using transistors
- Moore's Law and Dennard Scaling

Transistor




Transistor terminals

 

N-type transistor

Gate	Behavior
1	Closed Output=0
0	Open Output=Z



 


P-type transistor


Gate	Behavior
0	Closed Output=1
1	Open Output=Z

NOT Gate with Transistors


N-type		P-type	
Gate	Behavior	Gate	Behavior
1	Closed Output=0	0	Closed Output=1
0	Open Output=Z	1	Open Output=Z

   

Transistor Circuits (NAND gate)

 


Transistor Circuits (NAND gate)

 

A	B	Q
0	0	1

P-type ON when gate is 0
N-type ON when gate is 1


Transistor Circuits (NAND gate)

 

A	B	Q
0	0	1
0	1	1
1	0	0
1	1	0

P-type ON when gate is 0
N-type ON when gate is 1


Transistor Circuits (NAND gate)

 

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

P-type ON when gate is 0
N-type ON when gate is 1


Transistor Circuits (NAND gate)

 

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0


P-type ON when gate is 0
N-type ON when gate is 1

Transistor Circuits (NOR gate)

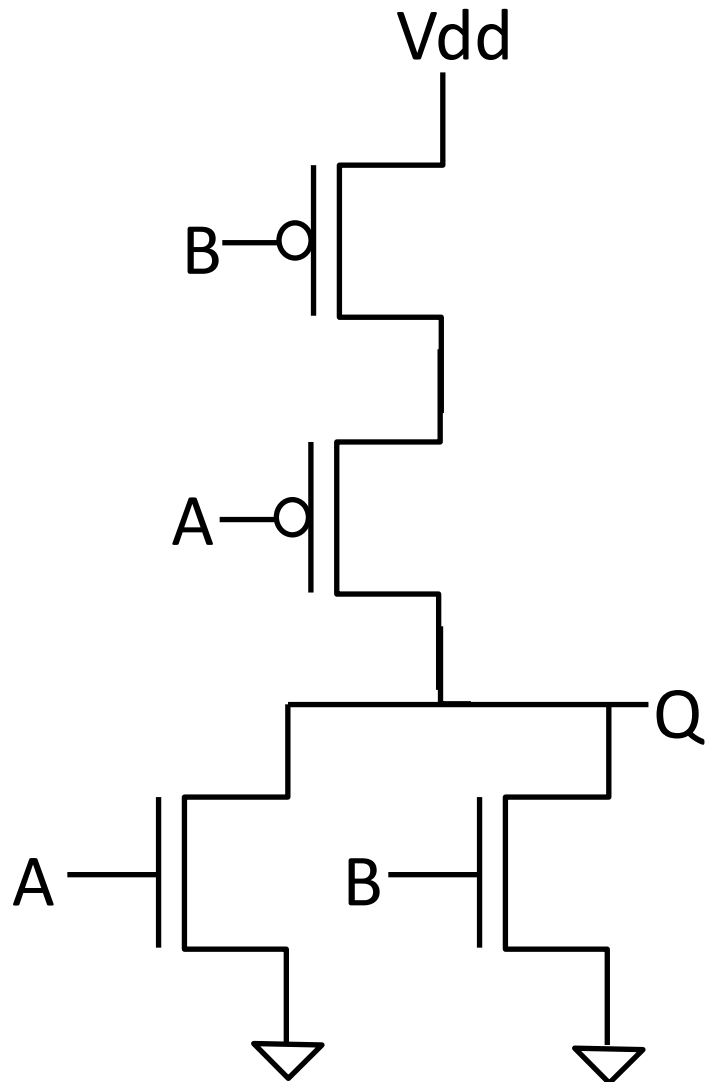

NOR Gate


Transistor Circuits (NOR gate)

 

A	B	Q
0	0	1

P-type ON when gate is 0
N-type ON when gate is 1


Transistor Circuits (NOR gate)

 

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

P-type ON when gate is 0
N-type ON when gate is 1


Transistor Circuits (NOR gate)

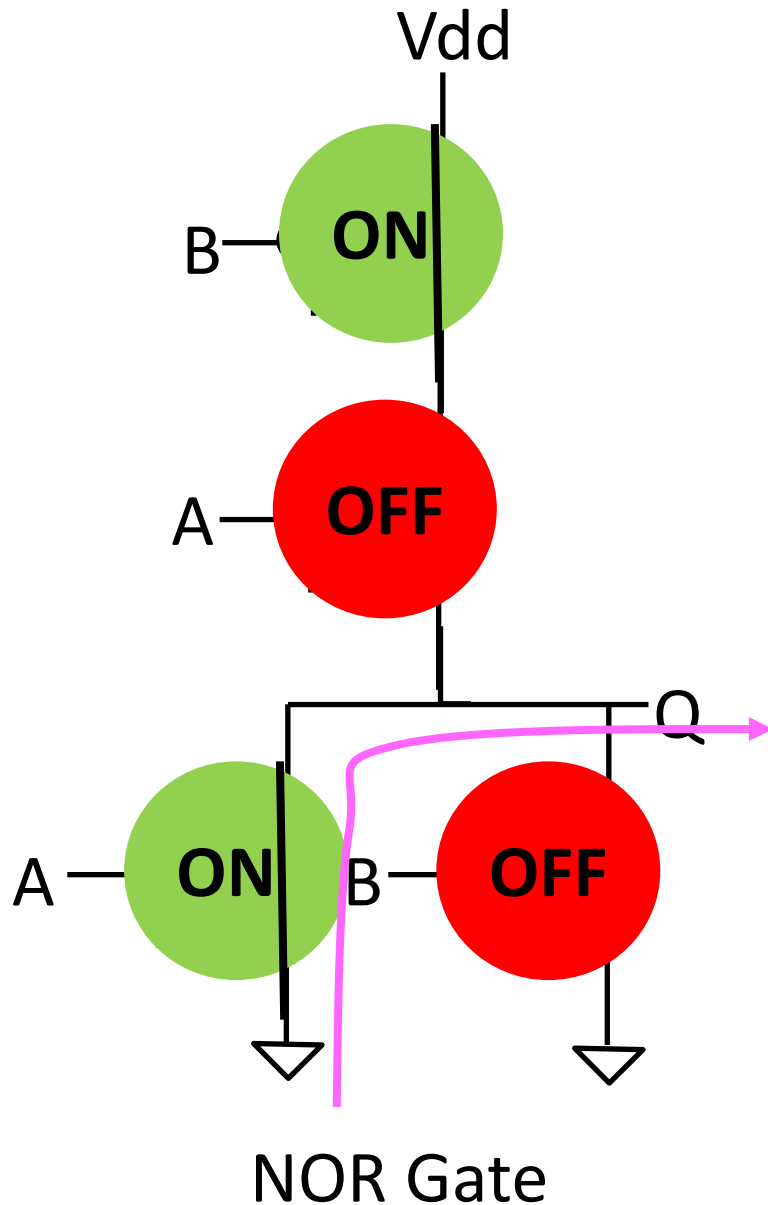

A	B	Q
0	0	1
0	1	0
1	0	0

P-type ON when gate is 0
N-type ON when gate is 1

Transistor Circuits (NOR gate)

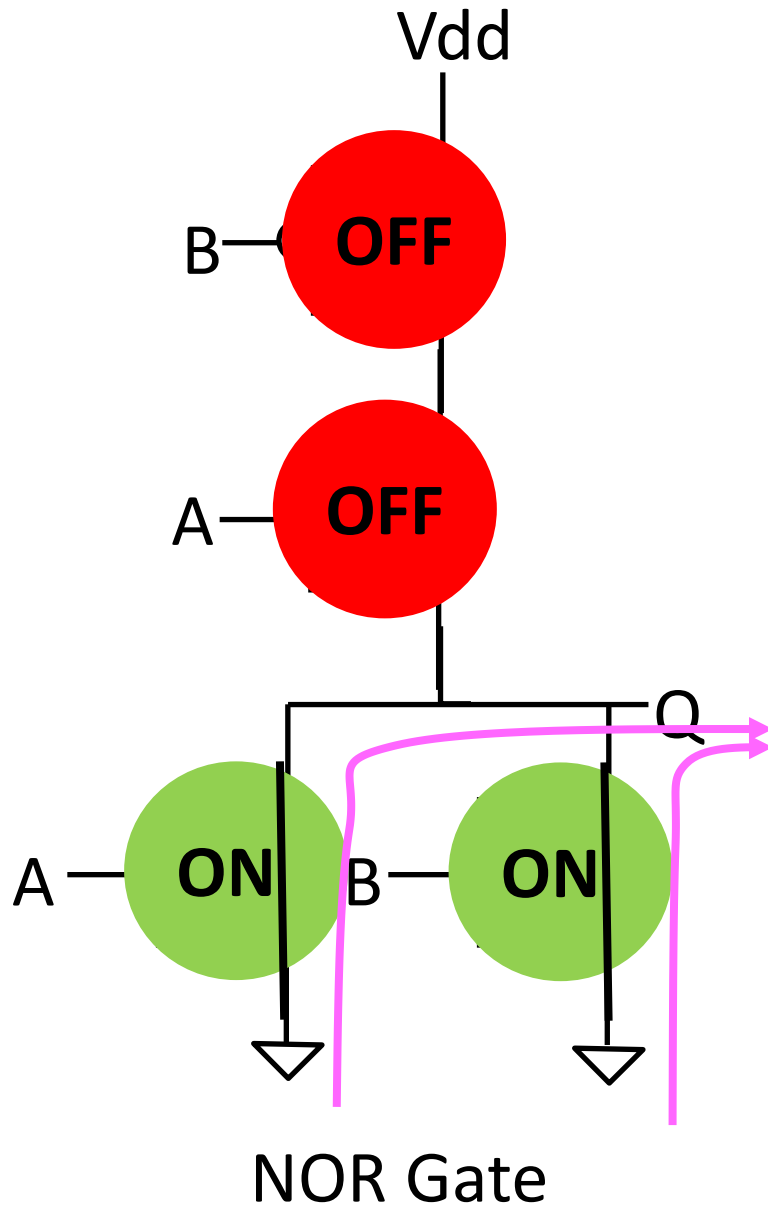


A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0


P-type ON when gate is 0
N-type ON when gate is 1

Delays (NOT ON TEST)


MORE
CURRENT

 

MORE
CURRENT

 


LESS
CURRENT

 


Delays (NOT ON TEST)


FASTER

 


FASTER

 


SLOWER

 

 
Gate delays and transistor delays
vary based on the input!




A	B	Q
0	0	

 

A	B	Q
0	0	0
0	1	

 

A	B	Q
0	0	0
0	1	1
1	0	

 

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0



That is an 8 transistor XOR gate!

Block	# Transistors
Basic elements	
NAND2	4
NOR2	4
NOT	2
AND2	6
OR2	6
AND (n inputs)	$2n+2$
OR (n inputs)	$2n+2$
MUX	40
Combined logic gates	
FA 1-bit	74
HA 1-bit	6
1-bit REG	40
3-to-8 Decoder	68
8-to-3 Encoder	30

Datapath modules	
FA 8-bit	592
CHECKZ 8-bit	32
NOT 8-bit	16
MUX 8-bit	320
8-bit REG	320
Microarchitecture blocks	
ALU	1000
Incrementor	48
State machine controller (control sigs)	274
State machine controller (next state)	1,450
Total AUX regs (9 8-bit REGS)	2,880
RF (32 8-bit REGs)	10,240
PM (16384 1-bit REGs)	655,360
RAM (16384 1-bit RGEs)	655,360
Total	1,326,612


	# Transistors	Year	Transistor size	Chip size
<u>Intel 4004</u>	2,300	1971	10 micron	12 mm ²
<u>Intel 8086</u>	29,000	1978	3 micron	33 mm ²
<u>Zilog Z80</u>	8,500	1976		
<u>Intel 80386</u>	275,000	1985	1.5 micron	104 mm ²
<u>Pentium</u>	3,100,000	1993	0.8 micro	294 mm ²
<u>Apple A7</u> (dual-core <u>ARM64</u> "mobile SoC")	1,000,000,000	2013	28 nm	102 mm ²
18-core Haswell	5,560,000,000	2014	22 nm	363 mm ²

Transistor physical diagram

  


Side view

 - Silicon by itself is semiconductor
 - Has 4 valence electrons and forms a co-valent bond with 4 neighbors
 - Hard to break and does not conduct ☹️



- Silicon by itself is insulator
 - Has 4 valence electrons and forms a co-valent bond with 4 neighbors
 - Had to break and does not conduct ☹️
- Silicon + Arsenic makes it filled with electrons and conducting
- Silicon + Boron makes it filled with “holes” and conducting


Transistor Operation

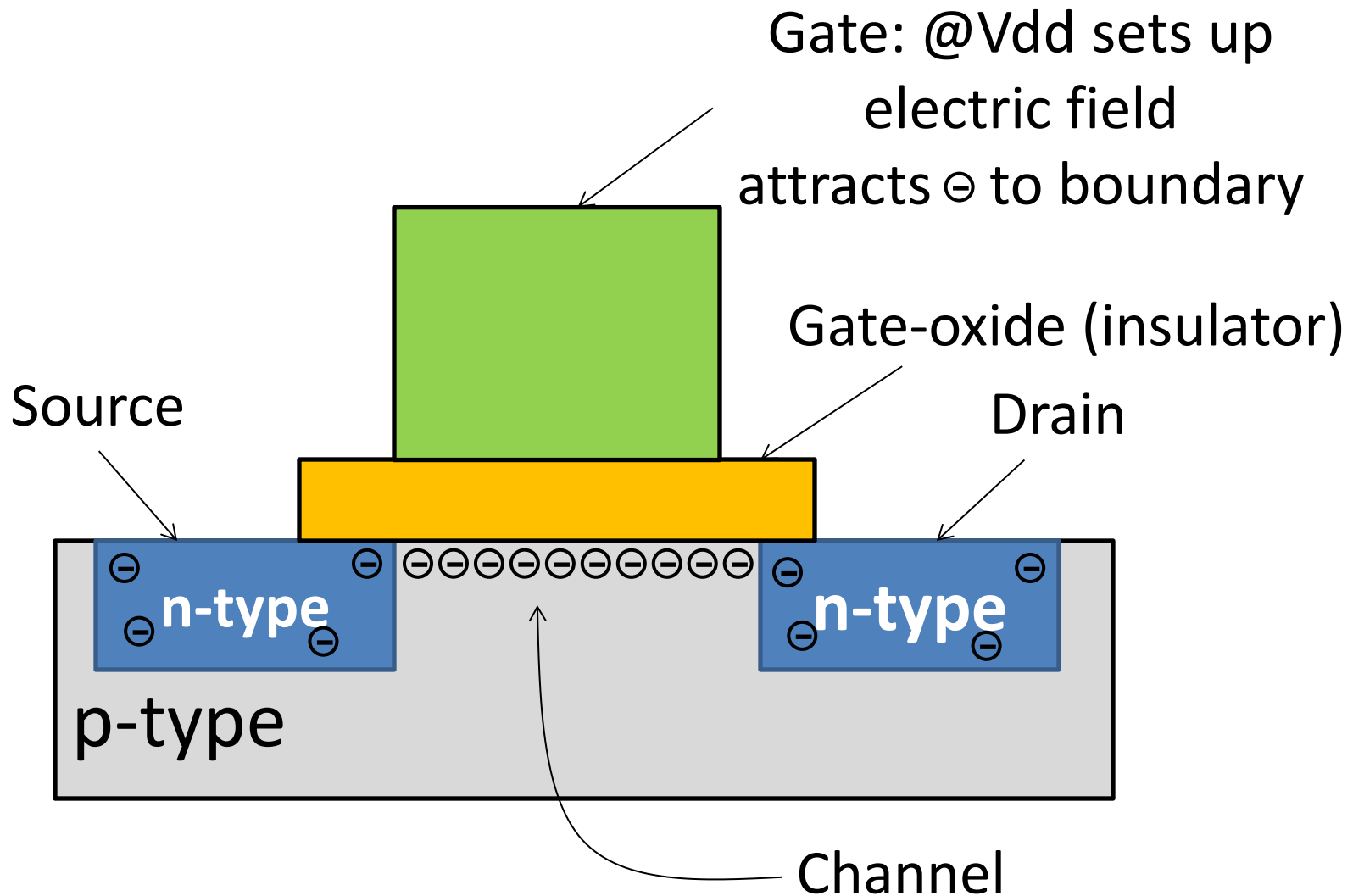

“Miracle Month” of November 17 to December 23, 1947



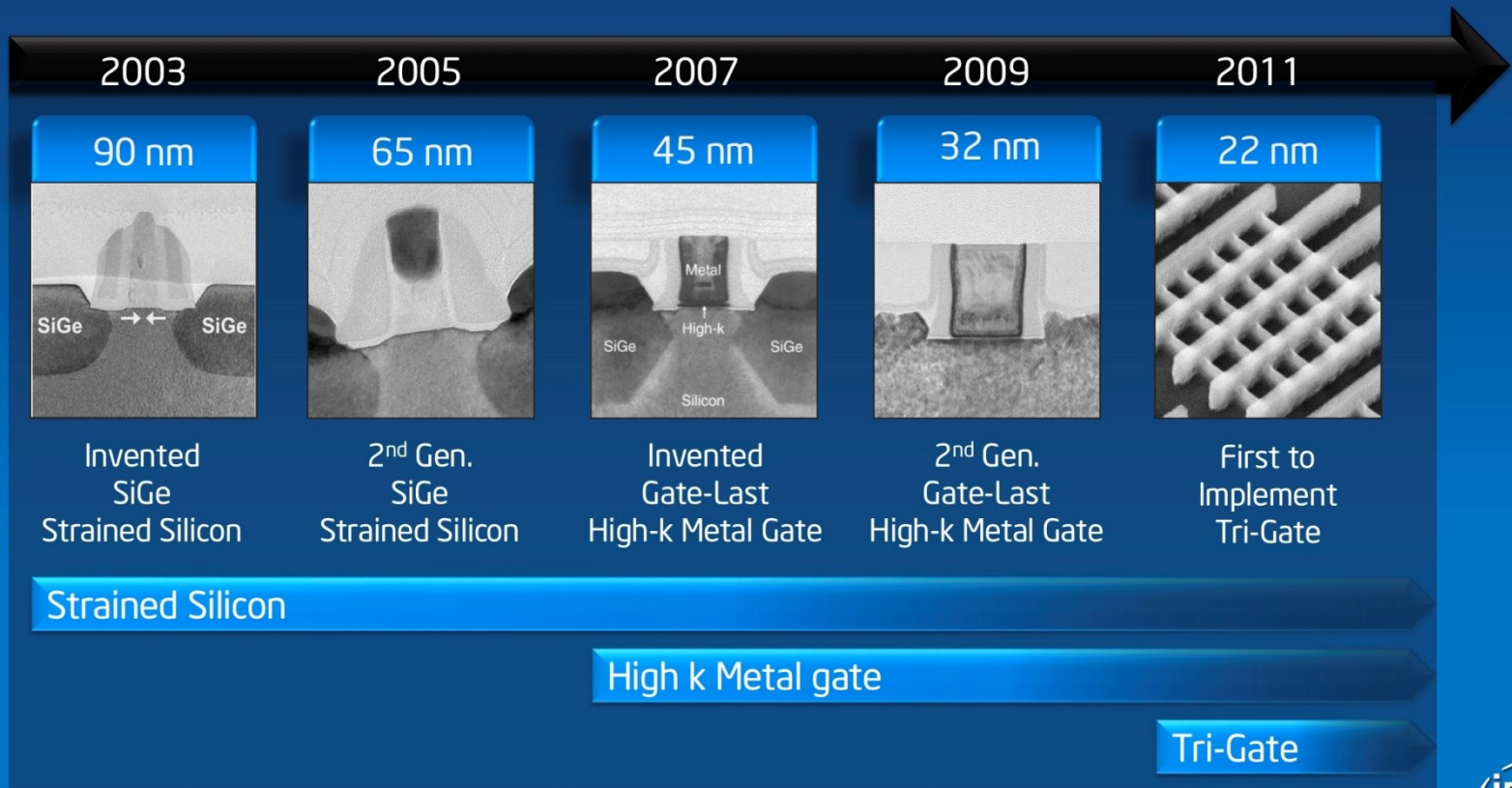Transistor Innovations Enable Technology Cadence



Moore's Law

- Number of transistors that can be cost-effectively integrated will double every 18 months
(revised to 24 and 36 months later)
- In practice:
 - Reduce the Length and width by 1.41
 - Area reduces by 2X
 - Can also reduce the thickness of the gate-oxide

Dennard Scaling



- Voltage can be reduced linearly with the channel Length
- Remember Moore's Law:
 - Since gate oxide thickness also reduces, capacitance reduces linearly
- Power consumption = $C * V^2 * Frequency$
- As C and V are each reduced by a factor of X every generation of transistors:
 - Power reduces by a cubic factor
 - Area reduces by a square

Bad news

- Dennard's scaling has ended
 - No more power benefit from building smaller transistors
- Moore's law is also likely ending or ended

This is GOOD news!

*More than ever it is important
to know how to use gates,
transistors, microarchitecture
to build power-efficient and
high-performance computers!*

 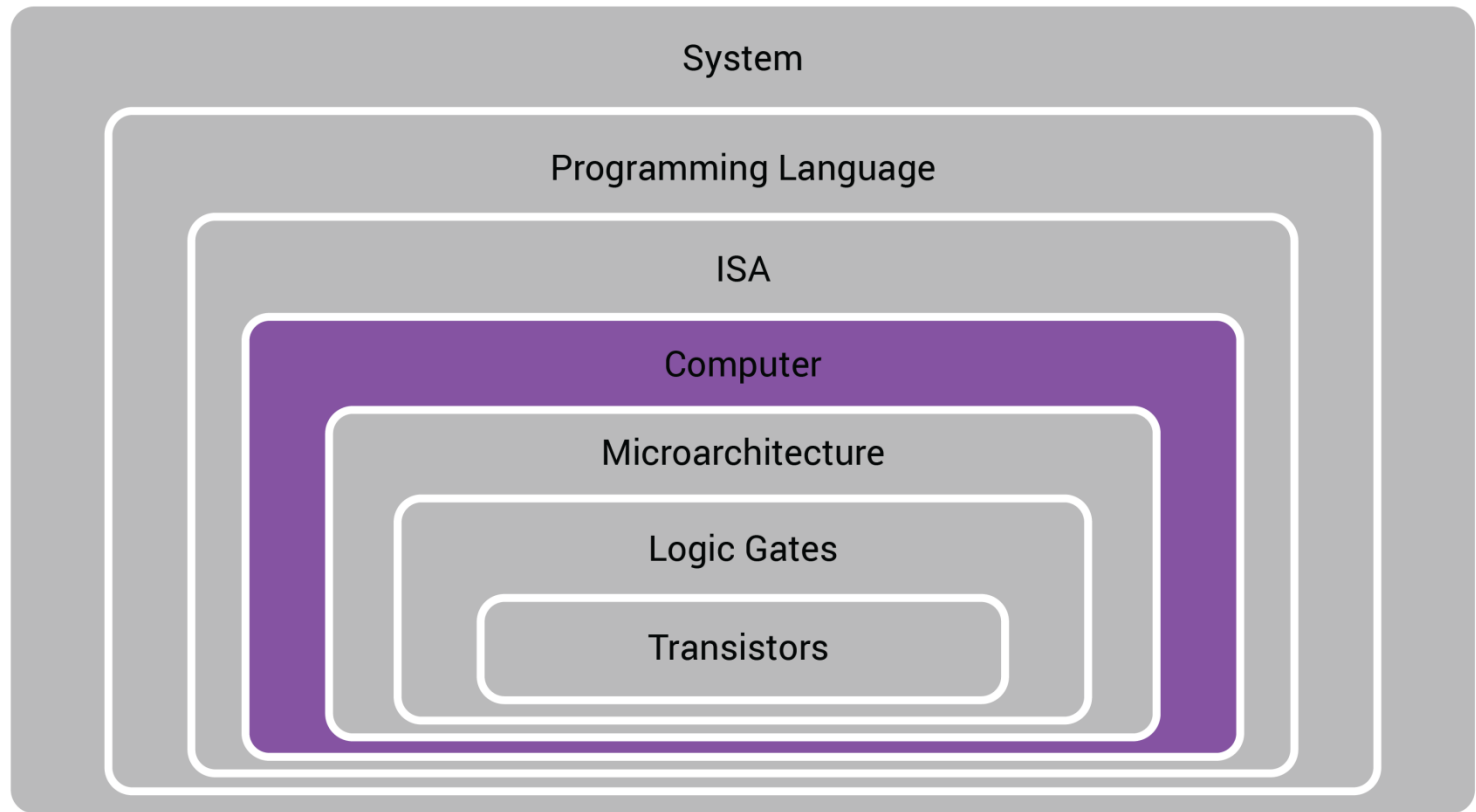

CS 252

Lecture 33; 2015 Dec 7th; Transcribed Lecture Notes

Transistors

Announcements

survey at end of class today
homework 8 due Friday, December 11th

Outline

- state transition diagram (Figure 8.1.5.4 and Figure 8.1.5.5)
- transistors
 - digital behavior
 - simple rules
 - truth table
- book survey

Transistor

3 terminals:

- gates (nothing to do with logical gate)
- source
- drain


Turns on or off depending on the voltage at gate

N-type transistor is turned on when gate input is high (1)


P-type transistor is turned on when gate input is low (0)

Fails in 8 through 10 years

 An inverter with transistors (figure below)




 A 2-input NAND gate with transistors (figure below)




NAND Gate

 A 3-input NAND gate with transistors (figure below)



 A 2-input NOR gate with transistors (figure below)




NOR Gate

Delays (NOT ON EXAM)

having 2 paths means more current and faster
gates delays and transistor delays vary based on inputs

A 2-input XOR gate with transistors

 

Transistor count

Basic elements

NAND2 (2-input NAND gate) takes 4 transistors

NOR2 takes 4 transistors

...

Combined logic gates


FA 1-bit takes 74 transistors

...


...

Total takes 1,326,612 transistors

Transistor physical diagram

 

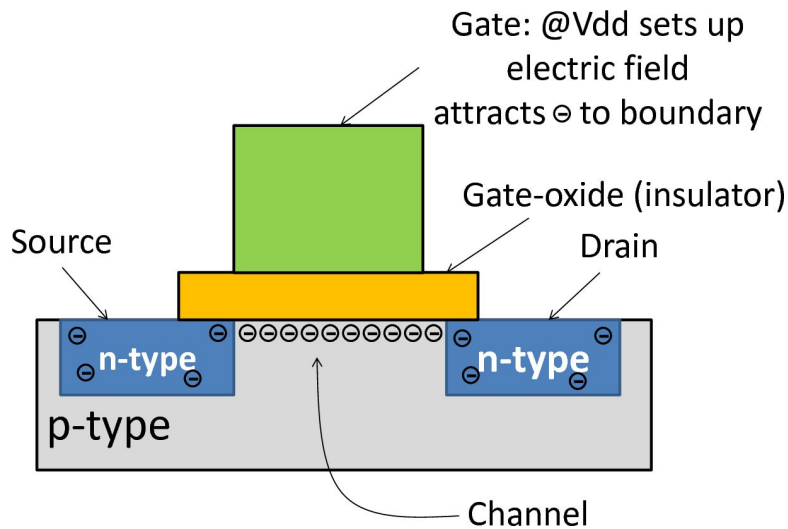gate oxide allows the gate to set up an electrical field for electrons to flow
distance between source to drain is the length and technology node
width is usually twice the length
build faster transistor by increasing width



the insulator (shown in yellow in the figure above) prevents electrons from flowing to gate terminal

transistor acts like a switch, capable of representing 0 and 1, so binary logic

World's first transistor experiments ran from Nov 17th to Dec 23rd in 1947.

Transistor innovations enable technology cadence

finFET uses multiple insulators to create electric field, used for <28nm transistors

Moore's law: an observation made by Gordon Moore that it will be cost effective to double the number of transistors on a single chip every 24 months

In practice, reduce length and width by 1.41X to reduce area by 2X, and reduce thickness

Dennard scaling: while you make a transistor smaller, you can also reduce the supply voltage of the transistor

Power consumption = $CV^2 \text{frequency}$

Bad news: Dennard scaling has ended as we can't simply reduce voltage anymore

Moore's law is also likely ending

Good news: good for this field since it is important to use transistor efficiently to build power-efficient and high-performance computers