

Homework 3 - Due at Lecture on Fri, Feb 24

Primary contact for this homework: Rebecca Lam [rjlam@cs.wisc.edu]


You must do this homework in groups of **two**. Please hand in ONE copy of the homework that lists the **section number**, **full** names (as they appear in Learn@UW) and **UW ID** numbers of all students. You must **staple** all pages of your homework together to receive full credit

Problem 1 (2 points)

- What is the decimal equivalent of the following IEEE floating point number: **0x42F74000**
- What is the 32-bit IEEE floating point representation of the decimal number **-629.375**?

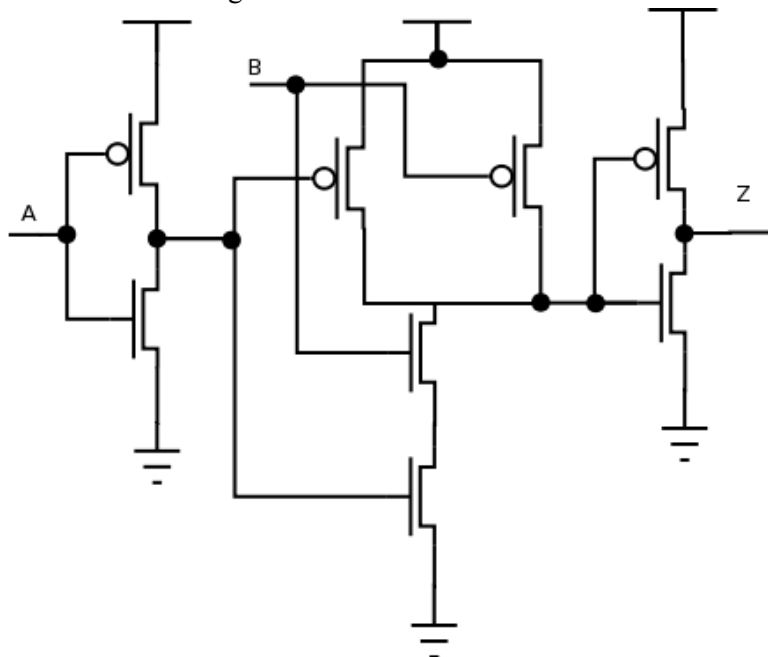Problem 2 (4 points)

Given the following transistor level circuit:



- Fill out the truth table for Z
- What is Z in terms of A and B


Problem 3 (4 points)

Given the logic equation $Z = A \text{ AND NOT(NOT(A) OR B)}$

- Fill out the truth table for Z
- Draw the gate-level circuit for Z using a **minimal** number of 2-input AND/OR gates and NOT gates

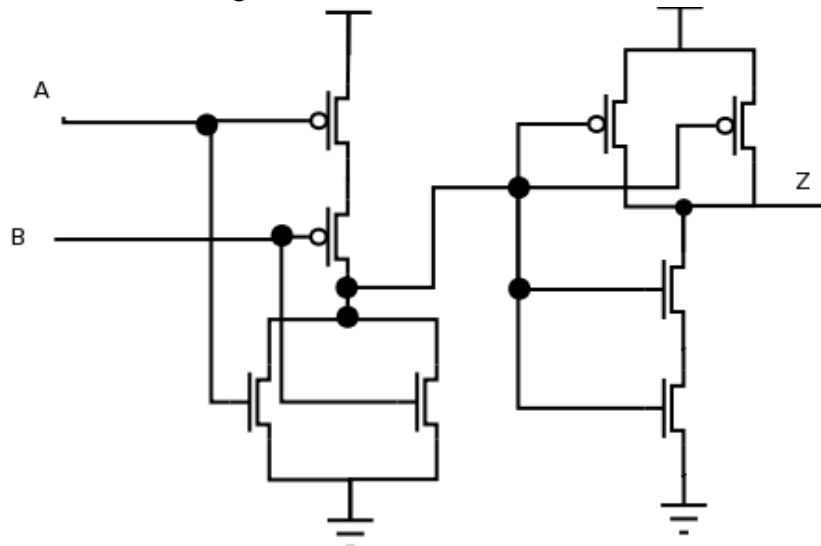Problem 4 (4 points)

Given the following transistor level circuit:



- Fill out the truth table for Z
- What is Z in terms of A and B

Problem 5 (4 points)

Given the logic equation $Z = \text{NOT}(A \text{ OR } (\text{NOT}(A) \text{ AND } B))$

- Fill out the truth table for Z
- Draw the transistor-level circuit for Z using a **minimal** number of 2-input NAND/NOR gates and NOT gates

Problem 6 (6 points)

Suppose A, B, and C are inputs to logic function Z with the following truth table

A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

- Draw the gate-level circuit using NOT gates and 3-input AND and OR gates.
- Convert the circuit of part a into one that uses only NAND gates.

Problem 7 (2 points)

Suppose A, B, and C are inputs to a logic function that outputs $Z = 1$ when the total number of 1s among the inputs is exactly two. Find the logic expression for Z (e.g. $Z = A \text{ AND } B$)

Problem 8 (2 points)

If the number of address bits in memory is increased by 4 bits and the addressability is halved, how is the size of memory affected?