

## Homework 3 - Due at Lecture on Fri, Feb 24

Primary contact for this homework: Rebecca Lam [rjlam@cs.wisc.edu]


You must do this homework in groups of **two**. Please hand in ONE copy of the homework that lists the **section number**, **full names** (as they appear in Learn@UW) and **UW ID** numbers of all students. You must **staple** all pages of your homework together to receive full credit

### Problem 1 (2 points)

- What is the decimal equivalent of the following IEEE floating point number: **0x42F74000**  
**123.625**
- What is the 32-bit IEEE floating point representation of the decimal number **-629.375**?  
**0xC41D5800**
 
### Problem 2 (4 points)

Given the following transistor level circuit:



- Fill out the truth table for Z

A	B	Z
0	0	0
0	1	1
1	0	0
1	1	0

- What is Z in terms of A and B  
 **$Z = \text{NOT}(A) \text{ AND } B$**


**Problem 3 (4 points)**

Given the logic equation  $Z = A \text{ AND NOT( NOT(A) OR B )}$


- a. Fill out the truth table for Z

A	B	Z
0	0	0
0	1	0
1	0	1
1	1	0

- b. Draw the gate-level circuit for Z using 2-input AND/OR gates and NOT gates

 **Problem 4 (4 points)**

Given the following transistor level

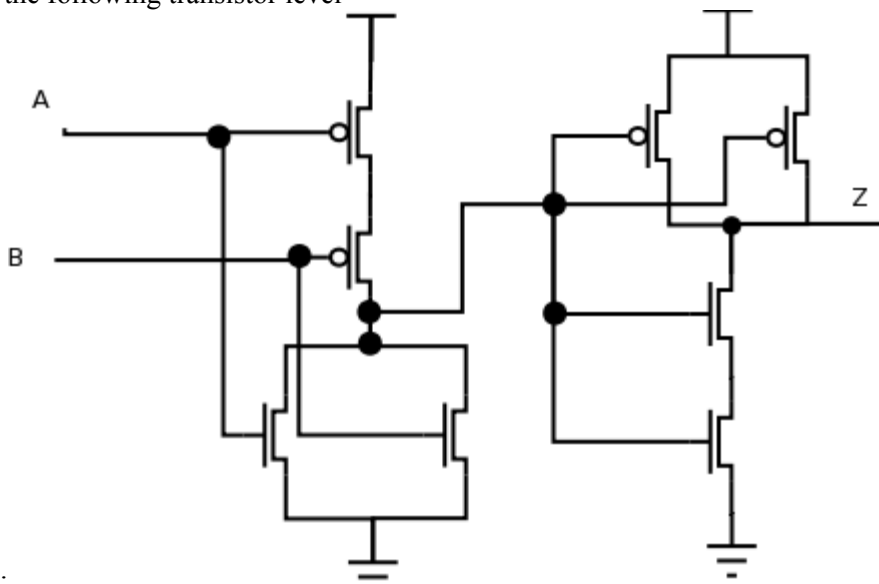

circuit:

- a. Fill out the truth table for Z

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

- b. What is Z in terms of A and B

$$Z = A \text{ OR } B$$


**Problem 5 (4 points)**

Given the logic equation  $Z = \text{NOT}(A \text{ OR } (\text{NOT}(A) \text{ AND } B))$

- a. Fill out the truth table for Z

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

 - b. Draw the transistor-level circuit for Z using a **minimal** number of 2-input NAND/NOR gates and NOT gates




**Problem 6 (6 points)**

Suppose A, B, and C are inputs to logic function Z with the following truth table:


A	B	C	Z
---	---	---	---

0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 
- a. Draw the gate-level circuit using NOT gates and 3-input AND and OR gates.



 - b. Convert the circuit of part a into one that uses only NAND gates.



Where the bubbles =

 

**Problem 7 (2 points)**

Suppose A, B, and C are inputs to a logic function that outputs  $Z = 1$  when the total number of 1s among the inputs is exactly two.

Fill out the truth table for Z:

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Write the logic expression for Z (e.g.  $Z = A \text{ AND } B$ )

$Z = (\text{NOT}(A) \text{ AND } B \text{ AND } C) \text{ OR } (A \text{ AND } \text{NOT}(B) \text{ AND } C) \text{ OR } (A \text{ AND } B \text{ AND } \text{NOT}(C))$

**Problem 8 (2 points)**

If the number of address bits in memory is increased by 4 bits and the addressability is halved, how is the size of memory affected?

Size of memory =  $2^{(\# \text{ address bits})} * \text{addressability}$

Thus, the new size of memory is  $2^4 * 2^{-1}$  times the old size  $\rightarrow 2^3 = 8$  times larger than before