

Homework 4 - Due at Lecture on Monday, March 5

Primary contact for this homework: Kamlesh Prakash [kprakash2@wisc.edu]

You must do this homework in groups of **two**. Please hand in ONE copy of the homework that lists the **section number**, **full** names (as they appear in Learn@UW) and **UW ID** numbers of all students. You must **staple** all pages of your homework together to receive full credit.

Problem 1 (6 points)

A logic circuit has two 2-bit unsigned binary numbers $X[1:0]$ and $Y[1:0]$ as the inputs and it has two 1-bit outputs. One of the outputs is EQUAL and the other is XGTY. The EQUAL output is true when $X[1:0]=Y[1:0]$ and the XGTY output is true when $X[1:0] > Y[1:0]$.

- Write a truth table for these two functions.
- Determine the needed logic equations.
- Draw the Gate level circuit for EQUAL using AND, OR and NOT gates.

a) Truth Table


X[1]	X[0]	Y[1]	Y[0]	EQUAL	XGTY
0	0	0	0	1	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	0	1

b)

$$\text{EQUAL} = \overline{X[1]} \overline{X[0]} \overline{Y[1]} \overline{Y[0]} + \overline{X[1]} X[0] \overline{Y[1]} Y[0] + X[1] \overline{X[0]} \overline{Y[1]} \overline{Y[0]} + X[1] X[0] \overline{Y[1]} Y[0]$$

$$\text{XGTY} = \overline{X[1]} X[0] \overline{Y[1]} \overline{Y[0]} + X[1] \overline{X[0]} \overline{Y[1]} \overline{Y[0]} + X[1] \overline{X[0]} \overline{Y[1]} Y[0] + X[1] X[0] \overline{Y[1]} \overline{Y[0]} + X[1] X[0] \overline{Y[1]} Y[0] + X[1] X[0] Y[1] \overline{Y[0]}$$

C) Gate level circuit for EQUAL:

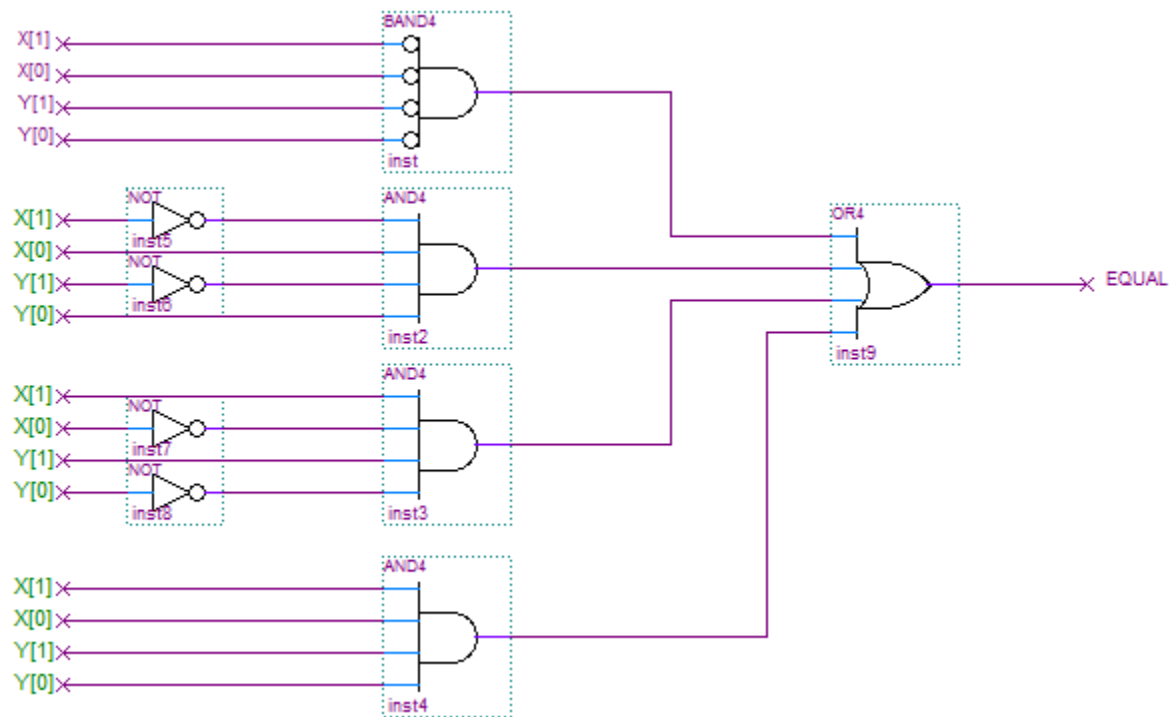

Problem 2 (4 points)


a) Using only one 1-to-2 decoder and one 2-to-1 multiplexer, draw a circuit that always outputs a 0.

b) Using only one 1-to-2 decoder and one 2-to-1 multiplexer, draw a circuit that always outputs a 1.

Note: Inputs cannot be set to constant values (0, 1) and no other gates should be used. Use decoders and mux as blocks.

Hint: Input to the 1-to-2 decoder is some variable “A” and the outputs of the decoder are fed as inputs to the 2-to-1 mux.


a)

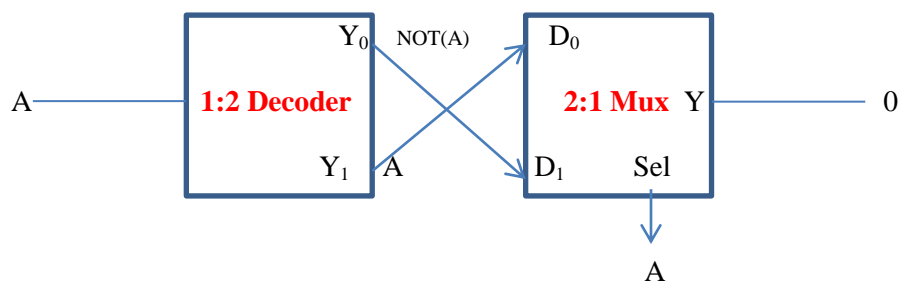

If A=0 => D₀ is selected => Y = A = 0

If A=1 => D₁ is selected => Y = NOT(A) = 0

b)

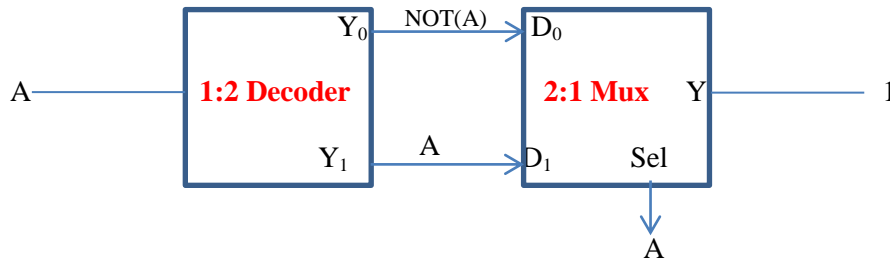

If $A=0 \Rightarrow D_0$ is selected $\Rightarrow Y = \text{NOT}(A) = 1$

If $A=1 \Rightarrow D_1$ is selected $\Rightarrow Y = A = 1$

Problem 3 (3 points)

Given that a certain machine has a clock cycle period of 0.5ns and takes 2 cycles to execute an instruction, find the following:

a) Clock Frequency

$$\text{Clock Frequency} = 1 / \text{clock cycle period} = 1 / 0.5\text{ns} = 2\text{GHz}$$

b) Instructions per second


$$\text{Inst. Per sec} = 1 / (\text{CPI} * \text{clock cycle time}) = 10^9 \text{ Inst/sec}$$

c) Suppose we have a program that has 500 instructions. How long will it take the program to run?

$$\text{Program time} = \text{Inst. per program} / (\text{Inst. per sec}) = 500\text{ns}$$

 Problem 4 (4 points)

Suppose a 64-bit instruction takes the following format:



There are 126 opcodes and 32 registers.

a. What is the minimum number of bits required to represent an OPCODE?

$$126 \text{ Opcodes} < 128 = 2^7 \quad 7 \text{ bits opcode}$$

b. What is the minimum number of bits required to represent a register?

$$32 \text{ registers} = 2^5 \quad 5 \text{ bits}$$

c. What is the maximum number of bits that can be used to represent the immediate field (IMM)?


$$64 - 7 - 5 - 5 = 47 \text{ bits IMM}$$

d. If the immediate (IMM) uses two's complement representation, what is its maximum range of values?

$$\text{IMM ranges from } -(2^{46}) \text{ to } (2^{46}) - 1$$

Problem 5 (6 points)

 - a. Draw a state diagram for a finite state machine that outputs 1 when it recognizes the pattern "100110". For instance, if we have an input of "1001100110" we should get an output of "0000010001". (This means that for the last 6 bits whenever it sees the pattern it outputs 1).




- b. How many flip-flops (storage elements) will be needed to implement the finite state machine designed in your answer to part a?


There are 7 states, hence we require 3 flip flops.

Problem 6 (4 points)

Draw a state machine that should output a 1'b1 if the number of 1's that have appeared on the input (including the current input bit) is a multiple of 2 **or** a multiple of 3.

 **Problem 7 (3 points)**

Prove that a NAND gate, by itself, is logically complete. (Hint: Construct a logic circuit that performs the AND function, a logic circuit that perform the OR function and a logic circuit that perform the NOT function. Use only NAND gates in these three logic circuits.)

 NOT using NAND:**AND using NAND:****OR using NAND:**