



ECE/CS 552: Single Cycle Datapath

© Prof. Mikko Lipasti

Lecture notes based in part on slides created by Mark Hill, David Wood, Guri Sohi, John Shen and Jim Smith


Processor Implementation

- Forecast – heart of 552 – key to project
 - Sequential logic design review (brief)
 - Clock methodology (FSD)
 - Datapath – 1 CPI
 - Single instruction, 2's complement, unsigned
- Next:
 - Control
 - Multiple cycle implementation (information only)
 - Microprogramming
 - Exceptions

Review Sequential Logic


- Logic is combinational if output is solely function of inputs
 - E.g. ALU of previous lecture
- Logic is sequential or “has state” if output function of:
 - Past and current inputs
 - Past inputs remembered in “state”
 - Of course, no magic

Review Sequential Logic

 


- Clock high, $Q = D$, $\bar{Q} = \bar{D}$ after prop. Delay
- Clock low Q , \bar{Q} remain unchanged
 - Level-sensitive latch

Review Sequential Logic

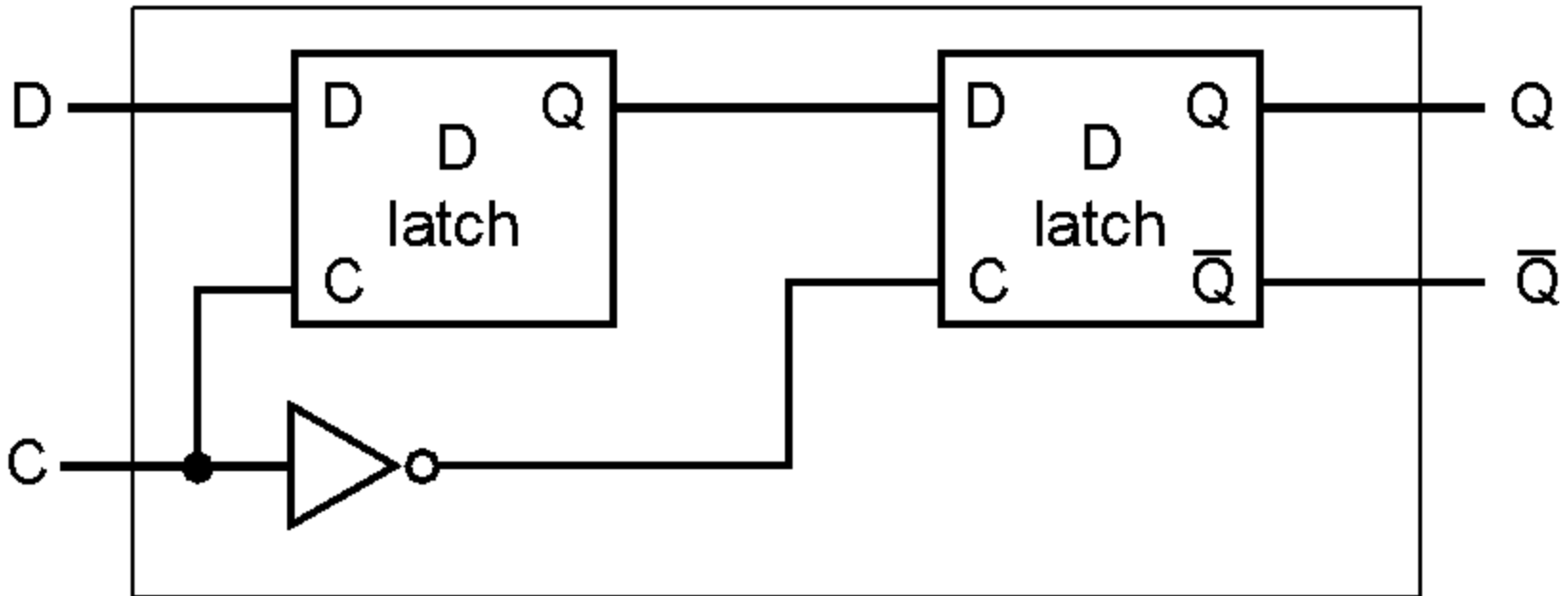

- Master/Slave D flip-flop
 - While clock high, Q_M follows D, but Q_S holds
 - At falling edge Q_M propagates to Q_S
 - *Opaque* except at falling (rising) clock edge

Review Sequential Logic

 


- Why can this fail for a latch?
 - Latch is transparent when clock is high (low)
 - Creates combinational loop
 - Increment evaluates unknown number of times

Clocking Methodology

- Motivation
 - Design data and control without considering clock
- Use Fully Synchronous Design (FSD)
 - Just a convention to simplify design process
 - Restricts design freedom
 - Eliminates complexity, can guarantee timing correctness
 - Not really feasible in real designs: off-chip I/O
 - Even in ECE 554 you will violate FSD


Our Methodology

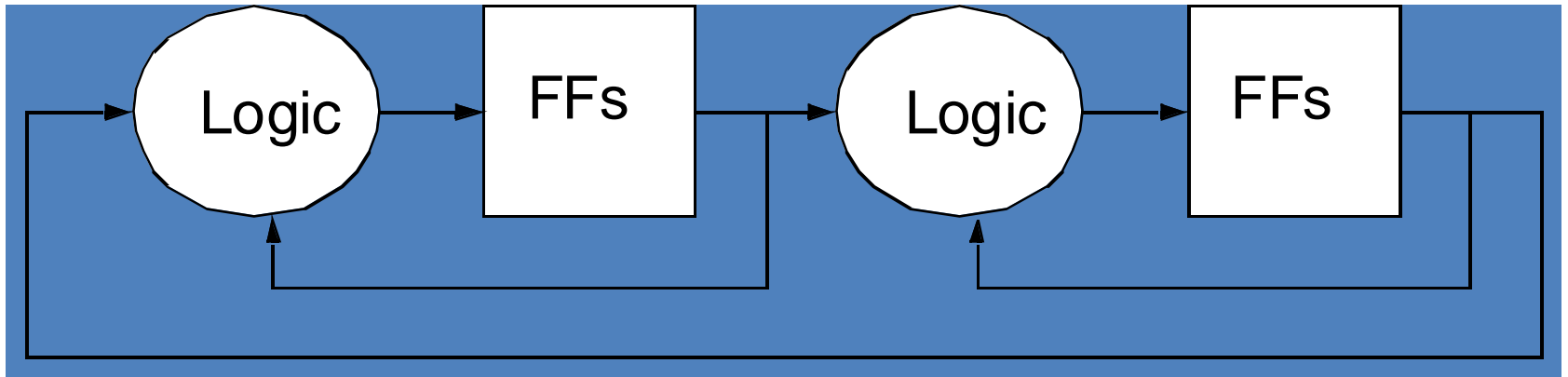- Only flip-flops
- All on the same edge (e.g. falling)
- All with same clock
 - No need to draw clock signals
- All logic finishes in one cycle




Our Methodology, cont'd

 
- No clock gating!
 - Book has bad examples



- Correct design:

 


Delayed Clocks (Gating)

 

- Problem:
 - Some flip-flops receive gated clock late
 - Data signal may violate setup & hold req't

FSD Clocking Rules

 


- T_{clock} = cycle time
- T_{setup} = FF setup time requirement
- T_{hold} = FF hold time requirement
- T_{FF} = FF combinational delay
- T_{comb} = Combinational delay
- FSD Rules:
 - $T_{\text{clock}} > T_{\text{FF}} + T_{\text{combmax}} + T_{\text{setup}}$
 - $T_{\text{FF}} + T_{\text{combmin}} > T_{\text{hold}}$

Datapath – 1 CPI

- Assumption: get whole instruction done in one long cycle
- Instructions:
 - and, lw, sw, & beq
- To do
 - For each instruction type
 - Putting it all together


Fetch Instructions

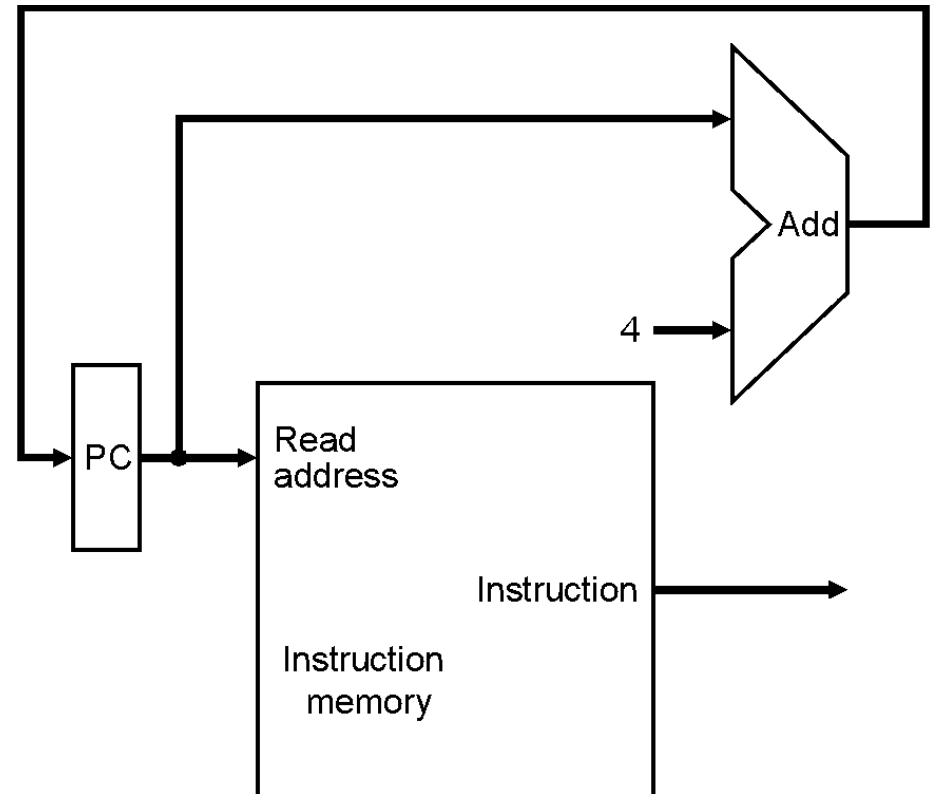- Fetch instruction, then increment PC
 - Same for all types
- Assumes
 - PC updated every cycle
 - No branches or jumps
- After this instruction fetch next one



ALU Instructions

- `and $1, $2, $3 # $1 <= $2 & $3`

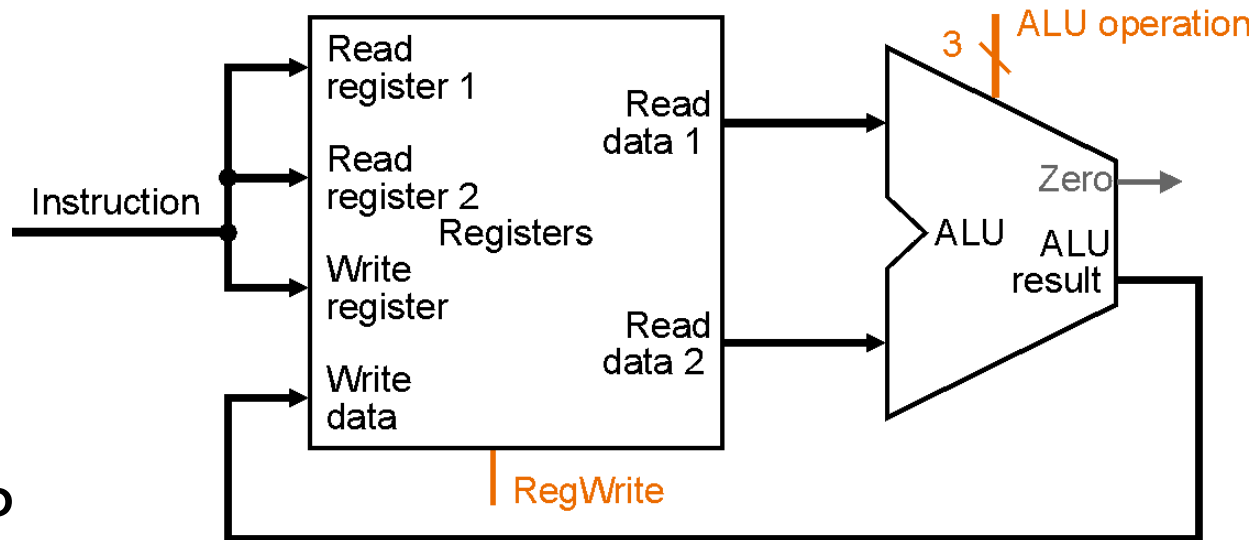


- E.g. MIP

Opcode	rs	rt	rd	shamt	function
6	5	5	5	5	6

Load/Store Instructions

- $lw \$1, immmed(\$2) \# \$1 \leftarrow M[SE(immmed)+\$2]$
- E.g. MIPS I-format:


Opcode	rt	rt	immed
6	5	5	16

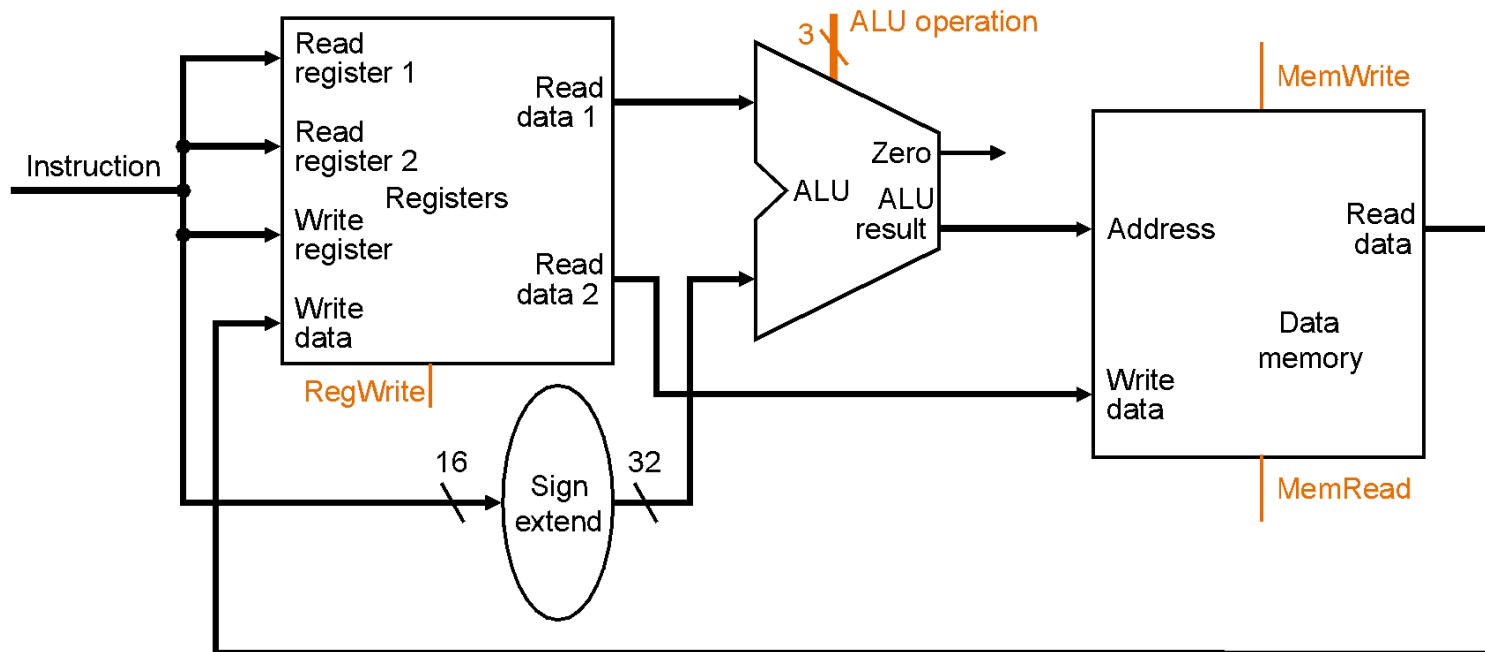


Branch Instructions

- `beq $1, $2, addr` # if ($\$1 == \2) $PC = PC + \text{addr} \ll 2$
- Actually
 - $\text{newPC} = PC + 4$
 - $\text{target} = \text{newPC} + \text{addr} \ll 2$ # in MIPS offset from newPC
 - if ($(\$1 - \$2) == 0$)
 - $PC = \text{target}$
 - else
 - $PC = \text{newPC}$


Branch Instructions

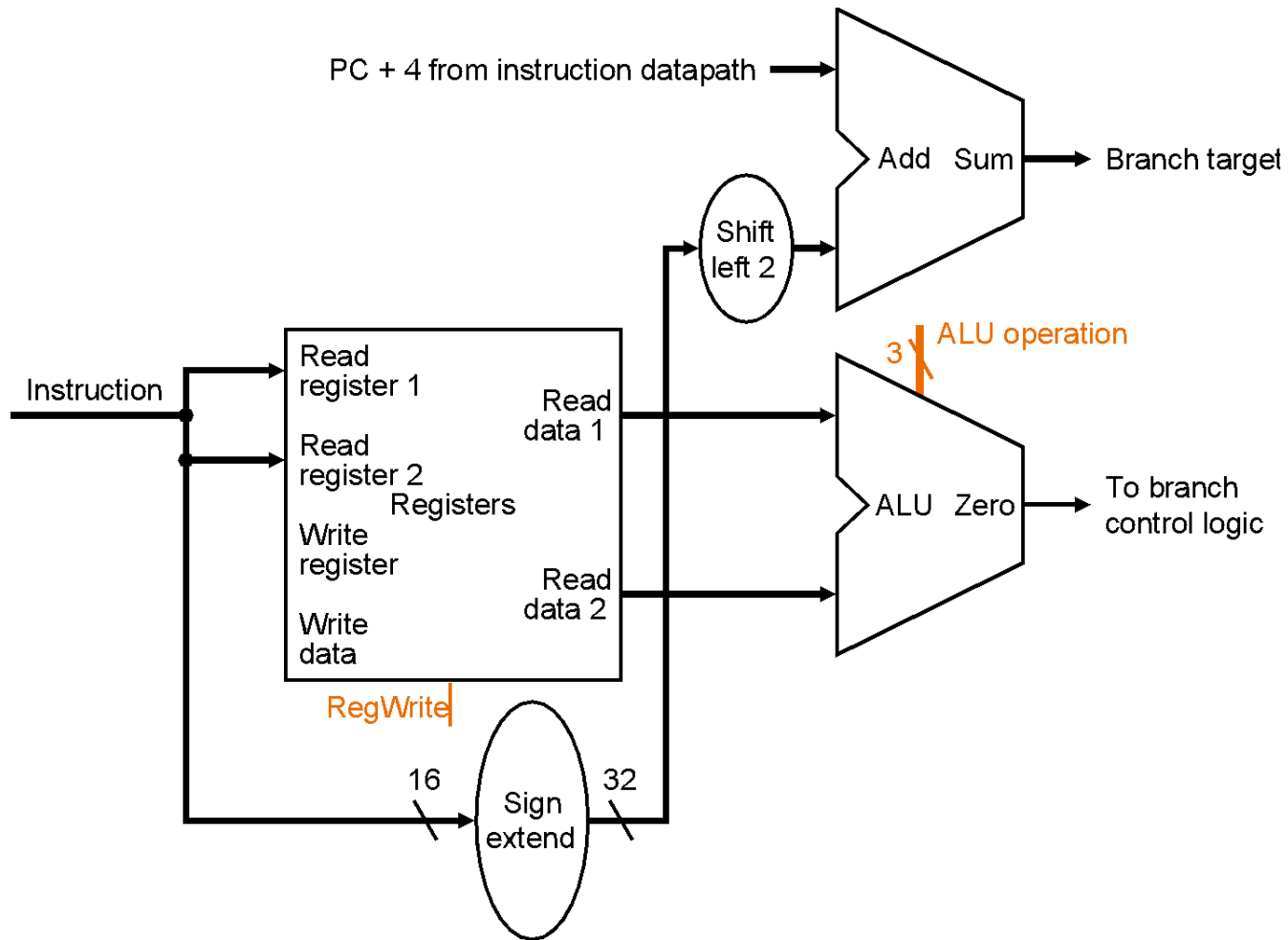

All Together

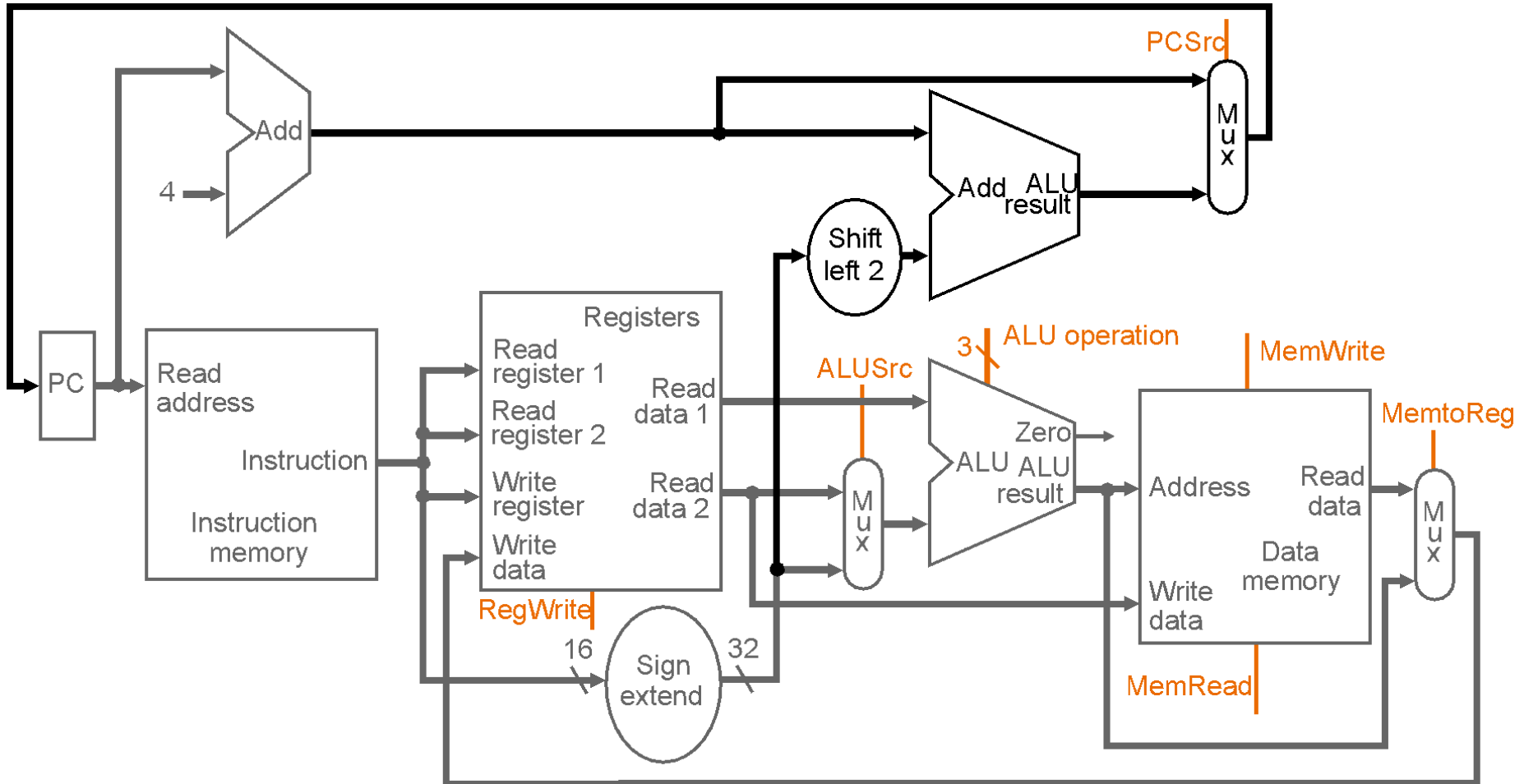

Register File?

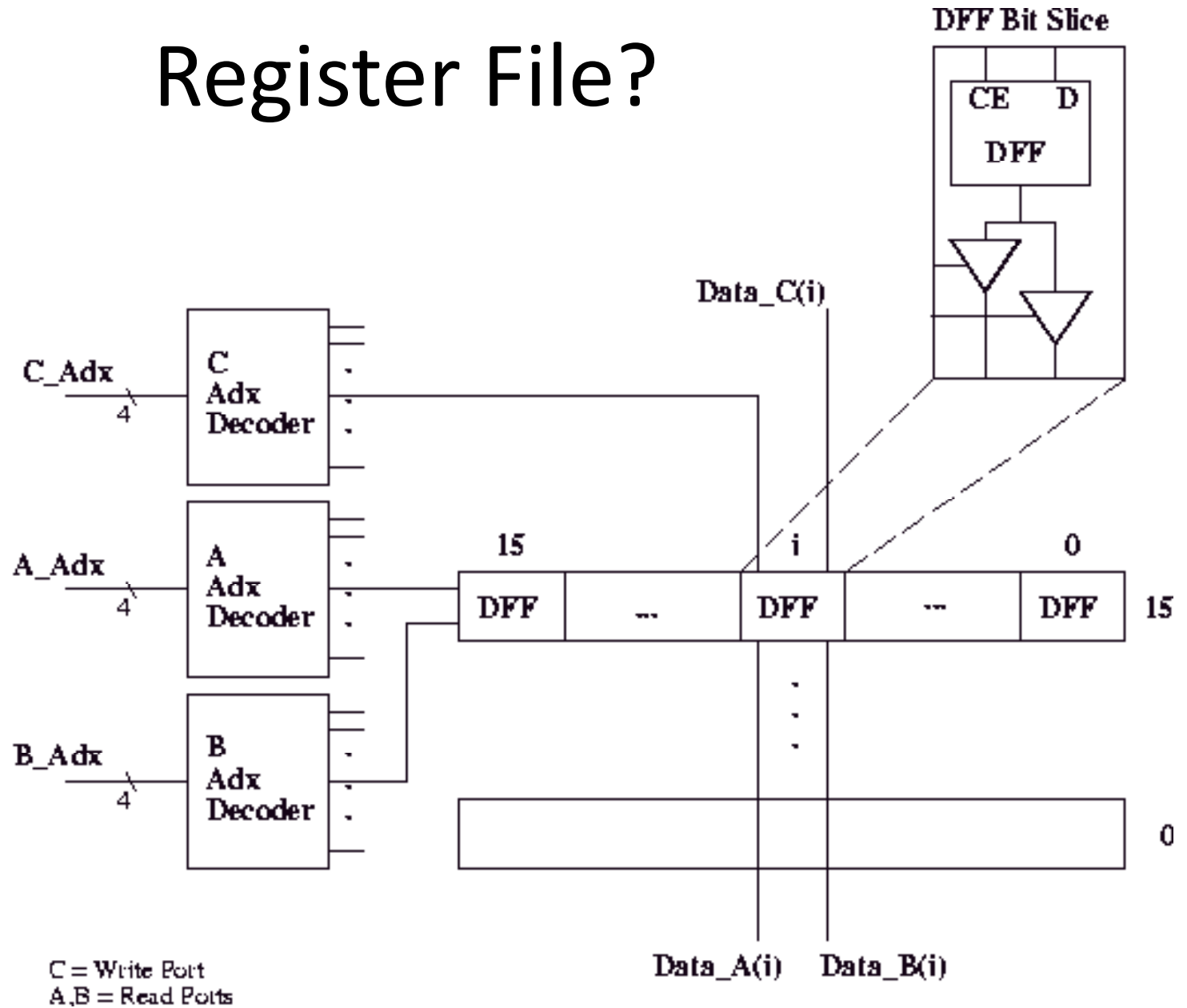

Summary

- Sequential logic design review (brief)
- Clock methodology (FSD)
- Datapath – 1 CPI
 - ALU, lw, sw, beq instructions