

# Verilog For Computer Design

CS/ECE 552  
Karu Sankaralingam

Based on slides from  
Derek Hower (UW-Madison), Andy Phelps (UW-Madison) and  
Prof. Milo Martin(University of Pennsylvania)

CS/ECE 552, Spring 2008

1


## Overview

- Why Verilog?
  - High-level description of Verilog
- Verilog Syntax
  - Primitives
  - Number Representation
  - Modules and instances
  - Wire and Reg Variables
  - Operators
  - Miscellaneous
    - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- Test bench structure
- Case study, Verilog tools and Demo

CS/ECE 552, Spring 2008

2
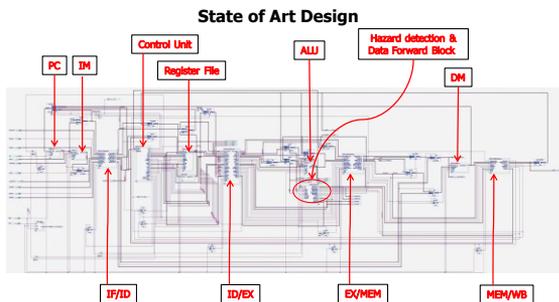
## Why Verilog and why not Manual design?



Do you want to design this Processor manually?

## How To Represent Hardware?

- If you're going to design a computer, you need to write down the design so that:
  - You can read it again later
  - Someone else can read and understand it
  - It can be simulated and verified
  - Even software people may read it!
  - It can be synthesized into specific gates
  - It can be built and shipped and make money(\$\$\$)

CS/ECE 552, Spring 2008

4

## Ways to represent hardware:

- Draw schematics
  - Hand-drawn (Seriously?)
  - Machine-drawn
- Write a netlist – ASCII representation of Interconnect of a schematic
  - Z52BH I1234 (N123, N234, N4567);
- Write primitive Boolean equations
  - $AAA = abc \text{ DEF} + ABC \text{ def}$
- Use a Hardware Description Language (HDL)
  - $\text{assign overflow} = c31 \wedge c32;$

CS/ECE 552, Spring 2008

5

## Hardware Description Languages (HDLs)

- Textual representation of a digital logic design
  - Can represent specific gates, like a netlist, or more abstract logic
- HDLs are not “programming languages”
  - No, really. Even if they look like it, they are not.
  - For many people, a difficult conceptual leap
- Similar development chain
  - Compiler: source code • assembly code • binary machine code
  - Synthesis tool: HDL source • gate-level specification • hardware

CS/ECE 552, Spring 2008

6

## What is an HDL? – “Think hardware”

if(x != 0) vs. if((x <= -1) || (x >= 1))  
What hardware is generated here ?

```
module counter(clk,rst_n,cnt);
  input clk,rst_n;
  output [3:0] cnt;
  reg [3:0] cnt;
  always @(posedge clk) begin
    if (~rst_n)
      cnt = 4'b0000;
    else
      cnt = cnt+1;
  end
endmodule
```


- It looks like a programming language
- It is **NOT** a programming language
  - ✓ It is always critical to recall you are describing hardware
  - ✓ This codes primary purpose is to generate hardware
  - ✓ The hardware this code describes (a counter) can be simulated on a computer. In this secondary use of the language it does act more like a programming language.

7
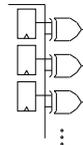
## Why an HDL is not a Programming Language

- In a program, we start at the beginning (e.g. “main”), and we proceed sequentially through the code as directed
- The program represents an algorithm, a step-by-step sequence of actions to solve some problem

```
for (i = 0; i < 10; i = i + 1) {
  if (newPattern == oldPattern[i]) match = i;
}
```
- Hardware is all active at once; there is no starting point



CS/ECE 552, Spring 2008

8

## Why Use an HDL?

- Enables Larger Designs
  - More abstracted than schematics, allows larger designs.
    - ✓ Register Transfer Level Description
    - ✓ Wide data paths (16, 32, or 64 bits wide) can be abstracted to a single vector
    - ✓ Synthesis tool does the bulk of the tedious repetitive work
    - ✓ Work at transistor/gate level for large designs: cumbersome
- Explore larger solution space
  - ✓ Synthesis options can help optimize (power, area, speed)
  - ✓ Synthesis options and coding styles can help examine tradeoffs
    - Speed | Power | area

CS/ECE 552, Spring 2008

## Why use an HDL? (continued)

- Easy to write and edit
- Compact
- Don't have to follow a maze of lines
- Easy to analyze with various tools

### Why not to use an HDL

- You still need to visualize the flow of logic
- A schematic can be a work of art
  - But often isn't! (My first Processor example ☹)

CS/ECE 552, Spring 2008

10

## Other Important HDL Features

- Are highly portable (text)
- Are self-documenting (when commented well)
- Describe multiple levels of abstraction
- Represent parallelism
- Provides many descriptive styles
  - Structural
  - Register Transfer Level (RTL)
  - Behavioral
- Serve as input for synthesis tools

11

## Starting with an example...

```
module fulladd (input A, B, Cin,
               output sum, Cout );

  assign sum = A ^ B ^ Cin;
  assign Cout = (A & B) | (A & Cin) | (B & Cin);
endmodule
```



CS/ECE 552, Spring 2008

12

## Pitfalls of trying to “program” in Verilog

- If you program sequentially, the synthesizer may add a lot of hardware to try to do what you say
  - In last example, need a priority encoder
- If you program in parallel (multiple “always” blocks), you can get non-deterministic execution – Race Condition
  - Which “always” happens first?
- You create lots of state that you didn’t intend
  - if (x == 1) out = 0;
  - if (y == 1) out = 1; // else out retains previous state? R-S latch!
- You don’t realize how much hardware you’re specifying
  - $x = x + 1$  can be a LOT of hardware
- Slight changes may suddenly make your code “blow up”
  - A chip that previously fit suddenly is too large or slow

## Two Roles of HDL and Related Tools

- **#1: Specifying digital logic**
  - Specify the logic that appears in final design
  - Either
    - Translated automatically (called *synthesis*) or
    - Optimized manually (automatically checked for equivalence)
- **#2: Simulating and testing a design**
  - High-speed simulation is crucial for large designs
  - Many HDL *interpreters* optimized for speed
  - Testbench: code to test design, but not part of final design

## Module Styles

- Modules can be specified different ways
  - Structural – connect primitives and modules
  - Dataflow– use continuous assignments
  - Behavioral – use initial and always blocks
- A single module can use more than one of the above 3 coding styles!

What are the differences?

## HDL Constructs

- **Structural** constructs specify actual hardware structures
  - Low-level, direct correspondence to hardware
    - Primitive gates (e.g., and, or, not)
    - Hierarchical structures via modules
  - Analogous to programming software in assembly
- **RTL/Dataflow** constructs specify an operation on bits
  - High-level, more abstract
    - Specified via equations, e.g.,  $out = (a \& b) | c$
- **Behavioral – Describes behavior of the circuit**
  - Always , initial blocks, procedural assignments
- **Not all behavioral constructs are synthesizable**
  - We’ve already talked about the pitfalls of trying to “program”
  - But even some combinational logic won’t synthesize well
  - $out = a \% b$  // modulo operation – what does this synthesize to?

CS/ECE 552, Spring 2008 We will not use: / % > >= < <= >> <<

## Structural Example

```
module majority (major, V1, V2, V3);
```


```
    output major;
    input V1, V2, V3;
```

```
    wire N1, N2, N3;
```

```
    and A0 (N1, V1, V2),
        A1 (N2, V2, V3),
        A2 (N3, V3, V1);
```

```
    or Or0 (major, N1, N2, N3);
```

```
endmodule
```

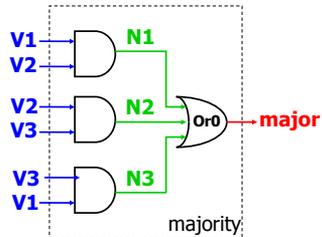

17


## RTL/Dataflow Example

Continuous Assignment Statement

```
module majority (major, V1, V2, V3);
```

```
    output major;
    input V1, V2, V3;
```

```
    assign major = V1 & V2
                 | V2 & V3
                 | V1 & V3;
endmodule
```

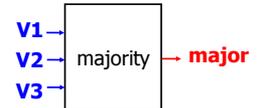

18


## Behavioral Example

```
module majority (major, V1, V2, V3);
```

```
    output reg major;
    input V1, V2, V3;
```

```
    always @(V1, V2, V3) begin
        if (V1 && V2 || V2 && V3
            || V1 && V3) major = 1;
        else major = 0;
    end
```

```
endmodule
```

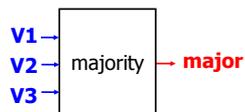

19

## Overview

- Why Verilog?
  - High-level description of Verilog
- Verilog Syntax
  - Primitives
  - Number Representation
  - Modules and instances
  - Wire and Reg Variables
  - Operators
  - Miscellaneous
    - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- Test bench structure
- Case study, Verilog tools and Demo

CS/ECE 552, Spring 2008

20

## Recall: Two Types of Digital Circuits

- **Combinational Logic**
  - Logic without state variables
  - Examples: adders, multiplexers, decoders, encoders
  - No clock involved
  - Not edge-triggered
  - All "inputs" (RHS nets/variables) are triggers
- **Sequential Logic (Details explained later)**
  - Logic with state variables
  - State variables: latches, flip-flops, registers, memories
  - Clocked - Edge-triggered by clock signal
  - State machines, multi-cycle arithmetic, processors
  - Only clock (and possibly reset) appear in trigger list
  - Can include combinational logic that feeds a FF or register

## Verilog Structural Primitives

No declaration; can only be instantiated  
Imp \* - All output ports appear in list before any input ports  
Optional drive strength, delay, name of instance  
Example: **and** N25 (Z, A, B, C); //instance name  
Example: **and** #10 (Z, A, B, X); // delay  
(X, C, D, E); //delay  
/\*Usually better to provide instance name for debugging.\*/

Example: **or** N30 (SET, Q1, AB, N5),  
N41 (N25, ABC, R1);  
Example: **and** #10 N33(Z, A, B, X); // name + delay

## Number Representation

Format: <size><base\_format><number>

### Examples:

```
6'b010_111 gives 010111
8'b0110    gives 0000110
8'b1110    gives 00001110
4'bx01     gives xx01
16'H3AB    gives 0000001110101011
24         gives 0...0011000
5'O36      gives 11100
16'Hx      gives xxxxxxxxxxxxxxxx
8'hz       gives zzzzzzzz
```

## Connections – Module Instantiations

- By position association

```
module 2_to_4_decode (A, E_n, D);
4_to_16_decode DX (X[3:2], W_n, word);
A = X[3:2], E_n = W_n, D = word
```
- By name association (**this is supposed to be used in HW s and Projects**)

```
module 2_to_4_decode (A, E_n, D);
C_2_4_decoder_with_enable DX (.E_n(W_n), .A(X[3:2]),
.D(word));
A = X[3:2], E_n = W_n, D = word
```

## Hierarchical Verilog Example

- Build up more complex modules using simpler modules
- Example: 4-bit wide mux from four 1-bit muxes
  - Again, just "drawing" boxes and wires


```
module mux2to1_4(  
    input [3:0] A,  
    input [3:0] B,  
    input Sel,  
    output [3:0] O );  
  
    mux2to1 mux0 (Sel, A[0], B[0], O[0]);  
    mux2to1 mux1 (Sel, A[1], B[1], O[1]);  
    mux2to1 mux2 (Sel, A[2], B[2], O[2]);  
    mux2to1 mux3 (Sel, A[3], B[3], O[3]);  
endmodule
```

## Variables

- Nets (Also called as wires)
  - ✓ Used for structural connectivity
- Registers
  - ✓ Abstraction of storage (May or may not be real physical storage)
- Properties of Both
  - ✓ Informally called signals
  - ✓ May be either scalar (one bit) or vector (multiple bits)
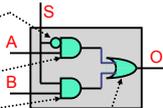
## Verilog Module Example of wires

```
module mux2to1(  
    input S, A, B,  
    output O );  
    wire S_, AnS_, BnS;  
  
    not (S_, S);  
    and (AnS_, A, S_);  
    and (BnS, B, S);  
    or (O, AnS_, BnS);  
endmodule
```



## Net (wire) Examples

- Wire vectors:
  - `wire [7:0] W1; // 8 bits, w1[7] is MSB`
  - Also called "buses"
- Operations
  - Bit select: `W1[3]`
  - Range select: `W1[3:2]`
  - Concatenate:
    - `vec = {x, y, z};`
    - `{carry, sum} = vec[0:1];`
  - e.g., swap high and low-order bytes of 16-bit vector
    - `wire [15:0] w1, w2;`
    - `assign w2 = {w1[7:0], w1[15:8]};`

## Wire and Vector Assignment

- Wire assignment: “continuous assignment”
  - Connect combinational logic block or other wire to wire input
  - **Order of statements not important to Verilog**, executed totally in parallel
  - But order of statements can be important to clarity of thought!
  - When right-hand-side changes, it immediately flows through to left
  - Designated by the keyword **assign**

```
wire c;  
assign c = a | b;  
wire c = a | b;    // same thing
```

## Register Assignment

- A register may be assigned value only within:
    - ✓ a procedural statement
    - ✓ a user-defined sequential primitive
    - ✓ a task, or
    - ✓ a function.
  - A reg object may never be assigned value by:
    - ✓ a primitive gate output
    - ✓ or a continuous assignment
- Examples:
- ```
reg a, b, c;  
reg [15:0] counter, shift_reg;  
reg [8:4] flops;
```

## When to use wire and when reg !

- Wire
  - ✓ Module declaration = Inputs(Yes), Outputs (Yes)
  - ✓ Module instantiation = Connect input and output ports
  - ✓ Must be driven by something, cannot store values
  - ✓ Only legal type on left side of an assign statement
  - ✓ Not allowed on left side of = or <= in an always@ block
  - ✓ Most of the times combinational logic
- Reg
  - ✓ Module instantiation = Input port (Yes) , Output Port (No)
  - ✓ Module declaration = Inputs(No), Outputs (Yes)
  - ✓ Only legal type on left side of = or <= in an always@ block
  - ✓ Only legal type on left side of initial block(test bench)
  - ✓ Not Allowed on left side of an assign statement
  - ✓ Used for both sequential and combinational logic

## Operators

- Operators similar to C or Java
- On wires:
  - & (and), | (or), ~ (not), ^ (xor)
- On vectors:
  - &, |, ~, ^ (bit-wise operation on all wires in vector)
    - E.g., assign vec1 = vec2 & vec3;
  - &, |, ^ (reduction on the vector)
    - E.g., assign wire1 = | vec1;
  - Even ==, != (comparisons)

Can be arbitrarily nested: (a & ~b) | c

## Conditional Operator

- Verilog supports the ?: conditional operator
  - Just like in C
  - But much more common in Verilog

- Examples:

```
assign out = S ? B : A;
```

```
assign out = sel == 2'b00 ? a :  
           sel == 2'b01 ? b :  
           sel == 2'b10 ? c :  
           sel == 2'b11 ? d : 1'b0;
```

- What do these do?

## Overview

- Why Verilog?
  - High-level description of Verilog
- Verilog Syntax
  - Primitives
  - Number Representation
  - Modules and instances
  - Wire and Reg Variables
  - Operators
  - Miscellaneous
    - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- Test bench structure
- Case study, Verilog tools and Demo

## Parameters

- Allow per-instantiation module parameters
  - Use "parameter" statement
- modname #(10, 20, 30) instname(in1, out1);
- Example:

```
module mux2to1_N(sel, A, B, O);  
    parameter N = 1;  
    input [N-1:0] A;  
    input [N-1:0] B;  
    input sel;  
    output [N-1:0] O;  
    mux2to1 mux0[N-1:0] (sel, A, B, O);  
endmodule  
...  
Mux2to1_N #(4) mux1 (S, in1, in2, out)
```

## Verilog Pre-Processor

- Like the C pre-processor
  - But uses ` (back-tick) instead of #
  - Constants: `define
    - No parameterized macros
    - Use ` before expanding constant macro
  - Conditional compilation: `ifdef, `endif
  - File inclusion: `include
- Parameter vs `define
  - Parameter only for "per instance" constants
  - `define for "global" constants

## Common Errors

- Tools are from a less gentle time
  - More like C, less like Java
  - Assume that you mean what you say
- Common errors:
  - Not assigning a wire a value
  - Assigning a wire a value more than once
- Avoid names such as:
  - clock, power, pwr, ground, gnd, vdd, vcc, init, reset
  - Some of these are "special" and will silently cause errors
  - We will use "clk" and "rst", but only for their intended uses

## Verilog in Project / Homework

- Use the primitive modules and other basic modules given in course webpage for your 'design'
- Follow the Verilog rules only for Design
- You are free to use your own test bench
- Only use the specified Verilog Keywords, allowed operators
- Go through the usage examples
  
- Ask TA s if you are experiencing any difficulty in following these guidelines.

## Non-binary Hardware Values

- A hardware signal can have four values
  - 0, 1
  - X: don't know, don't care
  - Z: high-impedance (no current flowing)
- Two meanings of "X"
  - Simulator indicating an unknown state
  - Or: You telling synthesis tool you don't care
    - Synthesis tool makes the most convenient circuit (fast, small)
    - Use with care, leads to synthesis dependent operation
- Uses for "z"
  - Tri-state devices drive a zero, one, or nothing (z)
  - Many tri-states drive the same wire, all but one must be "z"
    - Example: multiplexer

## Case Statements

```
case (<expr>)
  <match-constant1>:<stmt>
  <match-constant2>:<stmt>
  <match-constant3>,<match-constant4>:<stmt>
  default: <stmt>
endcase
```

## Case Statements

- Useful to make big muxes
- Very useful for “next-state” logic
- But they are easy to abuse
- If you don’t set a value, it retains its previous state
  - Which is a latch!
- We will allow case statements, but with some severe restrictions:
  - Every value is set in every case
  - Every possible combination of select inputs must be covered
  - Each case lives in its own “always” block, sensitive to changes in all of its input signals
  - This is our only use of “always” blocks

## Different types of Case statements

Verilog has three types of case statements:

**case**, **casex**, and **casez**

- Performs bitwise match of expression and case item
  - Both must have same bitwidth to match!
- **case**
  - Can detect **x** and **z**! (good for testbenches)
- **casez**
  - Uses **z** and **?** as “don’t care” bits in case items and expression
- **casex**
  - Uses **x**, **z**, and **?** as “don’t care” bits in case items and expression

## Case Statement Example

```
always @*
  casex ({goBack, currentState, inputA, inputB})
    6'b1_??_?_? : begin out = 0; newState = 3'b000; err=0; end
    6'b0_000_0_? : begin out = 0; newState = 3'b000; err=0; end
    6'b0_000_1_? : begin out = 0; newState = 3'b001; err=0; end
    6'b0_001_1_? : begin out = 0; newState = 3'b001; err=0; end
    6'b0_001_0_0 : begin out = 0; newState = 3'b010; err=0; end
    6'b0_001_0_1 : begin out = 0; newState = 3'b011; err=0; end
    6'b0_010_?_0 : begin out = 0; newState = 3'b010; err=0; end
    6'b0_010_?_1 : begin out = 0; newState = 3'b011; err=0; end
    6'b0_011_?_1 : begin out = 0; newState = 3'b011; err=0; end
    6'b0_011_?_0 : begin out = 0; newState = 3'b100; err=0; end
    6'b0_100_?_? : begin out = 1; newState = 3'b000; err=0; end
    6'b0_101_?_? : begin out = 0; newState = 3'b000; err=1; end
    6'b0_110_?_? : begin out = 0; newState = 3'b000; err=1; end
    6'b0_111_?_? : begin out = 0; newState = 3'b000; err=1; end
  default: begin out = 0; newState = 3'b000; err=1; end
endcase
```

## What happens if it's wrong?

Here are our rules:

- A case statement should always have a default
- Hitting this default is an error
- Every module has an “err” output
- Can be used for other checks, like illegal inputs
- OR together all “err” signals -- bring “err” all the way to top
- Our clock/reset module will print a message if err == 1

## System tasks

- Start with \$
- For output:

```
$display(<fmtstring><, signal>*);
```

```
$fdisplay (<fhandle>, <fmtstring><, signal>*);
```

  - Signal printf/fprintf

```
$monitor (<fmtstring><, signal>*);
```

  - Non-procedural printf, prints out when a signal changes

```
$dumpvars (1<, signal>*);
```

  - Similar to monitor
  - VCD format for waveform viewing (gtkwave)
  - Output is in dumpfile.vcd

## More System Tasks

- ```
$time
```
- Simulator's internal clock (64-bit unsigned)
  - Can be used as both integer and auto-formatted string
- ```
$finish
```
- Terminate simulation
- ```
$stop
```
- Pause simulation and debug
- ```
$readmemh (<fname>, <mem>, <start>, <end>);
```
- ```
$writememh (<fname>, <mem>, <start>, <end>);
```
- Load contents of ASCII file to memory array (and vice versa)
  - Parameters <start>, <end> are optional
  - Useful for loading initial images, dumping final images

## Overview

- Why Verilog?
  - High-level description of Verilog
- Verilog Syntax
  - Primitives
  - Number Representation
  - Modules and instances
  - Wire and Reg Variables
  - Operators
  - Miscellaneous
    - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- Test bench structure
- Case study, Verilog tools and Demo


## Sequential Logic in Verilog

Use the Homework Modules provided-  
Instantiate the dff module given for all FFs

```
module dff
(q, d, clk, rst);


output q;
input d;
input clk;
input rst;
reg state;

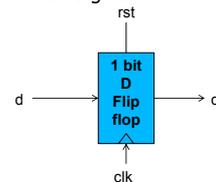assign #(1) q = state;
always @(posedge clk) begin
state = rst? 0 : d;
end
endmodule
```


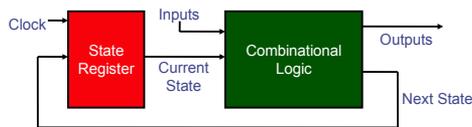
## Designing Sequential Logic

- CS/ECE 552 design rule: separate combinational logic from sequential state elements in lowest-level modules
  - Not enforced by Verilog, but a very good idea
  - Possible exceptions: counters, shift registers
- We'll give you a 1-bit flip-flop module (see previous slide)
  - Edge-triggered, not a latch
  - Use it to build n-bit register, registers with "load" inputs, etc.
- Example use: state machine



CS/ECE 552, Spring 2008

49

## Clocks Signals

- Clocks signals are not normal signals
- Travel on dedicated "clock" wires
  - Reach all parts of the chip
  - Special "low-skew" routing
- Ramifications:
  - Never do logic operations on the clocks
  - If you want to add a "write enable" to a flip-flop:
    - Use a mux to route the old value back into it
    - Do not just "and" the write-enable signal with the clock!
- Messing with the clock can cause errors
  - Often can only be found using timing simulation

CS/ECE 552, Spring 2008

50

## Overview

- Why Verilog?
  - High-level description of Verilog
- Verilog Syntax
  - Primitives
  - Number Representation
  - Modules and instances
  - Wire and Reg Variables
  - Operators
  - Miscellaneous
    - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- **Test bench structure**
- **Case study, Verilog tools and Demo**


CS/ECE 552, Spring 2008

51

## Verilog Simulation using Modelsim


- Testbench
- Setting up the mentor environment
- Using modelsim (simple example: 4 bit register)
  - Fixing compile errors
  - Debugging functional errors (with waveforms)
- Shortcut! Use wsruntime.pl
- Vcheck – check for illegal constructs
- Pattern/Sequence detector

## Testbench – variant 1

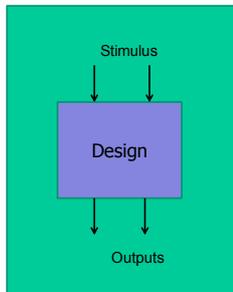


And "visually" inspect the outputs

## Testbench – variant 2

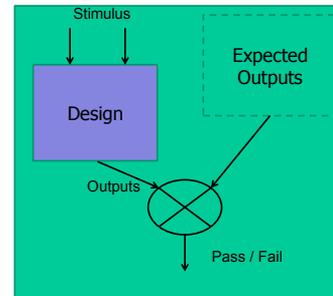
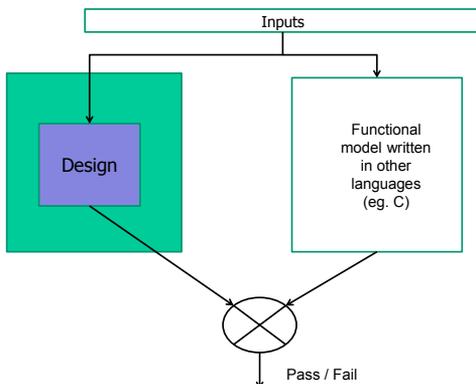
## Sophisticated Test Environment (To be used in the course project)



## Setting up the mentor environment

- Edit `.bashrc` or `.bashrc.local`
- Create mentor directory in home area, copy over `.location` and edit it
- Find detailed instructions at:

„Sidebar of Course home page -> "Tools" -> "Getting started with Mentor"

<http://pages.cs.wisc.edu/~karu/courses/cs552/spring2013/wiki/index.php/Main/GettingStartedWithMentor>

## Using modelsim (simple example: 4 bit register)

- Interfaces:


- What we are going to build:

```
module reg_4bit(out, in, wr_en, clk, rst)
```

- What we have to start with:

```
module dff (q, d, clk, rst);
```
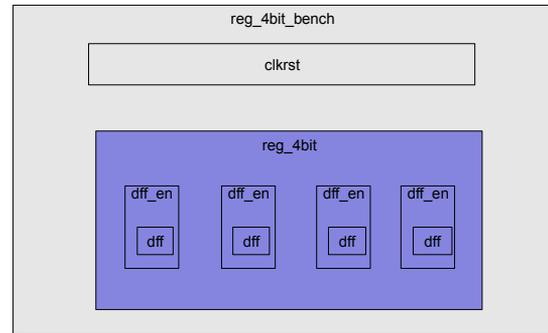
## Using modelsim (simple example: 4 bit register)



## Shortcut! Use wsruntime.pl

- `wsruntime.pl -wave reg4bit_bench *.v`

- Find detailed instructions at:

• Sidebar of Course home page -> "Command-line Simulation"

• <http://pages.cs.wisc.edu/~karu/courses/cs552/spring2013/wiki/index.php/Main/Command-lineVerilogSimulationTutorial>

## Vcheck – check for illegal constructs

- Limited subset of verilog constructs allowed in CS552

- **Restriction is only for the "Design"**

- **Testbench can use any valid verilog syntax**


- 3 ways to run the checks. Find detailed instructions at:

• Sidebar of Course home page -> "Tools" -> "Verilog Rules Check"

• <http://pages.cs.wisc.edu/~karu/courses/cs552/spring2013/wiki/index.php/Main/VerilogRulesCheck>

## Pattern/Sequence detector

Pattern: 1101

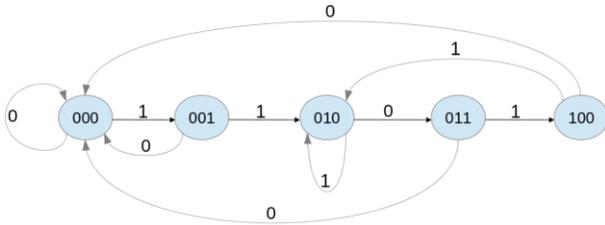

## Pattern/Sequence detector

- Use binary numbers to encode state
- Current state: 4 bit binary number:  $Q_2 Q_1 Q_0$
- Next state: 4 bit binary number:  $Q_{2_n} Q_{1_n} Q_{0_n}$

## Pattern/Sequence detector


Q2	Q1	Q0	InA	Q2 <sub>n</sub>	Q1 <sub>n</sub>	Q0 <sub>n</sub>
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	0
1	0	0	1	0	1	0
X	X	X	X	X	X	X

- $Out = f(Q_2, Q_1, Q_0)$
- $Q_{2_n} = f(Q_2, Q_1, Q_0, InA)$
- $Q_{1_n} = f(Q_2, Q_1, Q_0, InA)$
- $Q_{0_n} = f(Q_2, Q_1, Q_0, InA)$

- $Out = Q_2$
- $Q_{2_n} = Q_2' Q_1 Q_0 InA$
- $Q_{1_n} = Q_2' Q_1' Q_0 InA + Q_2' Q_1 Q_0' InA' + Q_2' Q_1 Q_0 InA + Q_2 Q_1' Q_0' InA$
- $Q_{0_n} = Q_2' Q_1' Q_0' InA + Q_2' Q_1 Q_0' InA'$
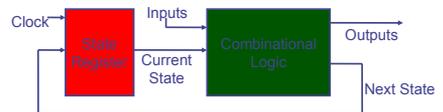
## Pattern/Sequence detector

- A sequence detector is sequential logic
- Design Rule: separate combinational logic from sequential sate elements in lowest-level modules
- We will give you a 1-bit flip-flop module to hold state and a clock/reset generator
- See the course web site



## Pattern/Sequence detector

---

- Two ways to implement the “Combinational logic” block.
  - 1) Implement the state equations using verilog bitwise logical operators
  - 2) Use a case statement to specify the state transitions