

U. Wisconsin CS/ECE 552

Introduction to Computer Architecture

Prof. Karu Sankaralingam

Arithmetic Part 1 (Chapter 3.1-3.5, B.5-B.6)

www.cs.wisc.edu/~karu/courses/cs552/

Slides combined and enhanced by Karu Sankaralingam from work by Falsafi, Hill, Marculescu, Nagle, Patterson, Roth, Rutenbar, Schmidt, Shen, Sohi, Sorin, Thottethodi, Vijaykumar, & Wood

Outline

- Representing Integers
 - Unsigned, 2's Complement
- Addition and subtraction
- Add/Sub ALU
 - full adder, ripple carry, subtraction,
- Carry lookahead
- Overflow
- Barrel shifter
- Defer: multiplication, division, floating-point

Unsigned Integers

- Recall:
 - n bits give rise to 2^n combinations
 - let us call a string of 32 bits as “ $b_{31} b_{30} \dots b_3 b_2 b_1 b_0$ ”
- $f(b_{31} \dots b_0) = b_{31} \times 2^{31} + \dots + b_1 \times 2 + b_0 \times 2^0$
- Treat as normal binary number
 - e.g., 0 . . . 011010101
 - $= 1 \times 2^7 + 1 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$
 - $= 128 + 64 + 16 + 4 + 1 = 213$
- $\max f(111 \dots 11) = 2^{32} - 1 = 4, 294, 967, 295$
- $\min f(000 \dots 00) = 0$
- range $[0, 2^{32}-1] \Rightarrow \# \text{ values } (2^{32} - 1) - 0 + 1 = 2^{32}$

More Generally

- Bits have no inherent meaning
- Conventions define meaning
 - E.g., represent negative integers?
 - Seek circuit simplicity & speed
- n bits can represent finite possibilities: 2^n
 - Integers countably infinite $\rightarrow$ overflow
 - Reals uncountably infinite $\rightarrow$ overflow, underflow, imprecise

Integer Representation

- Sign Magnitude: One's Complement Two's Complement

000 = +0	000 = +0	000 = +0
001 = +1	001 = +1	001 = +1
010 = +2	010 = +2	010 = +2
011 = +3	011 = +3	011 = +3
100 = -0	100 = -3	100 = -4
101 = -1	101 = -2	101 = -3
110 = -2	110 = -1	110 = -2
111 = -3	111 = -0	111 = -1
- Balance, number of zeros, **ease of arithmetic**

Two's Complement Integers

- $f(b_{31} b_{30} \dots b_1 b_0) = -b_{31} \times 2^{31} + \dots + b_1 \times 2 + b_0 \times 2^0$
 - $\max f(0111 \dots 11) = 2^{31} - 1 = 2147483647$
 - $\min f(100 \dots 00) = -2^{31} = -2147483648$
(asymmetric)
- range $[-2^{31}, 2^{31}-1] \Rightarrow \# \text{values } (2^{31}-1 - -2^{31} + 1) = 2^{32}$
- E.g., -6
- $000 \dots 0110 \rightarrow 111 \dots 1001 + 1 \rightarrow 111 \dots 1010$

Two's Complement Operations

- Negating a two's complement number: **invert all bits and add 1**

$$- 1010 \rightarrow 0101 + 1 = 0110$$

$$- 0110 \rightarrow 1001 + 1 = 1010$$

- Converting n bit numbers into numbers with more than n bits:

- copy the most significant bit (the sign bit)

$$0010 \rightarrow 0000 \ 0010$$

$$1010 \rightarrow 1111 \ 1010$$

- Called "**sign extension**"

Sign extension

- Consider representation of -2:

3bit (decimal)	2-bit (decimal)
011 (+3)	
010 (+2)	
001 (+1)	01 (+1)
000 (0)	00 (0)
111 (-1)	11 (-1)
110 (-2)	10 (-2)
101 (-3)	
100 (-4)	

Addition and Subtraction

- Similar to decimal (carry/borrow twos instead of tens)
- Identical operation for signed and unsigned

– E.g. **Unsigned** vs **Signed**

0011	3	3
1010	10	-6
1101	13	-3

Interesting cases

- Show computation in 4-bit 2's complement representation

$$4 + 4$$

$$(-4) + (-4)$$

- Overflow: later


ALU bit-slice

- Bit-wise operation

- and, or, add



- Full adder?

- Sub?

 


Full adder

  - Three inputs and two outputs
- $C_{out}, s = F(a, b, C_{in})$
 - C_{out} : only if **at least two** inputs are set
 - S : only if **exactly one** input or **all three** inputs are set
- Logic?




Subtract

 - $A - B = A + (-B)$
 - form two complement by invert and add one



Ripple-carry adder

 

Problem : Slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
 - Delay = 32x CP(Fast adder) + XOR
- Is there more than one way to do addition?
 - two extremes: ripple carry and sum-of-products
 - Flatten expressions to two levels

Can you see the ripple? How could you get rid of it?

$$c_1 = b_0c_0 + a_0c_0 + a_0b_0$$

$$c_2 = b_1c_1 + a_1c_1 + a_1b_1$$

$$c_3 = b_2c_2 + a_2c_2 + a_2b_2$$

$$c_4 = b_3c_3 + a_3c_3 + a_3b_3$$

$$c_2 = b_1(b_0c_0 + a_0c_0 + a_0b_0) + a_1(b_0c_0 + a_0c_0 + a_0b_0) + a_1b_1$$

$$c_2 = b_1b_0c_0 + b_1a_0c_0 + b_1a_0b_0 + a_1b_0c_0 + a_1a_0c_0 + a_1a_0b_0 + a_1b_1$$


$$c_3 = ?$$

$$c_{31} = ? \text{ Not feasible! Why? Exponential fanin}$$


Carry look-ahead

- An approach in-between our two extremes
- Motivation:
 - If we didn't know the value of carry-in, what could we do?
 - When would we always **generate** a carry?
 - $g_i = a_i b_i$
 - When would we **propagate** the carry?
 - $p_i = a_i + b_i$
- Did we get rid of the ripple?

CLA: Plumbing Analogy

 


Carry-lookahead adder

 

Carry-Lookahead Adder


- Waitamminute!
 - Nothing has changed
 - Fanin problems if you flatten!
 - Linear fanin, not exponential
 - Ripple problem if you don't!
- Enables divide-and-conquer
- Figure out Generate and Propagate for 4-bits together
- Compute hierarchically

Carry Lookahead adder

 


- Height of tree = $O(\lg(n))$
- 32 bit addition : $k * \lg(32) = k * 5$

Block level signals

 

Cascaded CLA

 

Carry-Lookahead Adder

- Hierarchy

- $G_{i,k} = G_{j+1,k} + P_{j+1,k} * G_{i,j} \quad (\text{assume } i < j + 1 < k)$

- $P_{i,k} = P_{i,j} * P_{j+1,k}$

- $G_{0,7} = G_{4,7} + P_{4,7} * G_{0,3}$

- $P_{0,7} = P_{0,3} * P_{4,7}$

- $G_{8,15} = G_{12,15} + P_{12,15} * G_{8,11}$


- $P_{8,15} = P_{8,11} * P_{12,15}$

- $G_{0,15} = G_{8,15} + P_{8,15} * G_{0,7}$

- $P_{0,15} = P_{0,7} * P_{8,15}$


(23)

Computing G's and P's

 

- Parallel algorithm in hardware


Computing C's

 


- Different tree.
- Note propagation order
- Worth spending some time to think about the intricacies

Carry-selection: Guess

$$CP(2n) = 2 * CP(n)$$

 

$$CP(2n) = CP(n) + CP(\text{mux})$$

 

Overflow

Decimal	Binary	Decimal	2's Complement
0	0000	0	0000
1	0001	-1	1111
2	0010	-2	1110
3	0011	-3	1101
4	0100	-4	1100
5	0101	-5	1011
6	0110	-6	1010
7	0111	-7	1001
		-8	1000



- **Examples: $7 + 3 = 10$ but ...**
 $-4 - 5 = -9$ but ...

$$\begin{array}{r}
 \begin{array}{cccccc}
 0 & 1 & 1 & 1 & & \\
 & \nearrow & \nearrow & \nearrow & \nearrow & \\
 & 0 & 1 & 1 & 1 & 7 \\
 + & 0 & 0 & 1 & 1 & 3 \\
 \hline
 & 1 & 0 & 1 & 0 & \underline{-6}
 \end{array}
 \end{array}$$

$$\begin{array}{r}
 \begin{array}{cccccc}
 1 & & & & & \\
 & \nearrow & & & & \\
 & 1 & 1 & 0 & 0 & -4 \\
 + & 1 & 0 & 1 & 1 & -5 \\
 \hline
 & 0 & 1 & 1 & 1 & \underline{7}
 \end{array}
 \end{array}$$


Overflow

- Overflow: the result is too large (or too small) to represent properly
 - Example: $-8 < \text{4-bit binary number} \leq 7$
- When adding operands with different signs, overflow cannot occur!
- Overflow occurs when adding:
 - 2 positive numbers and the sum is negative
 - 2 negative numbers and the sum is positive
- On your own: Prove you can detect overflow by:
 - Carry into MSB $\oplus$ Carry out of MSB

  


Overflow detection

 - Carry into MSB $\oplus$ Carry out of MSB
 - For N-bit ALU: $\text{Overflow} = \text{CarryIn}[N - 1] \text{ XOR } \text{CarryOut}[N - 1]$



X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

 

Negative, Zero

- Required for conditional branches
- Zero
 - How?
 - NOR all 32 bits
 - Avoid 33rd bit (carry out)
- Negative may be required on overflow
 - If (a<b) jump : jump taken if a-b is negative
- Tempting to consider MSB
 - E.g. if (-5 < 4) branch
 - Branch should be taken, but (-5-4) computation results in overflow... so MSB is 0
 - E.g. if (7 < -3) branch
 - Branch should not be taken but (7- (-3)) results in overflow... so MSB is 1.

Shift

- E.g., Shift left logical for $d<7:0>$ and $shamt<2:0>$
 - Using 2-1 muxes called $Mux(select, in0, in1)$
 - $stage0<7:0> = Mux(shamt<0>, d<7:0>, 0 || d<7:1>)$
 - $stage1<7:0> = Mux(shamt<1>, stage0<7:0>, 00 || stage0<6:2>)$
 - $dout<7:0> = Mux(shamt<2>, stage1<7:0>, 0000 || stage1<3:0>)$
- Other operations
 - Right shift
 - Arithmetic shifts
 - Rotate

Barrel Shifter

