

Verilog

For Computer Design

CS/ECE 552

Karu Sankaralingam

Based on slides from


Derek Hower (UW-Madison), Andy Phelps (UW-Madison) and
Prof. Milo Martin (University of Pennsylvania)

Overview

- Why Verilog?
 - High-level description of Verilog
- Verilog Syntax
 - Primitives
 - Number Representation
 - Modules and instances
 - Wire and Reg Variables
 - Operators
 - Miscellaneous
 - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- Test bench structure
- Case study, Verilog tools and Demo

Why Verilog and why not Manual design?

State of Art Design

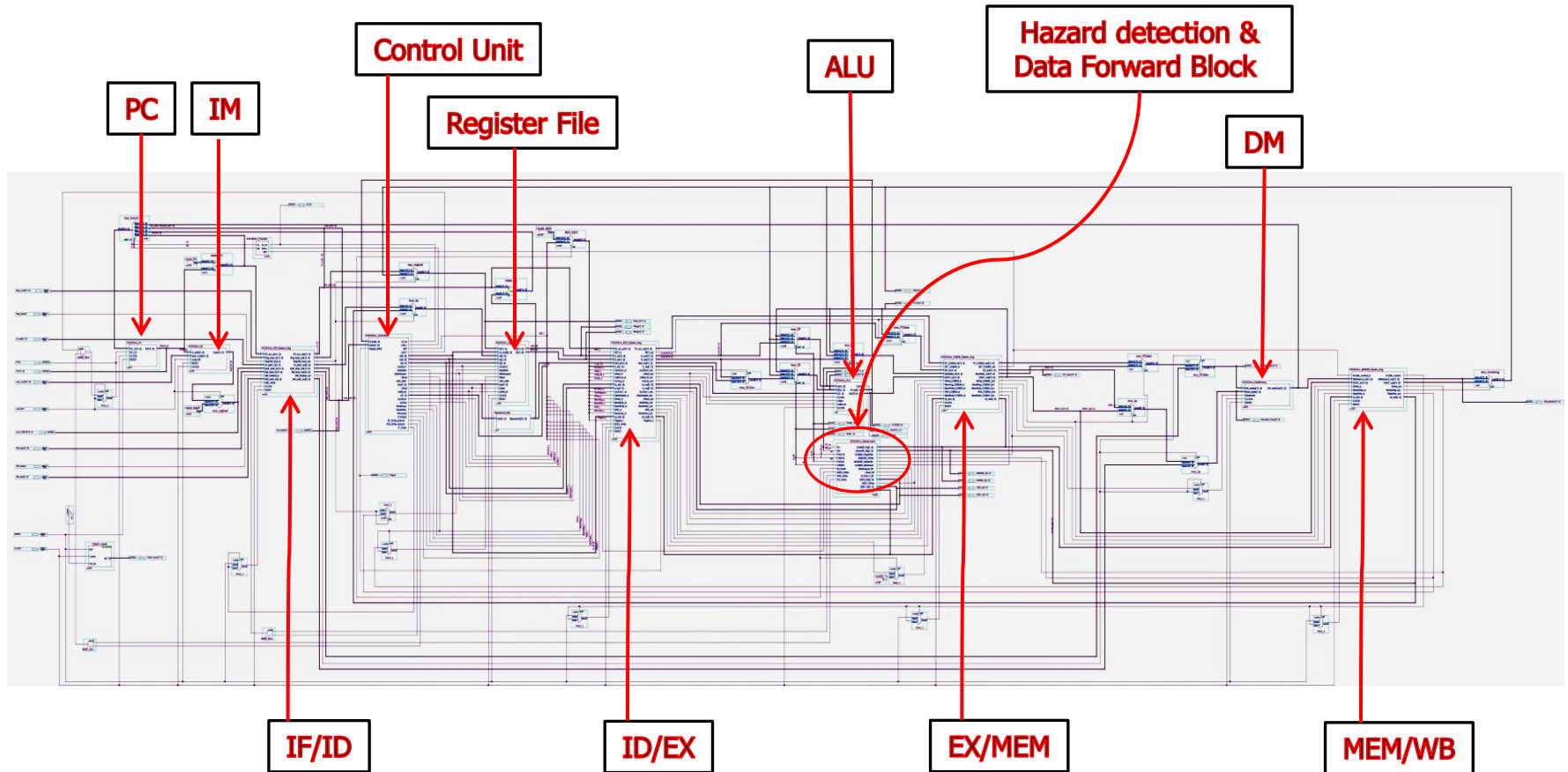

Do you want to design this Processor manually?

How To Represent Hardware?

- If you're going to design a computer, you need to write down the design so that:
 - You can read it again later
 - Someone else can read and understand it
 - It can be simulated and verified
 - Even software people may read it!
 - It can be synthesized into specific gates
 - It can be built and shipped and make money(\$\$\$)

Ways to represent hardware:

- Draw schematics
 - Hand-drawn (Seriously?)
 - Machine-drawn
- Write a netlist – ASCII representation of Interconnect of a schematic
 - Z52BH I1234 (N123, N234, N4567);
- Write primitive Boolean equations
 - AAA = abc DEF + ABC def
- Use a Hardware Description Language (HDL)
 - assign overflow = c31 ^ c32;

Hardware Description Languages (HDLs)

- Textual representation of a digital logic design
 - Can represent specific gates, like a netlist, or more abstract logic
- HDLs are not “programming languages”
 - No, really. Even if they look like it, they are not.
 - For many people, a difficult conceptual leap
- Similar development chain
 - Compiler: source code ▪ assembly code ▪ binary machine code
 - Synthesis tool: HDL source ▪ gate-level specification ▪ hardware

What is an HDL? – “Think hardware”

if(x != 0) vs. if((x <= -1) || (x >= 1))
What hardware is generated here ?


```
module counter(clk,rst_n,cnt);  
  
    input clk,rst_n;  
    output [3:0] cnt;  
  
    reg [3:0] cnt;  
  
    always @(posedge clk) begin  
        if (~rst_n)  
            cnt = 4'b0000;  
        else  
            cnt = cnt+1;  
        end  
    endmodule
```

- It looks like a programming language
- It is **NOT** a programming language
 - ✓ It is always critical to recall you are describing hardware
 - ✓ This codes primary purpose is to generate hardware
 - ✓ The hardware this code describes (a counter) can be simulated on a computer. In this secondary use of the language it does act more like a programming language.

Why an HDL is not a Programming Language

- In a program, we start at the beginning (e.g. "main"), and we proceed sequentially through the code as directed
- The program represents an algorithm, a step-by-step sequence of actions to solve some problem
 
```
for (i = 0; i < 10; i = i + 1) {  
    if (newPattern == oldPattern[i]) match = i;  
}
```
- Hardware is all active at once; there is no starting point



Why Use an HDL?

- Enables Larger Designs
 - More abstracted than schematics, allows larger designs.
 - ✓ Register Transfer Level Description
 - ✓ Wide data paths (16, 32, or 64 bits wide) can be abstracted to a single vector
 - ✓ Synthesis tool does the bulk of the tedious repetitive work
 - ✓ Work at transistor/gate level for large designs: cumbersome
- Explore larger solution space
 - ✓ Synthesis options can help optimize (power, area, speed)
 - ✓ Synthesis options and coding styles can help examine tradeoffs
 - Speed | Power | area

Why use an HDL? (continued)

- Easy to write and edit
- Compact
- Don't have to follow a maze of lines
- Easy to analyze with various tools

Why not to use an HDL


- You still need to visualize the flow of logic
- A schematic can be a work of art
 - But often isn't! (My first Processor example 😊)

Other Important HDL Features

- Are highly portable (text)
- Are self-documenting (when commented well)
- Describe multiple levels of abstraction
- Represent parallelism
- Provides many descriptive styles
 - Structural
 - Register Transfer Level (RTL)
 - Behavioral
- Serve as input for synthesis tools

Starting with an example...

```
module fulladd (input A, B, Cin,  
               output sum, Cout );  
  
    assign sum = A ^ B ^ Cin;  
    assign Cout = (A & B) | (A & Cin) | (B & Cin);  
endmodule
```

 

Pitfalls of trying to “program” in Verilog

- If you program sequentially, the synthesizer may add a lot of hardware to try to do what you say
 - In last example, need a priority encoder
- If you program in parallel (multiple “always” blocks), you can get non-deterministic execution – Race Condition
 - Which “always” happens first?
- You create lots of state that you didn’t intend
 - if (x == 1) out = 0;
 - if (y == 1) out = 1; // else out retains previous state? R-S latch!
- You don’t realize how much hardware you’re specifying
 - $x = x + 1$ can be a LOT of hardware
- Slight changes may suddenly make your code “blow up”
 - A chip that previously fit suddenly is too large or slow

Two Roles of HDL and Related Tools

- **#1: Specifying digital logic**
 - Specify the logic that appears in final design
 - Either
 - Translated automatically (called *synthesis*) or
 - Optimized manually (automatically checked for equivalence)
- **#2: Simulating and testing a design**
 - High-speed simulation is crucial for large designs
 - Many HDL *interpreters* optimized for speed
 - Testbench: code to test design, but not part of final design

Module Styles

- Modules can be specified different ways
 - Structural – connect primitives and modules
 - Dataflow– use continuous assignments
 - Behavioral – use initial and always blocks
- A single module can use more than one of the above 3 coding styles!

What are the differences?

HDL Constructs

- **Structural** constructs specify actual hardware structures
 - Low-level, direct correspondence to hardware
 - Primitive gates (e.g., and, or, not)
 - Hierarchical structures via modules
 - Analogous to programming software in assembly
- **RTL/Dataflow** constructs specify an operation on bits
 - High-level, more abstract
 - Specified via equations, e.g., $out = (a \& b) | c$
- **Behavioral – Describes behavior of the circuit**
 - Always , initial blocks, procedural assignments
- **Not all behavioral constructs are synthesizable**
 - We've already talked about the pitfalls of trying to "program"
 - But even some combinational logic won't synthesize well
 - $out = a \% b$ // modulo operation – what does this synthesize to?

Structural Example

```
module majority (major, V1, V2, V3) ;
```


```
    output major ;  
    input V1, V2, V3 ;
```

```
    wire N1, N2, N3;
```

```
    and A0 (N1, V1, V2),  
        A1 (N2, V2, V3),  
        A2 (N3, V3, V1);
```

```
    or Or0 (major, N1, N2, N3);
```

```
    endmodule
```

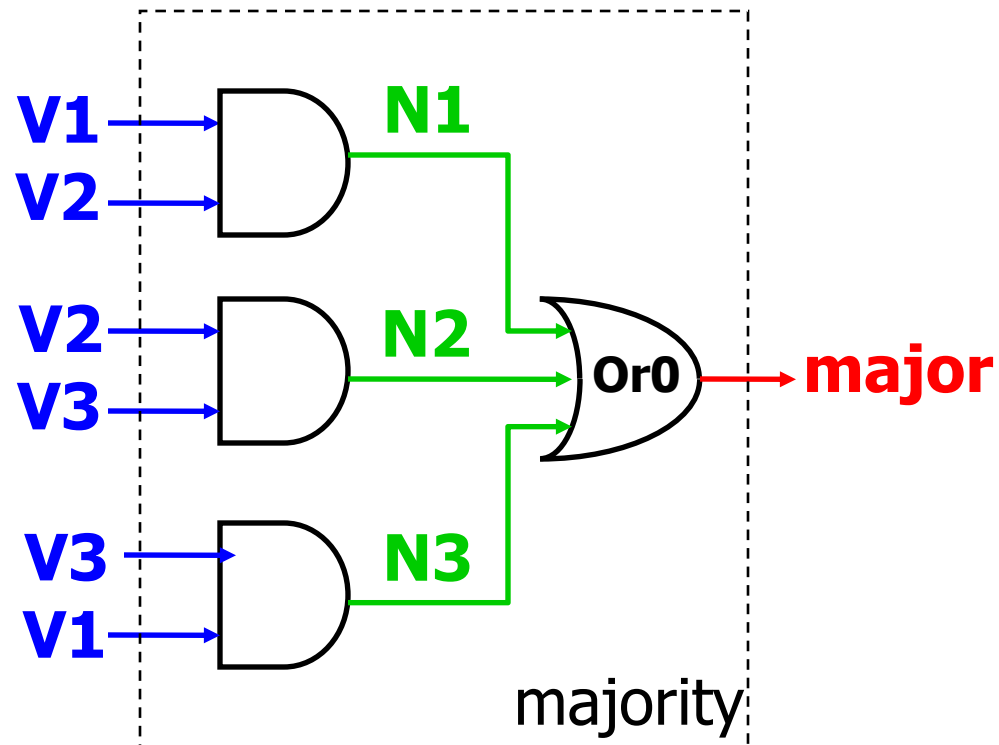

RTL/Dataflow Example

Continuous Assignment Statement


```
module majority (major, V1, V2, V3) ;
```

```
    output major ;
```

```
    input V1, V2, V3 ;
```

```
    assign major = V1 & V2  
              | V2 & V3  
              | V1 & V3;
```

```
    endmodule
```

 

Behavioral Example

```
module majority (major, V1, V2, V3) ;
```

```
    output reg major ;
```

```
    input V1, V2, V3 ;
```

```
    always @(V1, V2, V3) begin
```


```
        if (V1 && V2 || V2 && V3
```

```
            || V1 && V3) major = 1;
```

```
            else major = 0;
```

```
        end
```

```
    endmodule
```

 

Overview

- Why Verilog?
 - High-level description of Verilog
- Verilog Syntax
 - Primitives
 - Number Representation
 - Modules and instances
 - Wire and Reg Variables
 - Operators
 - Miscellaneous
 - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- Test bench structure
- Case study, Verilog tools and Demo

Recall: Two Types of Digital Circuits

- **Combinational Logic**
 - Logic without state variables
 - Examples: adders, multiplexers, decoders, encoders
 - No clock involved
 - Not edge-triggered
 - All “inputs” (RHS nets/variables) are triggers
- **Sequential Logic (Details explained later)**
 - Logic with state variables
 - State variables: latches, flip-flops, registers, memories
 - Clocked - Edge-triggered by clock signal
 - State machines, multi-cycle arithmetic, processors
 - Only clock (and possibly reset) appear in trigger list
 - Can include combinational logic that feeds a FF or register

Verilog Structural Primitives

No declaration; can only be instantiated

Imp * - All output ports appear in list before any input ports

Optional drive strength, delay, name of instance

Example: **and** N25 (Z, A, B, C); //instance name

Example: **and** #10 (Z, A, B, X); // delay
(X, C, D, E); //delay

/*Usually better to provide instance name for debugging.*/

Example: **or** N30 (SET, Q1, AB, N5),

N41 (N25, ABC, R1);

Example: **and** #10 N33(Z, A, B, X); // name + delay

Number Representation

Format: <size><base_format><number>

Examples:

6'b010_111	gives 010111
8'b0110	gives 00000110
8'b1110	gives 00001110
4'bx01	gives xx01
16'H3AB	gives 0000001110101011
24	gives 0...0011000
5'O36	gives 11100
16'Hx	gives xxxxxxxxxxxxxxxxx
8'hz	gives zzzzzzzz

Connections – Module Instantiations

- By position association

```
module 2_to_4_decode (A, E_n, D);  
  4_to_16_decode DX (X[3:2], W_n, word);  
  A = X[3:2], E_n = W_n, D = word
```

- By name association (**this is supposed to be used in HWs and Projects**)

```
module 2_to_4_decode (A, E_n, D);  
  C_2_4_decoder_with_enable DX (.E_n(W_n), .A(X[3:2]),  
    .D(word));  
  A = X[3:2], E_n = W_n, D = word
```


Hierarchical Verilog Example

- Build up more complex modules using simpler modules
- Example: 4-bit wide mux from four 1-bit muxes
 - Again, just “drawing” boxes and wires


```
module mux2to1_4(  
    input [3:0] A,  
    input [3:0] B,  
    input Sel,  
    output [3:0] O );  
  
    mux2to1 mux0 (Sel, A[0], B[0], O[0]);  
    mux2to1 mux1 (Sel, A[1], B[1], O[1]);  
    mux2to1 mux2 (Sel, A[2], B[2], O[2]);  
    mux2to1 mux3 (Sel, A[3], B[3], O[3]);  
  
endmodule
```

Variables

- Nets (Also called as wires)
 - ✓ Used for structural connectivity
- Registers
 - ✓ Abstraction of storage (May or may not be real physical storage)
- Properties of Both
 - ✓ Informally called signals
 - ✓ May be either scalar (one bit) or vector (multiple bits)

Verilog Module Example of wires
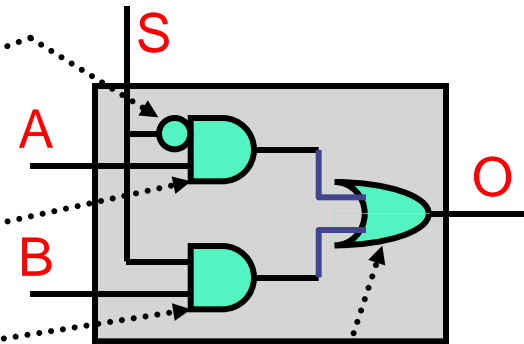
```
module mux2to1(  
    input S, A, B,  
    output O );  
    wire S_, AnS_, BnS;  
  
    not (S_, S);  
    and (AnS_, A, S_);  
    and (BnS, B, S);  
    or (O, AnS_, BnS);  
  
endmodule
```



Net (wire) Examples

- Wire vectors:

```
wire [7:0] w1;      // 8 bits, w1[7] is MSB
```

- Also called "buses"

- Operations

- Bit select: `w1[3]`

- Range select: `w1[3:2]`

- Concatenate:

```
vec = {x, y, z};
```

```
{carry, sum} = vec[0:1];
```

- e.g., swap high and low-order bytes of 16-bit vector

```
wire [15:0] w1, w2;
```

```
assign w2 = {w1[7:0], w1[15:8]}
```

Wire and Vector Assignment

- Wire assignment: “continuous assignment”
 - Connect combinational logic block or other wire to wire input
 - **Order of statements not important to Verilog**, executed totally in parallel
 - But order of statements can be important to clarity of thought!
 - When right-hand-side changes, it immediately flows through to left
 - Designated by the keyword **assign**

```
wire c;  
assign c = a | b;  
wire c = a | b;      // same thing
```

Register Assignment

- A register may be assigned value only within:
 - ✓ a procedural statement
 - ✓ a user-defined sequential primitive
 - ✓ a task, or
 - ✓ a function.
- A reg object may never be assigned value by:
 - ✓ a primitive gate output
 - ✓ or a continuous assignment

Examples:

```
reg a, b, c;
```

```
reg [15:0] counter, shift_reg;
```

```
reg [8:4] flops;
```

When to use wire and when reg !

■ Wire

- ✓ Module declaration = Inputs(Yes), Outputs (Yes)
- ✓ Module instantiation = Connect input and output ports
- ✓ Must be driven by something, cannot store values
- ✓ Only legal type on left side of an assign statement
- ✓ Not allowed on left side of = or <= in an always@ block
- ✓ Most of the times combinational logic

■ Reg

- ✓ Module instantiation = Input port (Yes) , Output Port (No)
- ✓ Module declaration = Inputs(No), Outputs (Yes)
- ✓ Only legal type on left side of = or <= in an always@ block
- ✓ Only legal type on left side of initial block(test bench)
- ✓ Not Allowed on left side of an assign statement
- ✓ Used for both sequential and combinational logic

Operators

- Operators similar to C or Java
- On wires:
 - $\&$ (and), $|$ (or), \sim (not), \wedge (xor)
- On vectors:
 - $\&$, $|$, \sim , \wedge (bit-wise operation on all wires in vector)
 - E.g., assign `vec1 = vec2 & vec3;`
 - $\&$, $|$, \wedge (reduction on the vector)
 - E.g., assign `wire1 = | vec1;`
 - Even `==`, `!=` (comparisons)

Can be arbitrarily nested: $(a \ \& \ \sim b) \ | \ c$

Conditional Operator

- Verilog supports the ?: conditional operator
 - Just like in C
 - But much more common in Verilog

- Examples:

```
assign out = S ? B : A;
```

```
assign out = sel == 2'b00 ? a :  
             sel == 2'b01 ? b :  
             sel == 2'b10 ? c :  
             sel == 2'b11 ? d : 1'b0;
```

- What do these do?

Overview

- Why Verilog?
 - High-level description of Verilog
- Verilog Syntax
 - Primitives
 - Number Representation
 - Modules and instances
 - Wire and Reg Variables
 - Operators
 - Miscellaneous
 - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- Test bench structure
- Case study, Verilog tools and Demo

Parameters

- Allow per-instantiation module parameters
 - Use “parameter” statement
- `modname #(10, 20, 30) instname(in1, out1);`
- Example:

```
module mux2to1_N(Sel, A, B, O);
    parameter N = 1
    input [N-1:0] A;
    input [N-1:0] B;
    input Sel;
    output [N-1:0] O;
    mux2to1 mux0[N-1:0] (Sel, A, B, O);
endmodule

...

Mux2to1_N #(4) mux1 (S, in1, in2, out)
```

Verilog Pre-Processor

- Like the C pre-processor
 - But uses ``` (back-tick) instead of `#`
 - Constants: ``define`
 - No parameterized macros
 - Use ``` before expanding constant macro
- ```
`define letter_A 8'h41
wire w = `letter_A;
```
- Conditional compilation: ``ifdef`, ``endif`
- File inclusion: ``include`
- Parameter vs ``define`
  - Parameter only for “per instance” constants
  - ``define` for “global” constants

# Common Errors

---

- Tools are from a less gentle time
  - More like C, less like Java
  - Assume that you mean what you say
- Common errors:
  - Not assigning a wire a value
  - Assigning a wire a value more than once
- Avoid names such as:
  - clock, power, pwr, ground, gnd, vdd, vcc, init, reset
  - Some of these are “special” and will silently cause errors
  - We will use “clk” and “rst”, but only for their intended uses

# Verilog in Project / Homework

---

- Use the primitive modules and other basic modules given in course webpage for your 'design'
- Follow the Verilog rules only for Design
- You are free to use your own test bench
- Only use the specified Verilog Keywords, allowed operators
- Go through the usage examples
  
- Ask TA s if you are experiencing any difficulty in following these guidelines.

# Non-binary Hardware Values

---

- A hardware signal can have four values
  - 0, 1
  - x: don't know, don't care
  - z: high-impedance (no current flowing)
- Two meanings of "x"
  - Simulator indicating an unknown state
  - Or: You telling synthesis tool you don't care
    - Synthesis tool makes the most convenient circuit (fast, small)
    - Use with care, leads to synthesis dependent operation
- Uses for "z"
  - Tri-state devices drive a zero, one, or nothing (z)
  - Many tri-states drive the same wire, all but one must be "z"
    - Example: multiplexer

# Case Statements

---

```
case (<expr>)
 <match-constant1>:<stmt>
 <match-constant2>:<stmt>
 <match-constant3>,<match-constant4>:<stmt>
 default: <stmt>
endcase
```



# Case Statements

---

- Useful to make big muxes
- Very useful for “next-state” logic
- But they are easy to abuse
- If you don’t set a value, it retains its previous state
  - Which is a latch!
- We will allow case statements, but with some severe restrictions:
  - Every value is set in every case
  - Every possible combination of select inputs must be covered
  - Each case lives in its own “always” block, sensitive to changes in all of its input signals
  - This is our only use of “always” blocks

# Different types of Case statements

---

Verilog has three types of case statements:

**case**, **casex**, and **casez**

- Performs bitwise match of expression and case item
  - Both must have same bitwidth to match!
- **case**
  - Can detect **x** and **z**! (good for testbenches)
- **casez**
  - Uses **z** and **?** as “don’t care” bits in case items and expression
- **casex**
  - Uses **x**, **z**, and **?** as “don’t care” bits in case items and expression

# Case Statement Example

---

```
always @*
 casex ({goBack, currentState, inputA, inputB})
 6'b1_???_?_? : begin out = 0; newState = 3'b000; err=0; end
 6'b0_000_0_? : begin out = 0; newState = 3'b000; err=0; end
 6'b0_000_1_? : begin out = 0; newState = 3'b001; err=0; end
 6'b0_001_1_? : begin out = 0; newState = 3'b001; err=0; end
 6'b0_001_0_0 : begin out = 0; newState = 3'b010; err=0; end
 6'b0_001_0_1 : begin out = 0; newState = 3'b011; err=0; end
 6'b0_010_?_0 : begin out = 0; newState = 3'b010; err=0; end
 6'b0_010_?_1 : begin out = 0; newState = 3'b011; err=0; end
 6'b0_011_?_1 : begin out = 0; newState = 3'b011; err=0; end
 6'b0_011_?_0 : begin out = 0; newState = 3'b100; err=0; end
 6'b0_100_?_? : begin out = 1; newState = 3'b000; err=0; end
 6'b0_101_?_? : begin out = 0; newState = 3'b000; err=1; end
 6'b0_110_?_? : begin out = 0; newState = 3'b000; err=1; end
 6'b0_111_?_? : begin out = 0; newState = 3'b000; err=1; end
 default: begin out = 0; newState = 3'b000; err=1; end
 endcase
```

# What happens if it's wrong?

---

Here are our rules:

- A case statement should always have a default
- Hitting this default is an error
- Every module has an "err" output
- Can be used for other checks, like illegal inputs
- OR together all "err" signals -- bring "err" all the way to top
- Our clock/reset module will print a message if `err == 1`

# System tasks

---

- Start with \$

- For output:

```
$display (<fmtstring><, signal>*) ;
```

```
$fdisplay (<fhandle>, <fmtstring><, signal>*) ;
```

- Signal printf/fprintf

```
$monitor (<fmtstring><, signal>*) ;
```

- Non-procedural printf, prints out when a signal changes

```
$dumpvars (1<, signal>*) ;
```

- Similar to monitor
- VCD format for waveform viewing (gtkwave)
- Output is in dumpfile.vcd

# More System Tasks

---

## `$time`

- Simulator's internal clock (64-bit unsigned)
- Can be used as both integer and auto-formatted string

## `$finish`

- Terminate simulation

## `$stop`

- Pause simulation and debug

`$readmemh (<fname>, <mem>, <start>, <end>) ;`

`$writememh (<fname>, <mem>, <start>, <end>) ;`

- Load contents of ASCII file to memory array (and vice versa)
- Parameters `<start>`, `<end>` are optional
- Useful for loading initial images, dumping final images

# Overview

---

- Why Verilog?
  - High-level description of Verilog
- Verilog Syntax
  - Primitives
  - Number Representation
  - Modules and instances
  - Wire and Reg Variables
  - Operators
  - Miscellaneous
    - Parameters, Pre-processor, case statements, Common errors, system tasks
- **Sequential logic**
- Test bench structure
- Case study, Verilog tools and Demo

# Sequential Logic in Verilog


---

Use the Homework Modules provided-  
Instantiate the dff module given for all FFs

```
module dff
(q, d, clk, rst);
```

```
output q;
input d;
input clk;
input rst;
reg state;
```
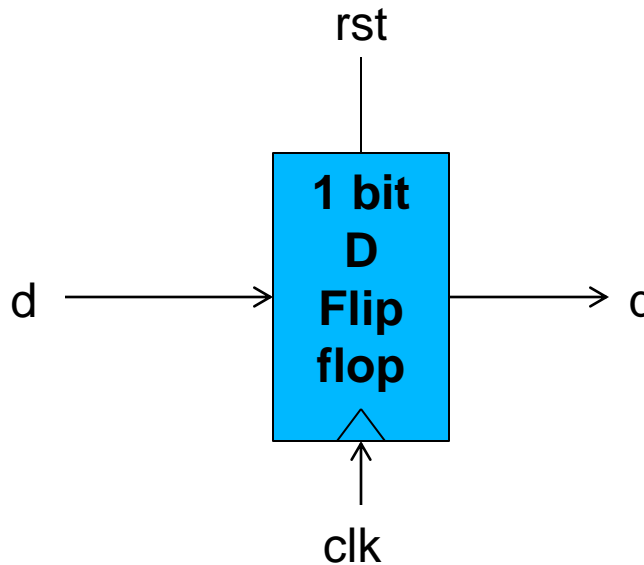
```
assign #(1) q = state;
always @(posedge clk) begin
state = rst? 0 : d;
end
endmodule
```





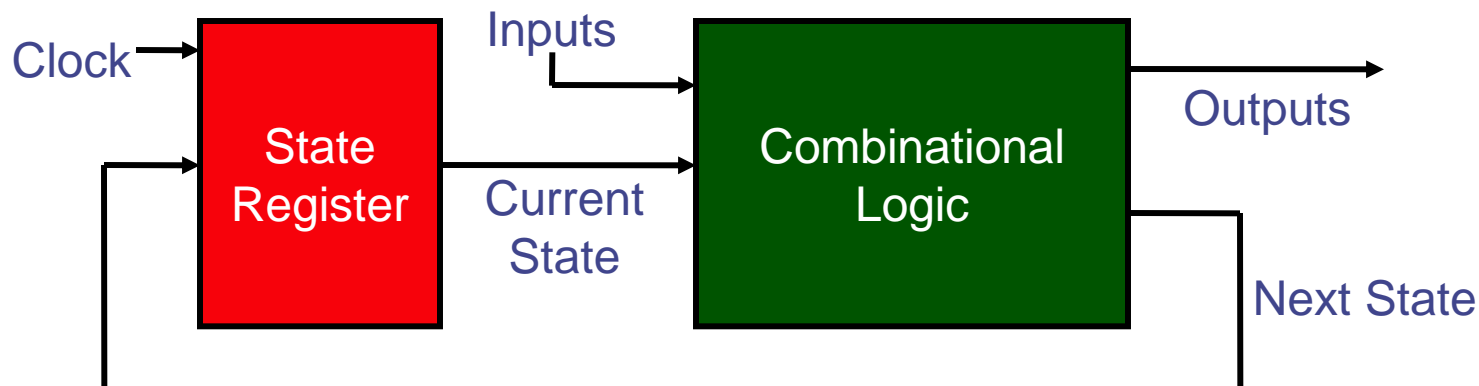
# Designing Sequential Logic

---

- CS/ECE 552 design rule: separate combinational logic from sequential state elements in lowest-level modules
  - Not enforced by Verilog, but a very good idea
  - Possible exceptions: counters, shift registers
- We'll give you a 1-bit flip-flop module (see previous slide)
  - Edge-triggered, not a latch
  - Use it to build n-bit register, registers with "load" inputs, etc.
- Example use: state machine



# Clocks Signals

---

- Clocks signals are not normal signals
- Travel on dedicated “clock” wires
  - Reach all parts of the chip
  - Special “low-skew” routing
- Ramifications:
  - Never do logic operations on the clocks
  - If you want to add a “write enable” to a flip-flop:
    - Use a mux to route the old value back into it
    - Do not just “and” the write-enable signal with the clock!
- Messing with the clock can cause errors
  - Often can only be found using timing simulation

# Overview

---

- Why Verilog?
  - High-level description of Verilog
- Verilog Syntax
  - Primitives
  - Number Representation
  - Modules and instances
  - Wire and Reg Variables
  - Operators
  - Miscellaneous
    - Parameters, Pre-processor, case statements, Common errors, system tasks
- Sequential logic
- **Test bench structure**
- **Case study, Verilog tools and Demo**


# Verilog Simulation using Modelsim

---

- Testbench
- Setting up the mentor environment
- Using modelsim (simple example: 4 bit register)
  - Fixing compile errors
  - Debugging functional errors (with waveforms)
- Shortcut! Use `wrun.pl`
- Vcheck – check for illegal constructs
- Pattern/Sequence detector

# Testbench – variant 1


---

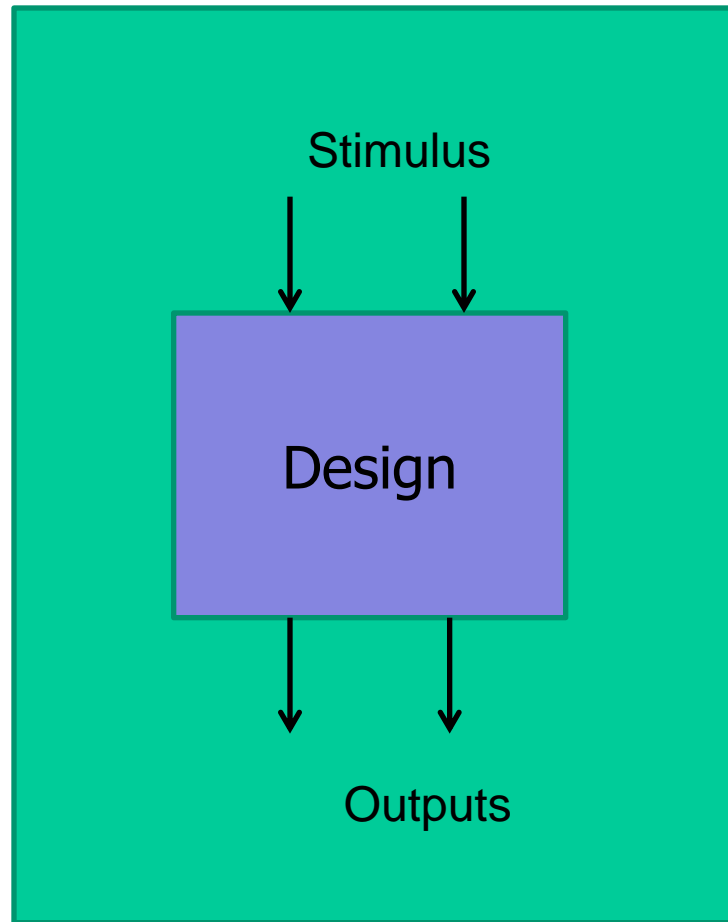

And “visually” inspect the  
outputs


# Testbench – variant 2

---

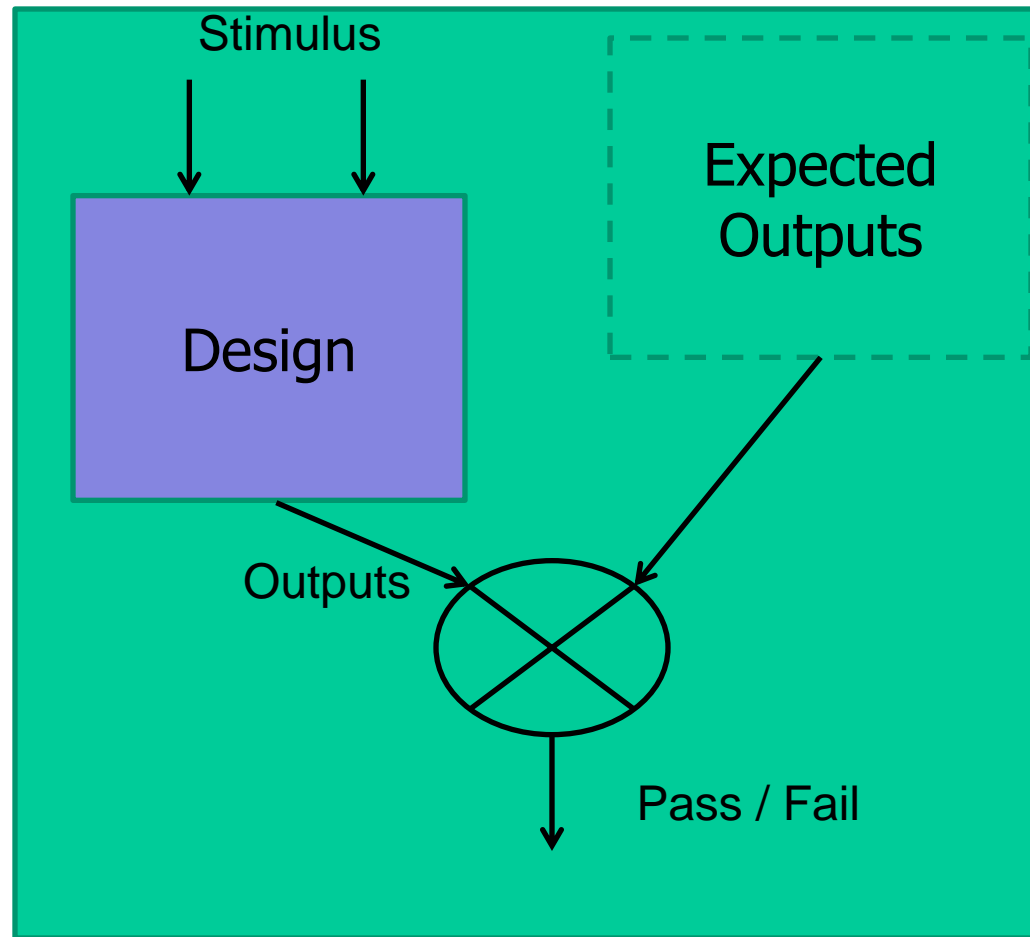

# Sophisticated Test Environment (To be used in the course project)

---

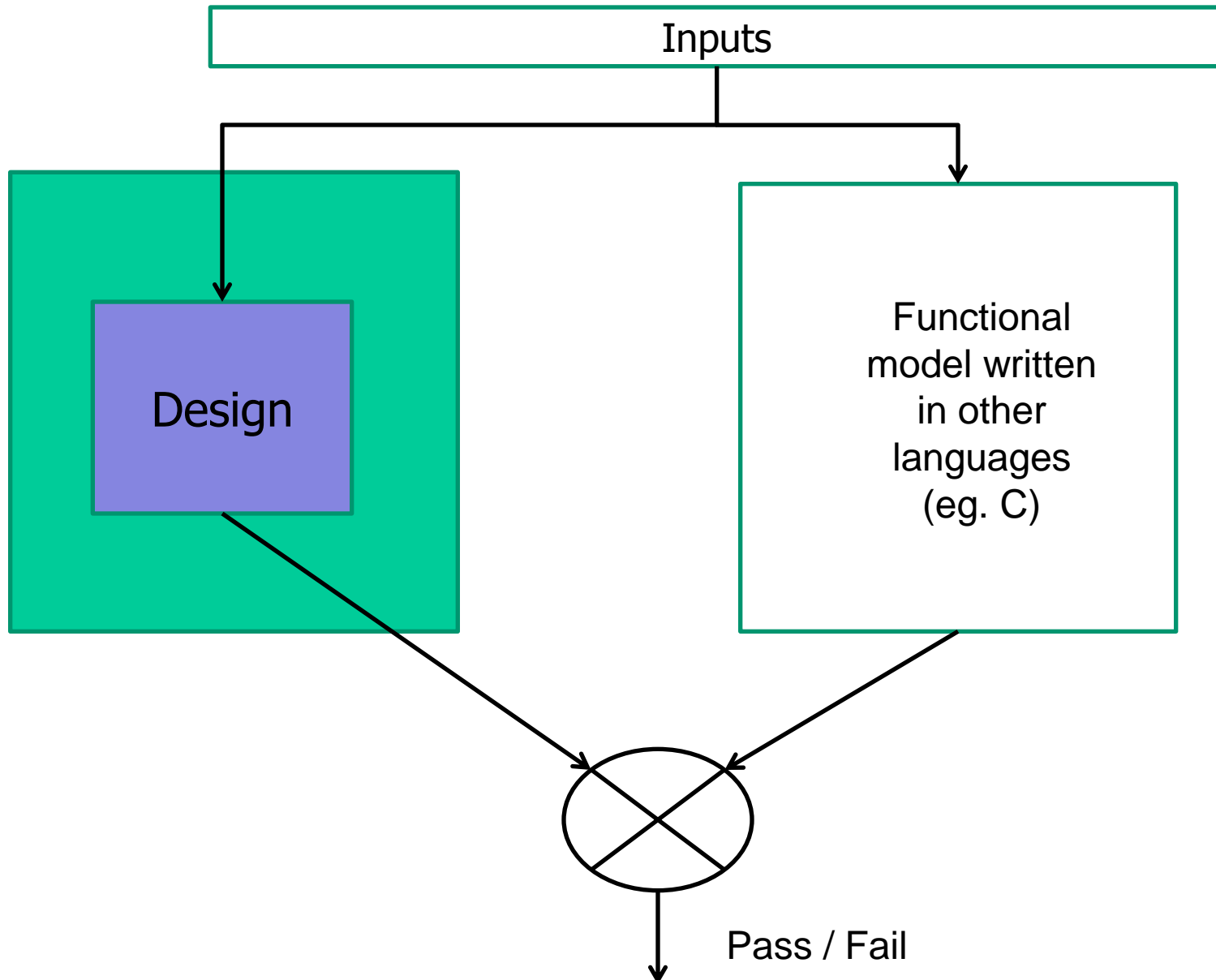

# Setting up the mentor environment

---

- Edit `.bashrc` or `.bashrc.local`
- Create mentor directory in home area, copy over `.location` and edit it
- Find detailed instructions at:
  - Sidebar of Course home page -> “Tools” -> “Getting started with Mentor”
  - <http://pages.cs.wisc.edu/~karu/courses/cs552/spring2013//wiki/index.php/Main/GettingStartedWithMentor>



# Using modelsim (simple example: 4 bit register)

---

- Interfaces:

- What we are going to build:

```
module reg_4bit(out, in, wr_en, clk, rst)
```

- What we have to start with:

```
module dff (q, d, clk, rst);
```

# Using modelsim (simple example: 4 bit register)

---

reg\_4bit\_bench

clkrst

reg\_4bit

dff\_en

dff

dff\_en

dff

dff\_en

dff

dff\_en

dff

# Shortcut! Use wsrun.pl

---

- `wsrun.pl -wave reg4bit_bench *.v`
- Find detailed instructions at:
  - Sidebar of Course home page -> “Command-line Simulation”
  - <http://pages.cs.wisc.edu/~karu/courses/cs552/spring2013//wiki/index.php/Main/Command-lineVerilogSimulationTutorial>

# Vcheck – check for illegal constructs


---

- Limited subset of verilog constructs allowed in CS552
- **Restriction is only for the “Design”**
- **Testbench can use any valid verilog syntax**
- 3 ways to run the checks. Find detailed instructions at:
  - Sidebar of Course home page -> “Tools” -> “Verilog Rules Check”
  - <http://pages.cs.wisc.edu/~karu/courses/cs552/spring2013/wiki/index.php/Main/VerilogRulesCheck>

# Pattern/Sequence detector

---

Pattern: 1101

 

# Pattern/Sequence detector

---

- Use binary numbers to encode state
- Current state: 4 bit binary number:  $Q_2 Q_1 Q_0$
- Next state: 4 bit binary number:  $Q_{2_n} Q_{1_n} Q_{0_n}$

# Pattern/Sequence detector

| Q2 | Q1 | Q0 | InA | Q2 <sub>n</sub> | Q1 <sub>n</sub> | Q0 <sub>n</sub> |
|----|----|----|-----|-----------------|-----------------|-----------------|
| 0  | 0  | 0  | 0   | 0               | 0               | 0               |
| 0  | 0  | 0  | 1   | 0               | 0               | 1               |
| 0  | 0  | 1  | 0   | 0               | 0               | 0               |
| 0  | 0  | 1  | 1   | 0               | 1               | 0               |
| 0  | 1  | 0  | 0   | 0               | 1               | 1               |
| 0  | 1  | 0  | 1   | 0               | 1               | 0               |
| 0  | 1  | 1  | 0   | 0               | 0               | 0               |
| 0  | 1  | 1  | 1   | 1               | 0               | 0               |
| 1  | 0  | 0  | 0   | 0               | 0               | 0               |
| 1  | 0  | 0  | 1   | 0               | 1               | 0               |
| X  | X  | X  | X   | X               | X               | X               |

- $Out = f ( Q2, Q1, Q0 )$
- $Q2_n = f ( Q2, Q1, Q0, InA )$
- $Q1_n = f ( Q2, Q1, Q0, InA )$
- $Q0_n = f ( Q2, Q1, Q0, InA )$

- $Out = Q2$

- $Q2_n = Q2' Q1 Q0 InA$


- $Q1_n = Q2' Q1' Q0 InA + Q2' Q1 Q0' InA' + Q2' Q1 Q0' InA + Q2 Q1' Q0' InA$

- $Q0_n = Q2' Q1' Q0' InA + Q2' Q1 Q0' InA'$
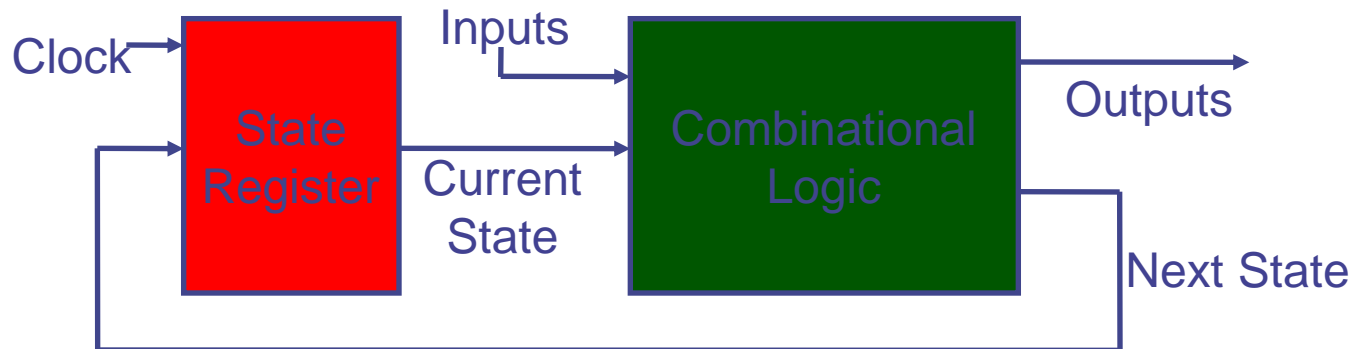
# Pattern/Sequence detector

---

- A sequence detector is sequential logic
- Design Rule: separate combinational logic from sequential state elements in lowest-level modules
- We will give you a 1-bit flip-flop module to hold state and a clock/reset generator
  - See the course web site





# Pattern/Sequence detector

---

- Two ways to implement the “Combinational logic” block.

- 1) Implement the state equations using verilog bitwise logical operators

- 2) Use a case statement to specify the state transitions