



ECE/CS 552: Arithmetic and Logic

© Prof. Mikko Lipasti

Lecture notes based in part on slides created by Mark Hill, David Wood, Guri Sohi, John Shen and Jim Smith

Basic Arithmetic and the ALU

- Number representations: 2's complement, unsigned
- Addition/Subtraction
- Add/Sub ALU
 - Full adder, ripple carry, subtraction
- Logical operations
 - and, or, xor, nor, shifts
- Overflow

Basic Arithmetic and the ALU

- Covered later in the semester:
 - Integer multiplication, division
 - Floating point arithmetic
- These are not crucial for the project

Background

- Recall
 - n bits enables 2^n unique combinations
- Notation: $b_{31} b_{30} \dots b_3 b_2 b_1 b_0$
- No inherent meaning
 - $f(b_{31} \dots b_0) \Rightarrow$ integer value
 - $f(b_{31} \dots b_0) \Rightarrow$ control signals

Background

- 32-bit types include
 - Unsigned integers
 - Signed integers
 - Single-precision floating point
 - MIPS instructions (refer to book)

Unsigned Integers

- $f(b_{31}...b_0) = b_{31} \times 2^{31} + ... + b_1 \times 2^1 + b_0 \times 2^0$
- Treat as normal binary number
E.g. 0...01101010101
 $= 1 \times 2^7 + 1 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^1 + 1 \times 2^0$
 $= 128 + 64 + 16 + 4 + 1 = 213$
- $\text{Max } f(111...11) = 2^{32} - 1 = 4,294,967,295$
- $\text{Min } f(000...00) = 0$
- $\text{Range } [0, 2^{32}-1] \Rightarrow \# \text{ values } (2^{32}-1) - 0 + 1 = 2^{32}$

Signed Integers



- 2's complement

$$f(b_{31}...b_0) = -b_{31} \times 2^{31} + \dots b_1 \times 2^1 + b_0 \times 2^0$$

- Max $f(0111...11) = 2^{31} - 1 = 2147483647$
- Min $f(100...00) = -2^{31} = -2147483648$
(asymmetric)
- Range $[-2^{31}, 2^{31}-1] \Rightarrow \# \text{ values } (2^{31}-1 - -2^{31}) + 1 = 2^{32}$
- Invert bits and add one: e.g. -6
– $000...0110 \Rightarrow 111...1001 + 1 \Rightarrow 111...1010$

Why 2's Complement

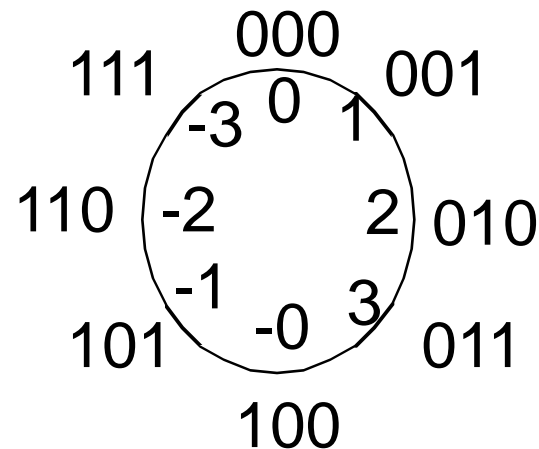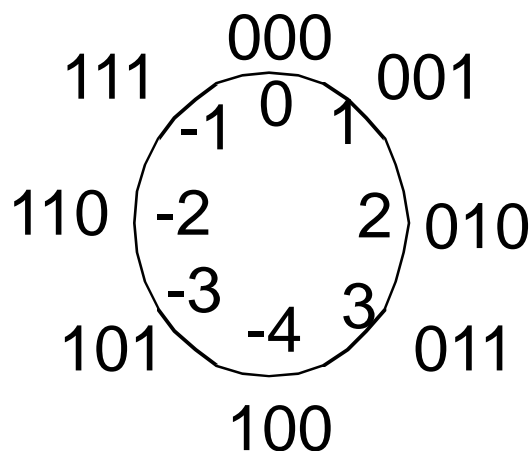- Why not use sign-magnitude?
- 2's complement makes hardware simpler
- Just like humans don't work with Roman numerals
- Representation affects ease of calculation, not correctness of answer



Addition and Subtraction

- 4-bit unsigned example

0	0	1	1		3
1	0	1	0		10
1	1	0	1		13

- 4-bit 2's complement – ignoring overflow

0	0	1	1		3
1	0	1	0		-6
1	1	0	1		-3

Subtraction

- $A - B = A + 2\text{'s complement of } B$
- E.g. $3 - 2$

0	0	1	1		3
1	1	1	0		-2
0	0	0	1		1


Full Adder

- Full adder $(a, b, c_{in}) \Rightarrow (c_{out}, s)$
- c_{out} = two or more of (a, b, c_{in})
- s = exactly one or three of (a, b, c_{in})

a	b	c_{in}	c_{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Ripple-carry Adder

- Just concatenate the full adders

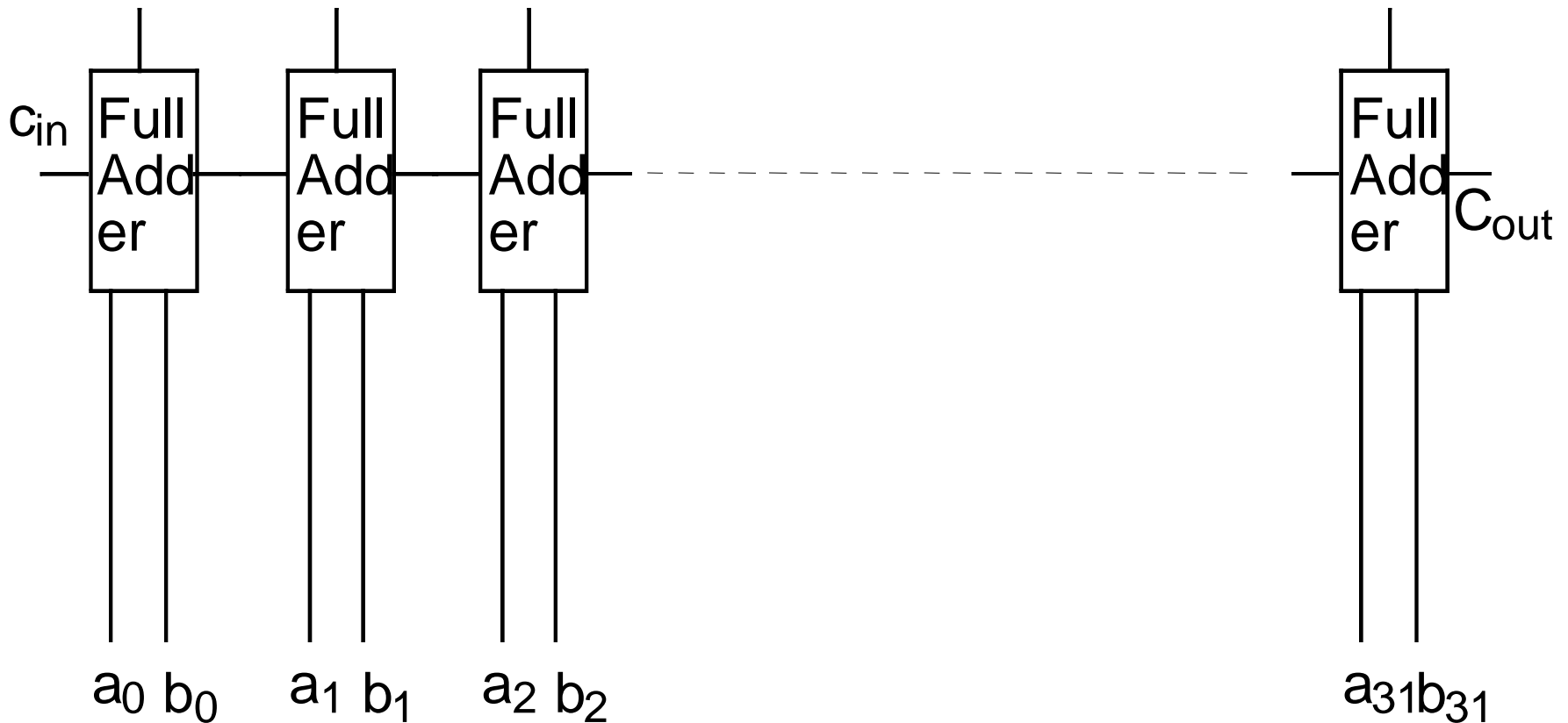


Ripple-carry Subtractor

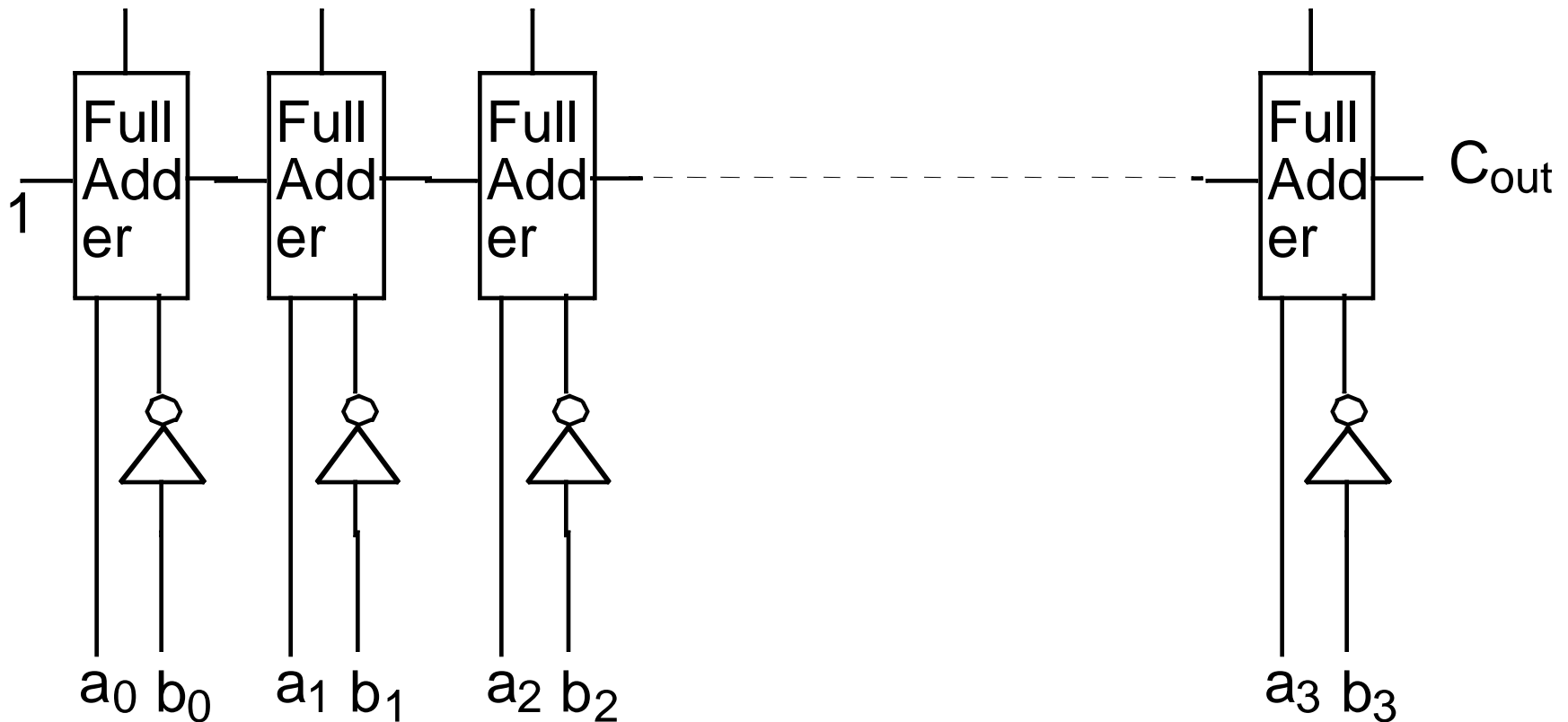- $A - B = A + (-B) \Rightarrow$ invert B and set c_{in} to 1



Combined Ripple-carry Adder/Subtractor

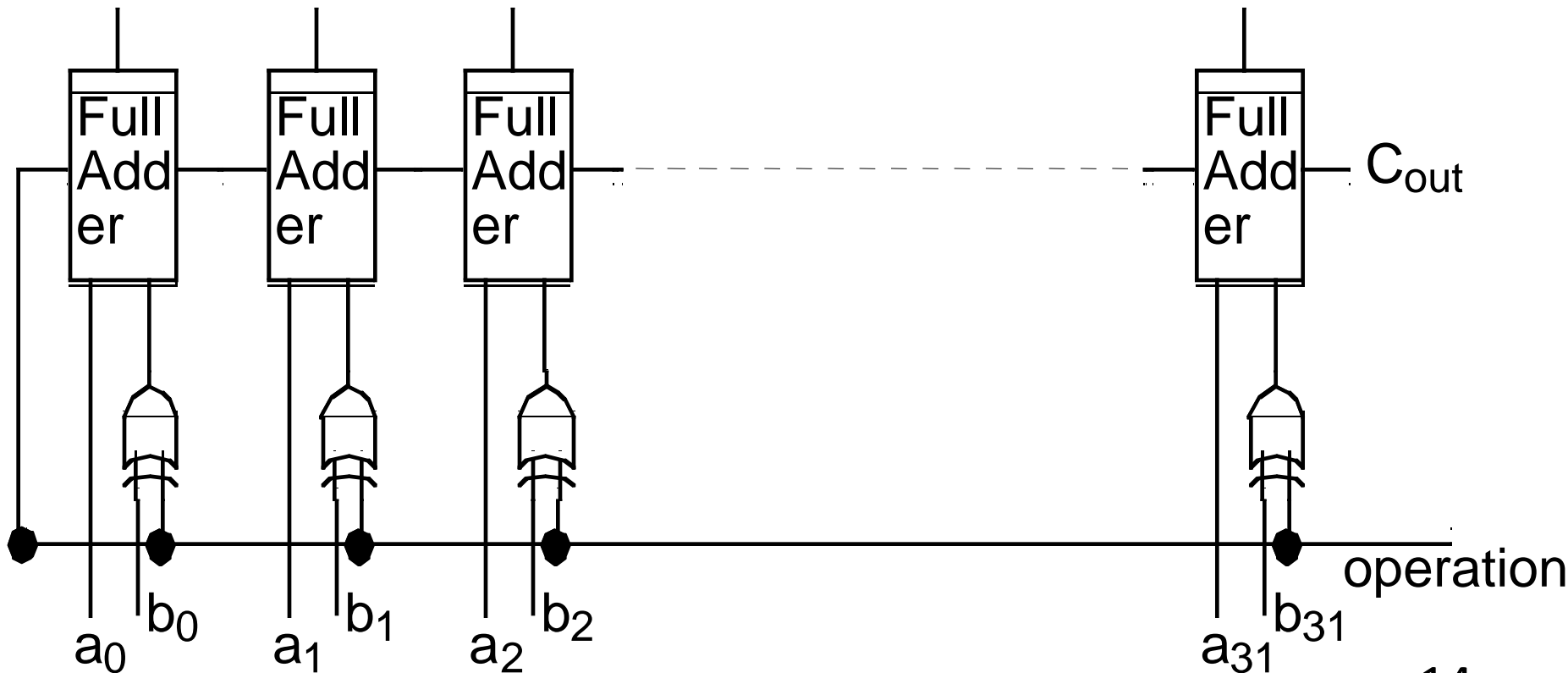
- Control = 1 => subtract
- XOR B with control and set c_{in0} to control



Logical Operations


- Bitwise AND, OR, XOR, NOR
 - Implement w/ 32 gates in parallel
- Shifts and rotates
 - rol => rotate left (MSB->LSB)
 - ror => rotate right (LSB->MSB)
 - sll -> shift left logical (0->LSB)
 - srl -> shift right logical (0->LSB)
 - sra -> shift right arithmetic (old MSB->new MSB)

Shifter

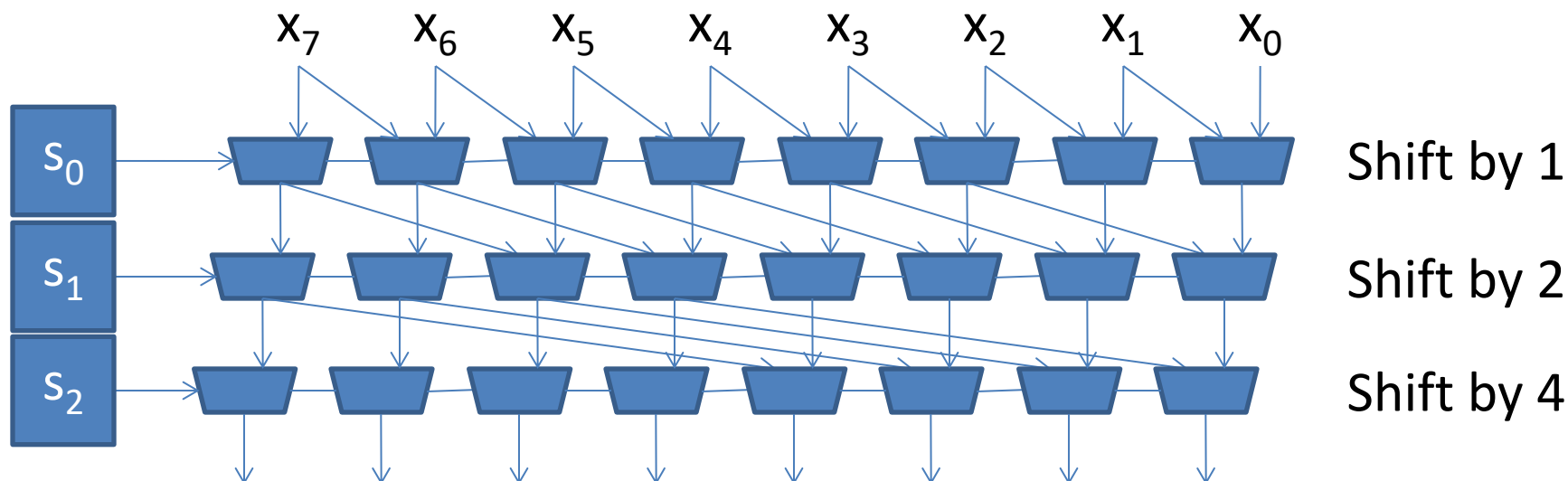

- Right shift logic shown: missing inputs are 0
 - Left shift logic similar
- Rotate: wraparound instead of 0 inputs

All Together

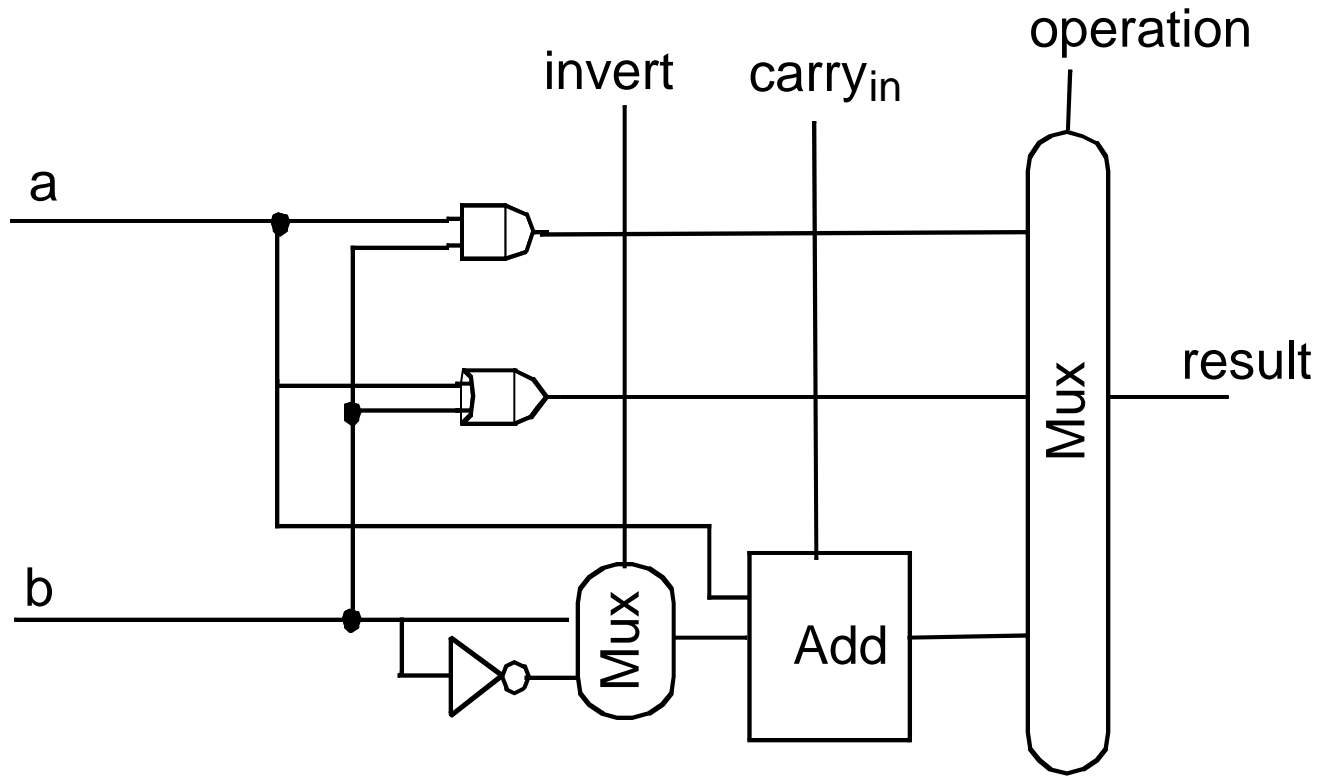

Overflow

- With n bits only 2^n combinations
 - Unsigned range $[0, 2^n-1]$
 - 2's complement range $[-2^{n-1}, 2^{n-1}-1]$

- Unsigned Add

$$5 + 6 > 7: 101 + 110 \Rightarrow 1011$$

$$f(3:0) = a(2:0) + b(2:0) \Rightarrow \text{overflow} = f(3)$$

Carryout from MSB

Overflow

- More involved for 2's complement
-1 + -1 = -2:
 $111 + 111 = 1110$
110 = -2 is correct
- Can't just use carry-out to signal overflow

Addition Overflow

- When is overflow NOT possible?
 $(p1, p2) > 0$ and $(n1, n2) < 0$
 $p1 + p2$
 $p1 + n1$ not possible
 $n1 + p2$ not possible
 $n1 + n2$
- Just checking signs of inputs is not sufficient

Addition Overflow

- $2 + 3 = 5 > 4$: $010 + 011 = 101 =? -3 < 0$
 - Sum of two positive numbers should not be negative
 - Conclude: overflow
- $-1 + -4$: $111 + 100 = 011 > 0$
 - Sum of two negative numbers should not be positive
 - Conclude: overflow

$$\text{Overflow} = f(2) * \sim(a2) * \sim(b2) + \sim f(2) * a(2) * b(2)$$

Subtraction Overflow

- No overflow on $a-b$ if signs are the same
- Neg – pos \Rightarrow neg ;; overflow otherwise
- Pos – neg \Rightarrow pos ;; overflow otherwise

$$\text{Overflow} = f(2) * \sim(a2)*(b2) + \sim f(2) * a(2) * \sim b(2)$$

What to do on Overflow?

- Ignore ! (C language semantics)
 - What about Java? (try/catch?)
- Flag – condition code
- Sticky flag – e.g. for floating point
 - Otherwise gets in the way of fast hardware
- Trap – possibly maskable
 - MIPS has e.g. add that traps, addu that does not
 - Useful for extended precision in software

Zero and Negative

- Zero = $\sim[f(2) + f(1) + f(0)]$
- Negative = $f(2)$ (sign bit)

Zero and Negative

- May also want correct answer even on overflow
- Negative = $(a < b) = (a - b) < 0$ even if overflow
- E.g. is $-4 < 2$?
 $100 - 010 = 1010$ ($-4 - 2 = -6$): Overflow!
- Work it out: negative = $f(2)$ XOR overflow

Summary

- Binary representations, signed/unsigned
- Arithmetic
 - Full adder, ripple-carry, adder/subtractor
 - Overflow, negative
- Logical
 - Shift, and, or
- Next: high-performance adders
 - Later: multiply/divide/FP




ECE/CS 552: Carry Lookahead

© Prof. Mikko Lipasti

Lecture notes based in part on slides created by Mark Hill, David Wood, Guri Sohi, John Shen and Jim Smith

Combined Ripple-carry Adder/Subtractor

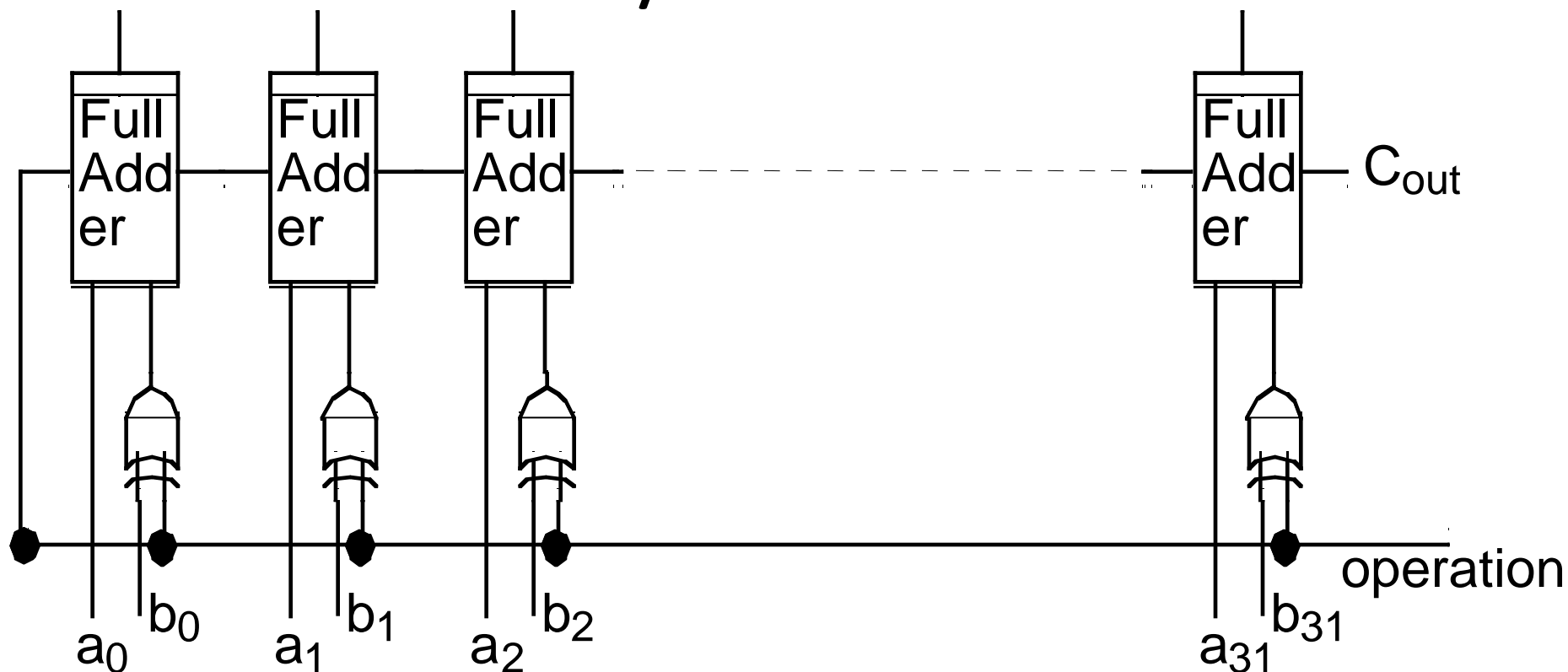

- The above ALU is too slow
 - Gate delays for add = $32 \times \text{FA} + \text{XOR} \approx 64$

Carry Lookahead

- Theoretically, in parallel
 - $\text{Sum}_0 = f(c_{\text{in}}, a_0, b_0)$
 - $\text{Sum}_i = f(c_{\text{in}}, a_i \dots a_0, b_i \dots b_0)$
 - $\text{Sum}_{31} = f(c_{\text{in}}, a_{31} \dots a_0, b_{31} \dots b_0)$
- Any boolean function in two levels, right?
 - Wrong! Too much fan-in!

Carry Lookahead

- Need compromise
 - Build tree so delay is $O(\log_2 n)$ for n bits
 - E.g. 2 x 5 gate delays for 32 bits
- We will consider basic concept with
 - 4 bits
 - 16 bits
- Warning: a little convoluted

Carry Lookahead

0101 0100

0011 0110

Need:

both 1 to generate carry

one or both 1s to propagate carry

Define: $g_i = a_i * b_i$ ## carry generate
 $p_i = a_i + b_i$ ## carry propagate

Recall: $c_{i+1} = a_i * b_i + a_i * c_i + b_i * c_i$
 $= a_i * b_i + (a_i + b_i) * c_i$
 $= g_i + p_i * c_i$

Carry Lookahead

- Therefore

$$c_1 = g_0 + p_0 * c_0$$


$$\begin{aligned} c_2 &= g_1 + p_1 * c_1 = g_1 + p_1 * (g_0 + p_0 * c_0) \\ &= g_1 + p_1 * g_0 + p_1 * p_0 * c_0 \end{aligned}$$

$$c_3 = g_2 + p_2 * g_1 + p_2 * p_1 * g_0 + p_2 * p_1 * p_0 * c_0$$


$$c_4 = g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0 + p_3 * p_2 * p_1 * p_0 * c_0$$

- Uses one level to form p_i and g_i , two levels for carry
- But, this needs $n+1$ fanin at the OR and the rightmost AND

4-bit Carry Lookahead Adder

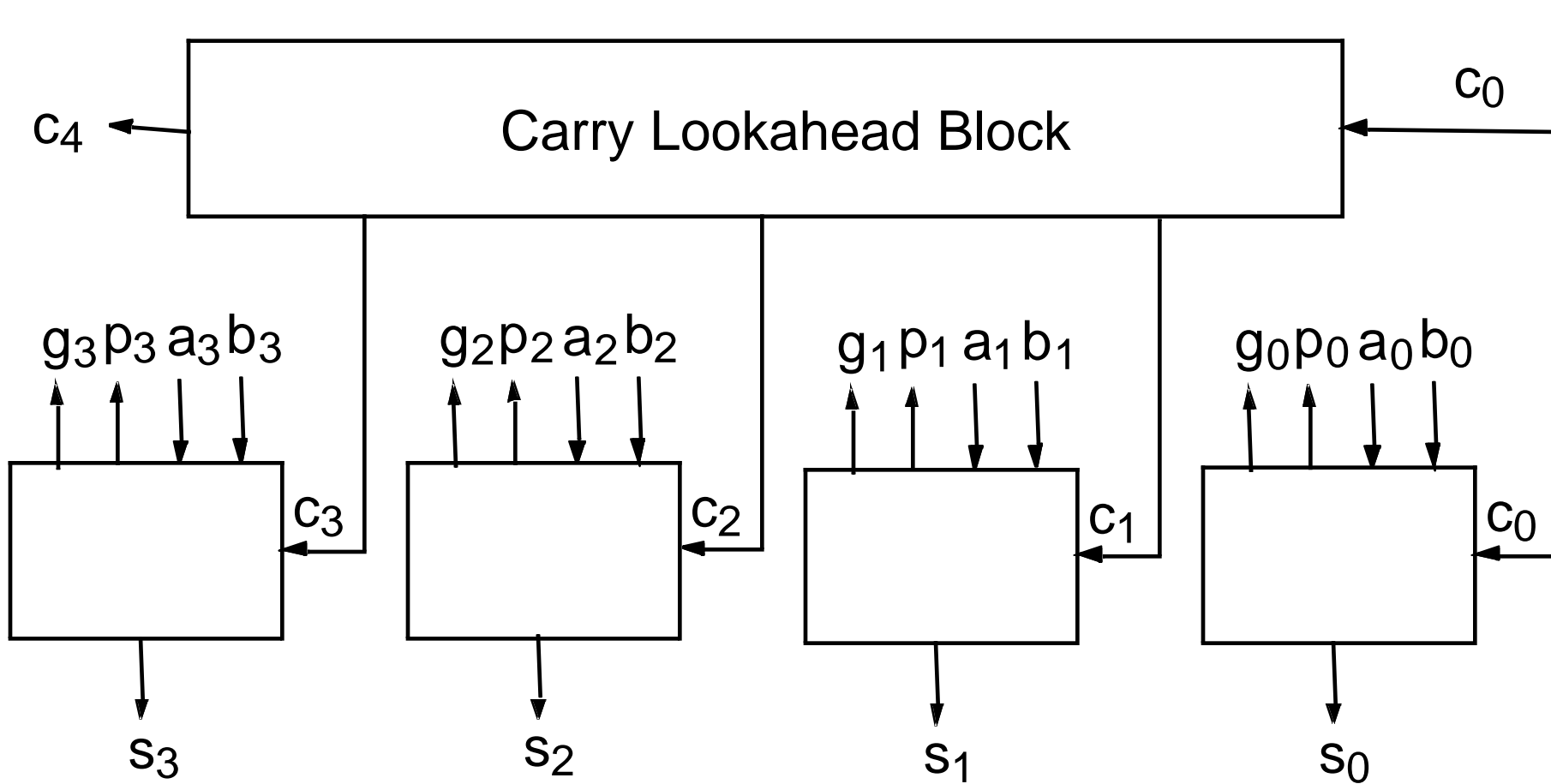

Hierarchical Carry Lookahead for 16 bits

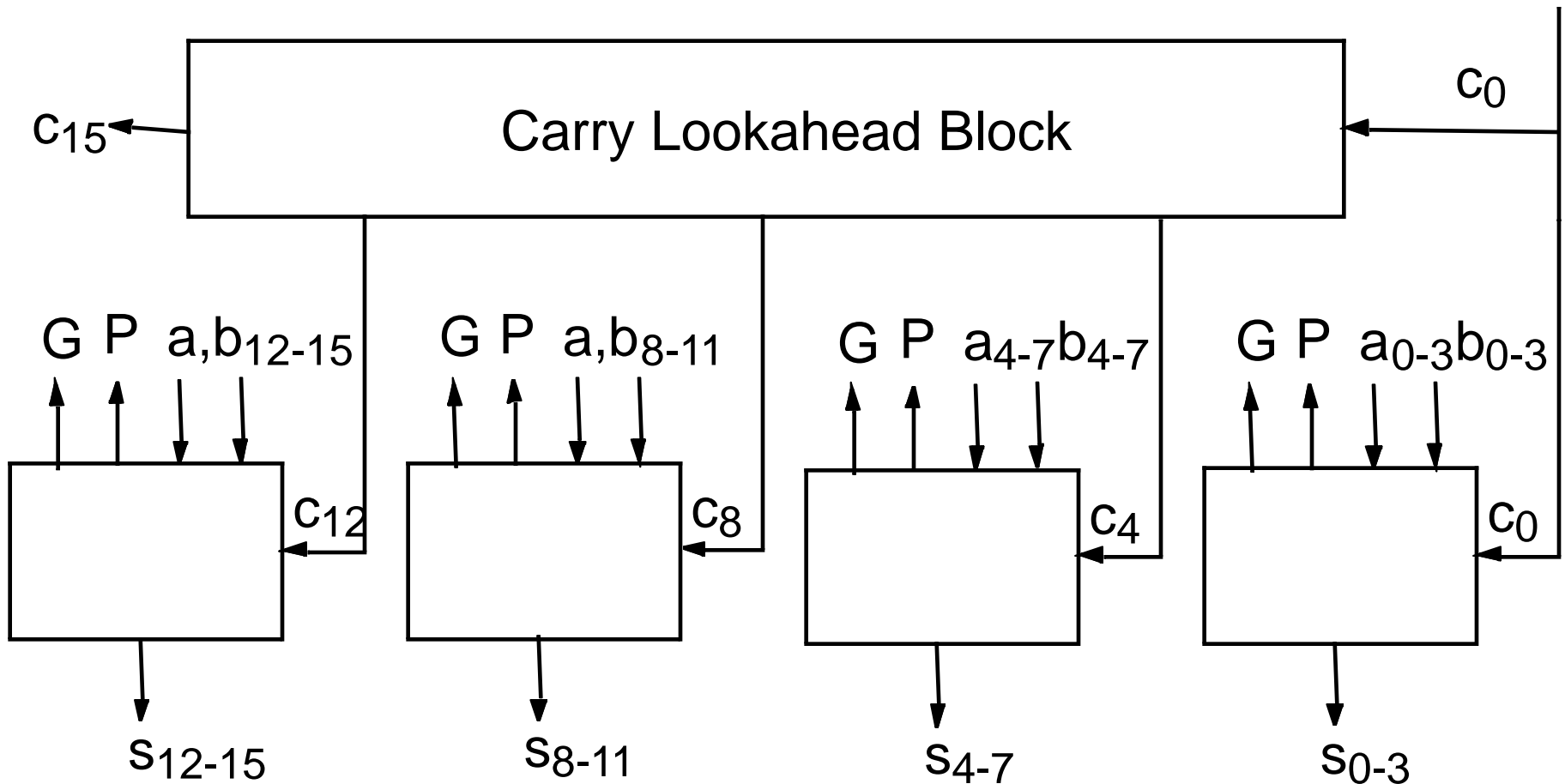

Hierarchical CLA for 16 bits

Build 16-bit adder from four 4-bit adders

Figure out G and P for 4 bits together

$$G_{0,3} = g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0$$

$$P_{0,3} = p_3 * p_2 * p_1 * p_0 \text{ (Notation a little different from the book)}$$

$$G_{4,7} = g_7 + p_7 * g_6 + p_7 * p_6 * g_5 + p_7 * p_6 * p_5 * g_4$$

$$P_{4,7} = p_7 * p_6 * p_5 * p_4$$

$$G_{12,15} = g_{15} + p_{15} * g_{14} + p_{15} * p_{14} * g_{13} + p_{15} * p_{14} * p_{13} * g_{12}$$

$$P_{12,15} = p_{15} * p_{14} * p_{13} * p_{12}$$

Carry Lookahead Basics

Fill in the holes in the G's and P's

$$G_{i,k} = G_{j+1,k} + P_{j+1,k} * G_{i,j} \quad (\text{assume } i < j+1 < k)$$

$$P_{i,k} = P_{i,j} * P_{j+1,k}$$

$$G_{0,7} = G_{4,7} + P_{4,7} * G_{0,3}$$

$$P_{0,7} = P_{0,3} * P_{4,7}$$


$$G_{8,15} = G_{12,15} + P_{12,15} * G_{8,11}$$

$$P_{8,15} = P_{8,11} * P_{12,15}$$


$$G_{0,15} = G_{8,15} + P_{8,15} * G_{0,7}$$

$$P_{0,15} = P_{0,7} * P_{8,15}$$

CLA: Compute G's and P's

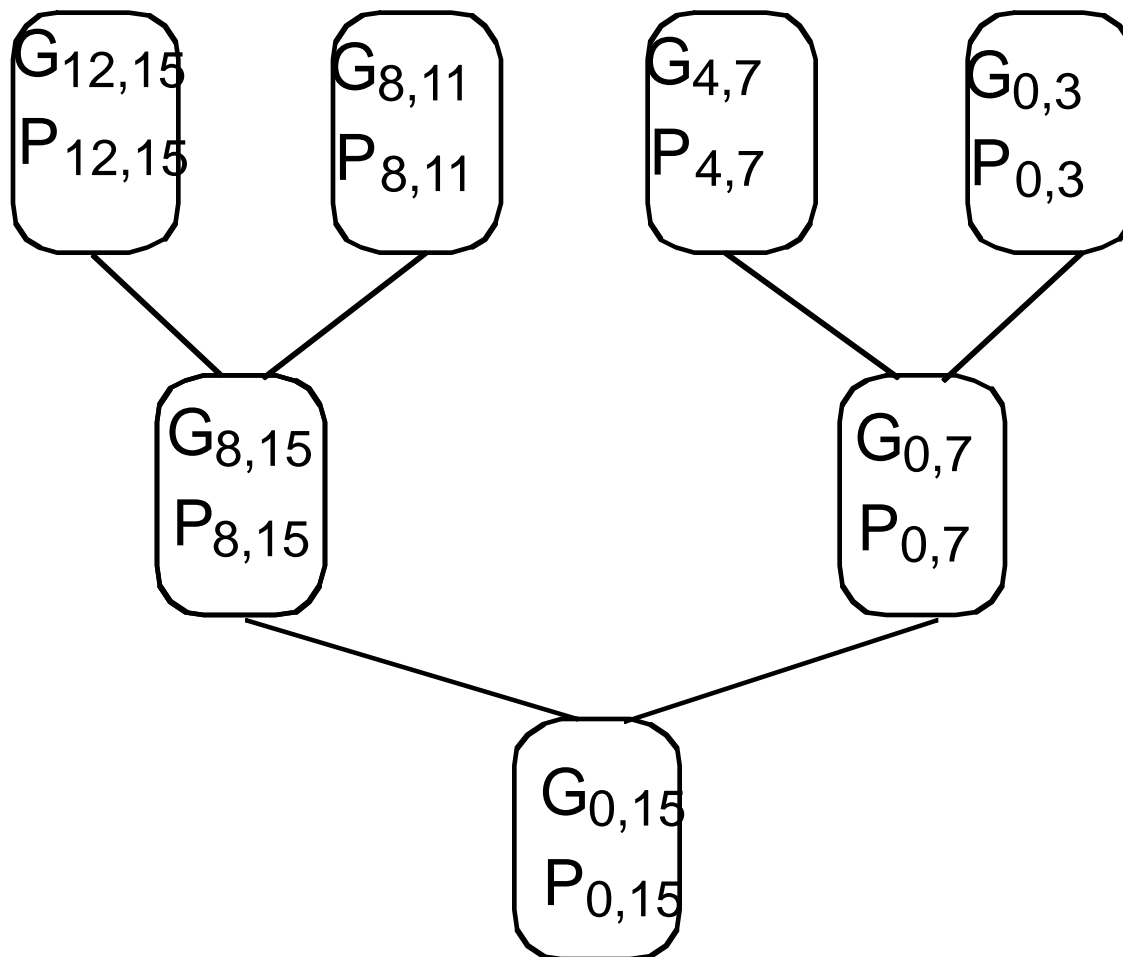


CLA: Compute Carries

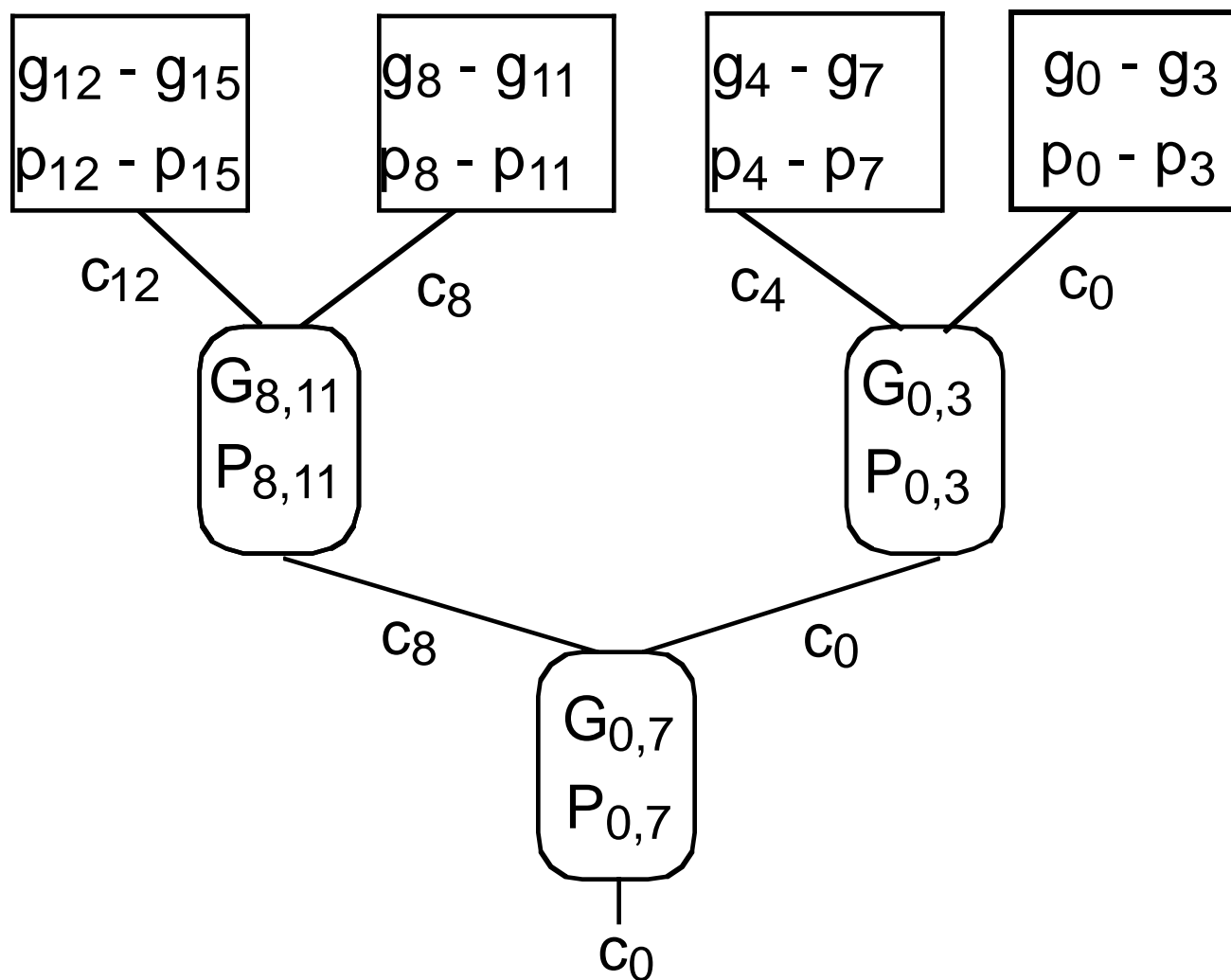

Other Adders: Carry Select

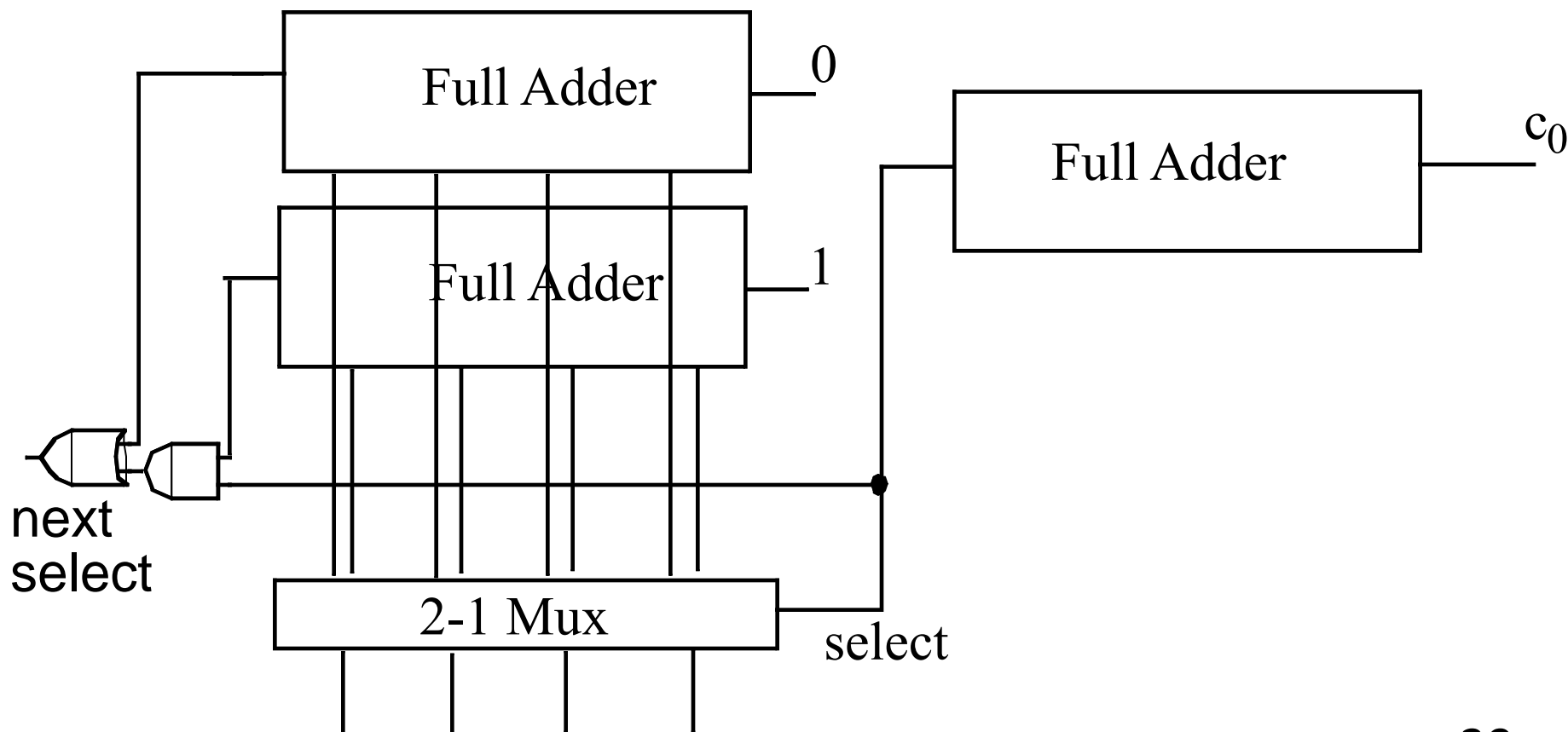- Two adds in parallel; with and without c_{in}
 - When C_{in} is done, select correct result



Other Adders: Carry Save


$A + B \Rightarrow S$

Save carries $A + B \Rightarrow S, C_{out}$


Use C_{in} $A + B + C \Rightarrow S1, S2$ (3# to 2# in parallel)

Used in combinational multipliers by building a Wallace Tree

	7	9
+	1	8
<hr/>		
C,S	0,8	1,7
Final	8+1=9	7

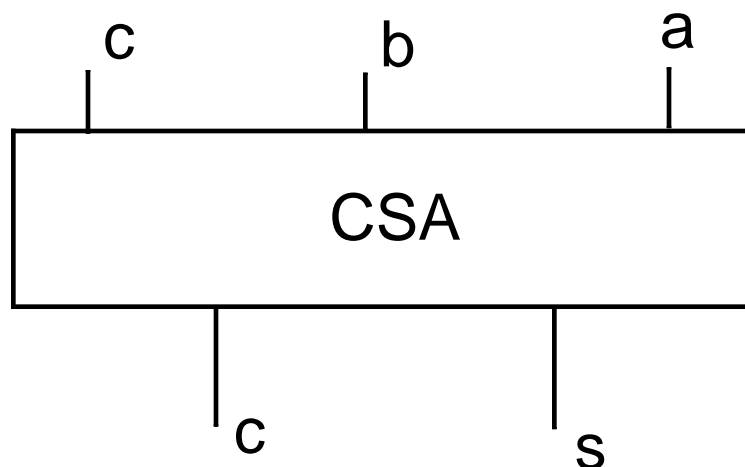

Adding Up Many Bits

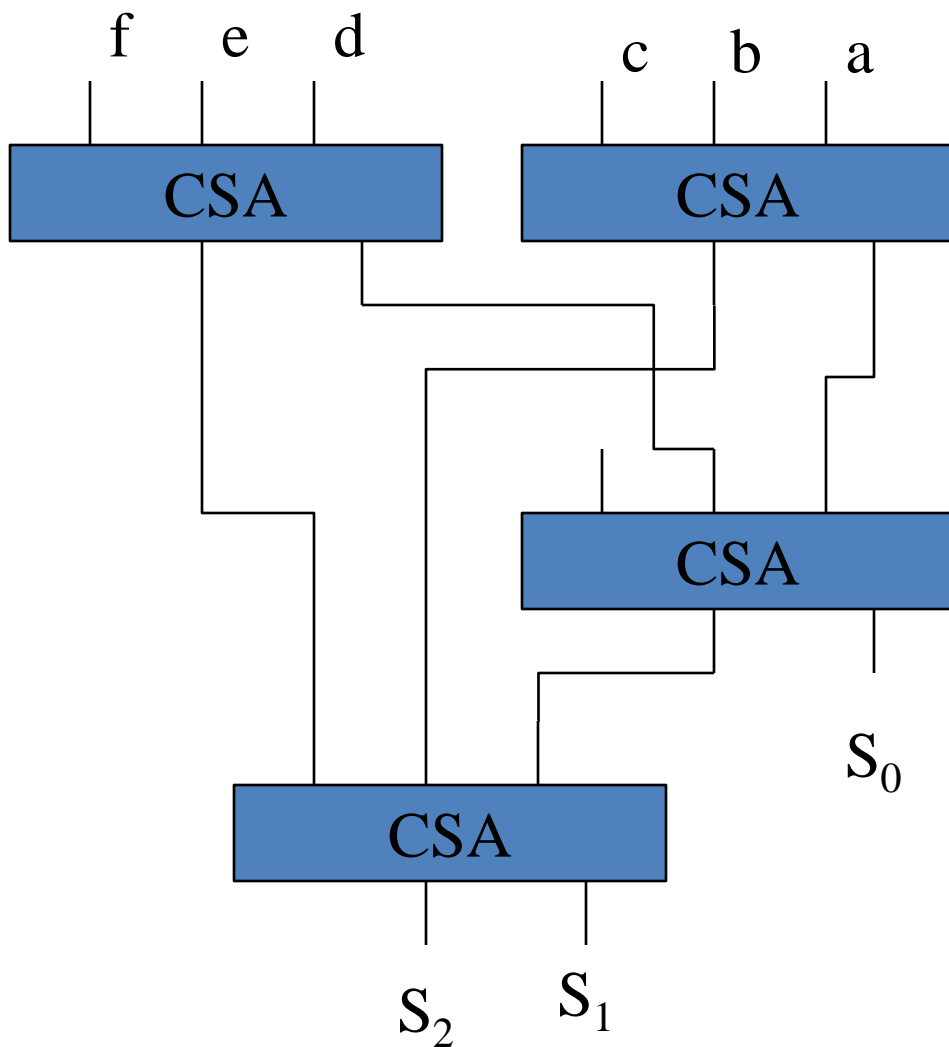

Summary

- Carry lookahead
- Carry-select, Carry-save
- State of the art: parallel prefix adders
 - aka. Brent-Kung, Kogge-Stone, ...
 - Generalization of CLA
 - Physical design (e.g. wiring) of primary concern
 - Covered in ECE 555