

# CS/ECE 252

# Exam 4 Review

11AM section  
2015 December 11



# Before we get started

Homework 8 due at beginning of lecture

Exam 4 on Monday, December 14th, during class

Today: Exam 4 Review

(Extra) office hours for HW8 and Exam4:

Dec 9th: Wednesday 12PM - 1PM in CS6367

Dec 9th: Wednesday 2:30PM - 3:30PM in CS7367

Dec 10th: Thursday 11AM - 4PM (possibly 5PM) in CS7367

Dec 10th: Thursday 12:45PM - 2:15PM in CS1308

Dec 11th: Friday 8AM - 8PM (minus class time) in CS1308

Dec 11th: Friday 12PM - 1PM in CS6367

Dec 11th: Friday 1PM - 2:30 in CS6352

Dec 11th: Friday 2:30PM - 3:30PM in CS7367


Dec 14th: Monday 8AM - 10AM in CS1308

Dec 14th: Monday 9:30AM - 11AM in CS1240

Quote of the day:


“Inspiration exists, but it has to find you working”

-- Pablo Picasso 1881 - 1973

 

# Cheatsheet


NOT GATE

 

A	B	Q
0	0	1
0	1	0

Text notation:  $\sim$

AND GATE

 

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

Text notation:  $\cdot$

OR GATE



A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

Text notation:  $+$

XOR GATE



A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

Text notation:  $\oplus$

NAND GATE



A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

NOR GATE



A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

XNOR GATE




A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

De Morgan's law

$$\sim(AB) = \sim A + \sim B$$


$$\sim(A + B) = (\sim A)(\sim B)$$

Using other gates

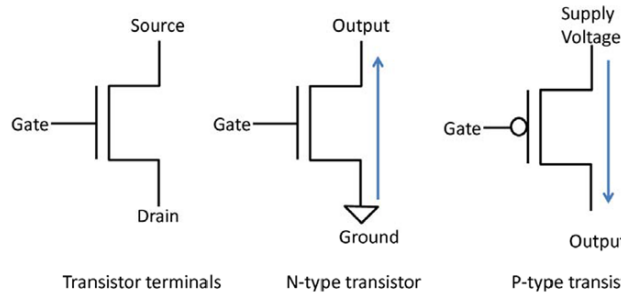

Gate	Behavior
1	Closed Output=0
0	Open Output=Z

Gate	Behavior
0	Closed Output=1
1	Open Output=Z

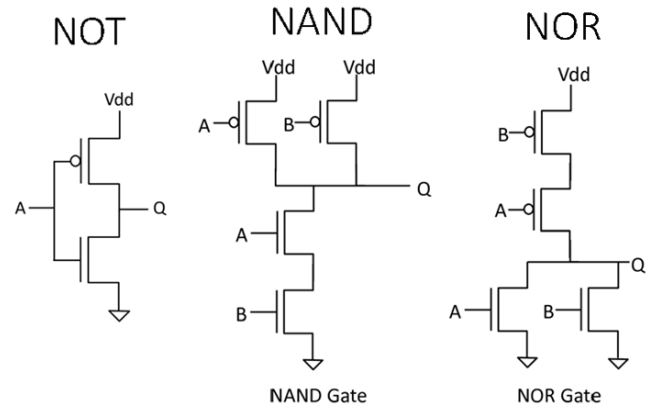

# Outline

## Chapter 8 Topics

Simple logic gates (AND, OR, NOT, XOR, NAND, NOR, XNOR)

Multiple inputs on any simple logic gates

Sum-of-products design for circuits

Take any truth table and design a circuit using AND, OR, and NOT gates

DeMorgan's Law

Simple circuits, such as multiplexers, full adders, half adders, decoders, encoders, and incrementors.

Principle behind control signal and next state circuits

R-S Latch, Gated D-Latch, Master-Slave flip-flop



Find the boolean expression for *Output* from following truth table. The boolean expression should be in terms of A and B and in sum-of-products (SOP) form.

A	B	C	output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$\text{output} = A'B'C + A'BC' + AB'C' + AB'C$$



Fill out the truth table for the following boolean equation.


$$\text{output} = ABC' + AB'C + A'B'C + A'BC' + A'B'C'$$

A	B	C	output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0



Implement the following boolean equation with logic gates.


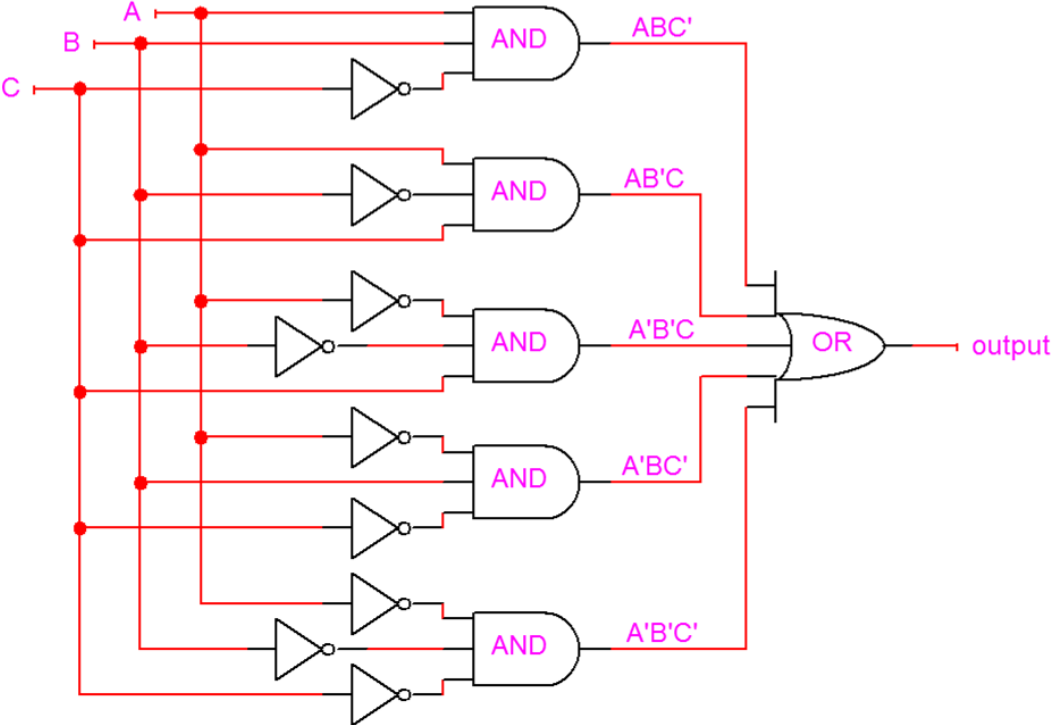
$$\text{output} = ABC' + AB'C + A'B'C + A'BC' + A'B'C'$$






Implement the following boolean equation with logic gates.

$$\text{output} = AB + A'B' + C$$

  



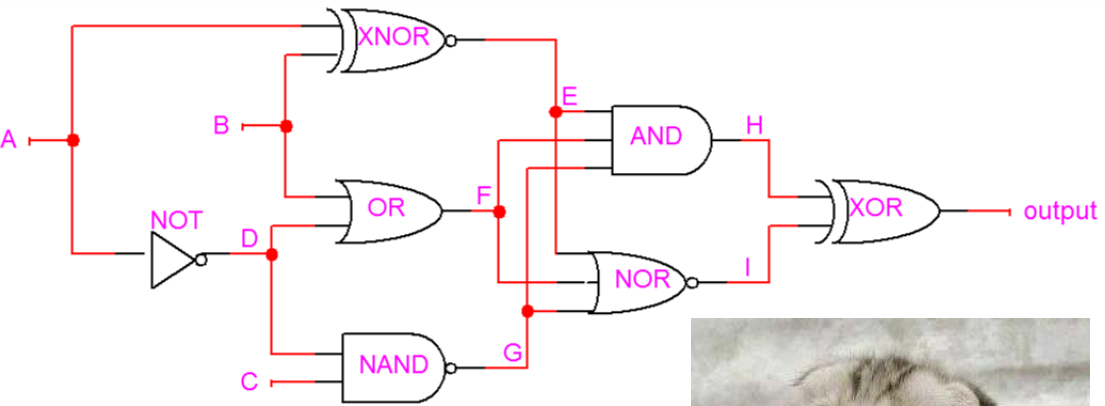Fill out the truth table for the logic gate level circuit below.



A	B	C	D	E	F	G	H	I	output
0	0	0	1	1	1	1	1	0	1
0	0	1	1	1	1	0	0	0	0
0	1	0	1	0	1	1	0	0	0
0	1	1	1	0	1	0	0	0	0
1	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	1	0	0	0
1	1	0	0	1	1	1	1	0	1
1	1	1	0	1	1	1	1	0	1

# De Morgan's Laws

$$\sim(AB) = \sim A + \sim B$$

given by cheatsheet

$$\sim(XY) = \sim X + \sim Y$$

by rewriting and changing variable name

$$(XY)' = X' + Y'$$

visualization

by rewriting and changing negation notation for better

$$(XYZ)' = X' + Y' + Z'$$

by expanding previous line to 3 product terms

$$\sim(A+B) = (\sim A)(\sim B)$$

given by cheatsheet

$$(X+Y+Z)' = X'Y'Z'$$

by applying same algorithm



Compute the negation of the following expression using DeMorgan's Law

$$AB'C + D'E + (A'+B)(C'+D+E')$$

Negation

$$= (AB'C + D'E + (A'+B)(C'+D+E'))' \text{ by negating entire expression}$$

$$= (AB'C)'(D'E)'((A'+B)(C'+D+E'))' \text{ by applying DeMorgan's Law on each of the 3 products}$$

$$= (AB'C)'(D'E)'((A'+B)' + (C'+D+E'))' \text{ by applying DeMorgan's Law on the rightmost product}$$

$$= (A'+B+C')(D+E)((AB') + (CD'E)) \text{ by applying DeMorgan's law on each sum on the rightmost product}$$

$$= (A'+B+C')(D+E)(AB'+CD'E) \text{ by removing unnecessary parentheses}$$



Compute the negation of the following expression using DeMorgan's Law

$$(A'+B+C')(D+E')(AB'+CD'E)$$

Negation

$$= ((A'+B+C')(D+E')(AB'+CD'E))' \text{ by negating entire expression}$$

$$= (A'+B+C)'+(D+E)'+(AB'+CD'E)' \text{ by applying DeMorgan's Law on each of the 3 sums}$$

$$= (AB'C)+(D'E)+((AB')'(CD'E)') \text{ by applying DeMorgan's Law on each sum}$$

$$= (AB'C)+(D'E)+((A'+B)(C'+D+E')) \text{ by applying DeMorgan's law on each product on the rightmost sum}$$

$$= AB'C+D'E+(A'+B)(C'+D+E') \text{ by removing unnecessary parentheses,}$$

which matches our original expression



# What is the difference between a latch and a flip-flop?

A flip-flop is edge triggered while latch isn't.



If the figure on the left is a (musical) conductor, then what is the figure on the right?



semiconductor



# Multiple Choice Question

What does 22nm transistors mean?

- a. the channel length is 22nm
- b. the distance between source and drain is 22nm
- c. the technology node is 22nm
- d. all of the above (correct answer)**
- e. none of the above





# Transistor Behavior

What are the three terminals on a transistor?


Gate, Source, Drain



How does a transistor (pmos) function when it is ON?

Voltage ( $V_{dd}$ ) is applied to the gate. An electric field is created so that electrons on the other side of the insulator create a channel, so that electrons can flow from the source to the drain.
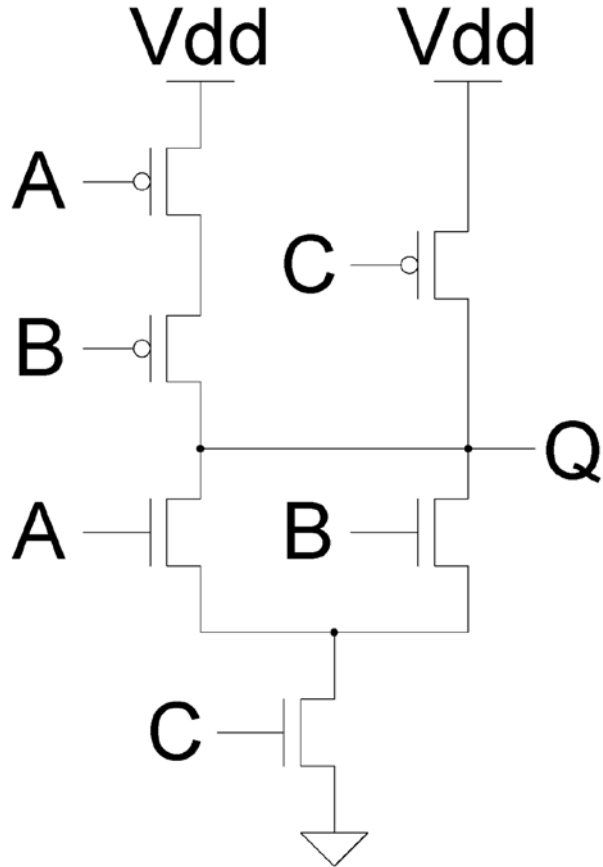
# Fill out the truth table for the following circuit



A	B	C	Q
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0



# What is Dennard Scaling?

Dennard scaling states that voltage scales down as length/size decreases.

Supply voltage is also acceptable

Voltage and/or current is also acceptable

Power density stays constant as transistor size scales is also acceptable

Power is proportional to area is also acceptable

