

CS/ECE 252: INTRODUCTION TO COMPUTER ENGINEERING

UNIVERSITY OF WISCONSIN—MADISON

Prof. Gurindar Sohi

TAs: Lisa Ossian, Minsub Shin, Sujith Surendran

Midterm Examination 2

In Class (50 minutes)

Friday, October 24, 2014

Weight: 17.5%

NO: BOOK(S), NOTE(S), OR CALCULATORS OF ANY SORT.

The exam has **nine** pages. **Circle your final answers.** Plan your time carefully since some problems are longer than others. You **must turn in the pages 1-9**. Use the blank sides of the exam for scratch work.

LAST NAME: _____

FIRST NAME: _____


ID#: _____

| Problem | Maximum Points | Points Earned |
|----------------|-----------------------|----------------------|
| 1 | 4 | |
| 2 | 6 | |
| 3 | 3 | |
| 4 | 5 | |
| 5 | 3 | |
| 6 | 9 | |
| Total | 30 | |


Problem 1**(4 Points)**

Consider the logic equation $Z = A \text{ OR } (B \text{ AND } C)$.

 
a. **(1 point)** Draw a **gate-level** circuit for Z using NOT gates and 2-input AND/OR gates.



 b. **(1 points)** Draw a **gate-level** circuit for Z using only 2-input NAND gates.




 c. **(2 points)** Implement a logic circuit for Z using a 4x1 multiplexer where A and B are connected to the select lines. Draw your answer using the 4x1 multiplexer below. **Do not use any additional logic gates.**



 Problem 2**(6 Points)**

The finite state machine (FSM) below (in Figure 1(a)) recognizes a certain bit sequence. The machine takes one input every clock cycle, which can be 1 or 0. The machine outputs a '1' when this certain bit sequence is recognized; otherwise it outputs a '0'. Each state is represented as S_1S_0 . For example, the state marked as "01" has $S_1 = 0$, and $S_0 = 1$. X is the output in each state. $S_1'S_0'$ represents the next state and the labels on each transition is the input value that triggers the transition. Assume that the initial state is 00.




| S_1 | S_0 | IN | S_1' | S_0' |
|-------|-------|----|--------|--------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 |

Figure 1

a. **(2 points)** Complete the Next State truth table for the FSM.

 b. **(3 Points)** Draw the logic circuit which implements the above FSM using combinational logic and flip flops. Use representation shown in figure 1(b) for any 1-bit flip flop required in the circuit (where CLK is the clock). You can use any kind of logic gates for implementing the combinational logic. Note: You should implement both the states (S_1 , S_0) as well as the output (X).




c. **(1 point)** Which bit sequence does the above FSM recognize? Your answer should be a string of bits (e.g, “1001” or “11001”).

110

 Problem 3

(3 Points)

Consider the following circuit containing a multiplexer, a single-bit full adder and a decoder. X and Y are inputs to this circuit, and the circuit produces an output Z. Fill in the truth table below for this combinational circuit.



| X | Y | Z |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


Problem 4**(5 Points)**

Consider the logic equation $Z = \text{NOT}(A \text{ AND } \text{NOT}(\text{NOT}(B) \text{ AND } \text{NOT}(C)))$. (Hint: You may want to use DeMorgan's law to simplify the equation.)

a. **(2 points)** Fill out the following truth table for Z.

| A | B | C | Z |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

 b. **(3 points)** Label the inputs on the transistor-level circuit below so that the circuit implements the logic function Z.



Problem 5**(3 Points)**

Suppose a 32-bit instruction takes the following format:

| | | | | |
|--------|----|----|--------|-----|
| OPCODE | SR | DR | UNUSED | IMM |
|--------|----|----|--------|-----|

Where SR = source register, DR= destination register, IMM = immediate value

Assuming that there are 257 opcodes and the IMM field is 11-bits wide, answer the following:

a. **(1 point)** What is the minimum number of bits required to represent the OPCODE?

$2^9 = 512 > 257$, so 9 bits

b. **(1 point)** If the source register (SR) and destination register (DR) each have 5 bits, what is the maximum number of registers supported by this instruction set architecture?

$2^5 = 32$ registers

c. **(1 point)** If the UNUSED bits were instead used for the register fields (SR and DR), how many more registers could we have in our computer?

$32 - 9 - 5 - 5 - 11 = 2$ bits in the UNUSED field. This means we can give $2/2 = 1$ bit to each the SR and DR field. So, we could represent $2^6 - 2^5 = 32$ more registers

Problem 6**(9 Points)**

a. **(2 points)** How many different n -input Boolean functions are possible? Show your work.

Given n inputs, 2^{2^n} functions are possible.

b. **(1 point)** How many select lines does an n -input mux have?

Let $n = 2^y$, since we know n must be a power of 2.

The number of select lines is y , or $\log_2 n$.

>> $\log_2 n$

c. **(1 point)** How many outputs does an n -input decoder have?

A decoder has n inputs and 2^n outputs

d. **(1 point)** What is the addressability (number of bytes per memory location) of a 1024 byte memory which uses 10 bits for each memory address? Show your work.

$$\begin{aligned} 1024 \text{ bytes} &= 2^{10} = 2^{10} \times 2^3 \text{ bits} \\ 2^{13} \text{ bits} \div 2^{10} \text{ bits} &= 2^3 \text{ bits} = 16 \text{ bits} \end{aligned}$$

e **(2 points)** How many n-type transistors are present in a 32-bit wide register? Show your work.

Each Gated D latch has 4 NAND gates and 1 inverter. Each NAND gate has 2 n-type transistors, and each inverter has 1 n-type transistor.

Therefore, we have $32 \times 4 \times 2 + 32 = 288$ n-type transistors.

f. **(1 point)** Mention two important things that happen during the FETCH phase of the instruction cycle.

Increment PC

Read the instruction, store in IR

g. **(1 Point)** Which of the following stages of instruction processing are required for the processing of an ADD instruction which reads value of 2 registers and stores the final value into another register. Circle all that apply:

Fetch

Decode

Evaluate address

Fetch operands from the memory

Execute Operation

Store result