

CS/ECE 252: INTRODUCTION TO COMPUTER ENGINEERING
COMPUTER SCIENCES DEPARTMENT
UNIVERSITY OF WISCONSIN-MADISON

Prof. Mark D. Hill & Prof. Mikko Lipasti
TAs Sanghamitra Roy, Eric Hill, Samuel Javner, Natalie Enright
Jerger & Guoliang Jin
Midterm Examination 2
In Class (50 minutes)
Friday, October 26, 2007
Weight: 15%

CLOSED BOOK, NOTE, CALCULATOR, PHONE, & COMPUTER.

The exam is two-sided and has 11 pages, including two blank pages at the end.

Plan your time carefully, since some problems are longer than others.

NAME: _____

SECTION: _____

ID# _____

Problem Number	Maximum Points	Actual Points
1	3	
2	4	
3	3	
4	2	
5	3	
6	4	
7	3	
8	4	
9	4	
Total	30	

Problem 1 (3 points)

Write the Boolean expression corresponding to the following truth table. You need not simplify the expression.

Inputs			Output
A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Problem 2 (4 points)

Suppose a 32-bit instruction takes the following format:


OPCODE	DR	SR1	SR2	UNUSED
--------	----	-----	-----	--------

If there are 225 opcodes and 120 registers:

- What is the minimum number of bits required to represent the OPCODE?
- What is the minimum number of bits required to represent the destination register DR, and source registers SR1 and SR2? (Give the total number of bits.)
- What is the maximum number of UNUSED bits in the instruction encoding?

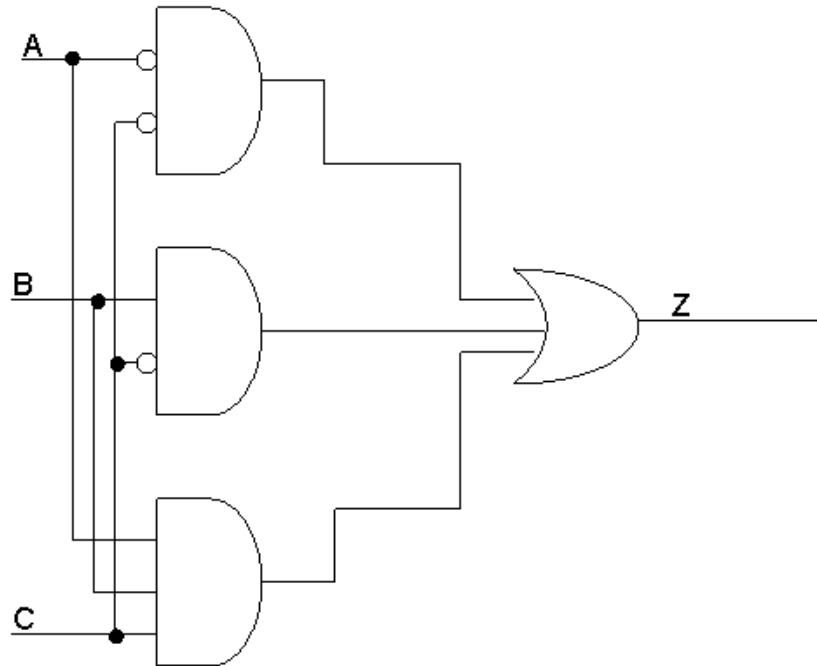Problem 3 (3 points)

The figure below shows a combinational logic circuit. Complete the truth table corresponding to this circuit.




Inputs			Output
A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Problem 4 (2 points)

You know a byte is 8 bits. A 4-bit quantity is called a nibble. If a byte-addressable memory has a 16-bit address, how many nibbles of storage are in this memory?

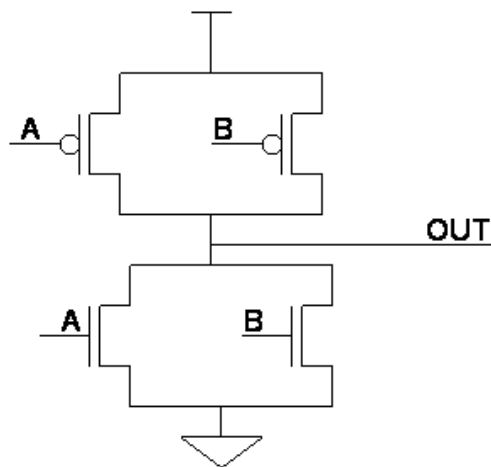
Problem 5 (3 points)

The circuit below has a major flaw. Can you identify it? Hint: Evaluate the circuit for all sets of inputs.



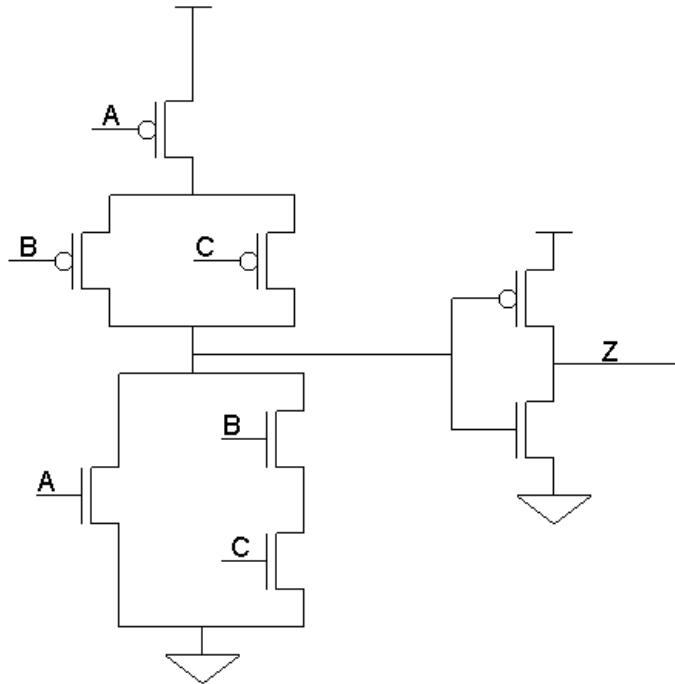Problem 6 (4 points)


Fill in the truth table for the following transistor level circuit. Note that two wires with the same name are assumed to be connected to each other.



Inputs			Output
A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

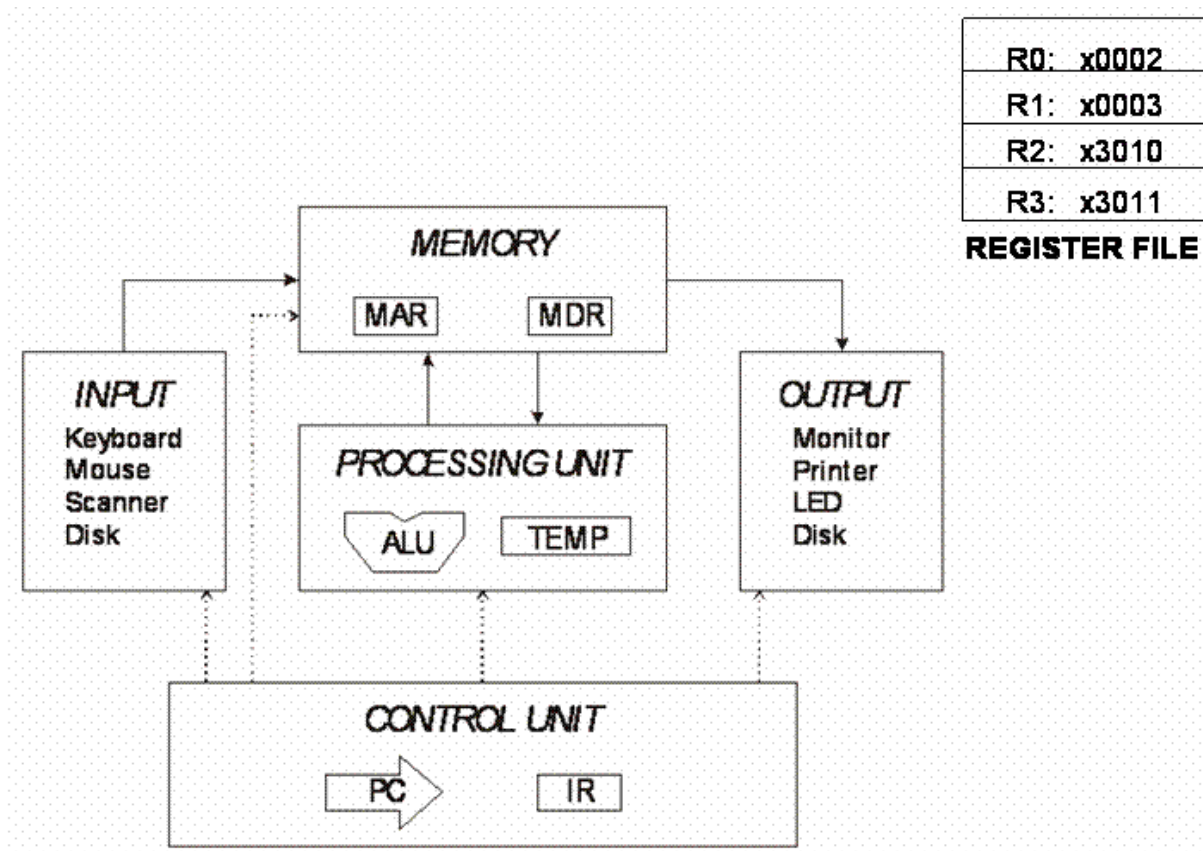Problem 7 (3 points)

The figure below shows a block diagram of the Von Neumann model.



List the steps in writing a value x0002 to a location x3010 in the memory. Your steps should mention the MAR and MDR where applicable.

- 1) _____
- 2) _____
- 3) _____

Problem 8 (4 points)

A Vending machine delivers a package of gum after 15 cents are deposited. It has a single coin slot which accepts only dimes (10 cents) or nickels (5 cents). (No other types of coins are accepted). The vending machine does not return back changes.

- I. Draw the finite state machine diagram for the vending machine. The machine takes one input every clock cycle which can be N, D or reset. The machine outputs a 1 when it opens to deliver a gum package, otherwise it outputs a 0.

- II. How many flip-flops (storage elements) will be needed to implement this finite state machine designed in your answer to part I?

Problem 9 (4 points)

Circle the correct answer for the following questions:

- I. Circuit A is a 1-bit adder calculating the sum only and no carry; circuit B is a 1 bit multiplier. Both the circuits are implemented using AND, OR and NOT gates only.
- Circuit A has more gates than circuit B
 - Circuit B has more gates than circuit A
 - Circuit A has the same number of gates as circuit B

(Hint: Construct the truth table for the adder and the multiplier)

- II. If the number of address bits in a memory is reduced by 2 and the addressability is doubled, the size of the memory (i.e., the number of bits stored in the memory)
- Doubles
 - Remains unchanged
 - Halves
 - Increases by $2^{(\text{address bits})/\text{addressability}}$
- III. The minimum number of transistors required to implement a CMOS 3 input OR gate is
- 4
 - 6
 - 8
 - 10
- IV. The Decode phase of the Instruction Cycle always examines which part of the instruction?
- Immediate (literal) value
 - Opcode
 - Offset
 - Register

Scratch Sheet 1 (in case you need additional space for some of your answers)

Scratch Sheet 2 (in case you need additional space for some of your answers)