

**CS/ECE 252: INTRODUCTION TO COMPUTER ENGINEERING  
COMPUTER SCIENCES DEPARTMENT  
UNIVERSITY OF WISCONSIN-MADISON**

Prof. Mark D. Hill  
TAs Marc de Kruijf & Sanghamitra Roy

Midterm Examination 2  
In Class (50 minutes)  
Wednesday, March 14, 2007  
Weight: 15%

**CLOSED BOOK, NOTE, CALCULATOR, PHONE, & COMPUTER.**

The exam is two-sided and has 9 pages, including two blank pages at the end.

Plan your time carefully, since some problems are longer than others.

NAME: \_\_\_\_\_

ID# \_\_\_\_\_

<b>Problem Number</b>	<b>Maximum Points</b>	<b>Actual Points</b>
1	3	MK
2	4	MK
3	4	MK
4	3	MK
5	4	MK
6	4	SR
7	4	SR
8	4	SR
Total	30	

**Problem 1 (3 points)**

Write the Boolean expression corresponding to the following truth table. You need not simplify the expression.

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$$\overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + A \overline{B} C$$

**Problem 2 (4 points)**

Suppose a 32-bit instruction takes the following format:

OPCODE	SR	DR	IMM
--------	----	----	-----

If there are 75 opcodes and 32 registers:

- a) What is the minimum number of bits required to represent the OPCODE?

$$\lceil \log_2 75 \rceil = 7$$

- b) What are the minimum number of bits required to represent SR and DR?


$$\lceil \log_2 32 \rceil = 5$$

- c) What is the range of values that can be represented by the immediate (IMM)?  
Assume IMM is a 2's complement value.

$$32 - 7 - 2 \times 5 = 15 \rightarrow 2^{15} \text{ values} \rightarrow \text{range: } -2^{14} \text{ to } 2^{14} - 1$$

 **Problem 3 (4 points)**

The figure below shows a combinational logic circuit. Complete the truth table corresponding to this circuit. What 3-input gate is equivalent to this logic circuit?



A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Equivalent 3-input gate is: **3-input OR gate**


**Problem 4 (3 points)**

A load to a memory uses a 14-bit address  $A[13:0]$  to obtain a 12-bit value  $V[11:0]$ . What is the total number of bits that can be stored in the memory?

$2^{14}$  addresses, 12 bits per address  $\rightarrow 2^{14} \times 12$  bits of memory total

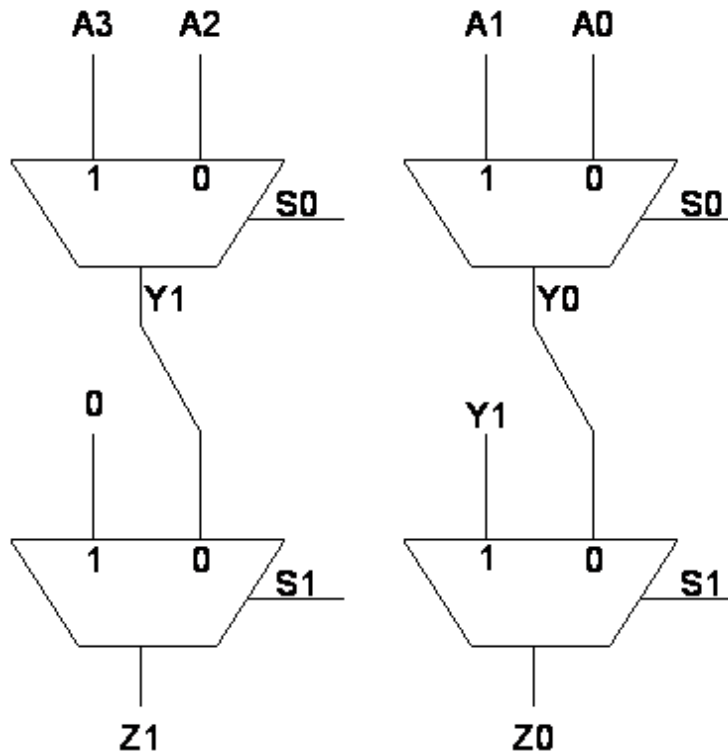**Problem 5 (4 points)**

The figure below shows a combinational logic circuit with 4 2-to-1 multiplexers. If  $S_0 = 1$  and  $S_1 = 0$ , what will be the values of  $Z_0$  and  $Z_1$ ? Express your answer in terms of  $A_0$ ,  $A_1$ ,  $A_2$  and  $A_3$ . Note that two wires with the same name are assumed to be connected to each other.




$Z_0 = A_1$

$Z_1 = A_3$

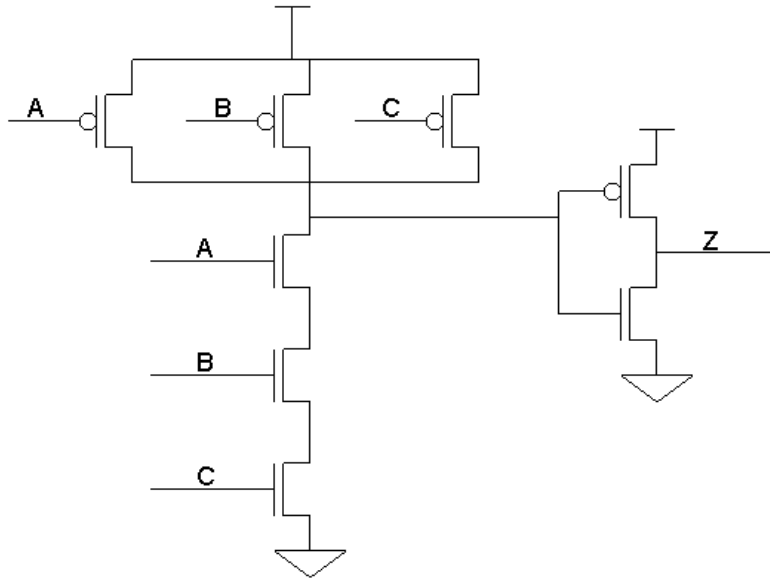**Problem 6 (4 points)**

Fill in the truth table for the following transistor level circuit. Note that two wires with the same name are assumed to be connected to each other.




A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

**Note:** This is the truth table for AND gate, if you did the truth table for a NAND gate overlooking the inverter, you received partial credit.

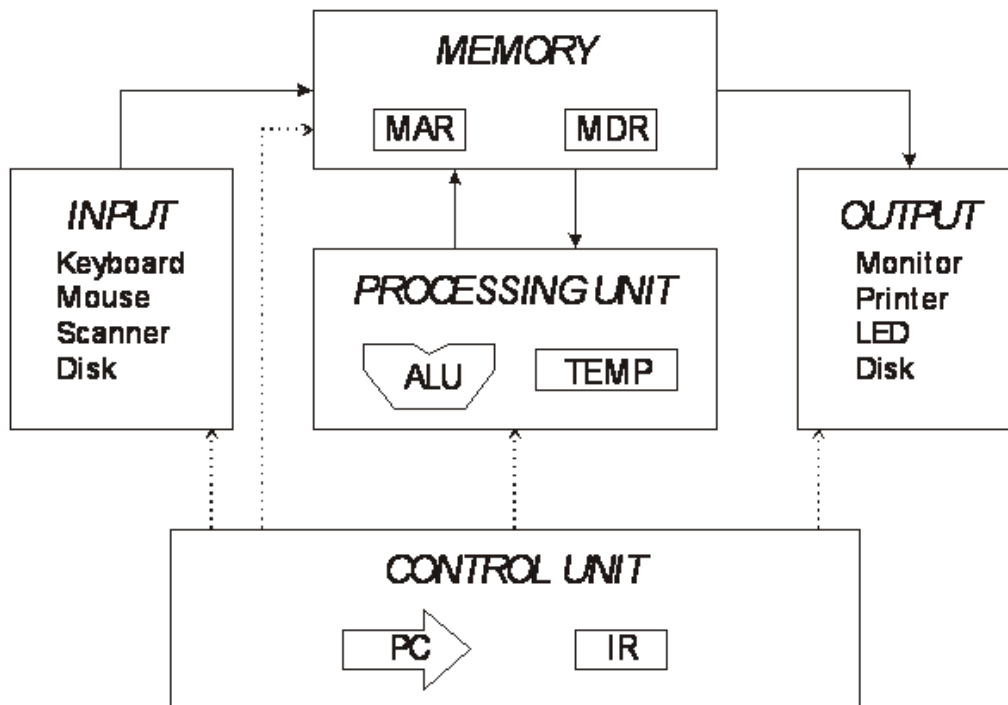**Problem 7 (4 points)**

The figure below shows a block diagram of the Von Neumann model.



List the steps in the FETCH stage of instruction processing in the Von Neumann model. A hint has been provided for you:

**Transfer contents of PC to MAR**

**Send “read” signal to memory**

**Read contents of MDR, store in IR**


**Increment PC**

**Problem 8 (4 points)**


A pattern detector is a finite state machine that outputs "1" when a particular sequence is detected and outputs "0" otherwise.

- a) Draw the finite state machine diagram for a pattern detector which detects the sequence '10'. The pattern detector takes a single bit (1 or 0) as input every clock cycle and outputs a 1 or 0 depending on whether or not the '10' sequence is seen in the input stream. Thus for an input stream '11000101' the output will be '00100010'

MOORE DESIGN

 

MEALY DESIGN

 

- b) How many flip-flops (storage elements) will be needed to implement this pattern detector?

**2 Flip-flops will be needed for the Moore machine design having 3 states.**

**1 Flip-flop will be needed for the Mealy machine design with 2 states.**

**Scratch Sheet 1 (in case you need additional space for some of your answers)**



**Scratch Sheet 2 (in case you need additional space for some of your answers)**