

**CS/ECE 252: INTRODUCTION TO COMPUTER ENGINEERING
COMPUTER SCIENCES DEPARTMENT
UNIVERSITY OF WISCONSIN-MADISON**

Prof. Mark D. Hill
TAs Marc de Kruijf & Sanghamitra Roy

Midterm Examination 2
In Class (50 minutes)
Wednesday, March 14, 2007
Weight: 15%

CLOSED BOOK, NOTE, CALCULATOR, PHONE, & COMPUTER.

The exam is two-sided and has 9 pages, including two blank pages at the end.

Plan your time carefully, since some problems are longer than others.

NAME: _____

ID# _____

Problem Number	Maximum Points	Actual Points
1	3	
2	4	
3	4	
4	3	
5	4	
6	4	
7	4	
8	4	
Total	30	

Problem 1 (3 points)

Write the Boolean expression corresponding to the following truth table. You need not simplify the expression.

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Problem 2 (4 points)

Suppose a 32-bit instruction takes the following format:


OPCODE	SR	DR	IMM
--------	----	----	-----

If there are 75 opcodes and 32 registers:

- What is the minimum number of bits required to represent the OPCODE?
- What are the minimum number of bits required to represent SR and DR?
- (2 points) What is the range of values that can be represented by the immediate (IMM)? Assume IMM is a two's complement value.

 Problem 3 (4 points)

The figure below shows a combinational logic circuit. Complete the truth table corresponding to this circuit. What 3-input gate is equivalent to this logic circuit?



A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Equivalent 3-input gate is:

Problem 4 (3 points)

A load to a memory uses a 14-bit address $A[13:0]$ to obtain a 12-bit value $V[11:0]$. What is the total number of bits that can be stored in all of the memory?

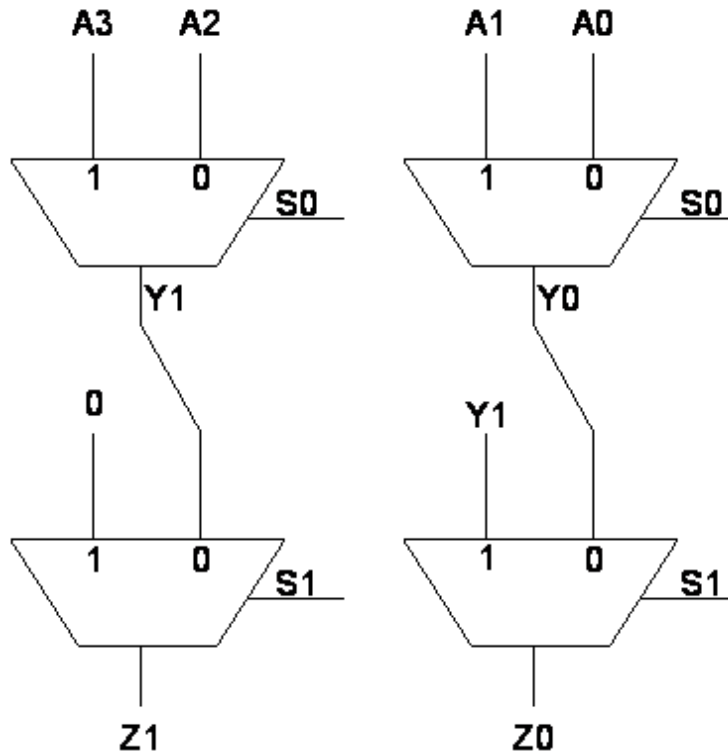Problem 5 (4 points)

The figure below shows a combinational logic circuit with four 2-to-1 multiplexers. If $S_0 = 1$ and $S_1 = 0$, what will be the values of Z_0 and Z_1 ? Express your answer in terms of A_0 , A_1 , A_2 and A_3 . Note that two wires with the same name are assumed to be connected to each other.




$Z_0 =$

$Z_1 =$

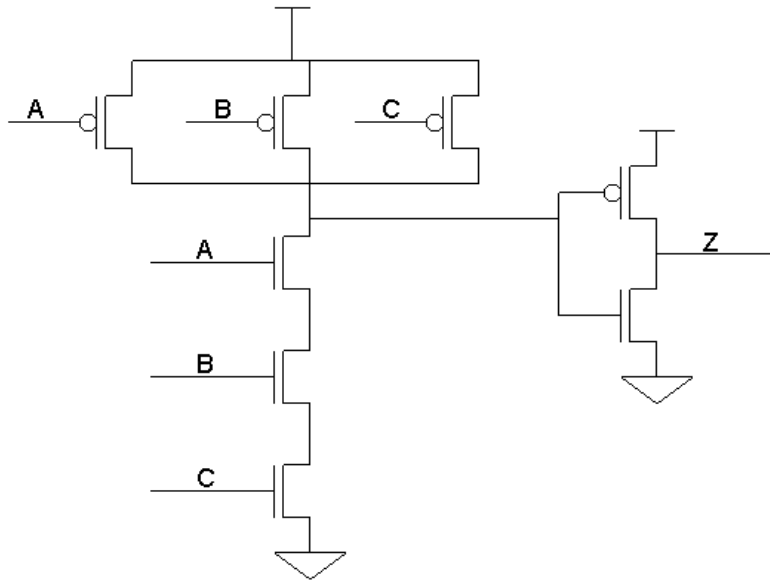Problem 6 (4 points)


Fill in the truth table for the following transistor level circuit. Note that two wires with the same name are assumed to be connected to each other.



A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

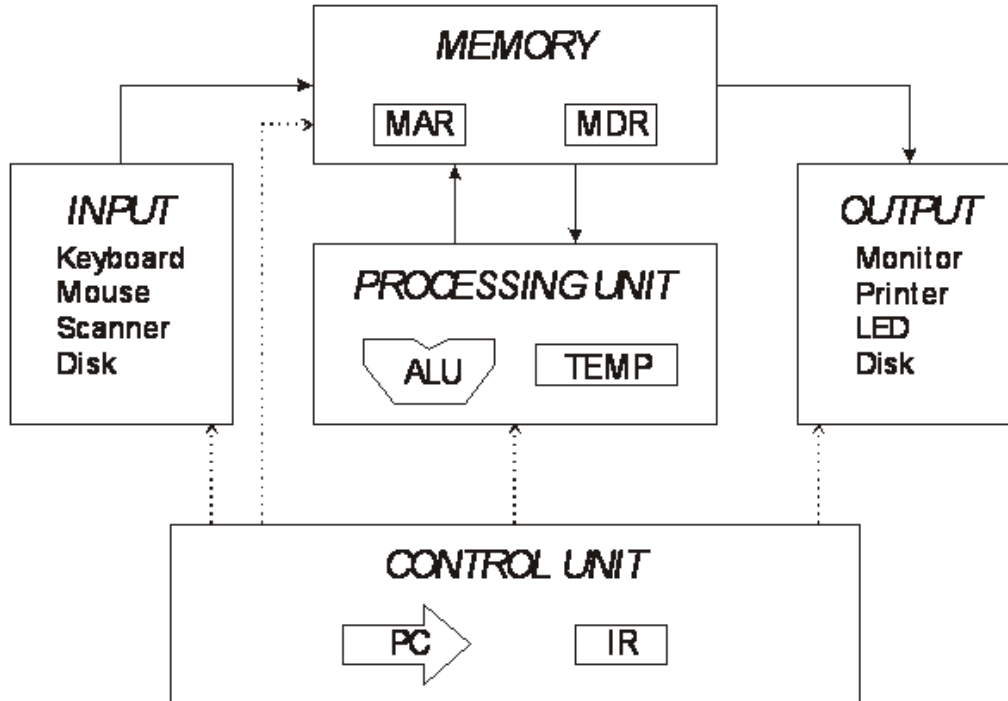Problem 7 (4 points)

The figure below shows a block diagram of the Von Neumann model.



List the steps in the **FETCH** stage of instruction processing in the von Neumann model. The **bold** text below begins your answer:

Transfer contents of PC to MAR

Problem 8 (4 points)

A pattern detector is a finite state machine that outputs "1" when a particular sequence is detected and outputs "0" otherwise.

- a) Draw the finite state machine diagram for a pattern detector which detects the sequence '10'. The pattern detector takes a single bit (1 or 0) as input every clock cycle and outputs a 1 or 0 depending on whether or not the '10' sequence is seen in the input stream. Thus for an input stream '11000101' the output will be '00100010'

- b) How many flip-flops (storage elements) will be needed to implement this pattern detector? Why?

Scratch Sheet 1 (in case you need additional space for some of your answers)

Scratch Sheet 2 (in case you need additional space for some of your answers)