

ECE 551 Homework #1

Michelle Joy Moravan

February 10, 2006

1. *Give the following numbers in Verilog notation:*

- (a) *Decimal 28 in binary digits, 10 bits*
`10'b11100`
- (b) *Octal 37 in decimal digits, 6 bits*
`6'd31`
- (c) *Decimal -42 in hex digits, 11 bits*
`-11h'2a`


2. *Write the following Verilog vector declarations:*

- (a) *Input variable A, 3 bits wide, rightmost bit with highest index, leftmost bit at index 0*
`input A[0:2];`
- (b) *Output variable X, 5 bits wide, leftmost bit with highest index, rightmost bit at index 2*
`output X[6:2];`

 3. *Complete the Modelsim tutorial.*

I have completed the Modelsim tutorial. If I had any problems with it, I discussed them with the TA either in person or through email.

The corresponding waveform appears in Figure 1.



Entity:t_proc Architecture: Date: Thu Jan 26 23:31:46 CST 2006 Row: 1 Page: 1

Figure 1: Tutorial Waveform

4. Create a structural description of the following logic equations...

```

module problem4(output x, y, input a, b, c, d);
    wire not_b, not_c, not_d;
    wire x1, x2, x3;
    wire y1, y2, y3;

    not(not_b, b);
    not(not_c, c);
    not(not_d, d);

    and(x1, a, not_b);
    and(x2, not_b, not_c);
    and(x3, a, c, not_d);

    and(y1, a, b);
    and(y2, b, c);
    and(y3, a, c);

    or(x, x1, x2, x3);

```

```
    or(y, y1, y2, y3);
endmodule

`timescale 1ns/1ns
module t_problem4();
    reg[4:0] stim;
    wire xout, yout;

    problem4 m1(xout, yout, stim[3], stim[2], stim[1], stim[0]);

    initial $monitor("%t: x=%b, y=%b, a=%b, b=%b, c=%b, d=%b",
        $time, xout, yout, stim[3], stim[2], stim[1], stim[0]);


    initial #150 $finish;

    initial begin
        for(stim = 0; stim < 16; stim = stim + 1) begin #5;
            end
        end
    end
endmodule
```

Here is the \$monitor output:

```
run 120
#           0: x=1, y=0, a=0, b=0, c=0, d=0
#           5: x=1, y=0, a=0, b=0, c=0, d=1
#          10: x=0, y=0, a=0, b=0, c=1, d=0
#          15: x=0, y=0, a=0, b=0, c=1, d=1
#          20: x=0, y=0, a=0, b=1, c=0, d=0
#          25: x=0, y=0, a=0, b=1, c=0, d=1
#          30: x=0, y=1, a=0, b=1, c=1, d=0
#          35: x=0, y=1, a=0, b=1, c=1, d=1
#          40: x=1, y=0, a=1, b=0, c=0, d=0
#          45: x=1, y=0, a=1, b=0, c=0, d=1
#          50: x=1, y=1, a=1, b=0, c=1, d=0
#          55: x=1, y=1, a=1, b=0, c=1, d=1
#          60: x=0, y=1, a=1, b=1, c=0, d=0
#          65: x=0, y=1, a=1, b=1, c=0, d=1
#          70: x=1, y=1, a=1, b=1, c=1, d=0
#          75: x=0, y=1, a=1, b=1, c=1, d=1
#          80: x=1, y=0, a=0, b=0, c=0, d=0
```

 The corresponding waveform appears in Figure 2.



Entity: t_problem4 Architecture: Date: Sun Jan 29 15:56:22 CST 2006 Row: 1 Page: 1

Figure 2: Problem 4 Waveform

5. *Structurally implement a gray-code counter...*

```
module comb_gray_code(output [2:0] out,
                      input [2:0] in);
    wire [2:0] not_in;
    wire x2a, x2b_x1b, x1a, x0a, x0b;

    not(not_in[2], in[2]);
    not(not_in[1], in[1]);
    not(not_in[0], in[0]);

    and(x2a, in[0], in[2]);
    and(x2b_x1b, not_in[0], in[1]);
    and(x1a, in[0], not_in[2]);
    and(x0a, not_in[1], not_in[2]);
    and(x0b, in[1], in[2]);

    or(out[2], x2a, x2b_x1b);
    or(out[1], x1a, x2b_x1b);
    or(out[0], x0a, x0b);
endmodule
```

```
endmodule

module problem5(output[2:0] out, input clk, rst);
    wire[2:0] next_state;

    comb_gray_code cgc(next_state, out);
    dff dff2(out[2], next_state[2], clk, rst);
    dff dff1(out[1], next_state[1], clk, rst);
    dff dff0(out[0], next_state[0], clk, rst);
endmodule

module t_problem5();
    wire [2:0] out;
    reg clk, rst;

    problem5 gray_counter(out, clk, rst);

    initial $monitor("%t out=%b, rst=%b", $time, out, rst);
    initial #500 $finish;


    initial begin
        clk = 0; forever #5 clk = ~clk;
    end

    initial begin
        rst = 1; #10 rst = 0;
    end
endmodule
```

Here is the \$monitor output:

```
run 90
#           0 out=xxx, rst=1
#           5 out=000, rst=1
#          10 out=000, rst=0
#          15 out=001, rst=0
#          25 out=011, rst=0
#          35 out=010, rst=0
#          45 out=110, rst=0
#          55 out=111, rst=0
#          65 out=101, rst=0
#          75 out=100, rst=0
#          85 out=000, rst=0
```

 The corresponding waveform appears in Figure 3.



Entity: t_problem5 Architecture: Date: Sun Jan 29 17:08:05 CST 2006 Row: 1 Page: 1

Figure 3: Problem 5 Waveform

6. Structurally design a finite state machine...

- (a) Draw a FSM diagram for the circuit.

The FSM diagram appears in Figure 4. The circles represent the states, and the bits in each circle represent the current state. The arcs show transitions; the corresponding bits show the inputs that lead to each transition. The bits are ordered: dec, inc, rst. All possible combinations that can lead to a transition are listed. If more than one is possible, the answers are comma separated. Finally, an x in an input indicates a don't care.

- (b) Write the structural Verilog to implement the circuit.

```
module counter(output [2:0] next_state, input [2:0] cur_state, input inc, dec);
    wire [2:0] cur_state_inv;
    wire inc_inv, dec_inv;

    wire ns2_max_a, ns2_max_b, ns2_max_c, ns2_max_d, ns2_max_e, ns2_max_f;
    wire ns1_max_a, ns1_max_b, ns1_max_c, ns1_max_d, ns1_max_e, ns1_max_f;
    wire ns0_max_a, ns0_max_b, ns0_max_c, ns0_max_d;

    not(cur_state_inv[2], cur_state[2]);
    not(cur_state_inv[1], cur_state[1]);
    not(cur_state_inv[0], cur_state[0]);
```

 


Figure 4: Problem 6a: Finite State Machine

```

not(inc_inv, inc);
not(dec_inv, dec);

and(ns2_max_a, inc_inv, dec, cur_state_inv[2], cur_state_inv[1],
    cur_state_inv[0]);
and(ns2_max_b, inc, dec_inv, cur_state_inv[2], cur_state[1], cur_state[0]);
and(ns2_max_c, inc_inv, dec_inv, cur_state[2]);
and(ns2_max_d, cur_state[2], cur_state[1], cur_state_inv[0]);
and(ns2_max_e, dec, cur_state[2], cur_state[0]);
and(ns2_max_f, inc, cur_state[2], cur_state_inv[1]);

and(ns1_max_a, inc_inv, dec_inv, cur_state[1]);
and(ns1_max_b, inc, dec, cur_state[1]);
and(ns1_max_c, inc, cur_state[1], cur_state_inv[0]);
and(ns1_max_d, inc_inv, dec, cur_state_inv[1], cur_state_inv[0]);
and(ns1_max_e, inc_inv, dec, cur_state[1], cur_state[0]);
and(ns1_max_f, inc, dec_inv, cur_state_inv[1], cur_state[0]);

and(ns0_max_a, inc_inv, dec_inv, cur_state[0]);

```

```

    and(ns0_max_b, inc, dec, cur_state[0]);
    and(ns0_max_c, inc_inv, dec, cur_state_inv[0]);
    and(ns0_max_d, inc, dec_inv, cur_state_inv[0]);

    or(next_state[2], ns2_max_a, ns2_max_b, ns2_max_c, ns2_max_d, ns2_max_e,
        ns2_max_f);
    or(next_state[1], ns1_max_a, ns1_max_b, ns1_max_c, ns1_max_d, ns1_max_e,
        ns1_max_f);
    or(next_state[0], ns0_max_a, ns0_max_b, ns0_max_c, ns0_max_d);
endmodule

module problem6(output [2:0] state, input clk, rst, inc, dec);
    wire [2:0] next_state;

    counter cnt(next_state, state, inc, dec);
    dff dff2(state[2], next_state[2], clk, rst);
    dff dff1(state[1], next_state[1], clk, rst);
    dff dff0(state[0], next_state[0], clk, rst);
endmodule

module t_problem6();
    wire [2:0] state;
    reg clk;
    reg [2:0] commands;

    problem6 p6counter(state, clk, commands[2], commands[1], commands[0]);

    initial $monitor("%t rst=%d, inc=%d, dec=%d, st2=%d, st1=%d, st0=%d",
        $time, commands[2], commands[1], commands[0], state[2], state[1], state[0]);

    initial #500 $finish;

    initial begin
        clk = 0; forever #5 clk = ~clk;
    end

    initial begin
        commands = 3'b100;
        #10 commands = 3'b010;
        #100 commands = 3'b011;
        #10 commands = 3'b001;
        #50 commands = 3'b100;
    end

endmodule

```

(c) *Output the results of simulation...*


```

run 10
#           0 rst=1, inc=0, dec=0, st2=x, st1=x, st0=x
#           5 rst=1, inc=0, dec=0, st2=0, st1=0, st0=0
run 100
#          10 rst=0, inc=1, dec=0, st2=0, st1=0, st0=0

```

```
#          15 rst=0, inc=1, dec=0, st2=0, st1=0, st0=1
#          25 rst=0, inc=1, dec=0, st2=0, st1=1, st0=0
#          35 rst=0, inc=1, dec=0, st2=0, st1=1, st0=1
#          45 rst=0, inc=1, dec=0, st2=1, st1=0, st0=0
#          55 rst=0, inc=1, dec=0, st2=1, st1=0, st0=1
#          65 rst=0, inc=1, dec=0, st2=1, st1=1, st0=0
#          75 rst=0, inc=1, dec=0, st2=1, st1=1, st0=1
#          85 rst=0, inc=1, dec=0, st2=0, st1=0, st0=0
#          95 rst=0, inc=1, dec=0, st2=0, st1=0, st0=1
#         105 rst=0, inc=1, dec=0, st2=0, st1=1, st0=0
run 10
#         110 rst=0, inc=1, dec=1, st2=0, st1=1, st0=0
run 50
#         120 rst=0, inc=0, dec=1, st2=0, st1=1, st0=0
#         125 rst=0, inc=0, dec=1, st2=0, st1=0, st0=1
#         135 rst=0, inc=0, dec=1, st2=0, st1=0, st0=0
#         145 rst=0, inc=0, dec=1, st2=1, st1=1, st0=1
#         155 rst=0, inc=0, dec=1, st2=1, st1=1, st0=0
#         165 rst=0, inc=0, dec=1, st2=1, st1=0, st0=1
run 10
#         170 rst=1, inc=0, dec=0, st2=1, st1=0, st0=1
#         175 rst=1, inc=0, dec=0, st2=0, st1=0, st0=0
```

 The corresponding waveform appears in Figure 5.



Entity: t_problem6 Architecture: Date: Mon Jan 30 21:08:25 CST 2006 Row: 1 Page: 1

Figure 5: Problem 6 Waveform