






Introduction to Computer Engineering

CS/ECE 252, Spring 2017

Rahul Nayar

**Computer Sciences Department
University of Wisconsin – Madison**

   

Chapter 3

Digital Logic

Structures

Slides based on set prepared by
Gregory T. Byrd, North Carolina State University

In Class Exercise

1. Convert “Transistor” to hex

2. Convert the results above to binary

00 nul	10 dle	20 sp	30 0	40 @	50 P	60 `	70 p
01 soh	11 dc1	21 !	31 1	41 A	51 Q	61 a	71 q
02 stx	12 dc2	22 "	32 2	42 B	52 R	62 b	72 r
03 etx	13 dc3	23 #	33 3	43 C	53 S	63 c	73 s
04 eot	14 dc4	24 \$	34 4	44 D	54 T	64 d	74 t
05 enq	15 nak	25 %	35 5	45 E	55 U	65 e	75 u
06 ack	16 syn	26 &	36 6	46 F	56 V	66 f	76 v
07 bel	17 etb	27 '	37 7	47 G	57 W	67 g	77 w
08 bs	18 can	28 (38 8	48 H	58 X	68 h	78 x
09 ht	19 em	29)	39 9	49 I	59 Y	69 i	79 y
0a nl	1a sub	2a *	3a :	4a J	5a Z	6a j	7a z
0b vt	1b esc	2b +	3b ;	4b K	5b [6b k	7b {
0c np	1c fs	2c ,	3c <	4c L	5c \	6c l	7c
0d cr	1d gs	2d -	3d =	4d M	5d]	6d m	7d }
0e so	1e rs	2e .	3e >	4e N	5e ^	6e n	7e ~
0f si	1f us	2f /	3f ?	4f O	5f _	6f o	7f del

In Class Exercise

- **0x 54 72 61 6e 73 69 73 74 6f 72**
- **0101 0100 0111 0010 0110 0001 0110 1110 0111 0011
0110 1001 0111 0011 0111 0100 0110 0110 1111 0111
0010**

In Class Exercise

- Using 8 bits for each number, write the 1's complement, 2's complement, and signed magnitude binary number of the decimal numbers in the table below:

Decimal	1's Complement	2's Complement	Signed Magnitude
19			
-10			

In Class Exercise

- Using 8 bits for each number, write the 1's complement, 2's complement, and signed magnitude binary number of the decimal numbers in the table below:

Decimal	1's Complement	2's Complement	Signed Magnitude
19	00010011	00010011	00010011
-10	11110101	11110110	10001010

In Class Exercise

- **Convert the following 32-bit single-precision IEEE floating point number into decimal value**
- **1 10000010 010011000000000000000000**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the following 32-bit single-precision IEEE floating point number into decimal value**
- **1 10000010 010011000000000000000000**
- **-10.375**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the following 32-bit single-precision IEEE floating point number into decimal value**
- **1 10000010 010011000000000000000000**
- **-10.375**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the decimal value -10.25 into its 32 bit IEEE single-precision floating point representation.**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the decimal value -10.25 into its 32 bit IEEE single-precision floating point representation.**
- **Step 1:**
- **Write -10.25 as binary “-1010.01”**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the decimal value -10.25 into its 32 bit IEEE single-precision floating point representation.**
- **Step 2:**
- **Normalize “-1.01001 x (2³)”**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the decimal value -10.25 into its 32 bit IEEE single-precision floating point representation.**
- **Step 3:**
- **Sign bit “1”**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the decimal value -10.25 into its 32 bit IEEE single-precision floating point representation.**
- **Step 4:**
- **Exponent must satisfy $x-127=3$, thus $x=130$**
- **$x= 128 +2$**
- **$x= 2^7+2^1$**
- **$x=10000010$**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the decimal value -10.25 into its 32 bit IEEE single-precision floating point representation.**
- **Step 5**
- **The fraction field consists of numbers on the right side of the decimal point in -1.01001 with 23 bit precision**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

In Class Exercise

- **Convert the decimal value -10.25 into its 32 bit IEEE single-precision floating point representation.**
- **Answer**
- **1 1000010 010010000000000000000000**

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

$$N = -1^S \times 0.\text{fraction} \times 2^{-126}, \quad \text{exponent} = 0$$

Transistor: Building Block of Computers

Microprocessors contain millions of transistors

- Intel Pentium II: **7 million**
- Compaq Alpha 21264: **15 million**
- Intel Pentium III: **28 million**

Logically, each transistor acts as a switch

Combined to implement logic functions

- **AND, OR, NOT**

Combined to build higher-level structures

- **Adder, multiplexer, decoder, register, ...**


Combined to build processor

- **LC-3**


Abstraction and Complexity

- **Abstraction helps us manage complexity**
- **Complex interfaces**
 - Specify **what** to do
 - Hide details of **how**
- Goal: Use abstractions yet still understand details

Scope of this course

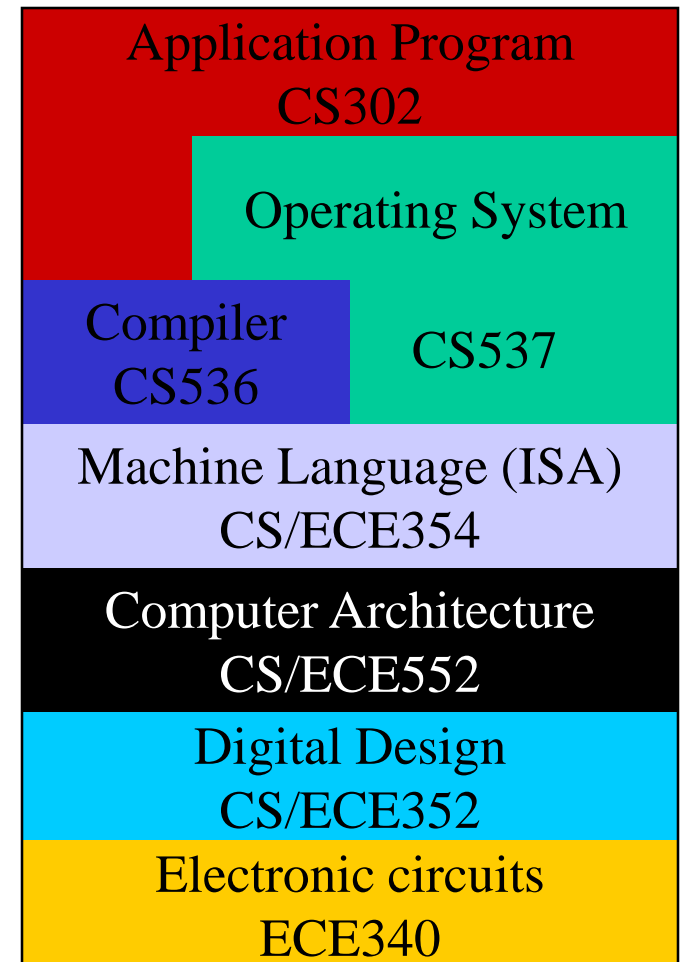

Simple Switch Circuit

 

Switch **open**:

- No current through circuit
- Light is **off**
- V_{out} is **+2.9V**

Switch **closed**:



- Short circuit across switch
- Current flows
- Light is **on**
- V_{out} is **0V**

Switch-based circuits can easily represent two states:
on/off, open/closed, voltage/no voltage.


“Miracle Month” of November 17 to December 23, 1947



Transistor physical diagram

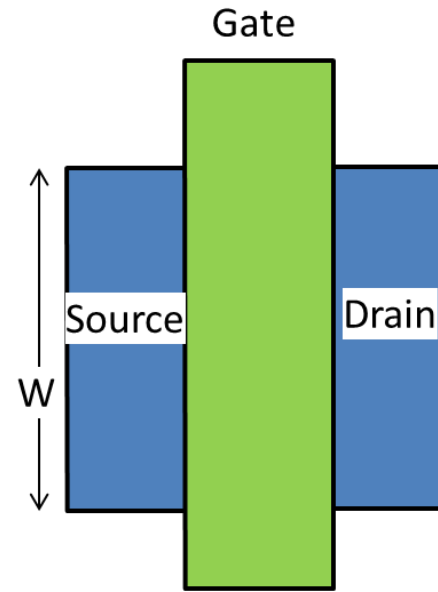 


Top view

 

Side view


 
- **Silicon by itself is semiconductor**
 - **Has 4 valence electrons and forms a co-valent bond with 4 neighbors**
 - **Hard to break and does not conduct ☹️**




	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18																																																								
1	1 H Hydrogen 1.00794	Atomic # Symbol Name Atomic Mass																2 He Helium 4.002602																																																								
2	3 Li Lithium 6.941	4 Be Beryllium 9.012182	<table border="1"> <tr> <td>C Solid</td> <td colspan="5">Metals</td> <td colspan="5">Nonmetals</td> </tr> <tr> <td>Hg Liquid</td> <td>Alkali metals</td> <td>Alkaline earth metals</td> <td>Lanthanoids</td> <td>Transition metals</td> <td>Poor metals</td> <td>Other nonmetals</td> <td>Noble gases</td> <td colspan="5"></td> </tr> <tr> <td>H Gas</td> <td colspan="2"></td> <td>Actinoids</td> <td colspan="5"></td> <td colspan="5"></td> </tr> <tr> <td>Rf Unknown</td> <td colspan="17"></td> </tr> </table>										C Solid	Metals					Nonmetals					Hg Liquid	Alkali metals	Alkaline earth metals	Lanthanoids	Transition metals	Poor metals	Other nonmetals	Noble gases						H Gas			Actinoids											Rf Unknown																		5 B Boron 10.811	6 C Carbon 12.0107	7 N Nitrogen 14.0067	8 O Oxygen 15.9994	9 F Fluorine 18.9984032	10 Ne Neon 20.1797
C Solid	Metals					Nonmetals																																																																				
Hg Liquid	Alkali metals	Alkaline earth metals	Lanthanoids	Transition metals	Poor metals	Other nonmetals	Noble gases																																																																			
H Gas			Actinoids																																																																							
Rf Unknown																																																																										
3	11 Na Sodium 22.98976928	12 Mg Magnesium 24.3050											13 Al Aluminium 26.9815386	14 Si Silicon 28.0855	15 P Phosphorus 30.973762	16 S Sulfur 32.065	17 Cl Chlorine 35.453	18 Ar Argon 39.948																																																								
4	19 K Potassium 39.0983	20 Ca Calcium 40.078	21 Sc Scandium 44.955912	22 Ti Titanium 47.887	23 V Vanadium 50.9415	24 Cr Chromium 51.9961	25 Mn Manganese 54.938045	26 Fe Iron 55.845	27 Co Cobalt 58.933195	28 Ni Nickel 58.6934	29 Cu Copper 63.546	30 Zn Zinc 65.38	31 Ga Gallium 69.723	32 Ge Germanium 72.64	33 As Arsenic 74.92160	34 Se Selenium 78.96	35 Br Bromine 79.904	36 Kr Krypton 83.798																																																								

- **Silicon by itself is insulator**
 - Has 4 valence electrons and forms a co-valent bond with 4 neighbors
 - Had to break and does not conduct ☹️
- **Silicon + Arsenic makes it filled with electrons and conducting**
- **Silicon + Boron makes it filled with “holes” and conducting**

nmos and pmos Transistors

  

Transistor Operation (nmos)

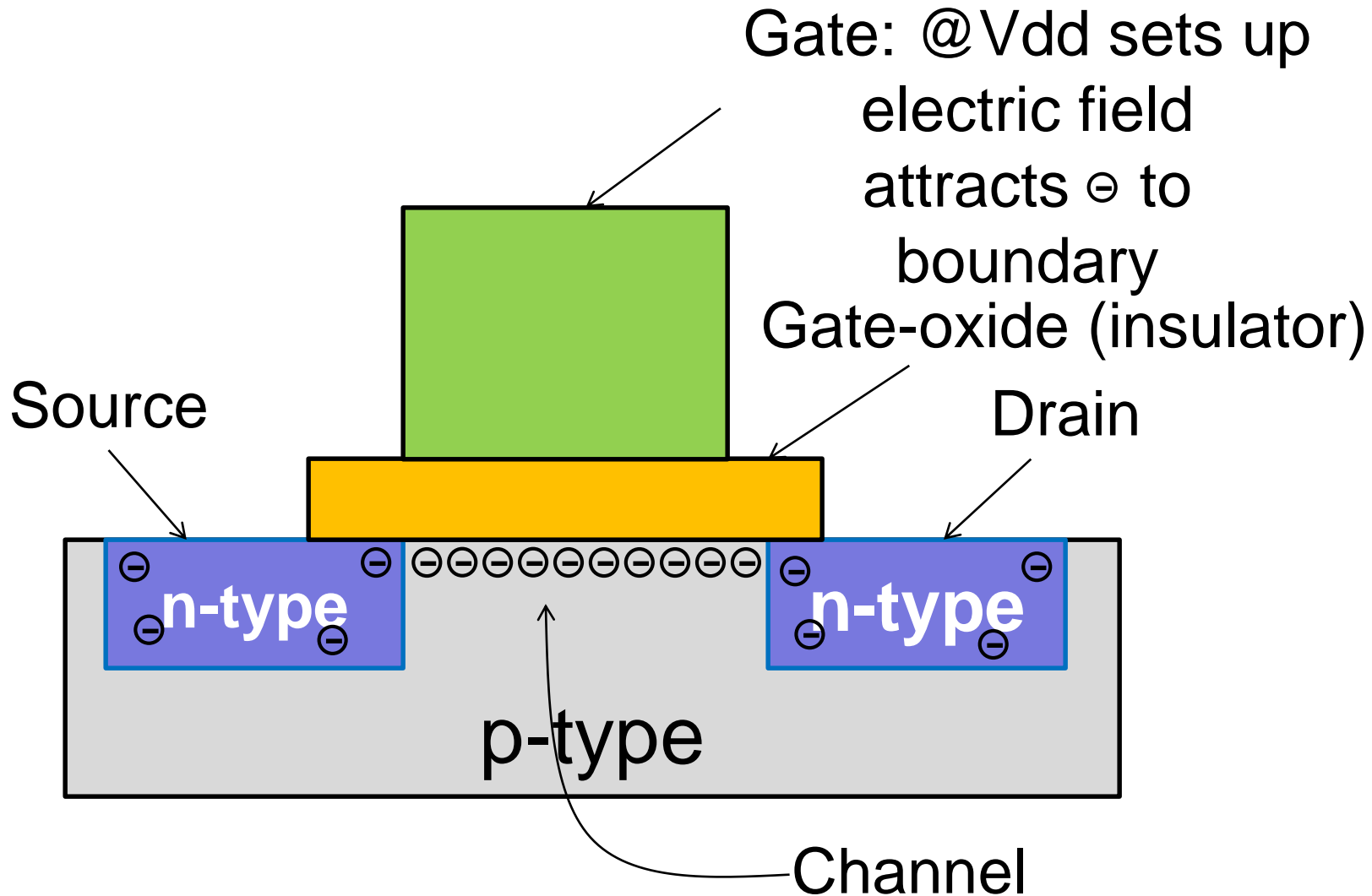

If the figure on the left is a (musical) conductor, then what is the figure on the right?



semiconductor


N-type MOS Transistor

MOS = Metal Oxide Semiconductor

- two types: N-type and P-type

N-type

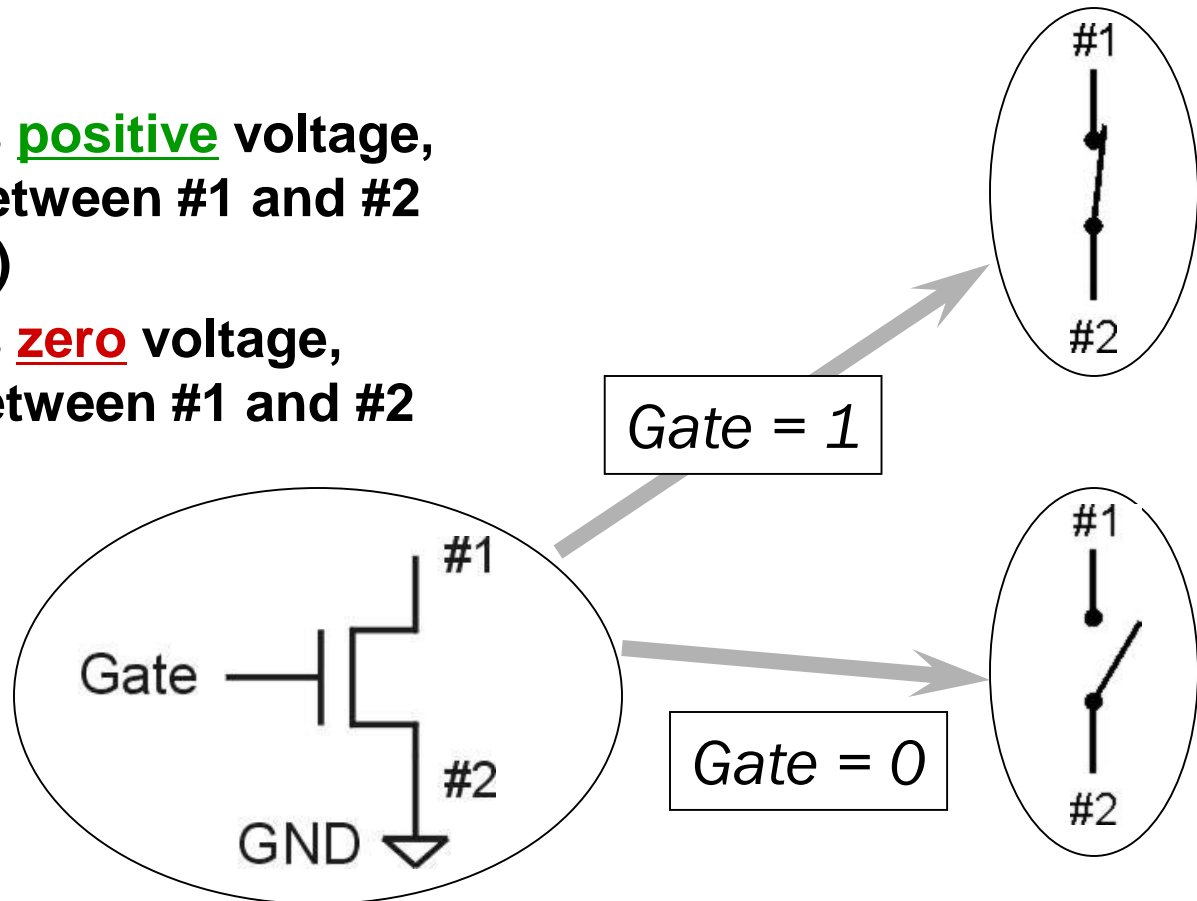- when Gate has **positive** voltage, short circuit between #1 and #2 (switch **closed**)
- when Gate has **zero** voltage, open circuit between #1 and #2 (switch **open**)




Terminal #2 must be connected to GND (0V).

P-type MOS Transistor

P-type is *complementary* to N-type

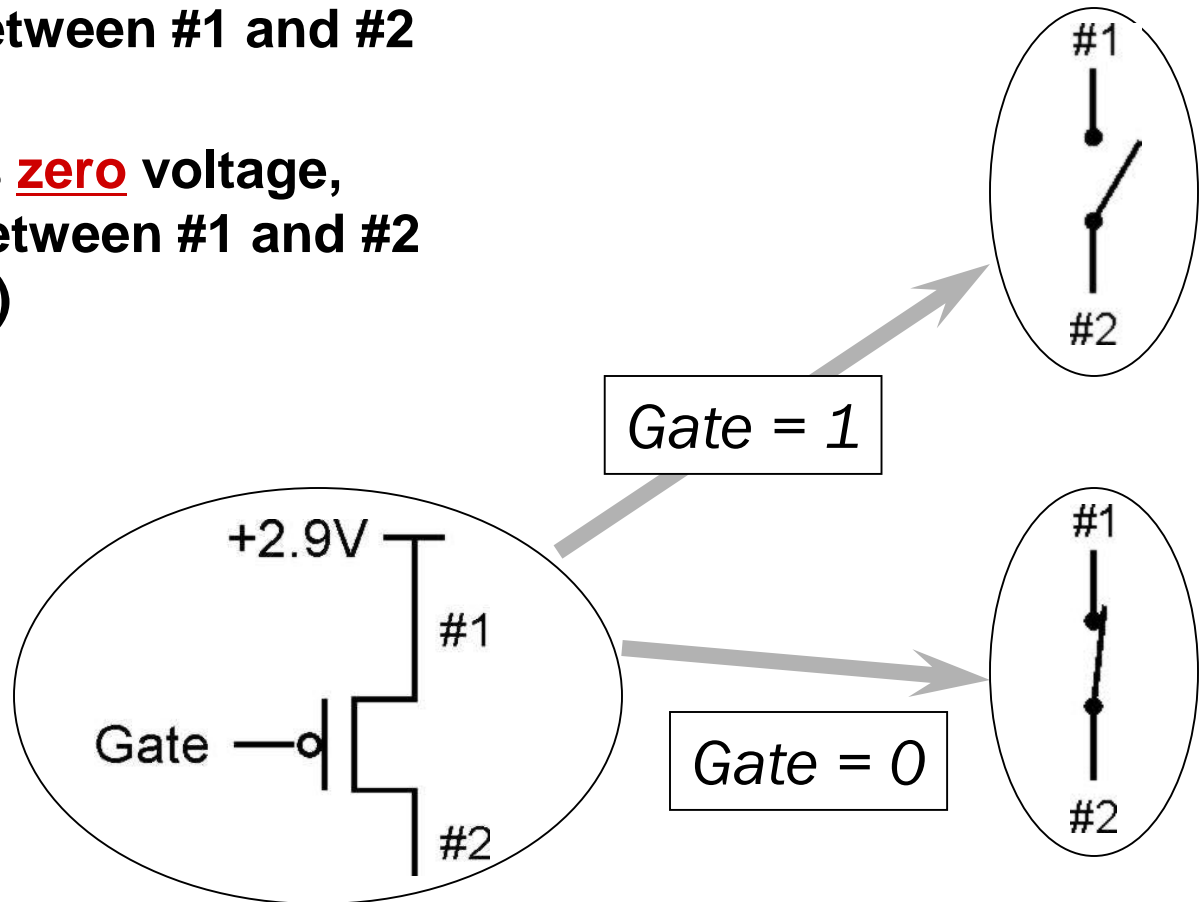- when Gate has **positive** voltage, open circuit between #1 and #2 (switch **open**)
- when Gate has **zero** voltage, short circuit between #1 and #2 (switch **closed**)



Terminal #1 must be connected to +2.9V.

Logic Gates

Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.

Digital symbols:

- recall that we assign a range of analog voltages to each digital (logic) symbol



- assignment of voltage ranges depends on electrical properties of transistors being used
 - typical values for "1": +5V, +3.3V, +2.9V, +1.1V
 - for purposes of illustration, we'll use +2.9V

CMOS Circuit


Complementary MOS

Uses both **N-type** and **P-type** MOS transistors

- **P-type**
 - Attached to + voltage
 - Pulls output voltage **UP** when input is zero
- **N-type**
 - Attached to **GND**
 - Pulls output voltage **DOWN** when input is one

For all inputs, make sure that output is either connected to GND or to +, but not both!

Transistor

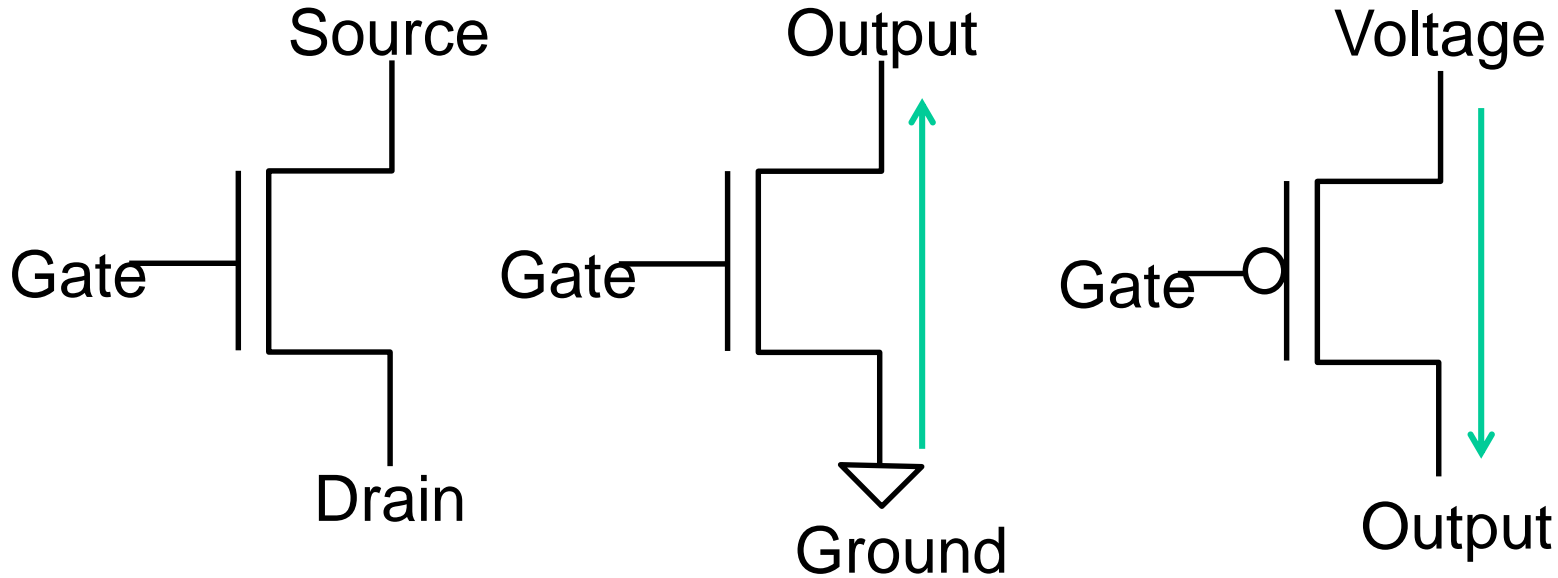


Transistor terminals N-type transistor

Gate	Behavior
1	Closed Output=0
0	Open Output=Z



P-type transistor

Gate	Behavior
0	Closed Output=1
1	Open Output=Z


NOT Gate with Transistors

 

Inverter (NOT Gate)

  



Truth table

 

In	Out
0 V	2.9 V
2.9 V	0 V

In	Out
0	1
1	0


NOR Gate

  

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Note: Serial structure on top, parallel on bottom.



OR Gate

 

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Add inverter to NOR.


NAND Gate (AND-NOT)

  

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Note: Parallel structure on top, serial on bottom.


AND Gate

 


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Add inverter to NAND.


Basic Logic Gates

 


NOT

 


OR

 

NOR

 

AND

 

NAND

In-Class Exercise



$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

Convert 777 to IEEE 32-bit floating point

Convert the results back to decimal

In-Class Exercise




$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$

Convert 777 to IEEE 32-bit floating point

- $777 = 1100001001 = 1.100001001 * 2^9$
- $9 = \text{exp} - 127$
- $\text{exp} = 136 = 10001000$
- $\text{sign} = 0$ since positive
- $0 \ 10001000 \ 100001001000000000000000$

Convert the results back to decimal

In-Class Exercise

 

$$N = -1^S \times 1.\text{fraction} \times 2^{\text{exponent}-127}, \quad 1 \leq \text{exponent} \leq 254$$


Convert 777 to IEEE 32-bit floating point

Convert the results back to decimal

- **0 10001000 100001001000000000000000**
- **0b10001000 = 0d136**
- $N = (-1)^S * 1.\text{fraction} * 2^{(\text{exp}-127)}$
- $N = (-1)^0 * 1.\text{100001001} * 2^{(136-127)}$
- $N = 1 * 1.\text{100001001} * 2^9$
- $N = 1\text{100001001.0}$
- $N = 777$

Take-home exercise

 
Fill out the truth table for the following transistor circuit




A	B	Q
0	0	
0	1	
1	0	
1	1	

Common Misconceptions


OR gate

 

NOT gate

 

AND gate

 


More than 2 Inputs?

AND/OR can take any number of inputs.

- **AND = 1 if all inputs are 1.**
- **OR = 1 if any input is 1.**
- **Similar for NAND/NOR.**

 Can implement with multiple two-input gates, or with single CMOS circuit.



Note for all

- **HW2 is due today (1st Feb)**
- **HW3 is out**
- **Solutions for HW2 will be posted after HW2 is graded**

Note for all


- **Exam 1 will be held on 10th Feb (Education Sciences 204)**
- **50 min exam**
- **NO**
 - **Books, notes, calculator or electronic devices of any sort**

Points Covered so far..

- **Semiconductor properties of silicon**
- **Using silicon to build transistor**
 - p type transistor
 - n type transistor
- **Using transistors to build logic gates**
 - NAND
 - NOR
 - NOT


Multiple input logic gates

3-input NAND gate with CMOS.

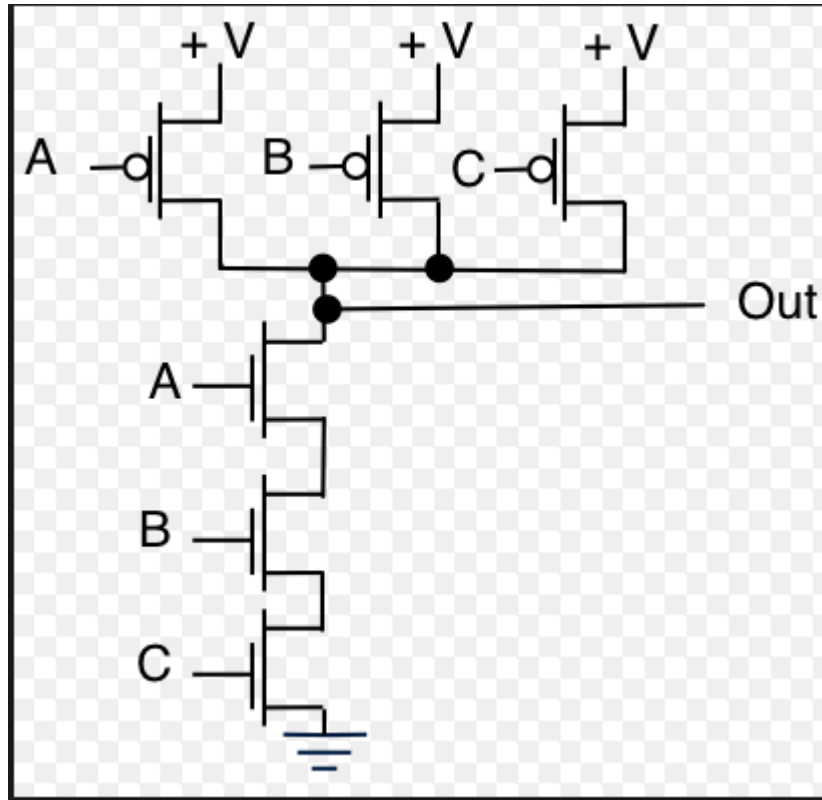

Take-home exercise

 
Fill out the truth table for the following transistor circuit



A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

$$Q = A \text{ (xor) } B$$

 
Fill out the truth table for the following transistor circuit




A	B	Q
0	0	
0	1	
1	0	
1	1	

Common Misconceptions


OR gate

 

NOT gate

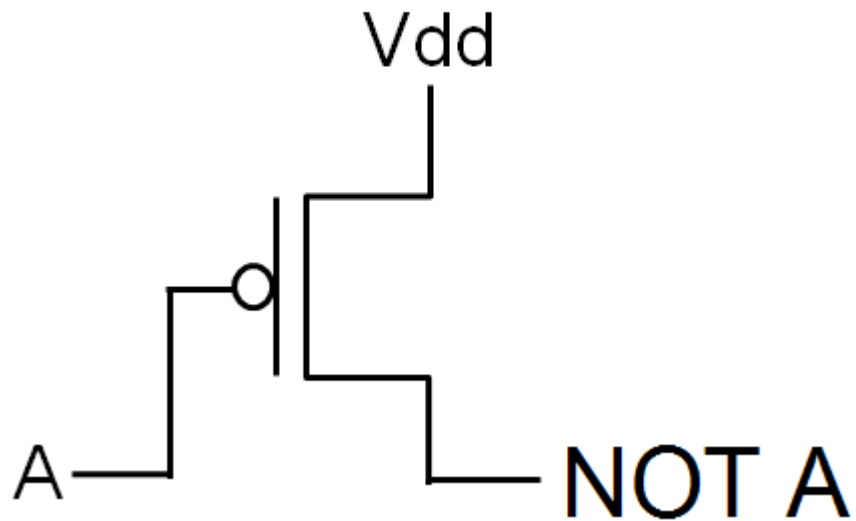


AND gate

 

Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 

1. AND combinations that yield a "1" in the truth table.
2. OR the results of the AND gates.

Practice

Implement the following truth table.

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Practice

Implement the following truth table.

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

$$C = A'B' + A'B + AB'$$


$$C = A'(B' + B) + AB'$$

$$C = A' + AB'$$

DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:

 


A	B	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1


Same as $A+B$

*To convert AND to OR
(or vice versa),
invert inputs and output.*

Half Adder

 



A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

$$S = A \text{ (XOR) } B$$

$$C = AB$$



Half Adder

  

$$S = A \text{ (XOR) } B$$

$$C = AB$$


Half Adder

  

$$S = A \text{ (XOR) } B$$


$$C = AB$$

Fill out the following truth table

 


A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Fill out the following truth table

 


A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Write the function of Z

 

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0


Write the function of Z

 

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$Z = A'B'C' + A'B'C + A'BC' + A'BC + AB'C'$$


Draw the gate implementation of Z

 


$$Z = A' + AB'C'$$

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0


Gate implementation

 

Gate implementation (NAND)

 

Gate implementation (NOR)

 

Summary

MOS transistors are used as switches to implement logic functions.

- **N-type: connect to GND, turn on (with 1) to pull down to 0**
- **P-type: connect to +2.9V, turn on (with 0) to pull up to 1**

Basic gates: NOT, NOR, NAND

- **Logic functions are usually expressed with AND, OR, and NOT**

Properties of logic gates

- **Completeness**
 - **can implement any truth table with AND, OR, NOT**
- **DeMorgan's Law**
 - **convert AND to OR by inverting inputs and output**

Building Functions from Logic Gates

We've already seen how to implement truth tables using AND, OR, and NOT -- an example of *combinational logic*.

Combinational Logic Circuit

- output depends only on the current inputs
- stateless

Sequential Logic Circuit


- output depends on the sequence of inputs (past and present)
- stores information (state) from past inputs

We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.



In-class exercise

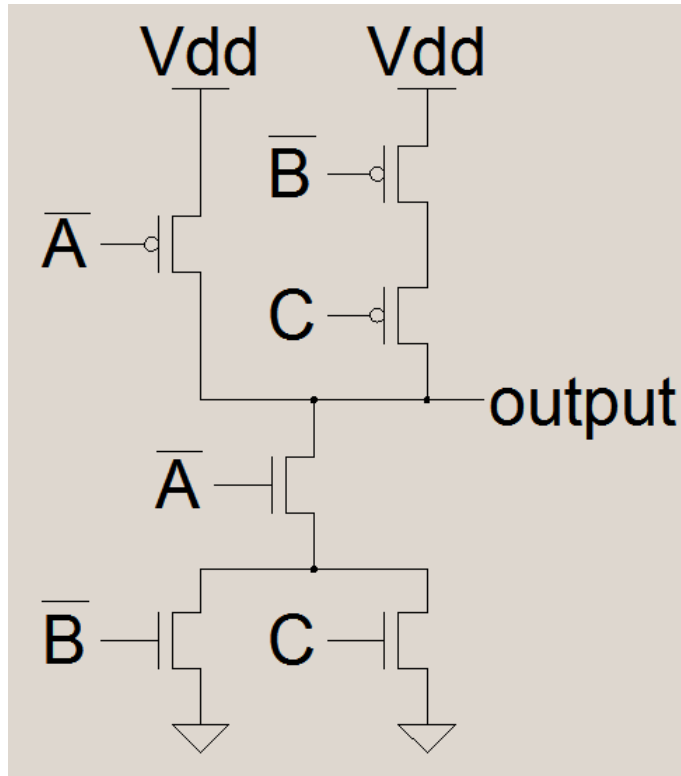Fill out the truth table for the following transistor circuit




A	B	C	output
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Use DeMorgan's Law to simplify

$\text{NOT}(\text{NOT}(A) \text{ AND } (\text{NOT}(B) \text{ OR } C))$

In-class exercise

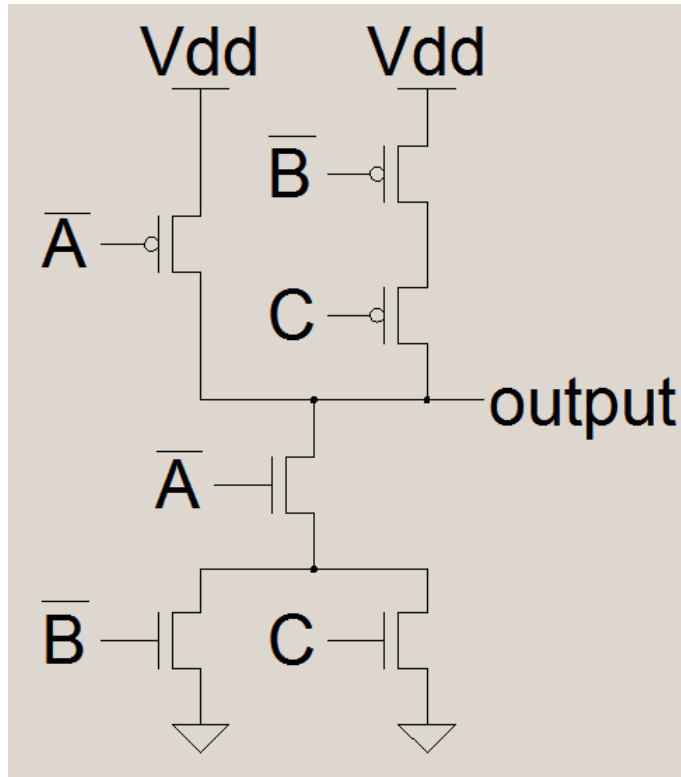Fill out the truth table for the following transistor circuit



A	B	C	output
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Use DeMorgan's Law to simplify

$\text{NOT}(\text{NOT}(A) \text{ AND } (\text{NOT}(B) \text{ OR } C))$


$\text{NOT}(\text{NOT}(A)) \text{ OR } \text{NOT}(\text{NOT}(B) \text{ OR } C)$

$A \text{ OR } (B \text{ AND } \text{NOT}(C))$

Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


1. AND combinations that yield a "1" in the truth table.
2. OR the results of the AND gates.

Decoder

n inputs, 2^n outputs


 
- exactly one output is 1 for each possible input pattern



Multiplexer (MUX)

n -bit selector and 2^n inputs, one output

  
- output equals one of the inputs, depending on selector



4-to-1 MUX

Half Adder

 
Add two bits,
produce one-bit sum and carry-out.



A	B	S	C _{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full Adder from Half Adder

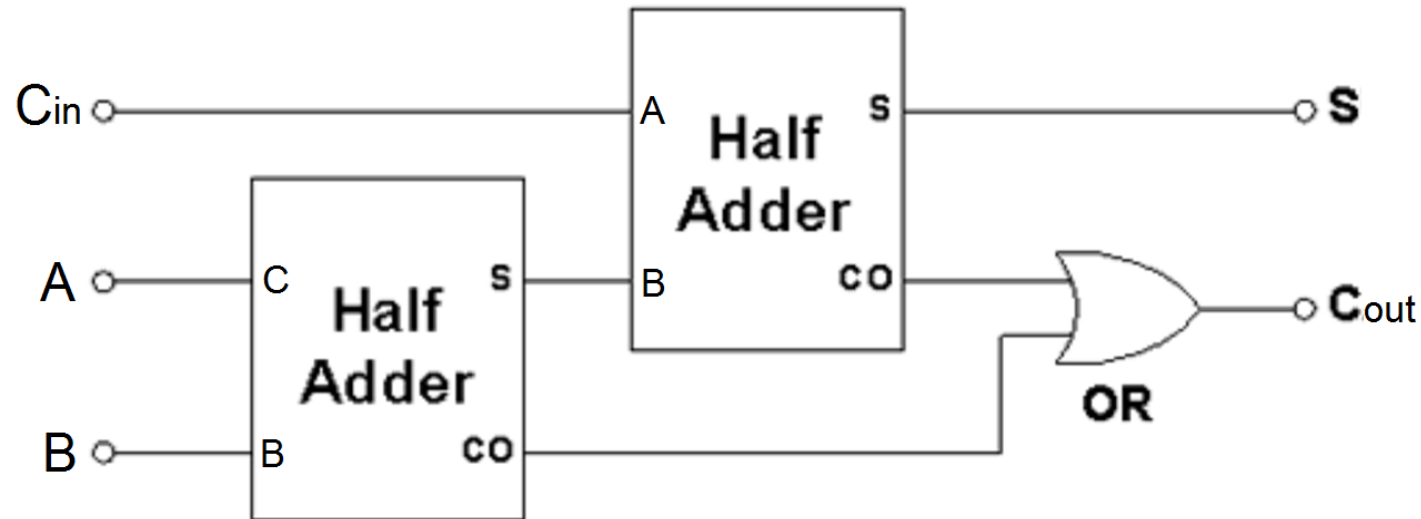
Add two bits and carry-in,
produce one-bit sum and carry-out.



A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Full Adder

 Add two bits and carry-in, produce one-bit sum and carry-out.



A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Four-bit Adder

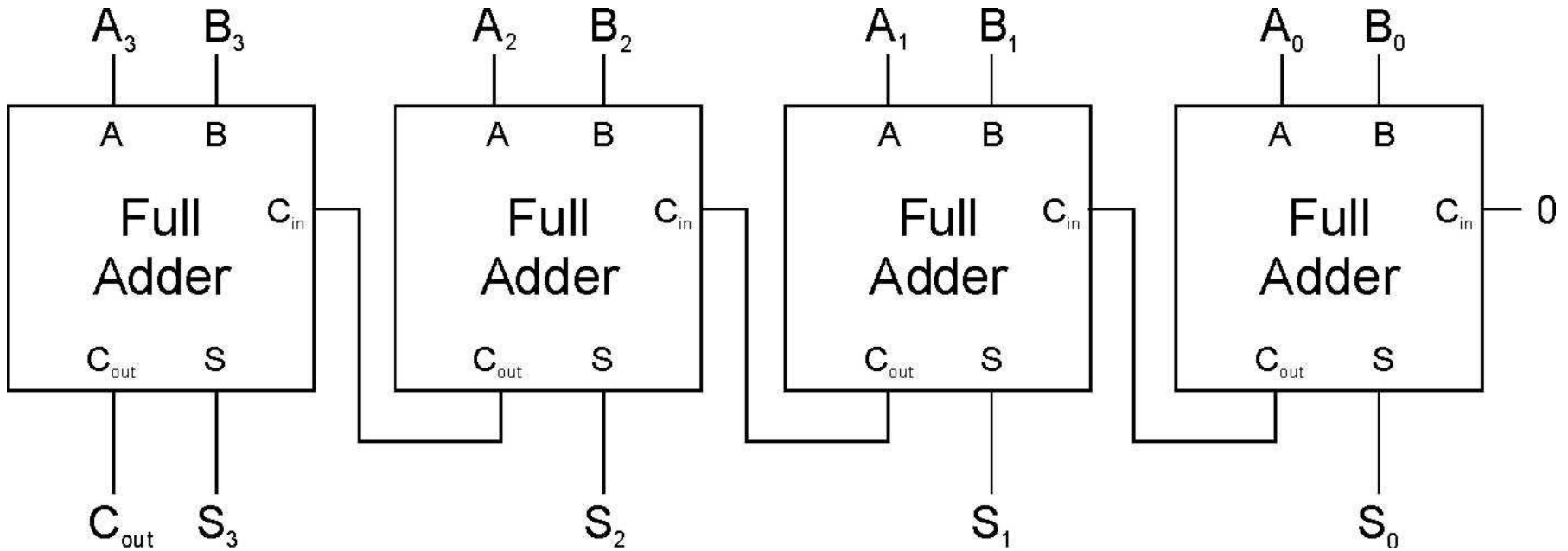

Combinational vs. Sequential

Combinational Circuit


- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs

Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
- *example:* ticket counter
 - advances when you push the button
 - output depends on previous state
- useful for building “memory” elements and “state machines”

In-Class Exercise

- Find A, B, C, D, E, and F

 

Note: Bits are numbered starting from 0 from right to left.

So if $X = 10110$, then

$X[4] = 1$,

$X[3] = 0$,


$X[2] = 1$,

$X[1] = 1$, and

$X[0] = 0$.

In-Class Exercise Solutions

- Find A, B, C, D, E, and F

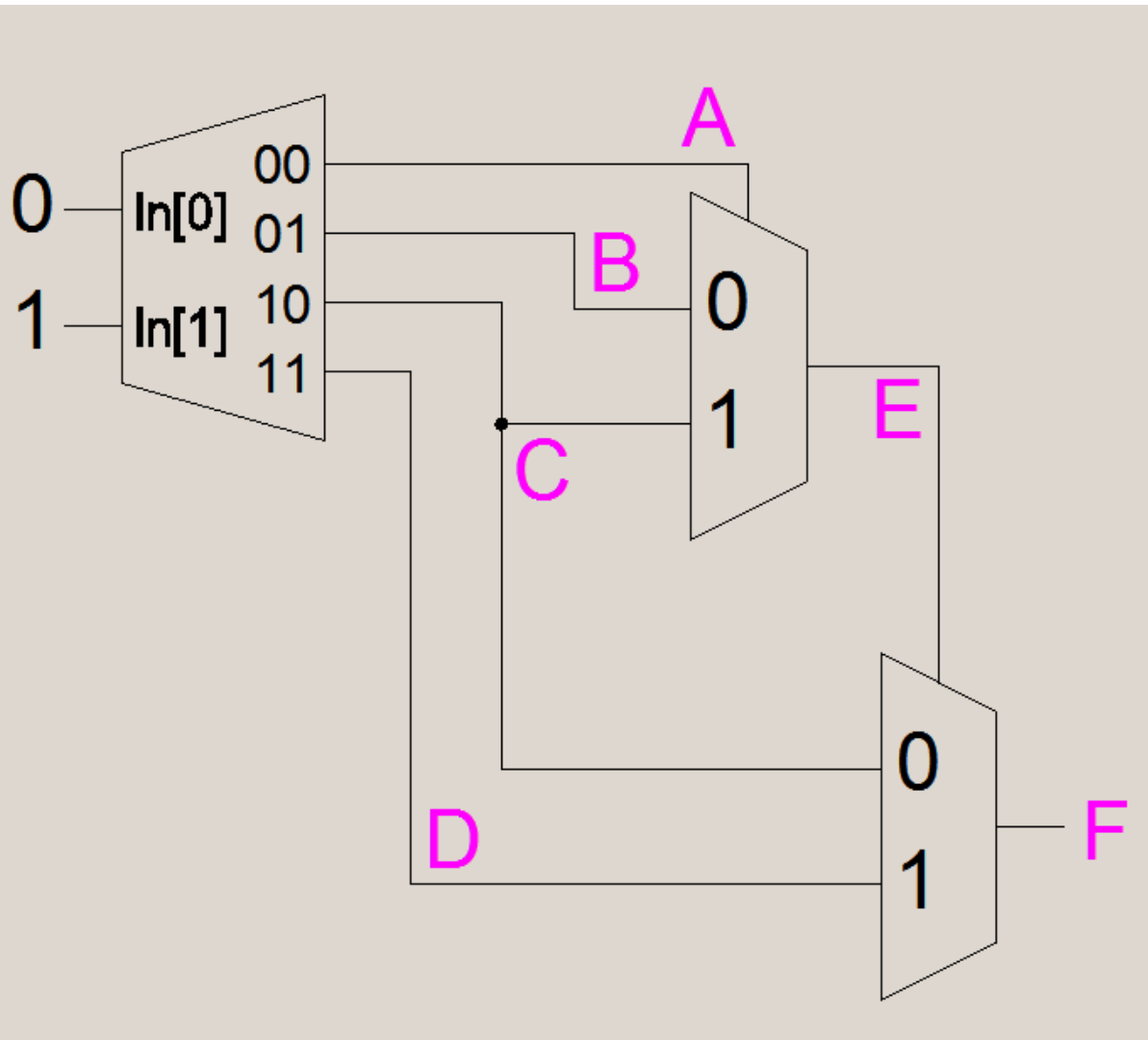

Note: Bits are numbered starting from 0 from right to left.

So if $X = 10110$, then

$X[4] = 1$,

$X[3] = 0$,

$X[2] = 1$,

$X[1] = 1$, and

$X[0] = 0$.

A=0

B=0

C=1




D=0

E=0

F=1

Cross-coupled inverters

  
 
Good news: holds on to value
Bad news: How do we write to it?



R-S Latch: Simple Storage Element

R is used to “reset” or “clear” the element – set it to zero.

  S is used to “set” the element – set it to one.




If both R and S are one, out could be either zero or one.


- “quiescent” state -- holds its previous value
- note: if a is 1, b is 0, and vice versa

Clearing the R-S latch

 Suppose we start with output = 1, then change R to zero.




Output changes to zero.

 


Then set $R=1$ to “store” value in quiescent state.

Setting the R-S Latch

 Suppose we start with output = 0, then change S to zero.



Output changes to one.

 

Then set S=1 to “store” value in quiescent state.

R-S Latch Summary

$R = S = 1$

- **hold current value in latch**

$S = 0, R=1$

- **set value to 1**

$R = 0, S = 1$

- **set value to 0**


$R = S = 0$

- **both outputs equal one**
- *Don't do it!*

Gated D-Latch

Two inputs: D (data) and WE (write enable)

 
- when **WE = 1**, latch is set to **value of D**
 - $S = \text{NOT}(D)$, $R = D$
- when **WE = 0**, latch holds **previous value**
 - $S = R = 1$



Register

A register stores a multi-bit value.

 - We use a collection of D-latches, all controlled by a common WE.
- When $WE=1$, n-bit value D is written to register.




Representing Multi-bit Values

Number bits from right (0) to left (n-1)

- just a convention -- could be left to right, but must be consistent

Use brackets to denote range:

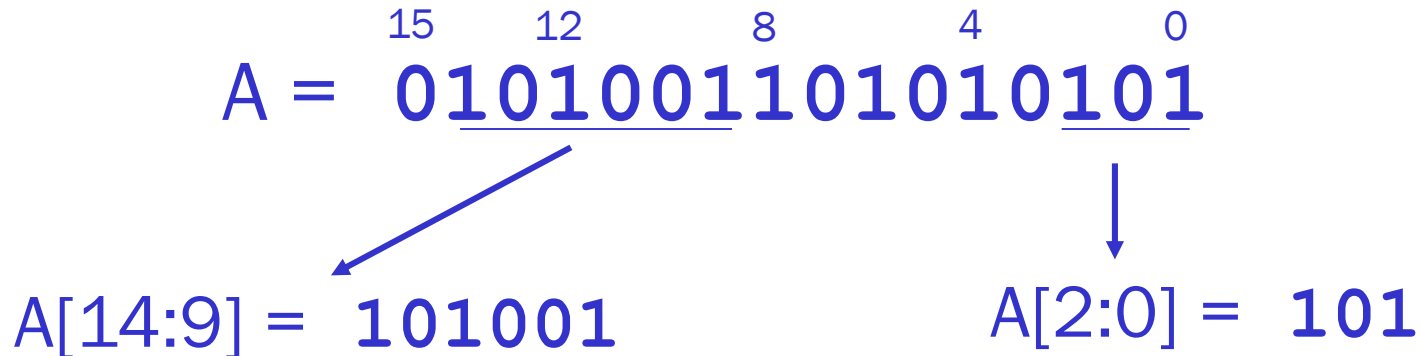$D[l:r]$ denotes bit l to bit r , from *left to right*




May also see $A\langle 14:9 \rangle$,
especially in hardware block diagrams.

Memory

Now that we know how to store bits, we can build a memory – a logical $k \times m$ array of stored bits.

Address Space:
number of locations
(usually a power of 2)


$k = 2^n$
locations

 

Addressability:
number of bits per location
(e.g., byte-addressable)

m bits

2² x 3 Memory

 

More Memory Details

This is a not the way actual memory is implemented.

- fewer transistors, much more dense,
relies on electrical properties

But the logical structure is very similar.

- address decoder
- word select line
- word write enable


Also, non-volatile memories: ROM, PROM, flash, ...

More Memory Details

Two basic kinds of **RAM** (Random Access Memory)


Static RAM (SRAM)

- fast, maintains data without power

 


Dynamic RAM (DRAM)

 - slower but denser, bit storage must be periodically refreshed




Also, non-volatile memories: ROM, PROM, flash, ...

In-class Exercise

 

Specify the value of "out" signal for each set of inputs for the RS latch.


Time	0	1	2	3	4	5	6	7	8
S	1	1	0	0	1	0	1	1	0
R	0	1	1	1	1	1	0	1	1
out	0	0							

 

Specify the value of "out" signal for each set of inputs for the gated d-latch.


Time	0	1	2	3	4	5	6	7	8
D	1	0	0	0	1	0	1	0	0
WE	1	0	1	0	1	1	0	0	1
out	1	1							

In-class Exercise Solution

 

Specify the value of "out" signal for each set of inputs for the RS latch.


Time	0	1	2	3	4	5	6	7	8
S	1	1	0	0	1	0	1	1	0
R	0	1	1	1	1	1	0	1	1
out	0	0	1	1	1	1	0	0	1

 

Specify the value of "out" signal for each set of inputs for the gated d-latch.


Time	0	1	2	3	4	5	6	7	8
D	1	0	0	0	1	0	1	0	0
WE	1	0	1	0	1	1	0	0	1
out	1	1							

In-class Exercise Solutions

 

Specify the value of "out" signal for each set of inputs for the RS latch.

Time	0	1	2	3	4	5	6	7	8
S	1	1	0	0	1	0	1	1	0
R	0	1	1	1	1	1	0	1	1
out	0	0	1	1	1	1	0	0	1


 


Specify the value of "out" signal for each set of inputs for the gated d-latch.

Time	0	1	2	3	4	5	6	7	8
D	1	0	0	0	1	0	1	0	0
WE	1	0	1	0	1	1	0	0	1
out	1	1	0	0	1	0	0	0	0

Combinational vs. Sequential

Two types of locks

  

Combinational



Success depends only on the **values**, not the order in which they are set.

Sequential

Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).


Points Covered

  - **Decoder n input (2^n) output**
 - **decoder asserts exactly one of its output bits**



Points Covered

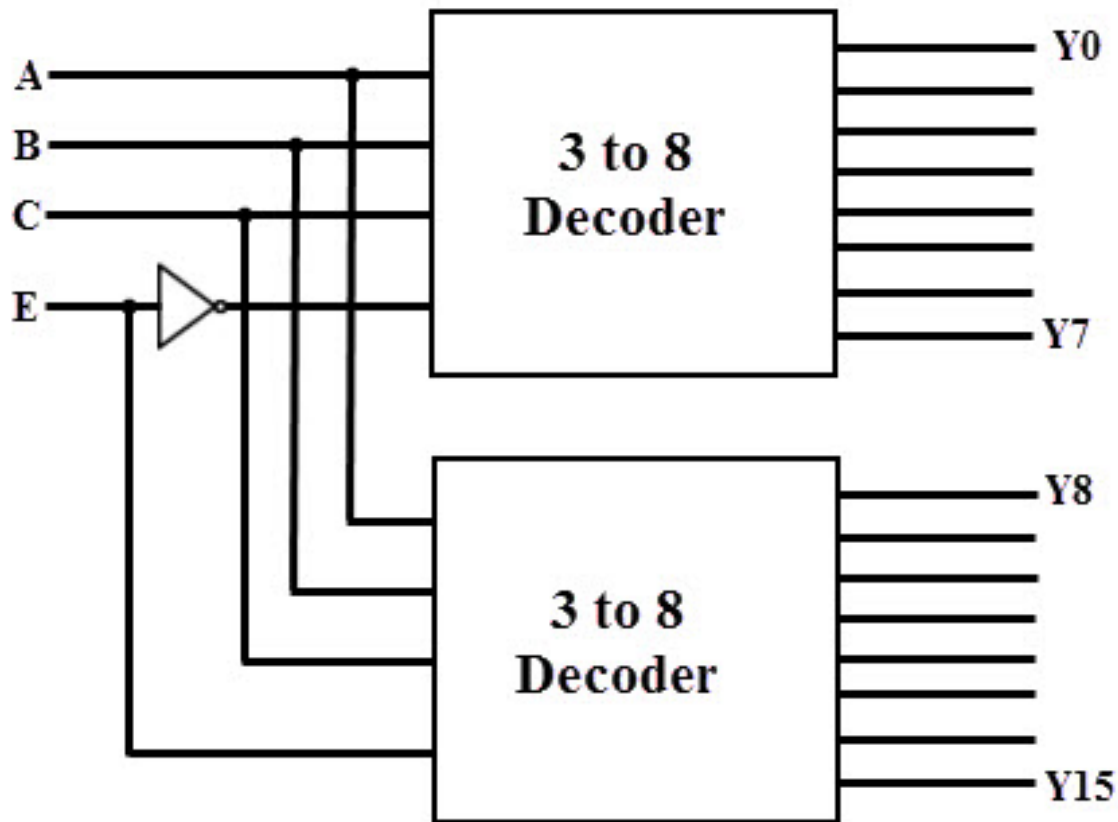Using two 3-to-8 decoder to get 4-to-16 decoder



Points Covered

- **Multiplexer**
- **Combinational circuits and Sequential circuits**
- **Using logic gates to make storage elements**
 - **Feedback path**
 - **RS latch**
 - **D latch**

R-S Latch Summary

$R = S = 1$

- **hold current value in latch**

$S = 0, R=1$

- **set value to 1**

$R = 0, S = 1$

- **set value to 0**

$R = S = 0$

- **both outputs equal one**
- *Don't do it!*

D Latch Summary

$D = X, WE=0$ ($X \rightarrow$ Don't care)

- **hold current value in latch**

$D = 1, WE=1$

- **set value to 1**


$D = 0, WE=1$

- **set value to 0**

State Machine

Another type of sequential circuit

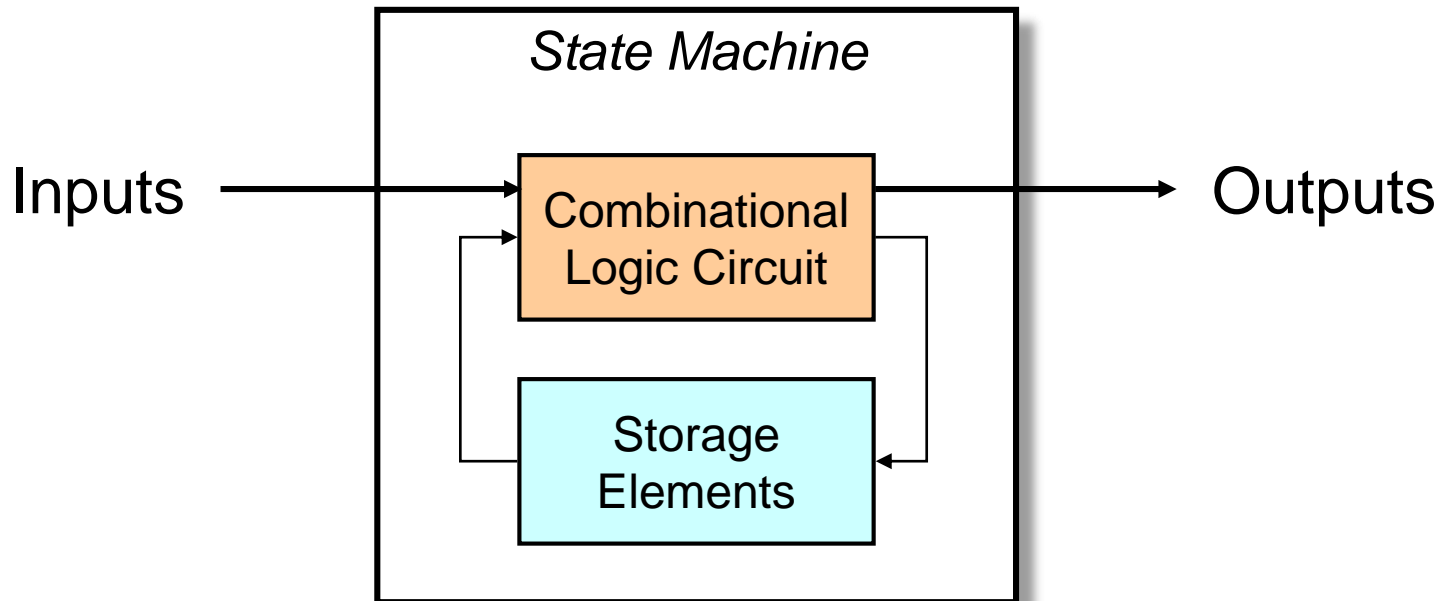- Combines combinational logic with storage
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**



State



The **state** of a system is a **snapshot** of **all the relevant elements** of the system at the moment the snapshot is taken.

Examples:

- The state of a basketball game can be represented by the scoreboard.
 - Number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board, and who's turn it is.

Sequential Lock

Two types of locks

  

Combinational

Success depends only on the **values**, not the order in which they are set.

Sequential

Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).


State of Sequential Lock

Our lock example has four different states, labelled A-D:

- A:** The lock is **not open**,
and no relevant operations have been performed.
- B:** The lock is **not open**,
and the user has completed the **R-13** operation.
- C:** The lock is **not open**,
and the user has completed **R-13**, followed by **L-22**.
- D:** The lock is **open**,
and the user has completed **R-13**, followed by **L-22**,
followed by **R-3**

State Diagram

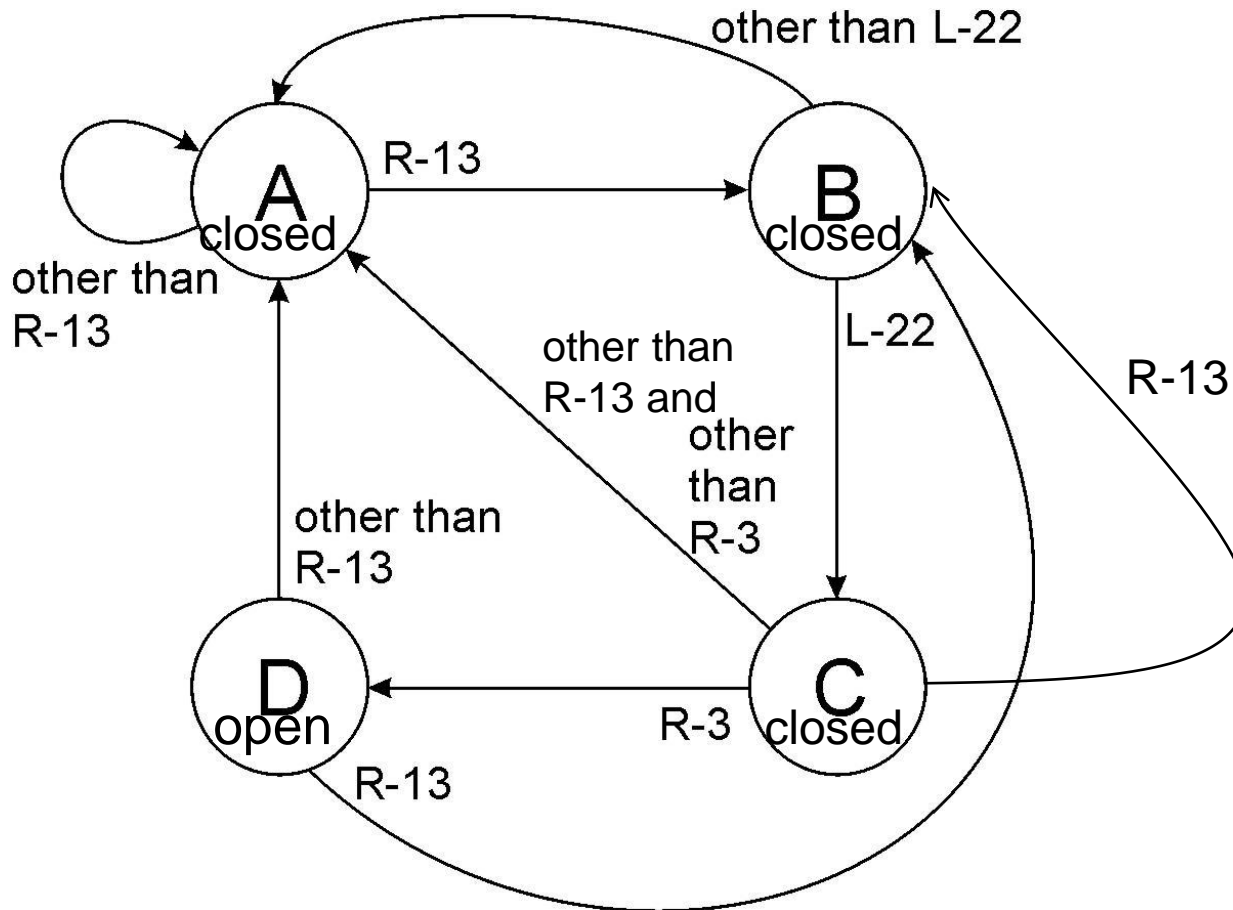
Shows **states** and **actions** that cause a **transition** between states.



Finite State Machine

A description of a system with the following components:

 1. A finite number of **states**
2. A finite number of external **inputs**
3. A finite number of external **outputs**
4. An explicit specification of all **state transitions**
5. An explicit specification of what causes each external **output value**.




Often described by a state diagram.

- Inputs may cause state transitions.
- Outputs are associated with each state (or with each transition).

The Clock

 Frequently, a **clock circuit** triggers transition from one state to the next.



At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.

- Not always required. In lock example, the input itself triggers a transition.


Implementing a Finite State Machine

Combinational logic

- Determine outputs and next state.


Storage elements

- Maintain state representation.

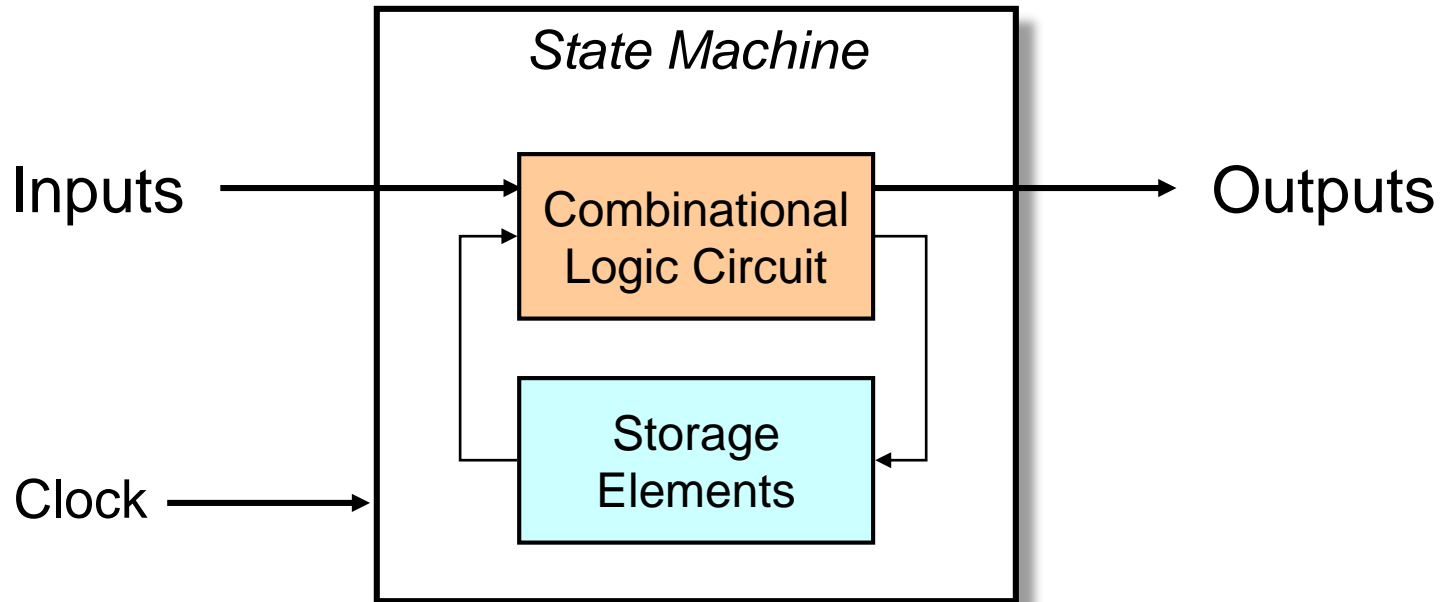

Storage: Master-Slave Flipflop


 
A pair of gated D-latches,
to isolate *next* state from *current* state.




During 1st phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.

During 2nd phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.

Storage: Master-Slave Flipflop

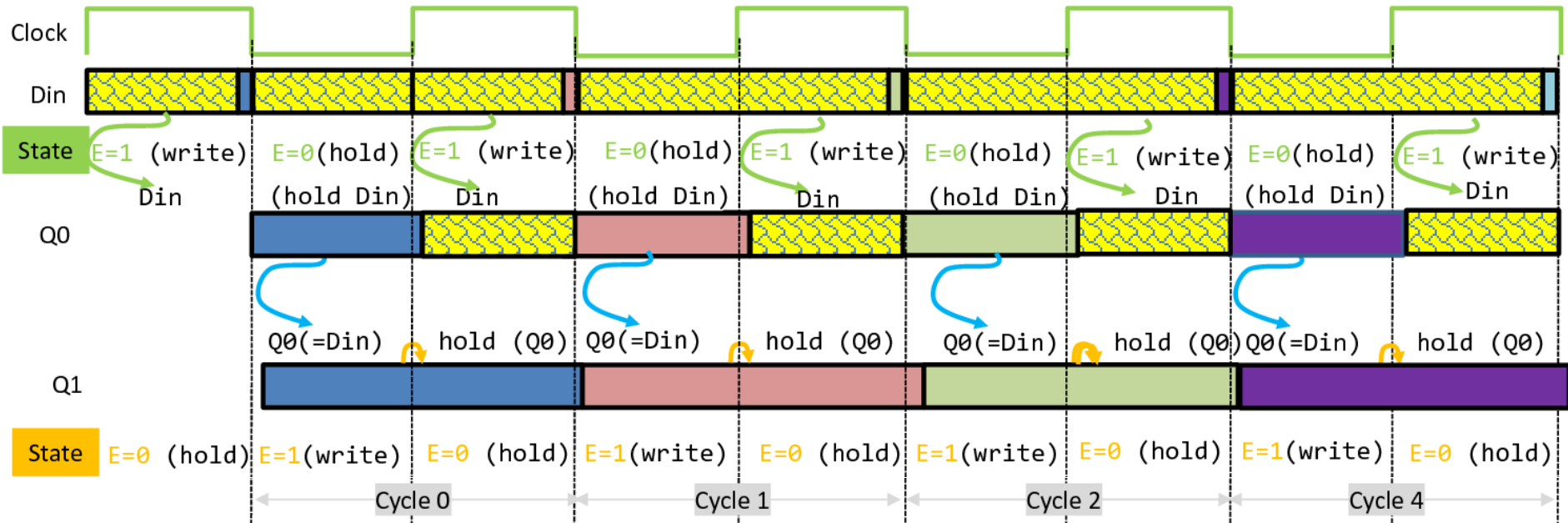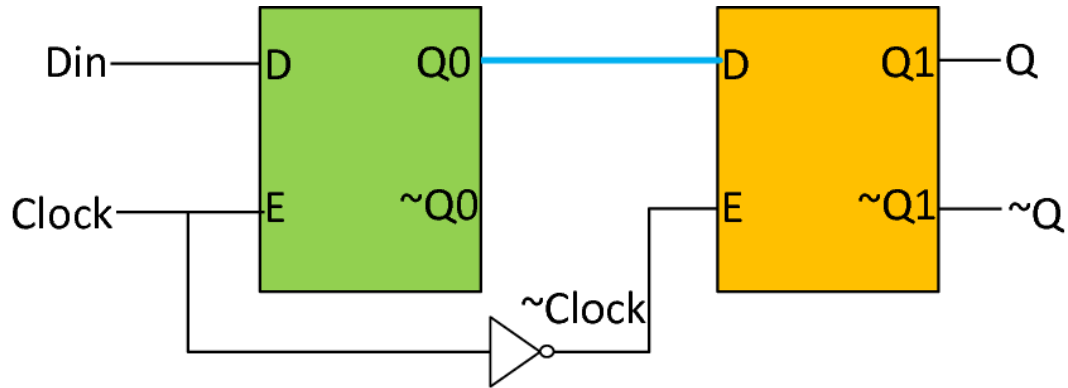


In-class Exercise

 

Specify the value of “Q0” and “Q1” signal for each set of inputs for the master-slave flipflop.

Time	0	0.3	0.4	0.5	.7	1	1.2	1.5	1.7	1.8	2	2.2	2.3	2.4	2.5
Clock	1	1	1	0	0	1	1	0	0	0	1	1	1	1	0
Din	0	1	0	1	1	0	1	0	1	0	1	0	1	0	0
Q0	0	1													
Q1	1	1													

In-class Exercise Solutions

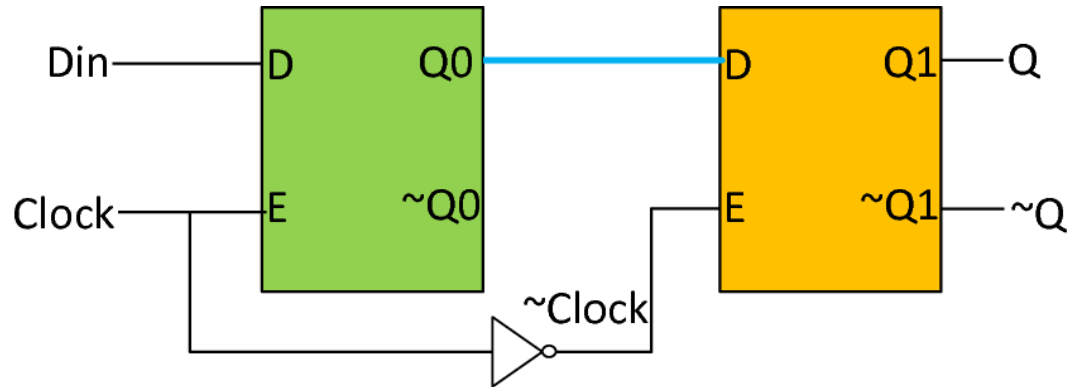


Specify the value of “Q0” and “Q1” signal for each set of inputs for the master-slave flipflop.

Time	0	0.3	0.4	0.5	.7	1	1.2	1.5	1.7	1.8	2	2.2	2.3	2.4	2.5
Clock	1	1	1	0	0	1	1	0	0	0	1	1	1	1	0
Din	0	1	0	1	1	0	1	0	1	0	1	0	1	0	0
Q0	0	1	0	0	0	0	1	1	1	1	1	0	1	0	0
Q1	1	1	1	0	0	0	0	1	1	1	1	1	1	1	0

In-class Exercise 1

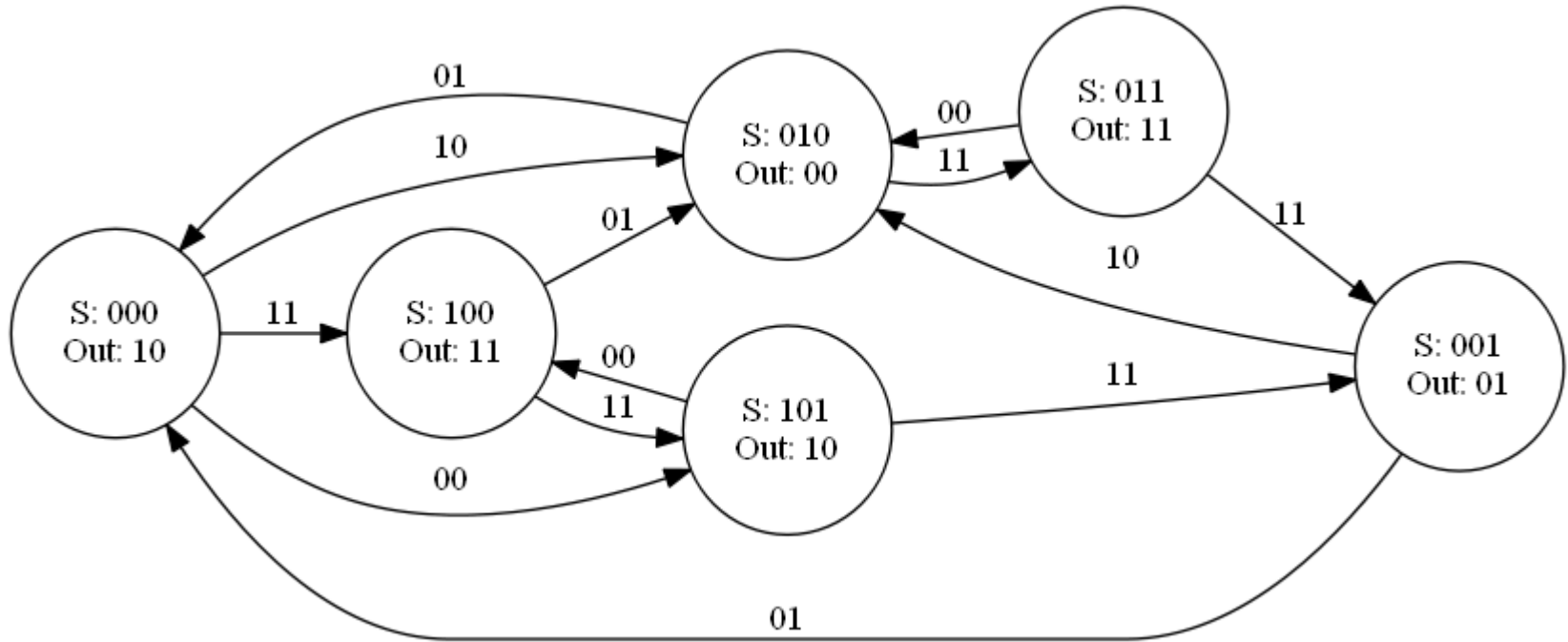
Specify the next State and Out for each set of inputs.



Time	0	1	2	3	4	5	6	7	8	9	10
State	000	100	010								
Input	11	01	01	00	11	10	11	11	01	10	11
Output	10	11	00								

In-class Exercise 1 Solutions

 Specify the next State and Out for each set of inputs.




Time	0	1	2	3	4	5	6	7	8	9	10
State	000	100	010	000	101	001	010	011	001	000	010
Input	11	01	01	00	11	10	11	11	01	10	11
Output	10	11	00	10	10	01	00	11	01	10	00

Storage


Each master-slave flipflop stores one state bit.

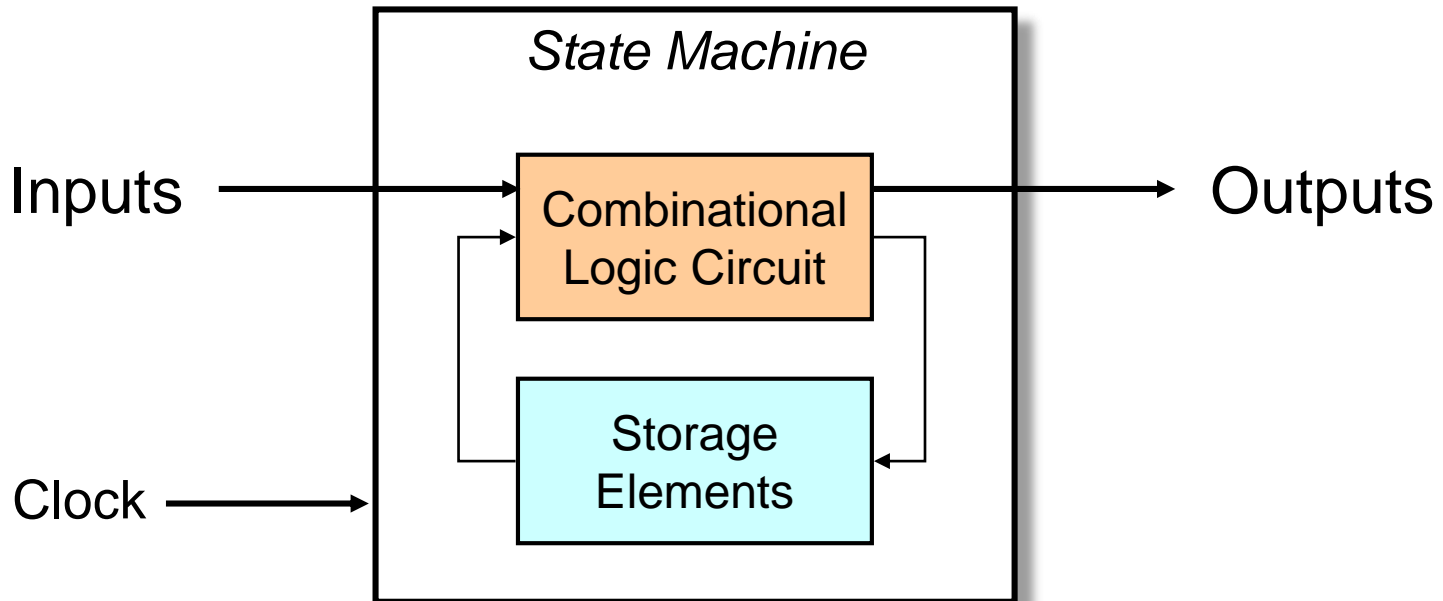Examples:


- Sequential lock
 - Four states – two bits




In-class Exercise 2

 


 
Given the clock/enable and data signal, specify the “Latch” and “Flip-Flop” signal.



In-class Exercise 2 Solutions

 

  
Given the clock/enable and data signal, specify the “Latch” and “Flip-Flop” signal.



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Complete Example

A blinking traffic sign

 
- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)




Complete Example

A blinking traffic sign

 - No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Traffic Sign State Diagram

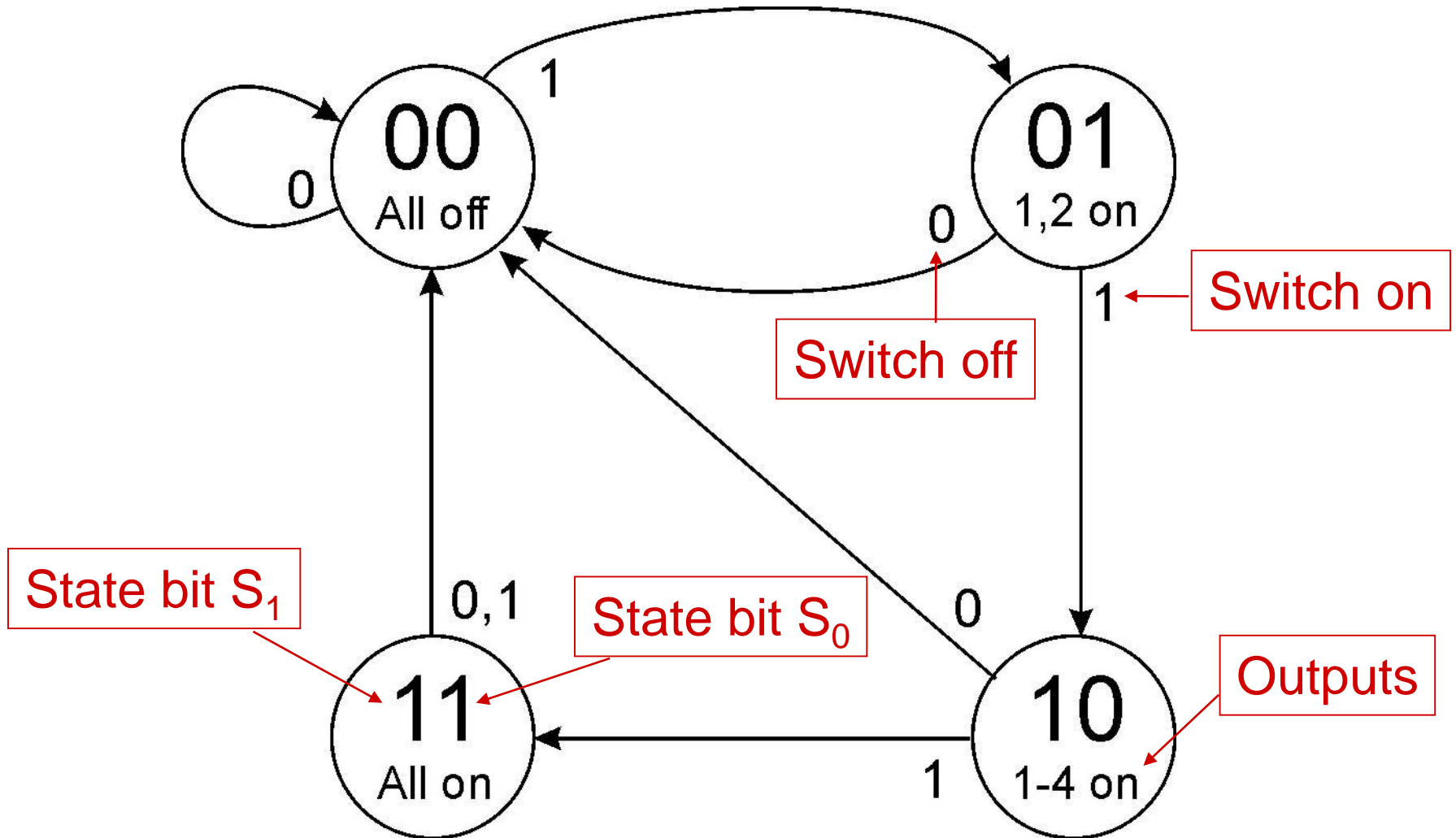

Transition on each clock cycle.

Traffic Sign Truth Tables

Outputs

(depend only on state: $S_1 S_0$)

S_1	S_0	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1

Lights 1 and 2 → Z
 Lights 3 and 4 → Y
 Light 5 → X

Next State: $S_1' S_0'$


(depend on state and input)

In	S_1	S_0	S_1'	S_0'
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Switch → In

Whenever In=0, next state is 00.

Traffic Sign Logic

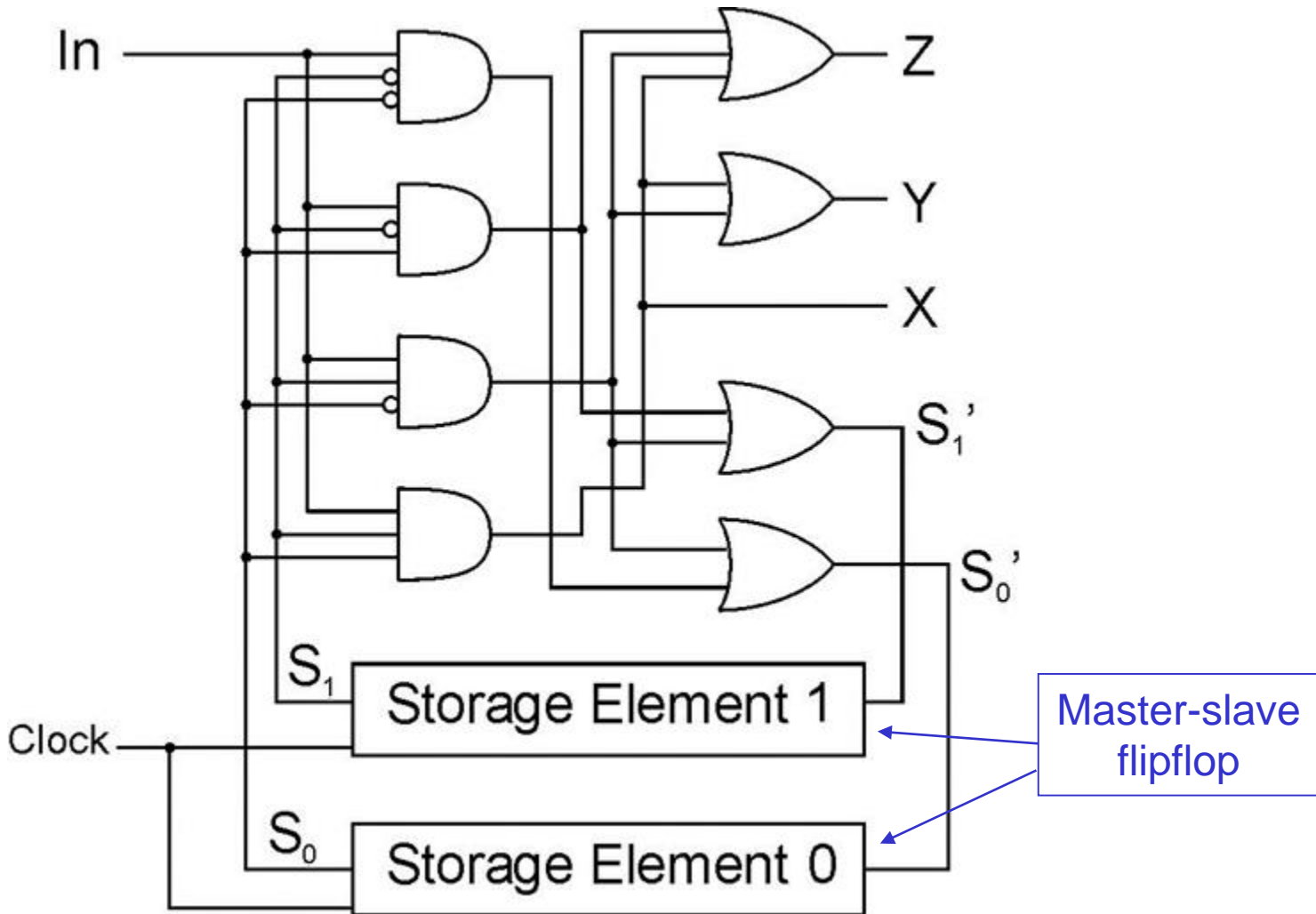

From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-3 on next slide.

Combinational Logic

- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

LC-3 Data Path

