



CS/ECE 552: Single Cycle Datapath

Prof. Matthew D. Sinclair

Lecture notes based in part on slides created by Mark Hill,
Mikko Lipasti, David Wood, Guri Sohi, John Shen
and Jim Smith


Processor Implementation

- Forecast – heart of 552 – key to project
 - Sequential logic design review (brief)
 - Clock methodology (FSD)
 - Datapath – 1 CPI
 - Single instruction, 2's complement, unsigned
- Next:
 - Control
 - Multiple cycle implementation (information only)
 - Microprogramming
 - Exceptions

Review Sequential Logic


- Logic is combinational if output is solely function of inputs
 - E.g., ALU of previous lecture
- Logic is sequential or “has state” if output function of:
 - Past and current inputs
 - Past inputs remembered in “state”
 - Of course, no magic

Review Sequential Logic: Building Block

 


- Clock high, $Q = D$, $\sim Q = \sim D$ after prop. Delay
- Clock low Q , $\sim Q$ remain unchanged
 - Level-sensitive latch

Review Sequential Logic

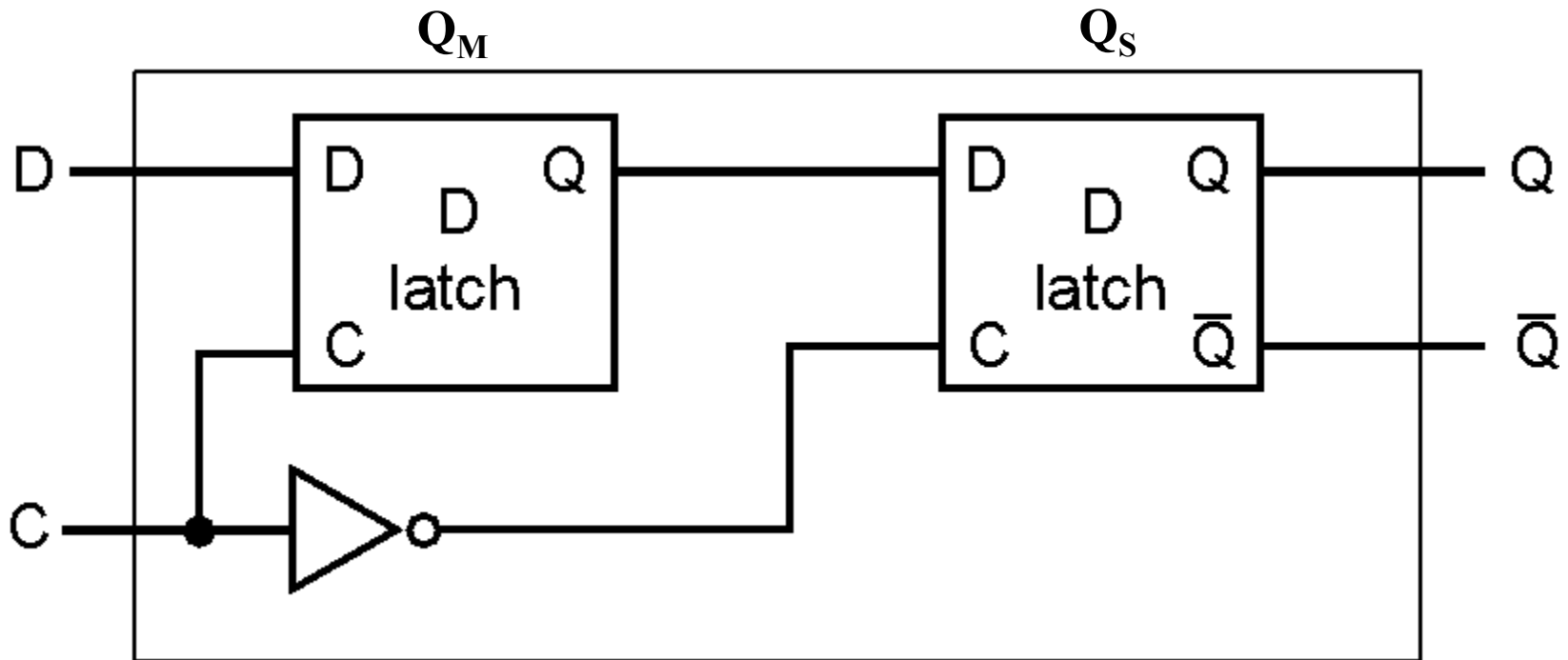

- Master/Slave D flip-flop
 - While clock high, Q_M follows D , but Q_S holds
 - At falling edge Q_M propagates to Q_S
 - *Opaque* except at falling (rising) clock edge

Review Sequential Logic

 


- Why can this fail for a latch?
 - Latch is transparent when clock is high (low)
 - Creates combinational loop
 - Increment evaluates unknown number of times

Clocking Methodology

- Motivation
 - Design data and control without considering clock
- Use Fully Synchronous Design (FSD)
 - Just a convention to simplify design process
 - Restricts design freedom
 - Eliminates complexity, can guarantee timing correctness
 - Not really feasible in real designs: off-chip I/O
 - Even in ECE 554 you will violate FSD


552 Methodology

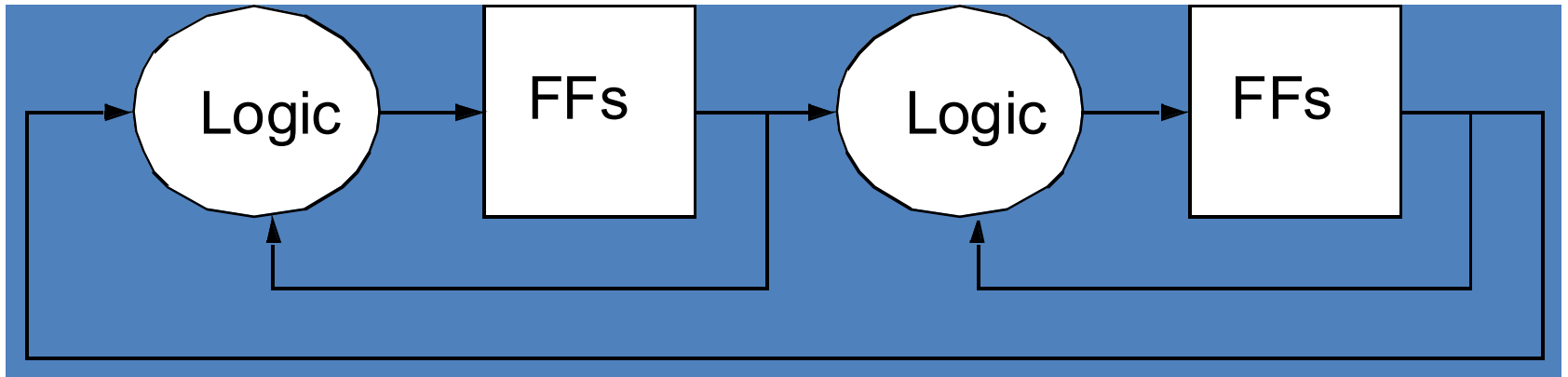- Only flip-flops: clkrst.v
- All on the same edge (rising in clkrst.v)
- All use the same clock
 - No need to draw clock signals (implicit)
- All logic you design should finish in 1 cycle




552 Methodology (Cont.)

 
- No clock gating!
 - Book has bad examples



- Correct design:

 

Delayed Clocks (Gating)

 


- Problem:
 - Some flip-flops receive gated clock late
 - Data signal may violate setup & hold req'ts

Datapath – 1 CPI

- Assumption: get whole instruction done in one long cycle
- Instructions:
 - and, lw, sw, & beq
- For each instr. our single cycle processor must:
 - For each instruction type: some comb and seq logic
 - How to connect the components


Fetch Instructions

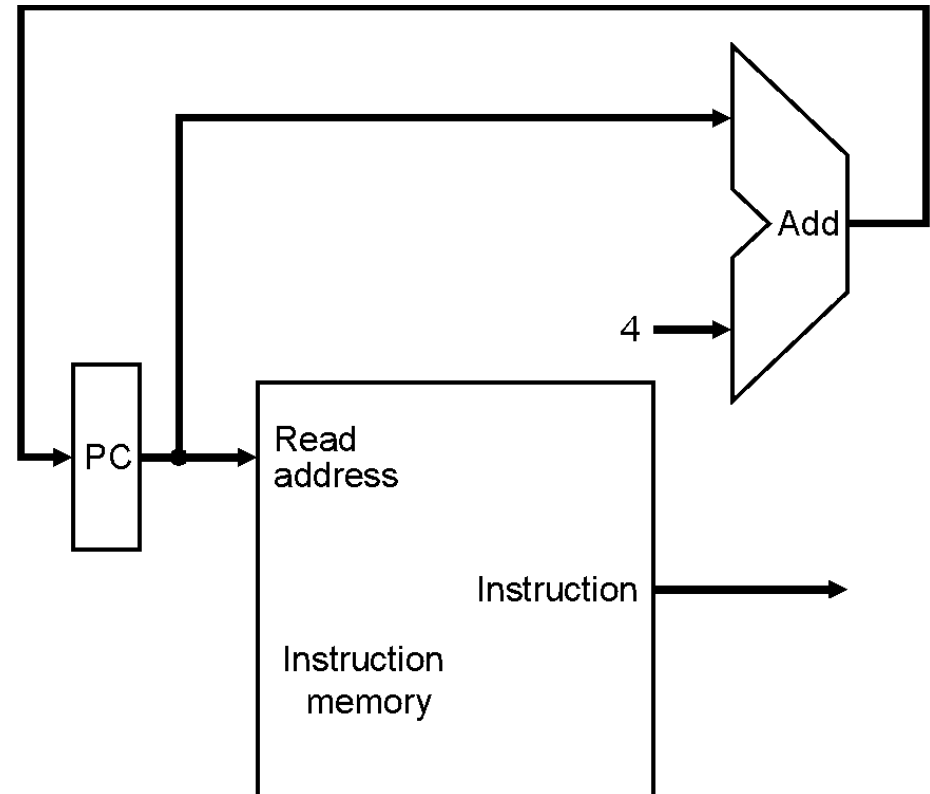- Fetch instruction, then increment PC
 - Same for all types
- Assumes
 - PC updated every cycle
 - No branches or jumps
- After this instruction fetch next one



ALU Instructions

- and \$1, \$2, \$3 # \$1 <= \$2 & \$3

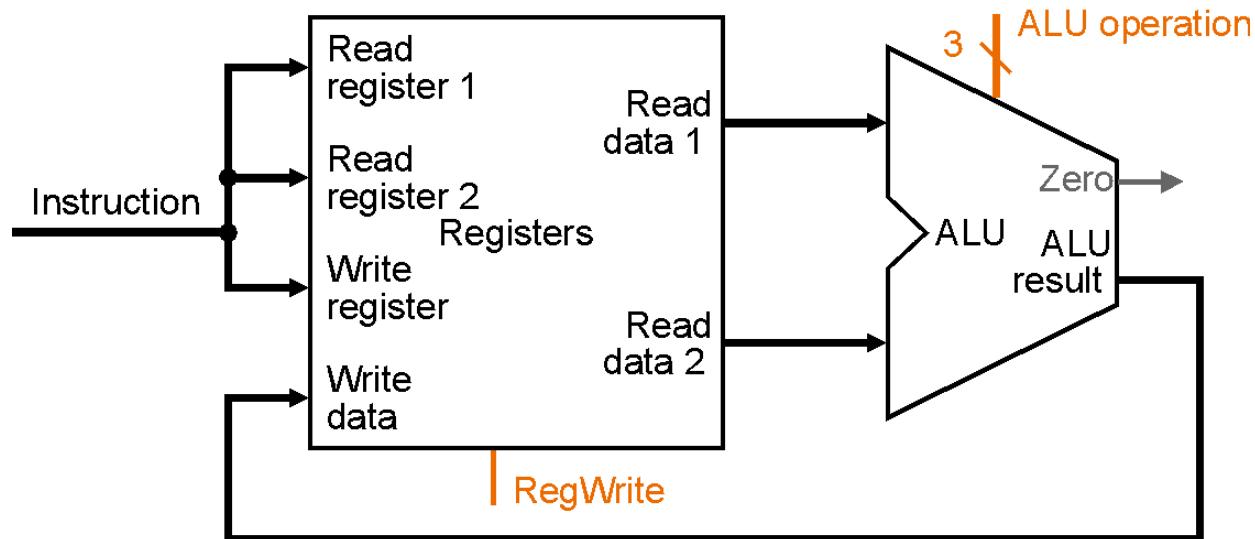

- E.g., MIPS R-format


add rd, rs, rt

Opcode	rs	rt	rd	shamt	function
6	5	5	5	5	6

Load/Store Instructions

- `lw $1, immmed($2) # $1 <= M[SE(immmed)+$2]`
- E.g., MIPS I-format:
`lw rt, immmed(rs)`


Opcode	rs	rt	immmed
6	5	5	16

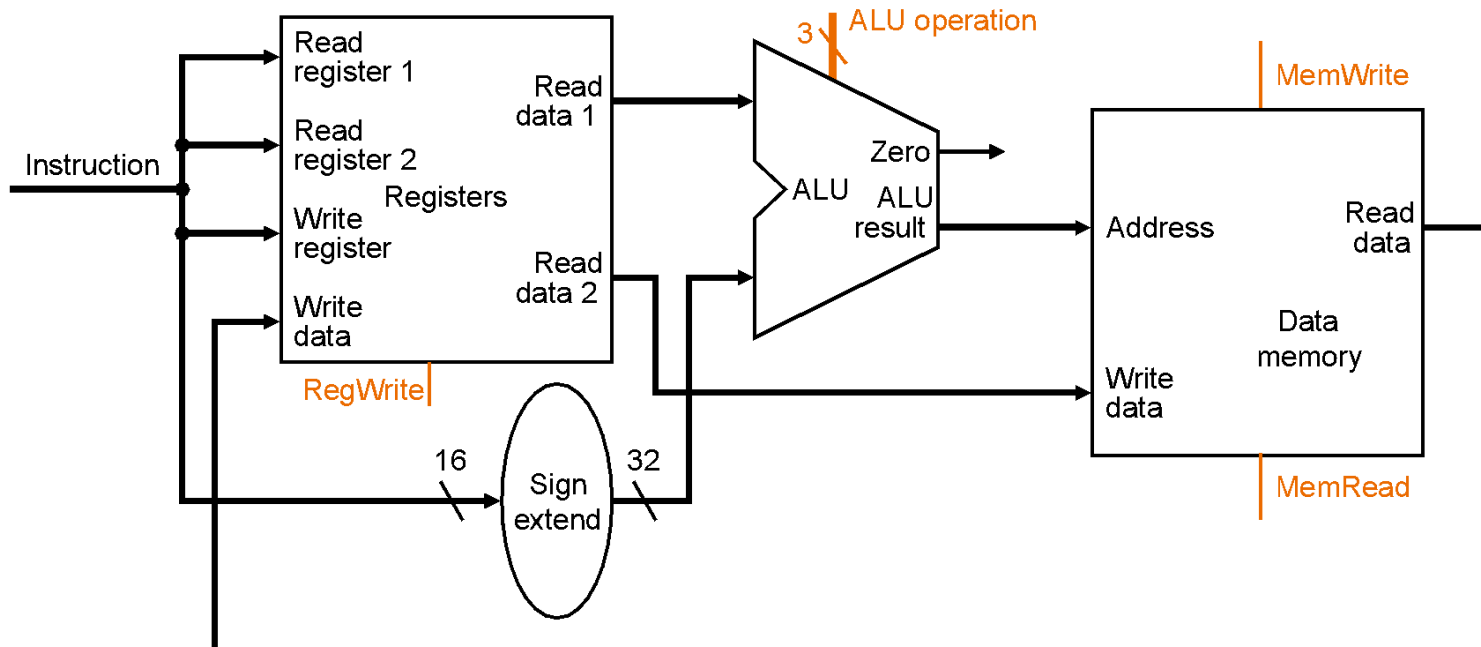


Branch Instructions

- `beq $1, $2, addr` # if ($\$1 == \2) $PC = PC + \text{addr} \ll 2$
`beq rt, rs, immed`
- Actually
 $\text{newPC} = PC + 4$
 $\text{target} = \text{newPC} + \text{addr} \ll 2$ # in MIPS offset from newPC
 if ($(\$1 - \$2) == 0$)
 $PC = \text{target}$
 else
 $PC = \text{newPC}$


Branch Instructions

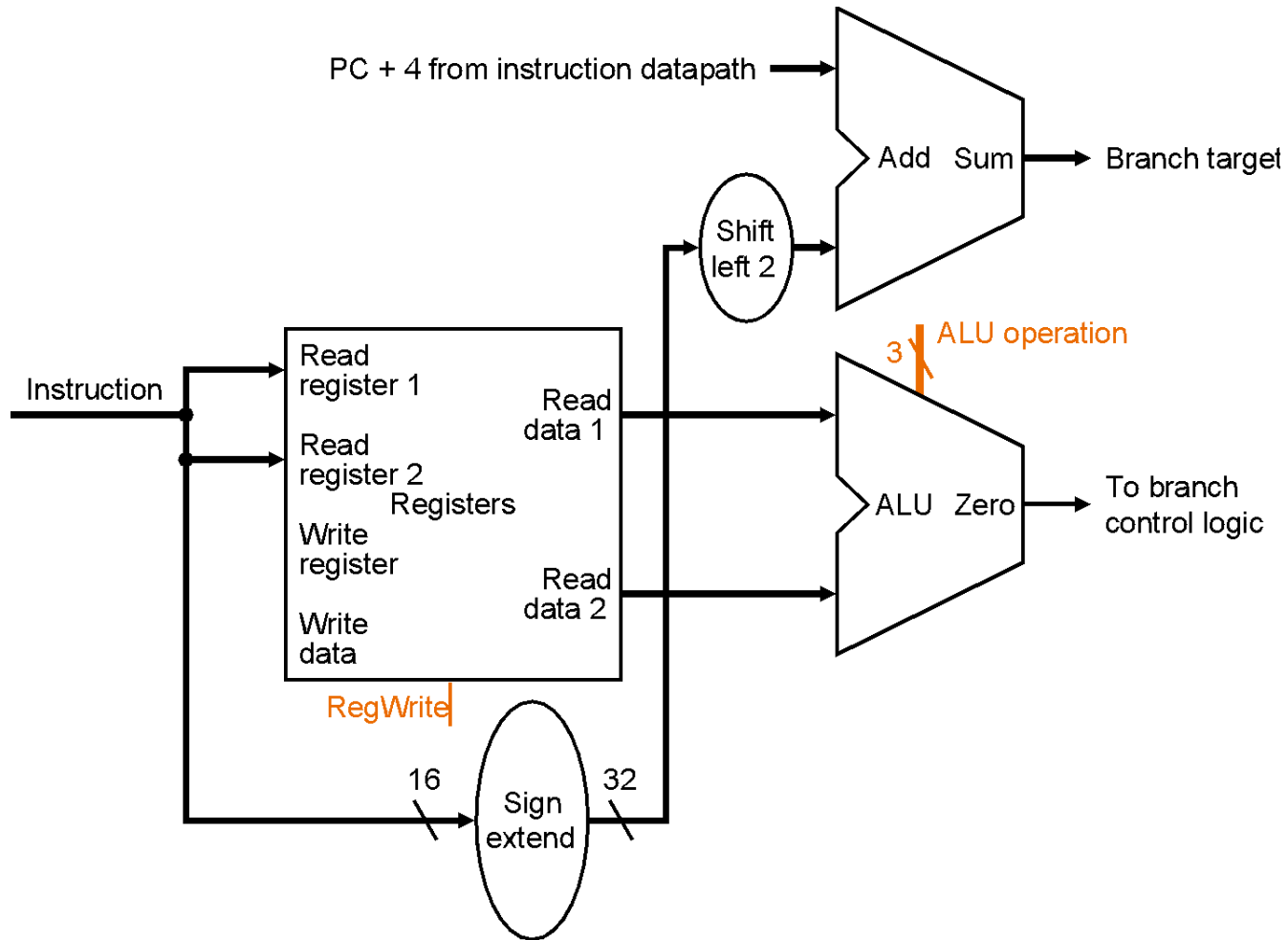

All Together

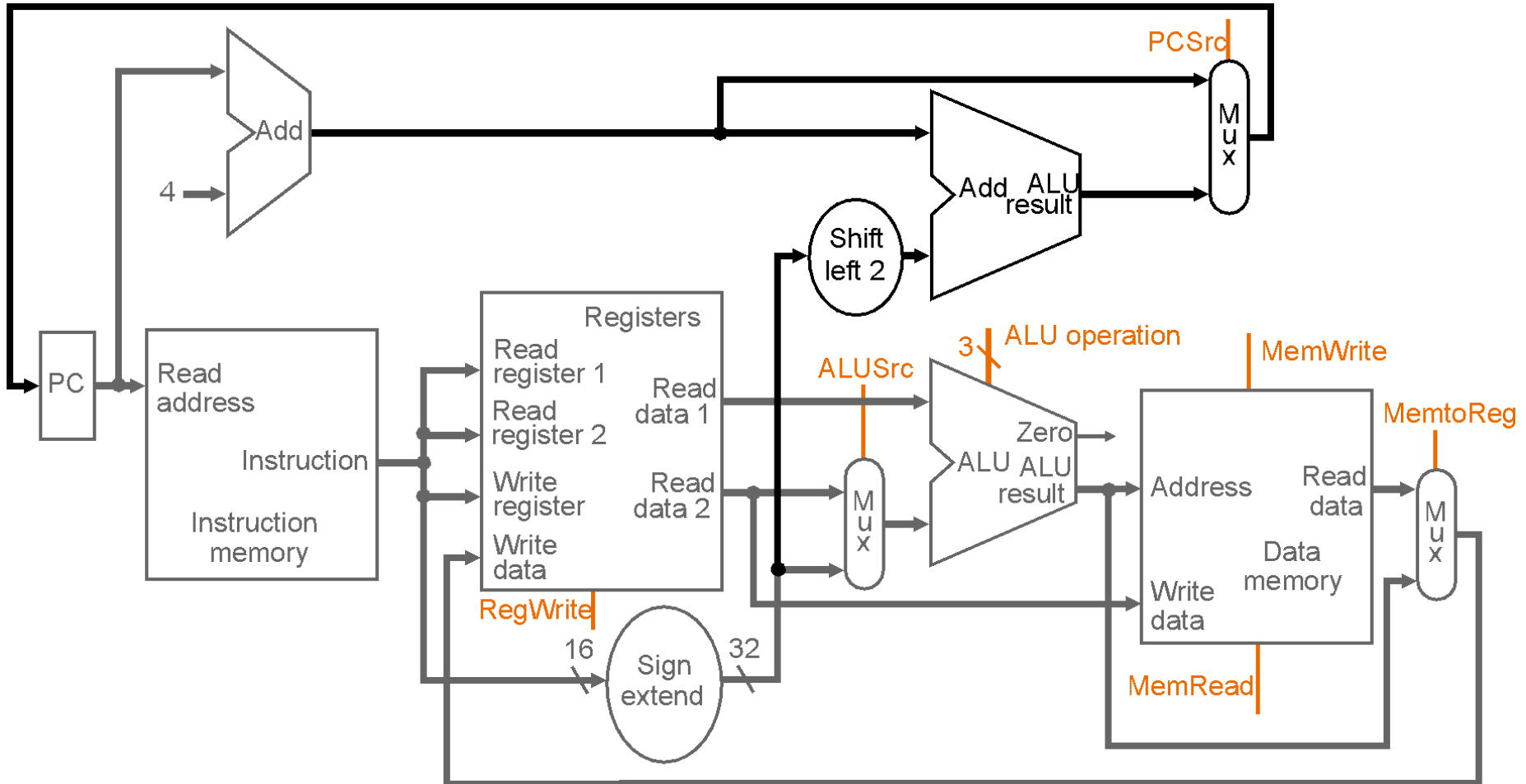

Register File?

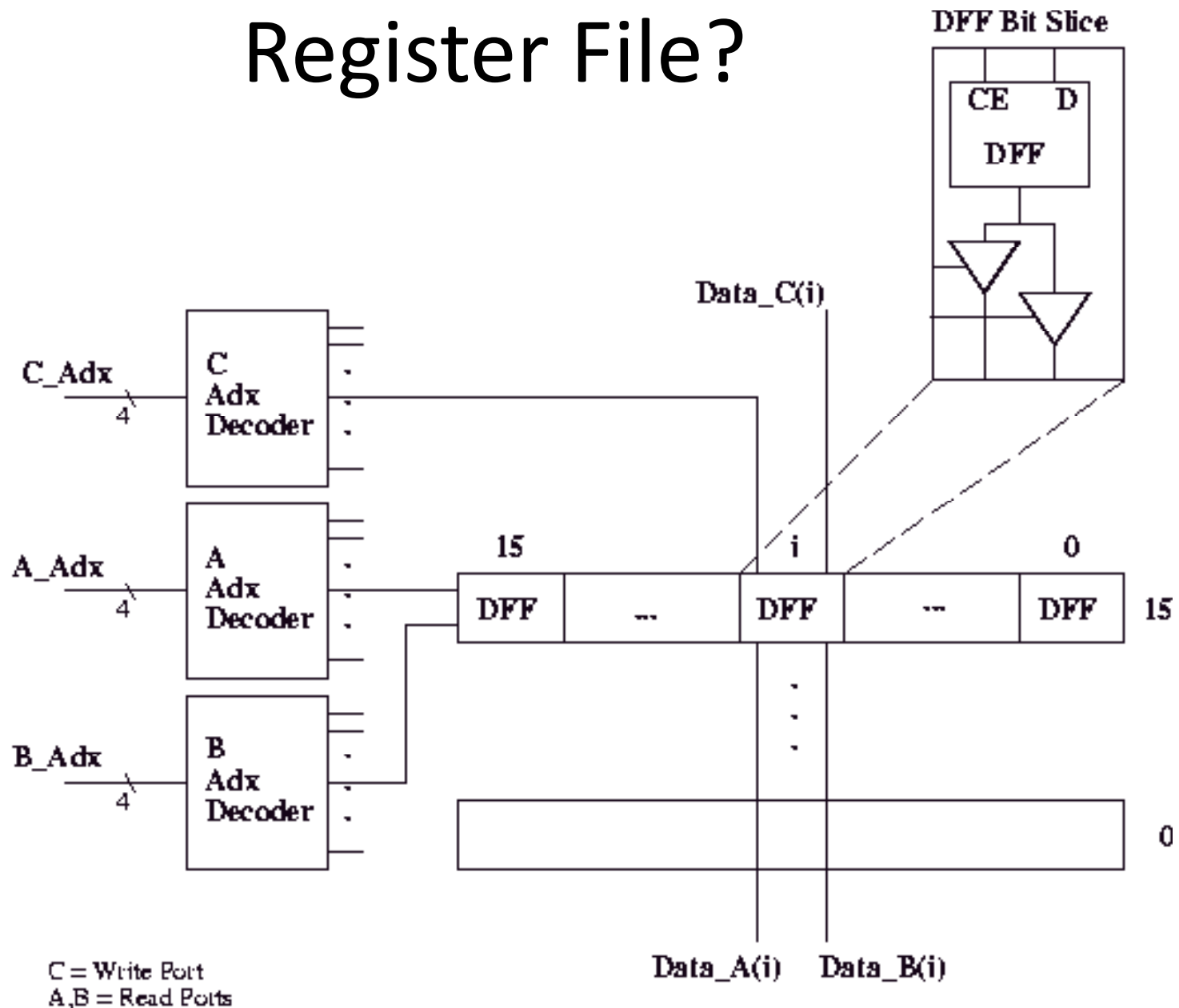

Summary

- Sequential logic design review (brief)
- Clock methodology (FSD)
- Datapath – 1 CPI
 - ALU, lw, sw, beq instructions