




CS/ECE 552: Carry Lookahead

Prof. Matthew D. Sinclair

Lecture notes based in part on slides created by Mark Hill,
David Wood, Mikko Lipasti, Guri Sohi, John Shen and
Jim Smith

Combined Ripple-carry Adder/Subtractor

 

- The above ALU is too slow
 - Gate delays for add = $32 \times \text{FA} + \text{XOR} \approx 64$

Carry Lookahead

- Theoretically, in parallel
 - $\text{Sum}_0 = f(c_{in}, a_0, b_0)$
 - $\text{Sum}_i = f(c_{in}, a_i \dots a_0, b_i \dots b_0)$
 - $\text{Sum}_{31} = f(c_{in}, a_{31} \dots a_0, b_{31} \dots b_0)$
- Any boolean function in two levels, right?
 - Wrong! Too much fan-in!

Carry Lookahead

- Need compromise
 - Build tree so delay is $O(\log_2 n)$ for n bits
 - E.g. 2 x 5 gate delays for 32 bits
- We will consider basic concept with
 - 4 bits
 - 16 bits
- Warning: a little convoluted

Carry Lookahead

0101 0100

0011 0110

Need:

both 1 to generate carry

one or both 1s to propagate carry

Define: $g_i = a_i * b_i$ ## carry generate
 $p_i = a_i + b_i$ ## carry propagate

Recall: $c_{i+1} = a_i * b_i + a_i * c_i + b_i * c_i$
 $= a_i * b_i + (a_i + b_i) * c_i$
 $= g_i + p_i * c_i$

Carry Lookahead

- Therefore

$$c_1 = g_0 + p_0 * c_0$$


$$\begin{aligned} c_2 &= g_1 + p_1 * c_1 = g_1 + p_1 * (g_0 + p_0 * c_0) \\ &= g_1 + p_1 * g_0 + p_1 * p_0 * c_0 \end{aligned}$$

$$c_3 = g_2 + p_2 * g_1 + p_2 * p_1 * g_0 + p_2 * p_1 * p_0 * c_0$$

$$c_4 = g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0 + p_3 * p_2 * p_1 * p_0 * c_0$$


- Uses one level to form p_i and g_i , two levels for carry
- But, this needs $n+1$ fanin at the OR and the rightmost AND

4-bit Carry Lookahead Adder

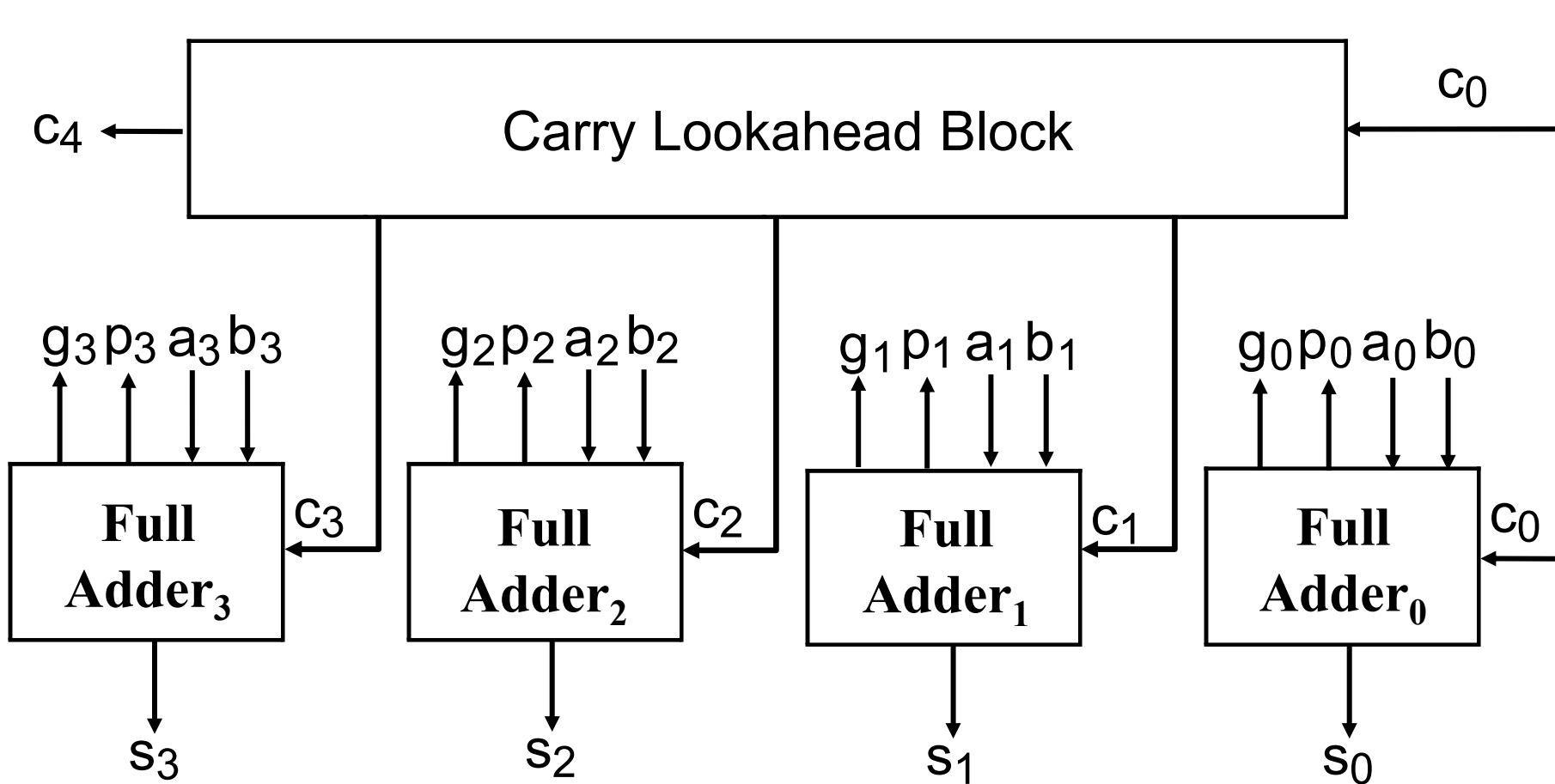

Aside: Do we still need c_{out} 's from Full Adders?

Hierarchical Carry Lookahead for 16 bits

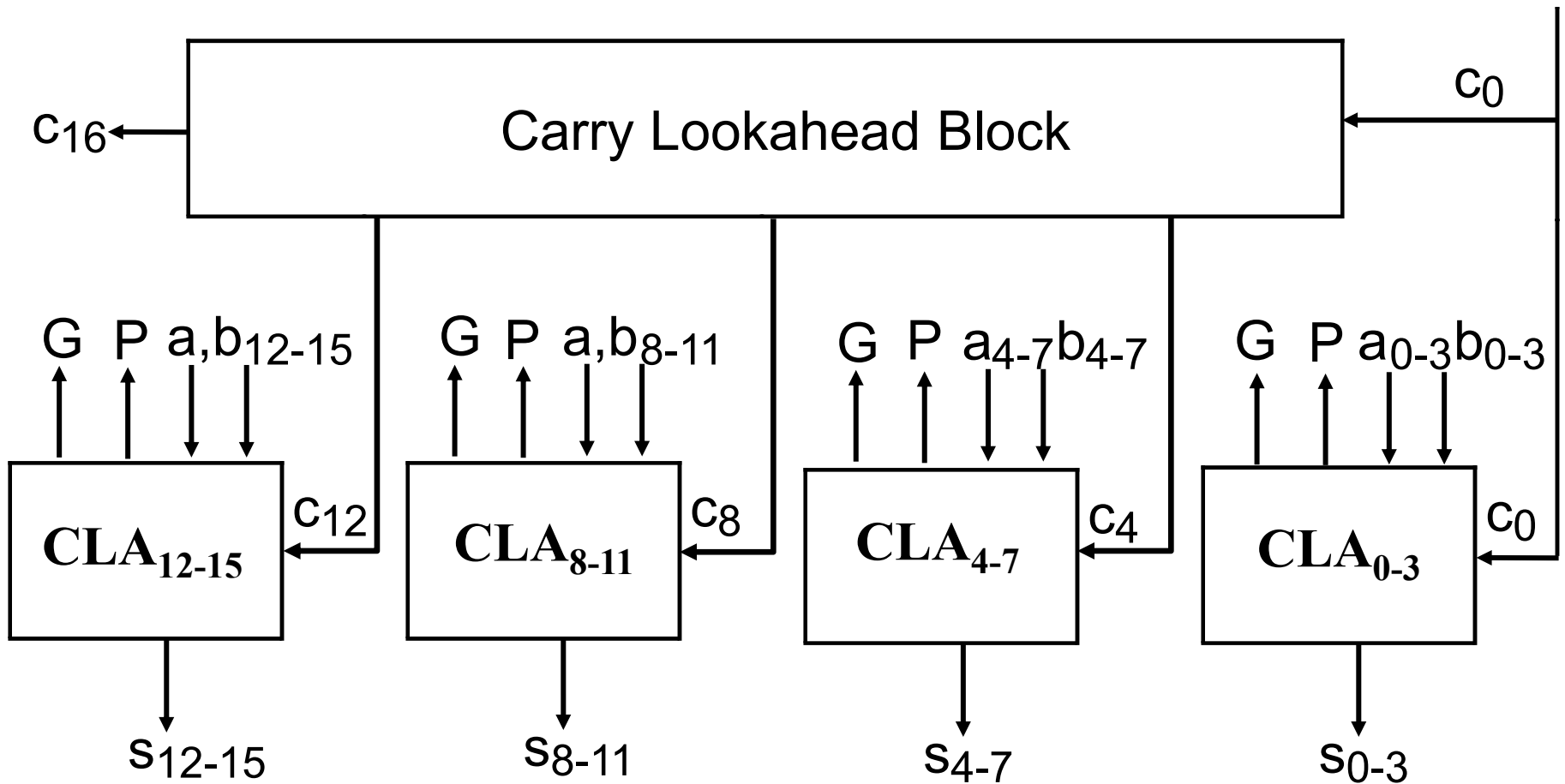

Aside: Do we still need c_{out} 's from CLA4's?

Hierarchical CLA for 16 bits

Build 16-bit adder from four 4-bit adders

Figure out G and P for 4 bits together

$$G_{0,3} = g_3 + p_3 * g_2 + p_3 * p_2 * g_1 + p_3 * p_2 * p_1 * g_0$$

$$P_{0,3} = p_3 * p_2 * p_1 * p_0 \text{ (Notation a little different from the book)}$$

$$G_{4,7} = g_7 + p_7 * g_6 + p_7 * p_6 * g_5 + p_7 * p_6 * p_5 * g_4$$

$$P_{4,7} = p_7 * p_6 * p_5 * p_4$$

$$G_{12,15} = g_{15} + p_{15} * g_{14} + p_{15} * p_{14} * g_{13} + p_{15} * p_{14} * p_{13} * g_{12}$$

$$P_{12,15} = p_{15} * p_{14} * p_{13} * p_{12}$$

Carry Lookahead Basics

Fill in the holes in the G's and P's

$$G_{i,k} = G_{j+1,k} + P_{j+1,k} * G_{i,j} \quad (\text{assume } i < j+1 < k)$$

$$P_{i,k} = P_{i,j} * P_{j+1,k}$$

$$G_{0,7} = G_{4,7} + P_{4,7} * G_{0,3}$$

$$P_{0,7} = P_{0,3} * P_{4,7}$$


$$G_{8,15} = G_{12,15} + P_{12,15} * G_{8,11}$$

$$P_{8,15} = P_{8,11} * P_{12,15}$$


$$G_{0,15} = G_{8,15} + P_{8,15} * G_{0,7}$$

$$P_{0,15} = P_{0,7} * P_{8,15}$$

CLA: Compute G's and P's

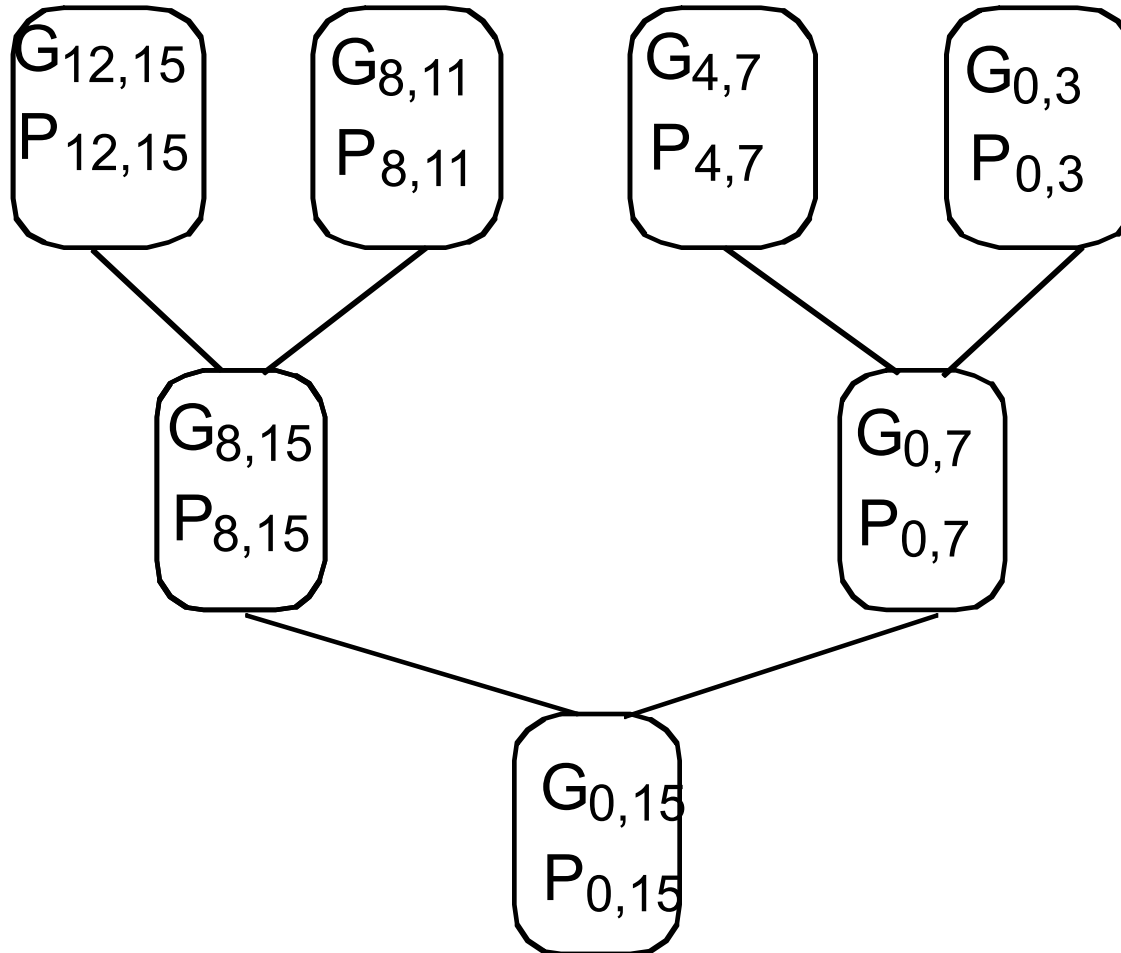


CLA: Compute Carries

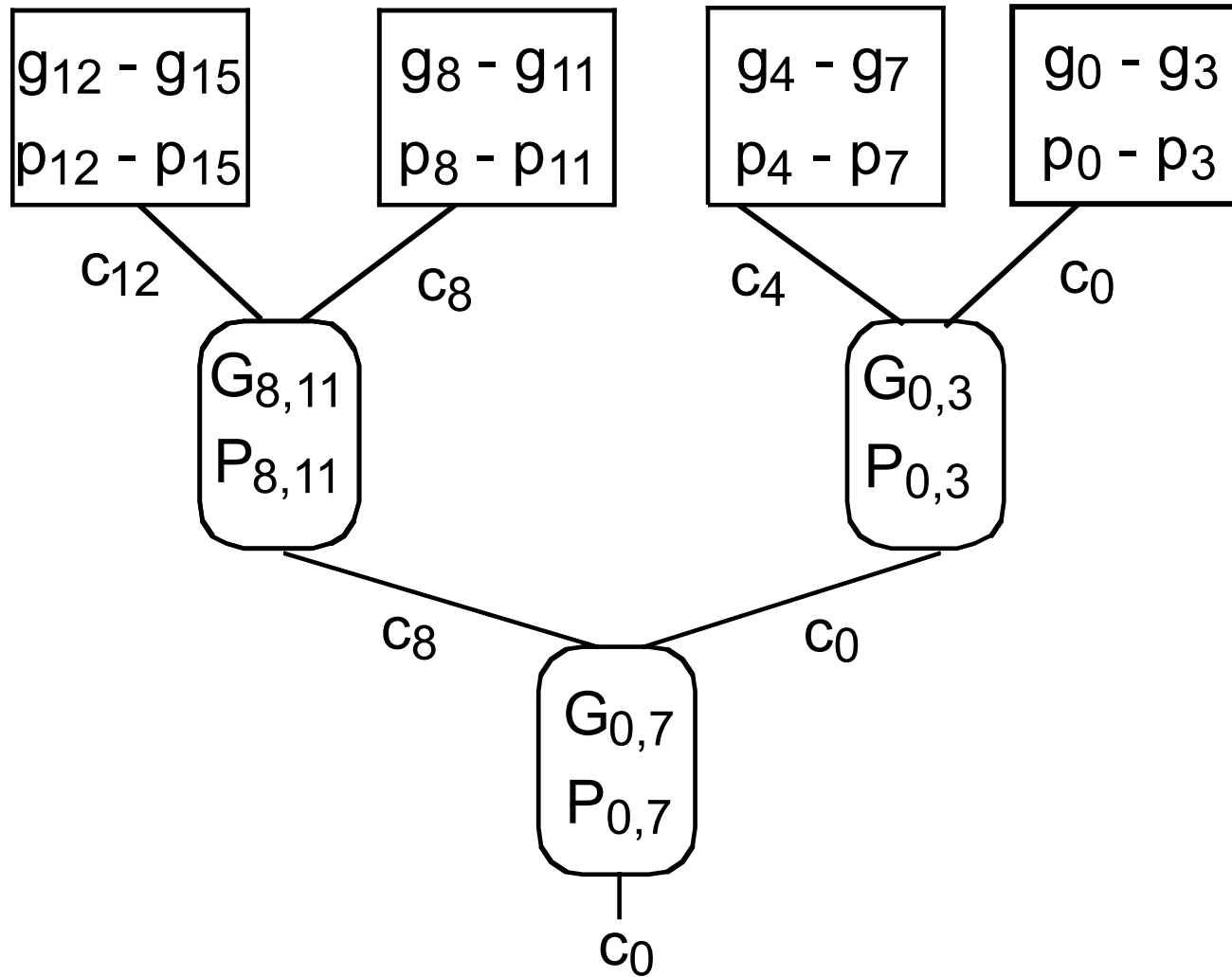

Other Adders: Carry Select

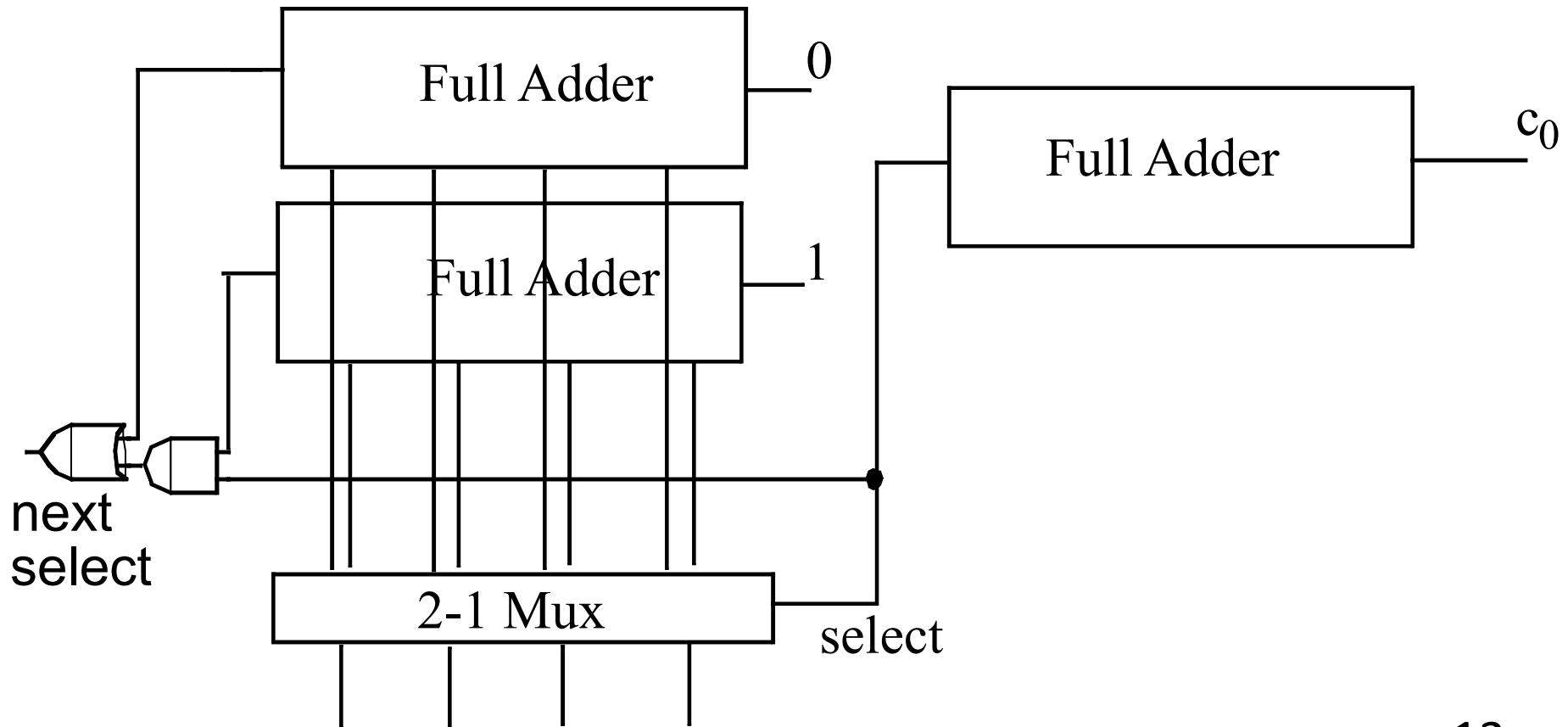- Two adds in parallel; with and without c_{in}
 - When C_{in} is done, select correct result



Other Adders: Carry Save


$A + B \Rightarrow S$

Save carries $A + B \Rightarrow S, C_{out}$


Use C_{in} $A + B + C \Rightarrow S1, S2$ (3# to 2# in parallel)

Used in combinational multipliers by building a Wallace Tree

	7	9
+	1	8
C,S	0,8	1,7
Final	8+1=9	7

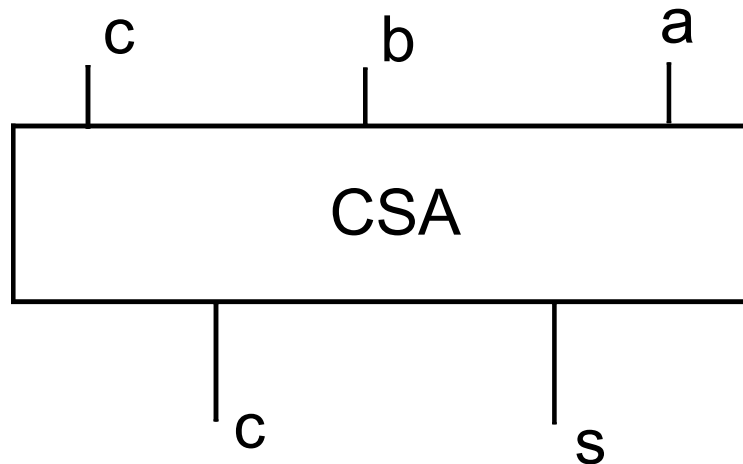

Adding Up Many Bits

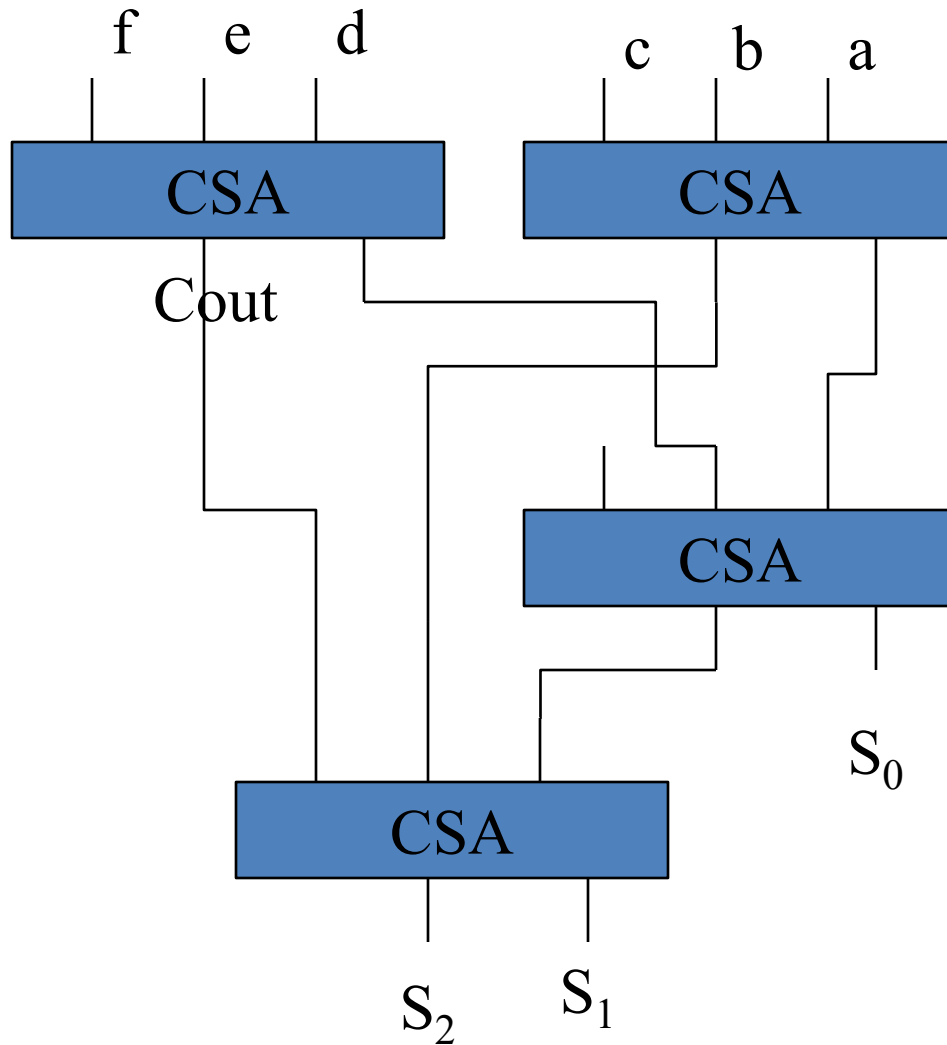

Summary

- Carry lookahead
- Carry-select, Carry-save
- State of the art: parallel prefix adders
 - aka. Brent-Kung, Kogge-Stone, ...
 - Generalization of CLA
 - Physical design (e.g. wiring) of primary concern
 - Covered in ECE 555