

CS/ECE 752: Advanced Computer Architecture I



Professor Matthew D. Sinclair
Memories

Slide History/Attribution Diagram:

UW Madison
Hill, Sohi,
Smith, Wood

UPenn
Amir Roth,
Milo Martin

Various Universities
Asanovic, Falsafi, Hoe, Lipasti,
Shen, Smith, Vijaykumar

UW Madison
Hill, Sohi, Wood,
Sankaralingam, Sinclair

UCLA
Nowatzki

Announcements 10/7/20

- Midterm next Wednesday
- Midterm review on Monday
 - Bring questions
- No class Friday
- Project Preliminary Ideas due Friday


Midterm

- Will be similar in format to past exams
 - Samples available on course website
 - Because electronic: a bit more focus on advanced problems
 - Overall: combination of math and essay problems
- Logistics
 - 24 hours to complete (due 215 PM on 10/14)
 - Post questions on Piazza
 - I will be available during lecture time (BBC Ultra)
 - Will run all solutions through software to detect academic misconduct
 - Can be hand-written or typed
- Likely will use Gradescope to grade

SRAM Technology


- **SRAM**: static RAM
 - **Static**: bits directly connected to power/ground
 - Naturally/continuously “refreshed”, never decay (contrast DRAM)
 - Designed for speed
 - Implements all storage arrays in real processors
 - Register file, caches, branch predictor, etc.
 - Everything except pipeline latches
- Latches vs. SRAM
 - Latches: singleton word, always read/write same one
 - SRAM: array of words, can read/write different ones
 - Address indicates which one

(CMOS) Memory Components

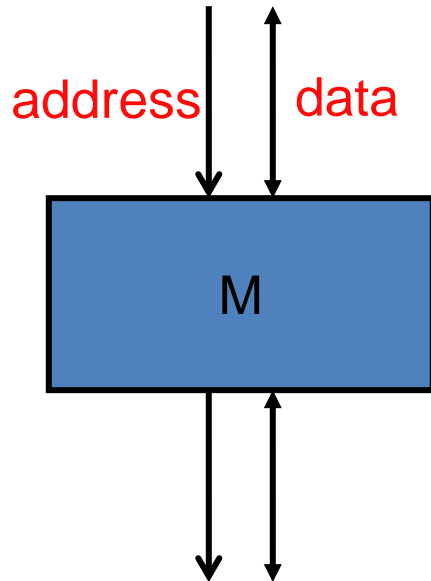


- Interface
 - N-bit **address** bus (on N-bit machine)
 - **Data** bus
 - Can have read/write on same data bus
 - Or, can have dedicated read/write buses
 - Can have multiple **ports**: address/data bus pairs

SRAM: First Cut

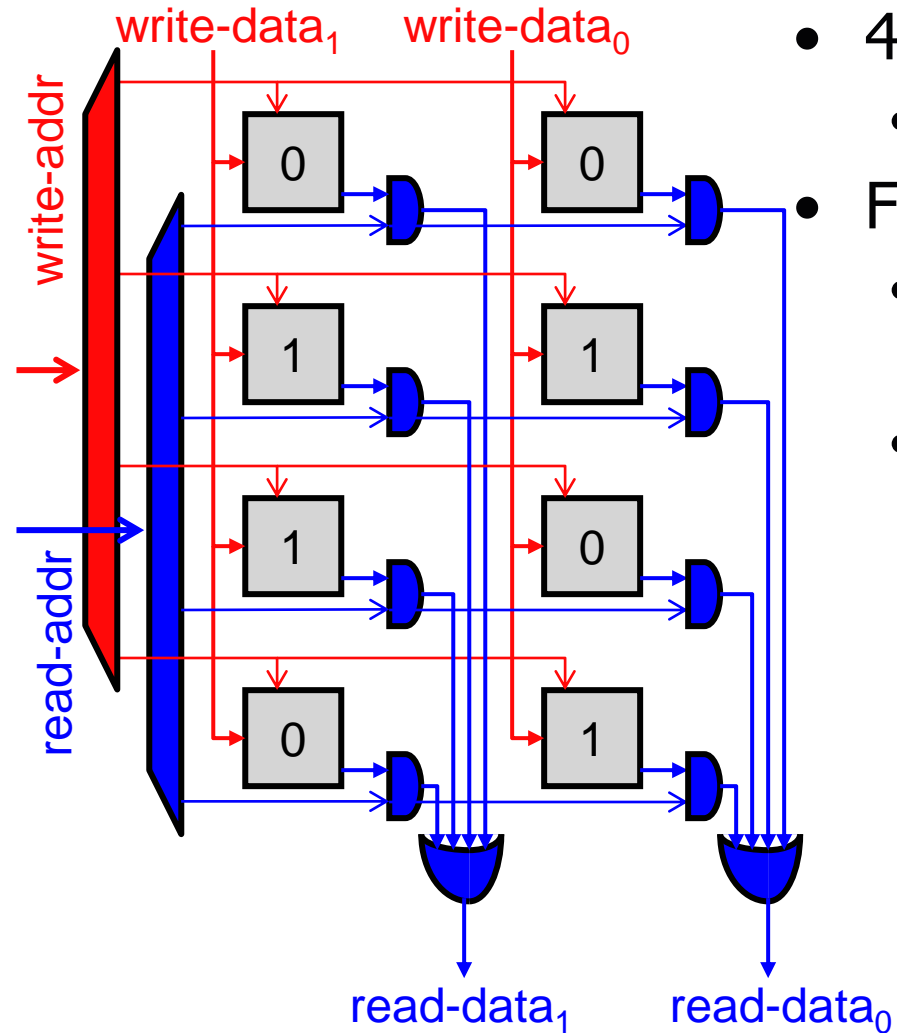


- 4x2 (4 2-bit words) RAM
 - 2-bit addr
- First cut: bits are D-Latches
 - **Write port**
 - Addr **decodes** to enable signals
 - **Read port**
 - Addr **decodes** to mux selectors
 - 1024 input OR gate?
 - Physical layout of output wires
 - RAM width $\propto M$
 - Wire delay \propto wire length

SRAM: Second Cut

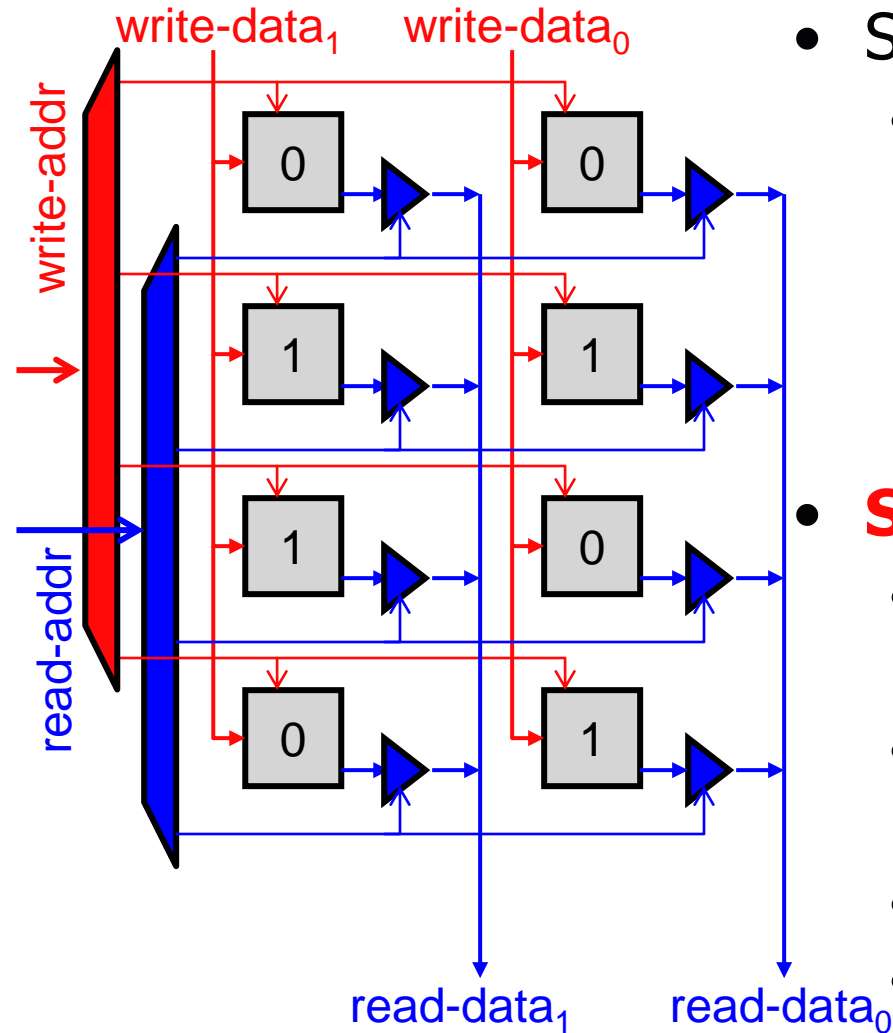

- Second cut: tri-state wired-OR
 - Read mux using **tri-states**
 - + Scalable, distributed “muxes”
 - + Better layout of output wires
 - RAM width independent of M
- **Standard RAM**
 - Bits in word connected by **wordline**
 - 1-hot decode address
 - Bits in position connected by **bitline**
 - Shared input/output wires
 - **Port**: one set of wordlines/bitlines
 - Grid-like design

SRAM: Third Cut

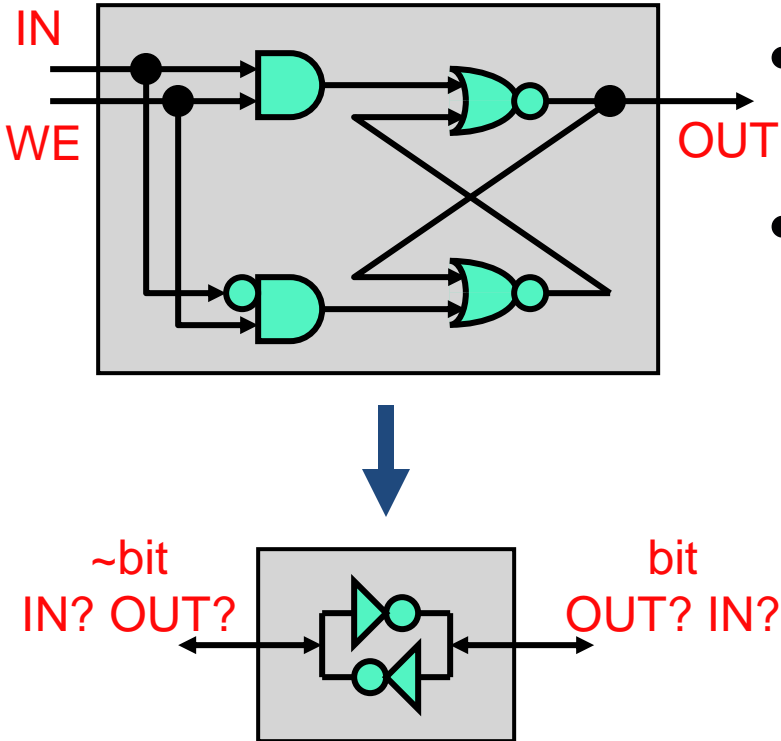


- Third cut: replace latches with...
 - 28 transistors per bit
- **Cross-coupled inverters (CCI)**
 - + 4 transistors
 - Convention
 - Right node is **bit**, left is **~bit**
 - Non-digital interface
 - What is the input and output?
 - Where is write enable?
 - Implement ports in “analog” way
 - Transistors, not full gates

SRAM: Register Files and Caches


- Two different SRAM port styles
 - **Regfile style**
 - Modest size: <4KB
 - Many ports: some read-only, some write-only
 - Write and read both take half a cycle (write first, read second)
 - **Cache style**
 - Larger size: >8KB
 - Few ports: read/write in a single port
 - Write and read can both take full cycle

Regfile-Style Read Port

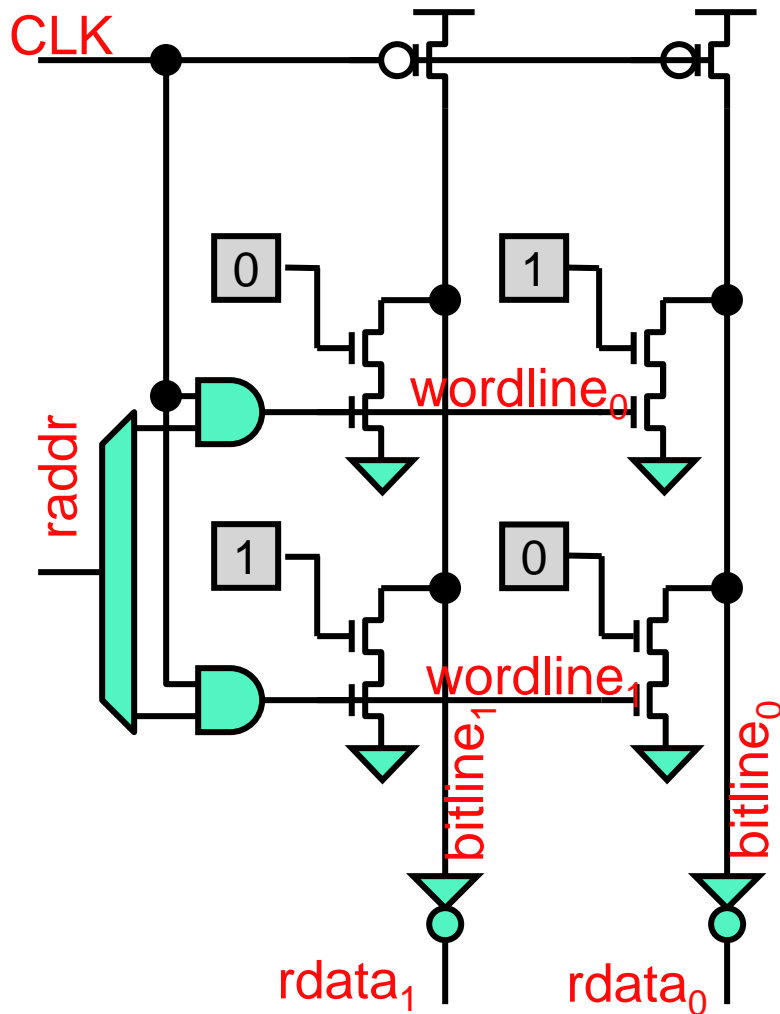


- Two phase read
 - Phase I: clk = 0
 - Pre-charge bitlines to 1
 - Negated bitlines are 0
 - Phase II: clk = 1
 - One wordline goes high
 - All "1" bits in that row discharge their bitlines to 0
 - Negated bitlines go to 1

Read Port In Action: Phase I

 


- $CLK = 0$
 - p-transistors conduct
 - Bitlines "pre-charge" to 1
 - $rdata_{1-0}$ are 0

Read Port In Action: Phase II

 

- $raddr = 1$
- $CLK = 1$
 - p-transistors close
 - $wordline_1 = 1$
 - "1" bits on $wordline_1$ create path from bitline to ground
 - $SRAM[1]$
 - Corresponding bitlines discharge
 - $bitline_1$
 - Corresponding rdata bits go to 1
 - $rdata_1$
- That's a read


Regfile-Style Write Port

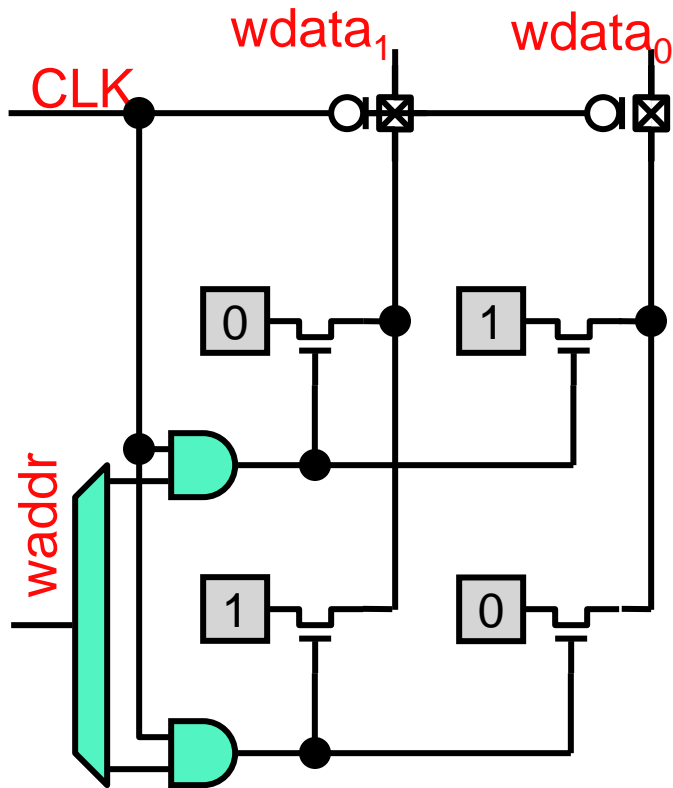


- Two phase write
 - Phase I: $clk = 1$
 - Stabilize one wordline high
 - Phase II: $clk = 0$
 - Open pass-transistors
 - "Overwhelm" bits in selected word
- Actually: two clocks here
 - Both phases in first half

 **pass transistor**: like a tri-state buffer

A 2-Read Port 1-Write Port Regfile

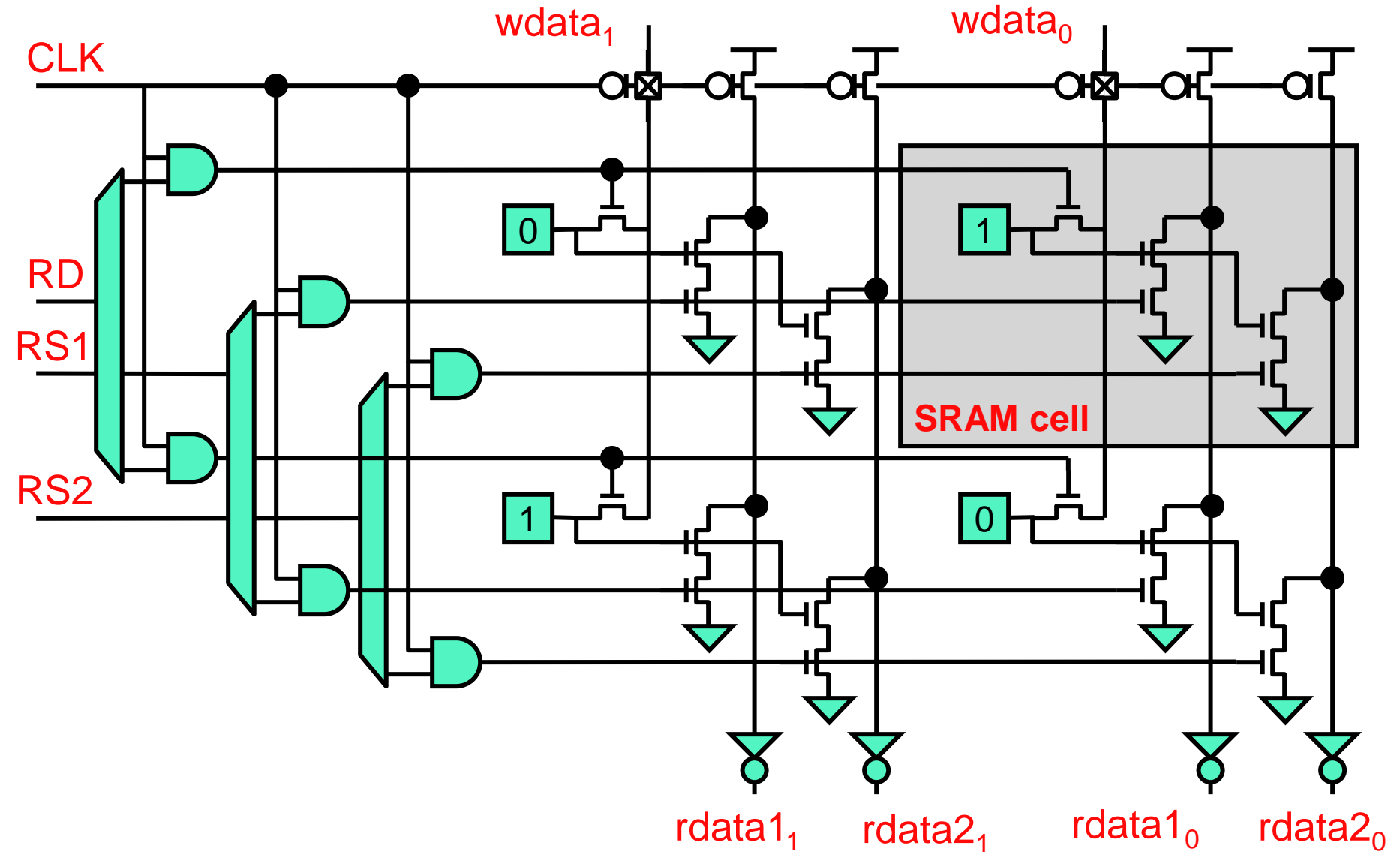

Cache-Style Read/Write Port


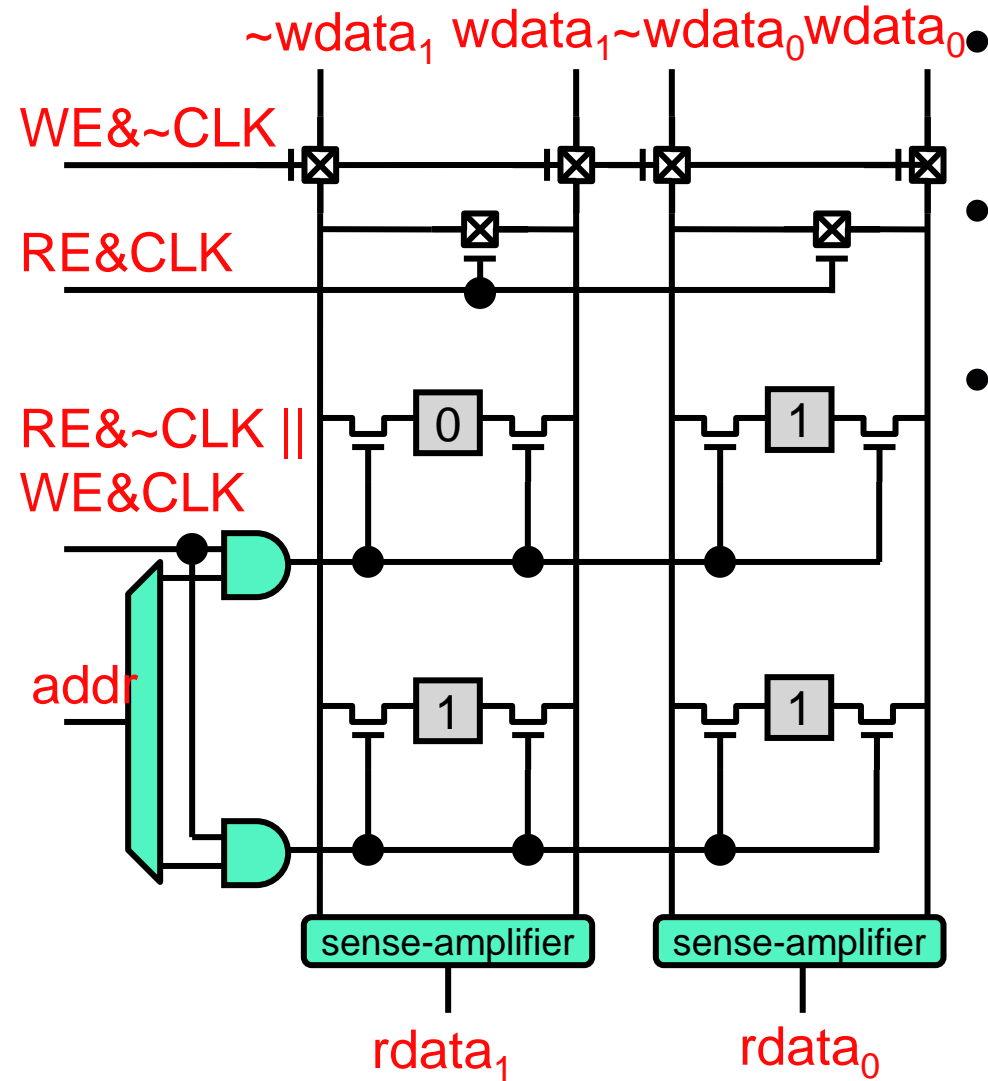


Double-ended bitlines

- Connect to both sides of bit
- Two-phase write
 - Just like a register file
- Two phase read
 - Phase I: $clk = 1$
 - Equalize bitline pair voltage
 - Phase II: $clk = 0$
 - One wordline high
 - "1 side" bitline swings up
 - "0 side" bitline swings down
 - Sens-amp translates swing



Read/Write Port in Read Action: Phase I

 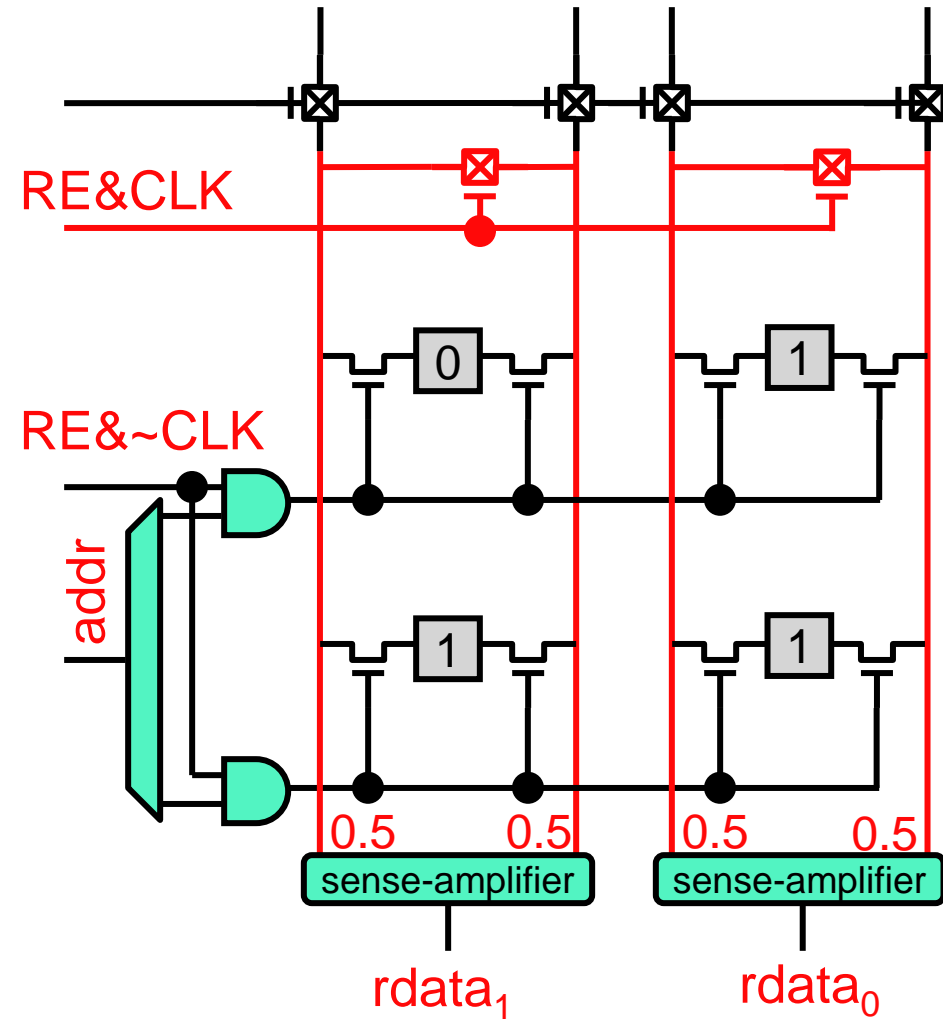- Phase I: $\text{clk} = 1$
 - Equalize voltage on bitline pairs
 - To (nominally) 0.5




Read/Write Port in Read Action: Phase II

 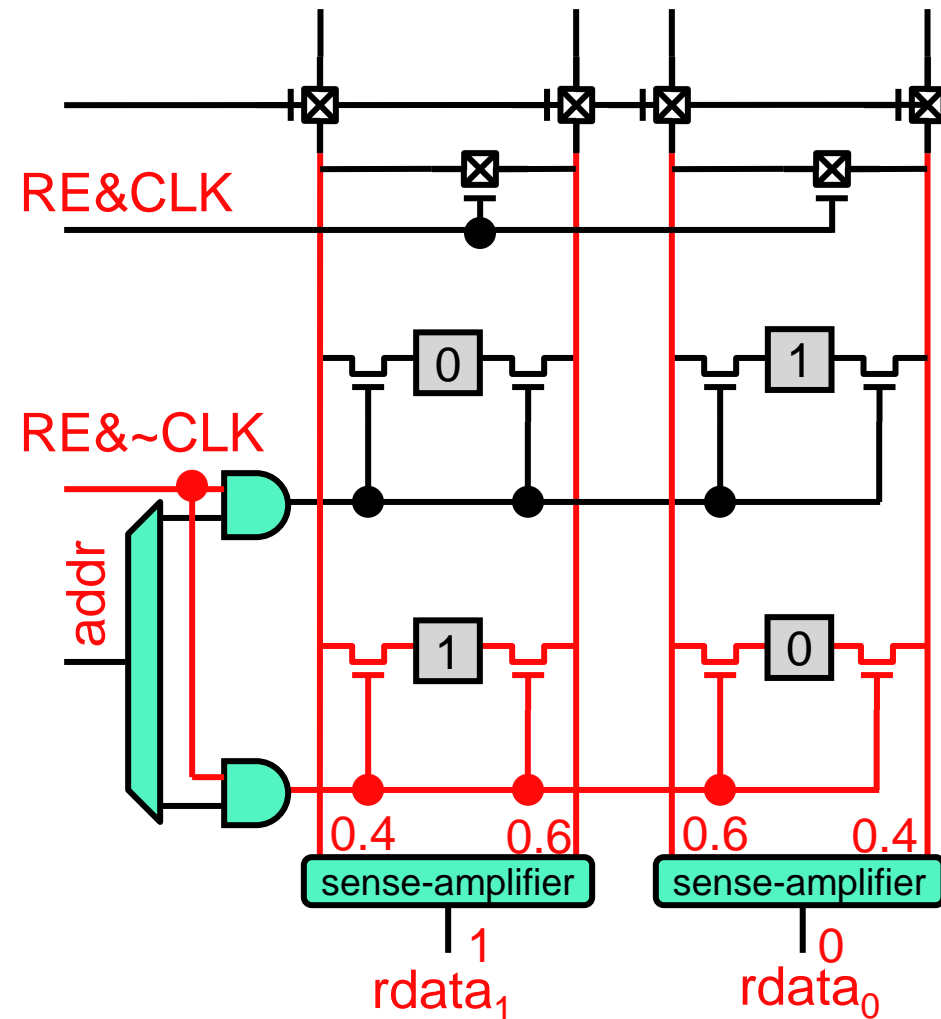- Phase II: $\text{clk} = 0$
 - wordline_1 goes high
 - "1 side" bitlines swing high 0.6
 - "0 side" bitlines swing low 0.4
 - Sens-amps interpret swing





Cache-Style SRAM Latency

- Assume
 - M N-bit words
 - Some minimum wire spacing L
 - CCIs occupy no space
- 4 major latency components: taken in series
 - **Decoder**: $\propto \log_2 M$
 - **Wordlines**: $\propto 2NL$ (cross $2N$ bitlines)
 - **Bitlines**: $\propto ML$ (cross M wordlines)
 - **Muxes + sense-amps**: constant
 - 32KB SRAM: red components contribute about equally
- Latency: $\propto (2N+M)L$
 - Maximize storage for some max latency: make SRAMs as square as possible: minimize $2N+M$
- Latency: $\propto \sqrt{\# \text{total bits}}$

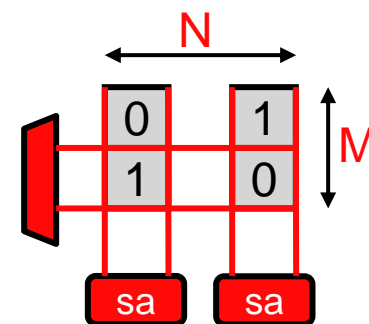

Multi-Ported Cache-Style SRAM Latency

- Previous calculation had hidden constant
 - Number of ports **P**
- Recalculate latency components
 - Decoder: $\propto \log_2 M$ (unchanged)
 - Wordlines: $\propto 2NLP$ (cross $2NP$ bitlines)
 - Bitlines: $\propto MLP$ (cross MP wordlines)
 - Muxes + sense-amps: constant (unchanged)
- Latency: $\propto (2N+M)LP$
- **Latency: $\propto \sqrt{\#bits} * \#ports$**
- How does latency scale? (P)
- How does power scale? (P^2)
 - Both length and number active increase

  


Multi-Porting an SRAM

- Why multi-porting?
 - Multiple accesses per cycle
- **True multi-porting** (physically adding a port) not good
 - + Any combination of accesses will work
 - Increases access latency, energy $\propto P$, area $\propto P^2$
- Another option: **pipelining**
 - Timeshare single port on clock edges (wave pipelining: no latches)
 - + Negligible area, latency, energy increase
 - Not scalable beyond 2 ports
- Yet another option: **replication**
 - Don't laugh: used for register files, even caches (Alpha 21164)
 - Smaller and faster than true multi-porting $2 \cdot P^2 < (2 \cdot P)^2$
 - + Adds read bandwidth, any combination of reads will work
 - Doesn't add write bandwidth, not really scalable beyond 2 ports


Banking an SRAM

- Divide SRAM into banks, interleave the addresses
- Allow parallel access to different banks
- Two accesses to same bank?
bank-conflict, one waits
- Low area, latency overhead for routing requests to banks
- Few bank conflicts given sufficient number of banks
 - Rule of thumb: N simultaneous accesses $\rightarrow 2N$ banks
- How to divide words among banks?
 - **Round robin**: using address LSB (least significant bits)
 - Example: 16 word RAM divided into 4 banks
 - **b0**: 0,4,8,12; **b1**: 1,5,9,13; **b2**: 2,6,10,14; **b3**: 3,7,11,15
 - Why? Spatial locality

 


Full-Associativity with CAMs

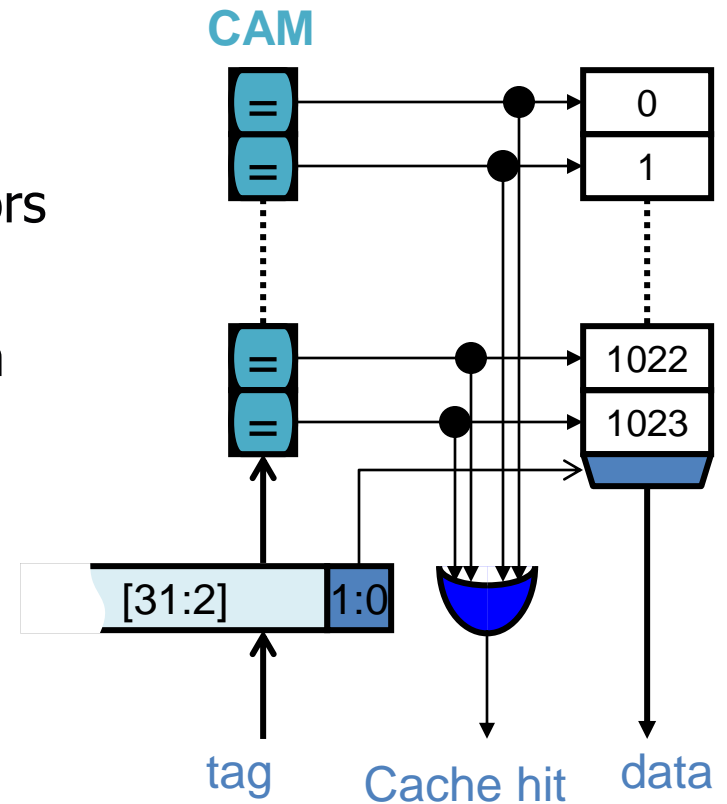- **CAM**: content associative memory
 - Array of words with built-in comparators
 - Matchlines instead of bitlines
 - Output is “one-hot” encoding of match
- FA cache?
 - Tags as CAM
 - Data as RAM
- **Hardware is not software**
 - No such thing as software CAM




CAM Circuit

 


- CAM: reverse RAM
 - Bitlines are inputs
 - Called **matchlines**
 - Wordlines are outputs
- Two phase match
 - Phase I: $clk=0$
 - Pre-charge wordlines
 - Phase II: $clk=1$
 - Enable matchlines
 - Non-matching bits dis-charge wordlines

CAM Circuit In Action: Phase I

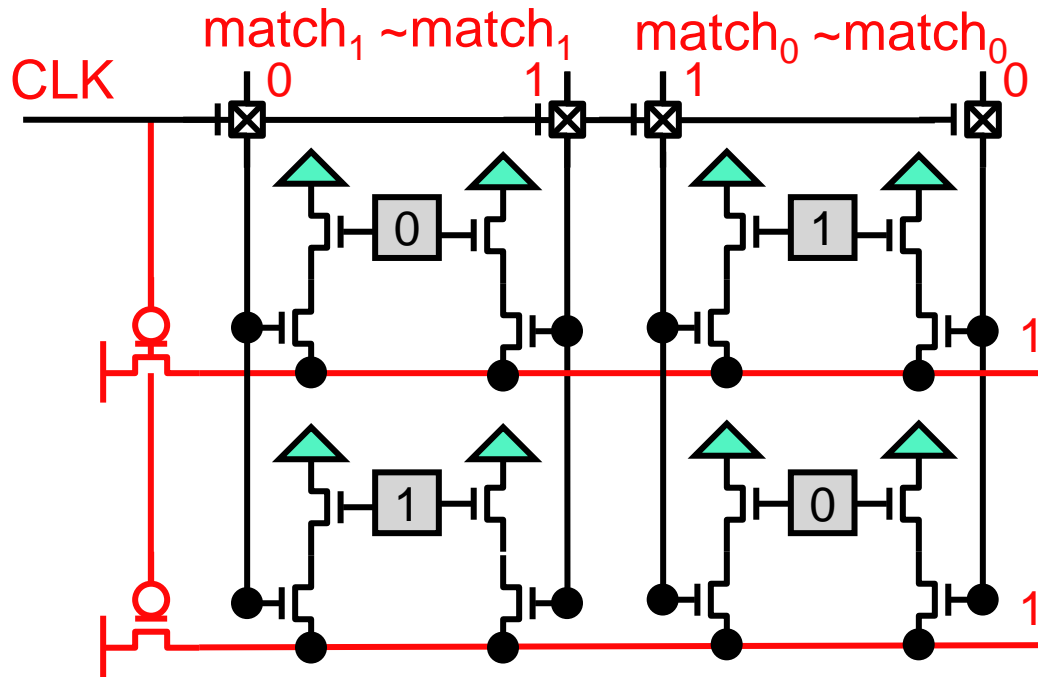


- Phase I: $clk=0$
 - Pre-charge wordlines

CAM Circuit In Action: Phase II

 

 - Phase II: $clk=1$
 - Enable matchlines
 - Note: bits flipped
 - Non-matching bit discharges wordline
 - ANDs matches
 - NORs non-matches
- Similar technique for doing a fast OR for hit detection




CAM Upshot

- CAMs: effective but expensive
 - Matchlines are very expensive (for nasty EE reasons)
 - Used but only for 16 or 32 way (max) associativity
 - Not for 1024-way associativity

Bonus


Multi-Ported Cache-Style SRAM Power

- Same four components for power
 - Decoder: $\propto \log_2 M$
 - Wordlines: $\propto 2NLP$
 - Huge Capacitance(C) per wordline (drives 2N gates)
 - + But only one ever high at any time (overall consumption low)
 - Bitlines: $\propto MLP$
 - C lower than wordlines, but large
 - + $V_{\text{swing}} \ll V_{\text{DD}}$ ($C * V_{\text{swing}}^2 * f$)
 - Muxes + **sense-amps**: constant
 - 32KB SRAM: sense-amps are 60–70%
- How does power scale?

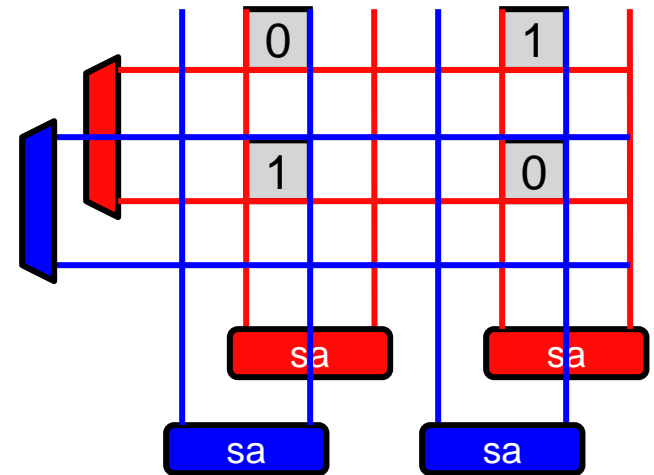

A Banked Cache

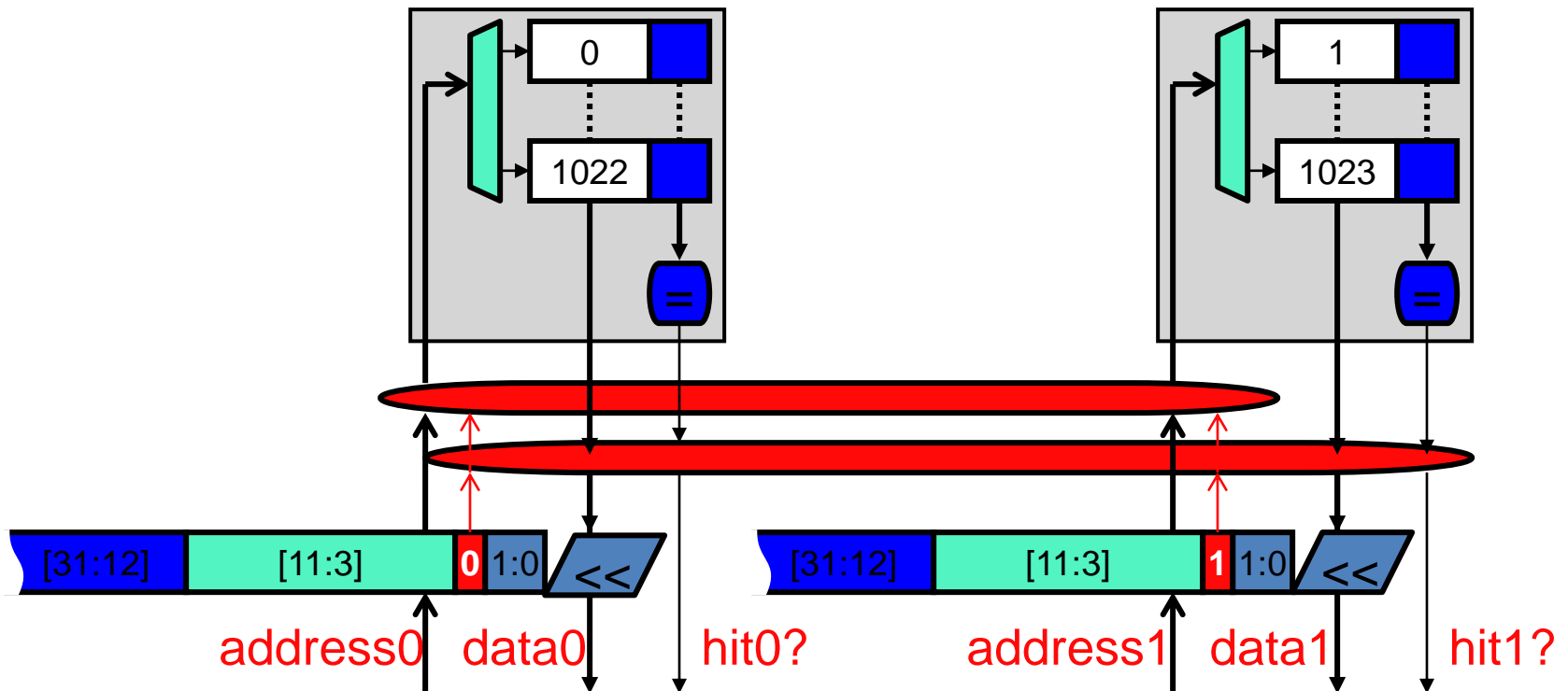- **Banking** a cache
 - Simple: bank SRAMs
 - Which address bits determine bank? LSB of index
 - **Bank network** assigns accesses to banks, resolves conflicts
 - Adds some latency too




SRAM Summary

- Large storage arrays are not implemented “digitally”
- SRAM implementation exploits analog transistor properties
 - Inverter pair bits much smaller than latch/flip-flop bits
 - Wordline/bitline arrangement gives simple “grid-like” routing
 - Basic understanding of read, write, read/write ports
 - Wordlines select words
 - Overwhelm inverter-pair to write
 - Drain pre-charged line or swing voltage to read
 - Latency proportional to $\sqrt{\#bits} * \#ports$


Aside: Physical Cache Layout I

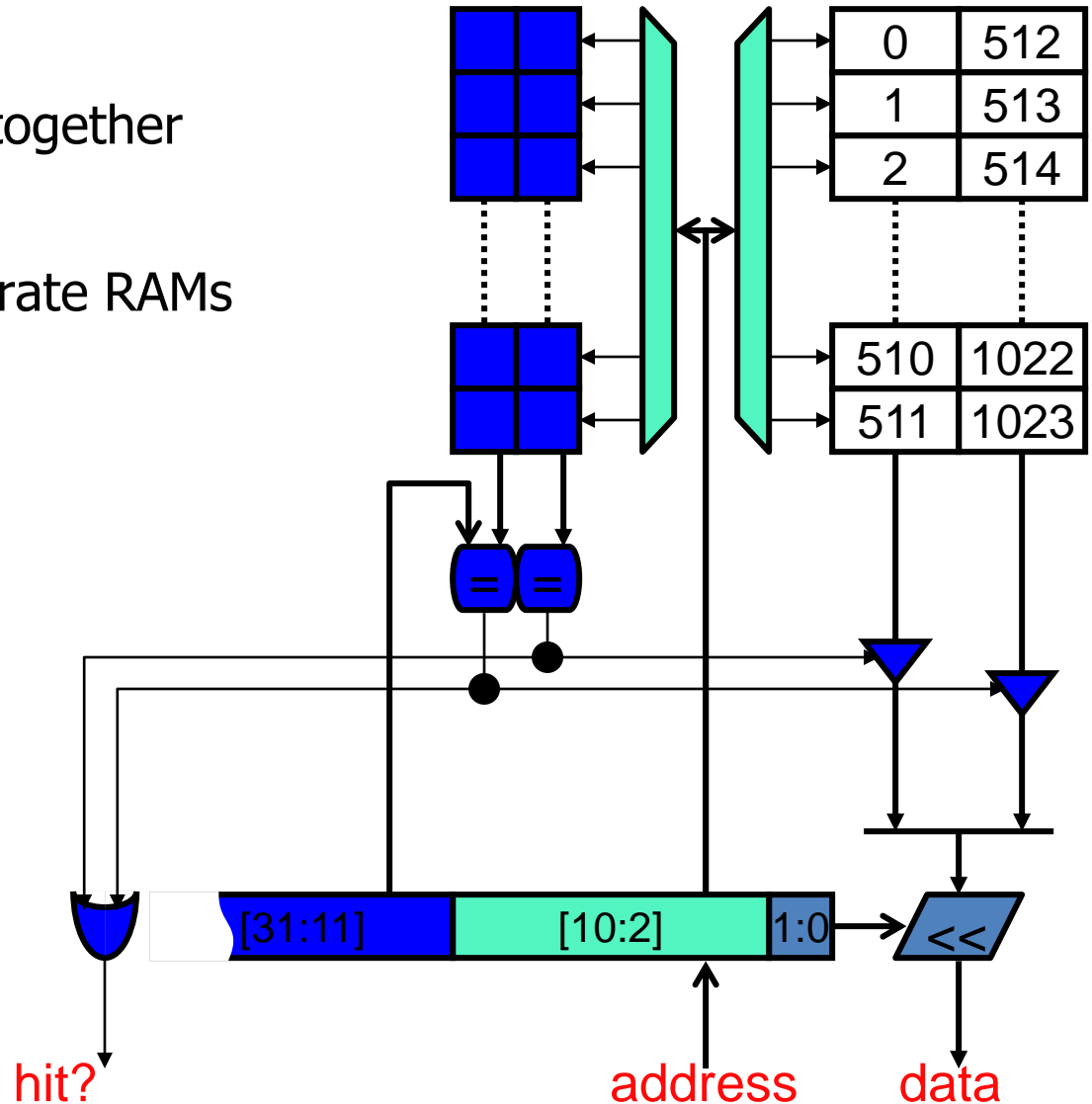- Logical layout
 - Data and tags mixed together
- Physical layout
 - Data and tags in separate RAMs





Physical Cache Layout II

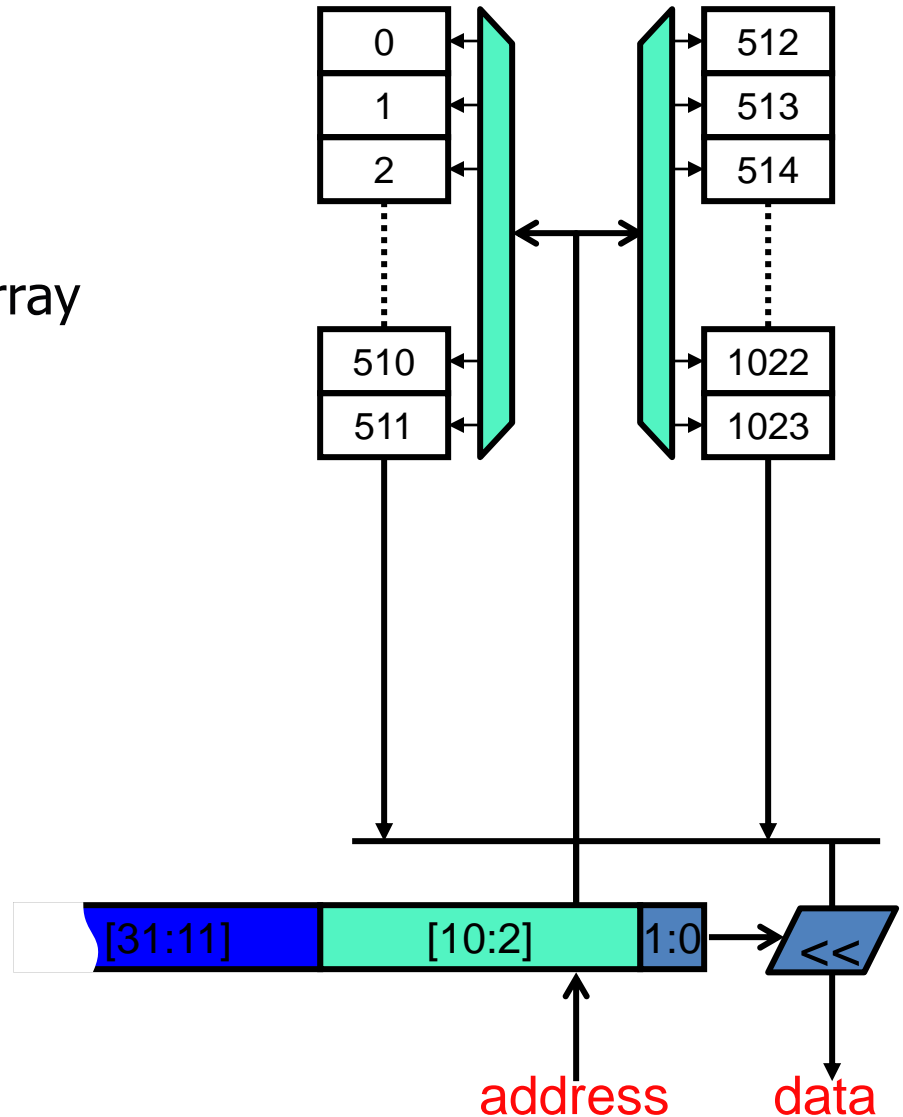- Logical layout
 - Data array is monolithic
- Physical layout
 - Each data "way" in separate array





Physical Cache Layout III

  - Logical layout
 - Data blocks are contiguous
- Physical layout
 - Only if full block needed on read
 - E.g., I\$ (read consecutive words)
 - E.g., L2 (read block to fill D\$,I\$)
 - For D\$ (access size is 1 word)...
 - Words in same data blocks are bit-interleaved
 - Word₀.bit₀ adjacent to word₁.bit₀




Physical Cache Layout IV

  - Logical layout
 - Arrays are vertically contiguous
- Physical layout
 - Vertical partitioning to minimize wire lengths
 - **H-tree**: horizontal/vertical partitioning layout
 - Applied recursively
 - Each node looks like an H




Physical Cache Layout

 - Arrays and h-trees make caches easy to spot in μ graphs



Full-Associativity

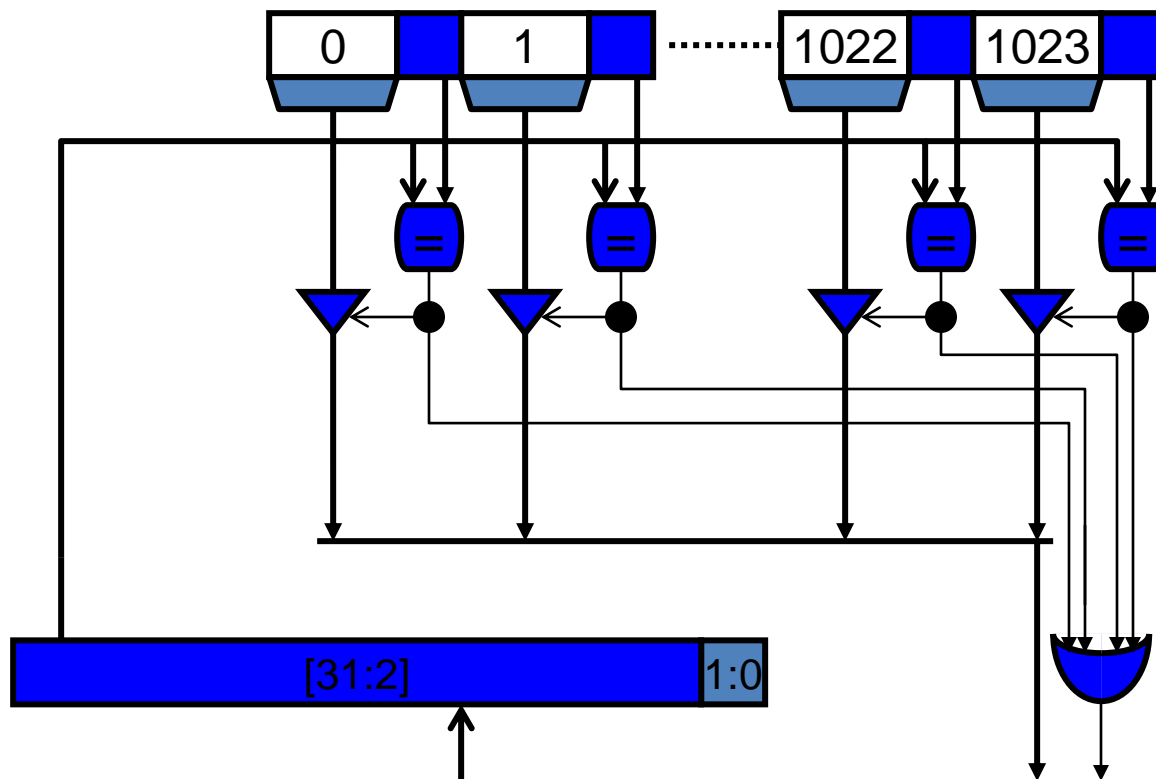

- How to implement full (or at least high) associativity?
 - 1K tag matches? unavoidable, but at least tags are small
 - 1K data reads? Terribly inefficient