




Introduction to Computer Engineering

CS/ECE 252, Spring 2013

Prof. Guri Sohi

**Computer Sciences Department
University of Wisconsin – Madison**

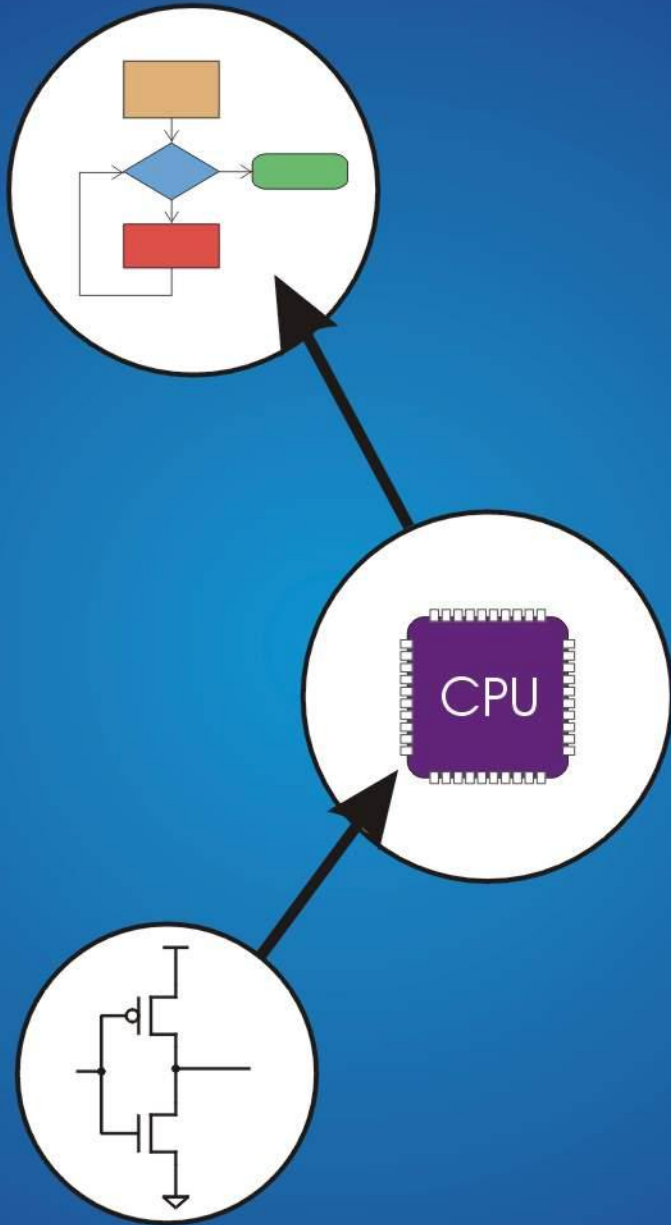

Chapter 3

Digital Logic Structures

Slides based on set prepared by
Gregory T. Byrd, North Carolina State University

Transistor: Building Block of Computers

Microprocessors contain millions of transistors

- Intel Pentium II: **7 million**
- Compaq Alpha 21264: **15 million**
- Intel Pentium III: **28 million**

Logically, each transistor acts as a switch

Combined to implement logic functions

- **AND, OR, NOT**


Combined to build higher-level structures

- **Adder, multiplexer, decoder, register, ...**

Combined to build processor

- **LC-3**

Simple Switch Circuit

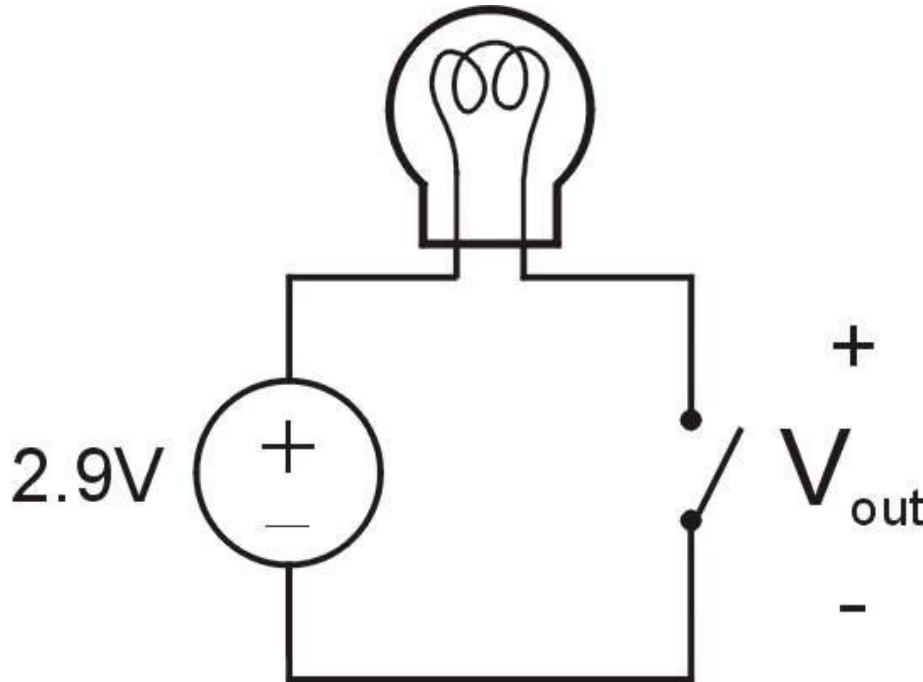

Switch **open**:

- No current through circuit
- Light is **off**
- V_{out} is **+2.9V**

Switch **closed**:

- Short circuit across switch
- Current flows
- Light is **on**
- V_{out} is **0V**

Switch-based circuits can easily represent two states:
on/off, open/closed, voltage/no voltage.


N-type MOS Transistor

MOS = Metal Oxide Semiconductor

- two types: N-type and P-type

N-type

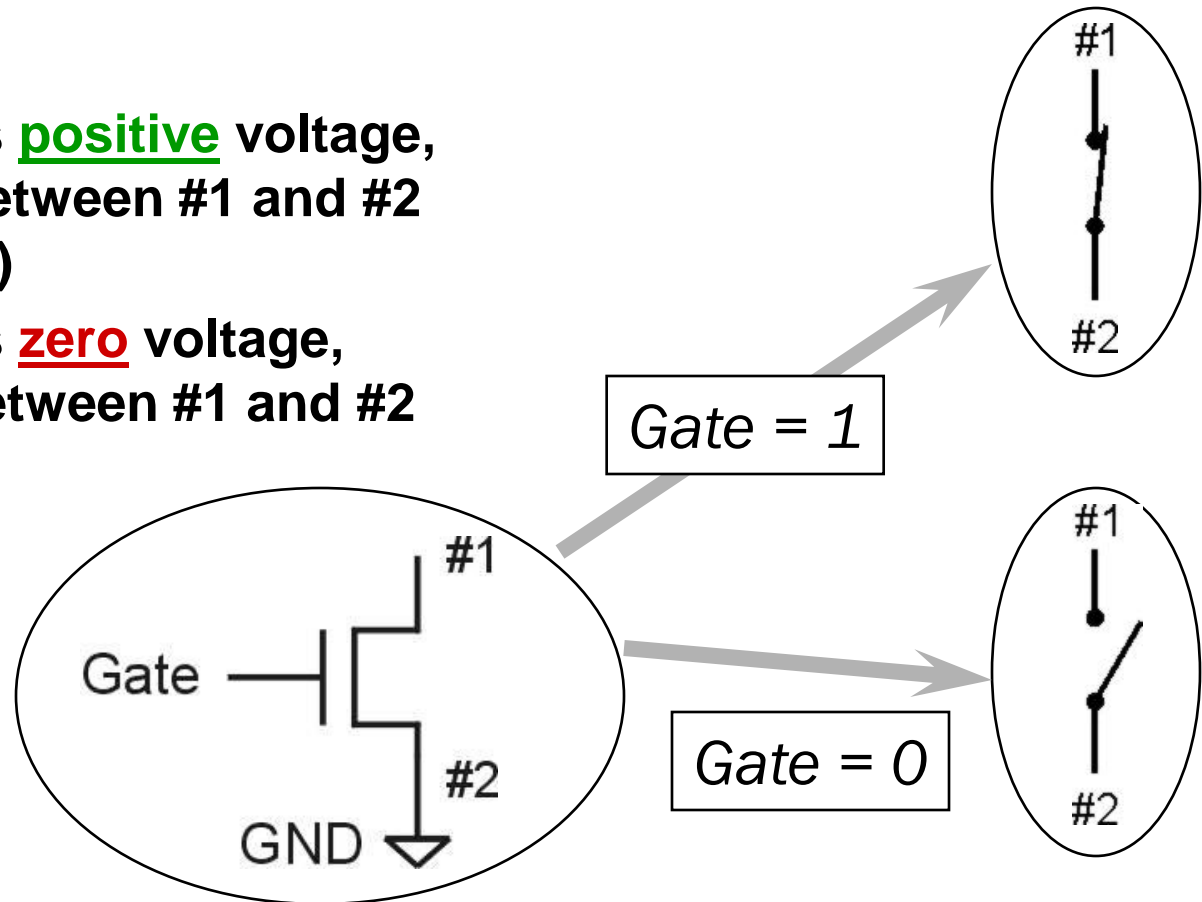- when Gate has positive voltage, short circuit between #1 and #2 (switch closed)
- when Gate has zero voltage, open circuit between #1 and #2 (switch open)




Terminal #2 must be connected to GND (0V).

P-type MOS Transistor

P-type is *complementary* to N-type

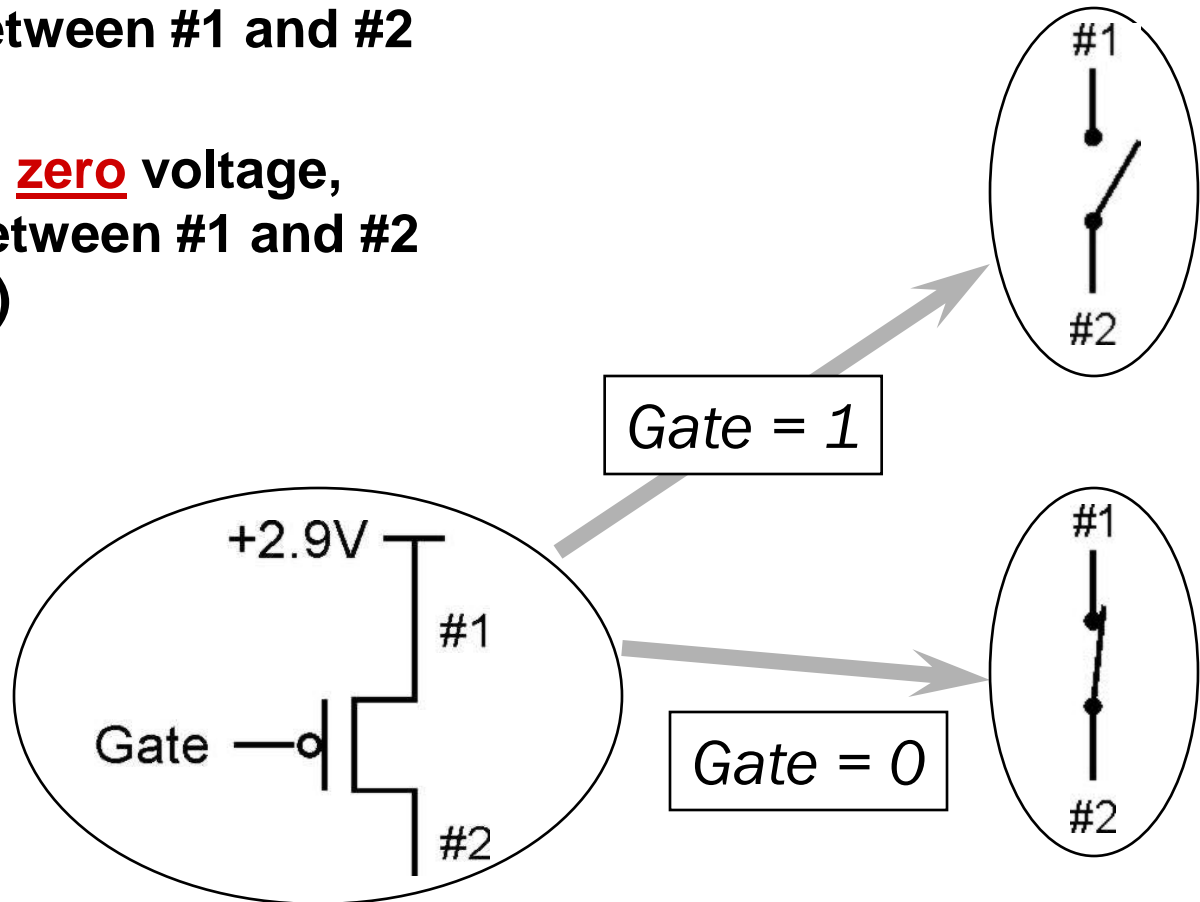- when Gate has positive voltage, open circuit between #1 and #2 (switch open)
- when Gate has zero voltage, short circuit between #1 and #2 (switch closed)



Terminal #1 must be connected to +2.9V.

Logic Gates

Use switch behavior of MOS transistors to implement logical functions: AND, OR, NOT.

Digital symbols:

- recall that we assign a range of analog voltages to each digital (logic) symbol



- assignment of voltage ranges depends on electrical properties of transistors being used
 - typical values for "1": +5V, +3.3V, +2.9V, +1.1V
 - for purposes of illustration, we'll use +2.9V

CMOS Circuit




Complementary MOS

Uses both **N-type** and **P-type** MOS transistors

- **P-type**
 - Attached to + voltage
 - Pulls output voltage UP when input is zero
- **N-type**
 - Attached to GND
 - Pulls output voltage DOWN when input is one

For all inputs, make sure that output is either connected to GND or to +, but not both!

Inverter (NOT Gate)

  
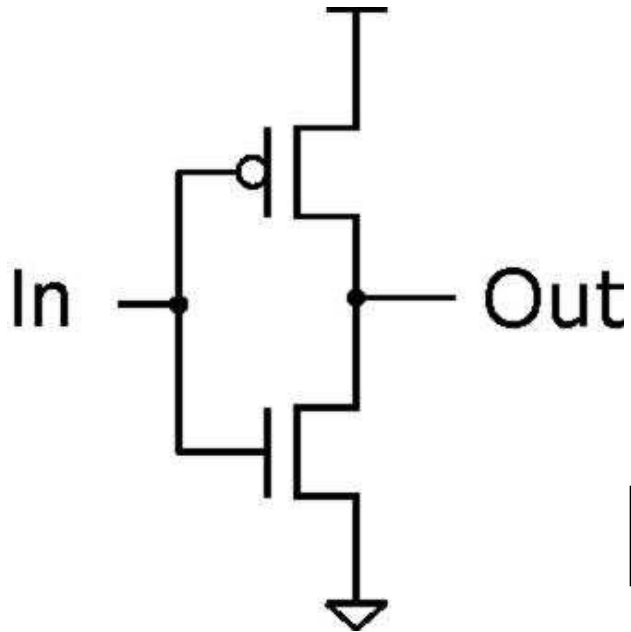


Truth table

In	Out
0 V	2.9 V
2.9 V	0 V

In	Out
0	1
1	0


NOR Gate

  

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Note: Serial structure on top, parallel on bottom.



OR Gate

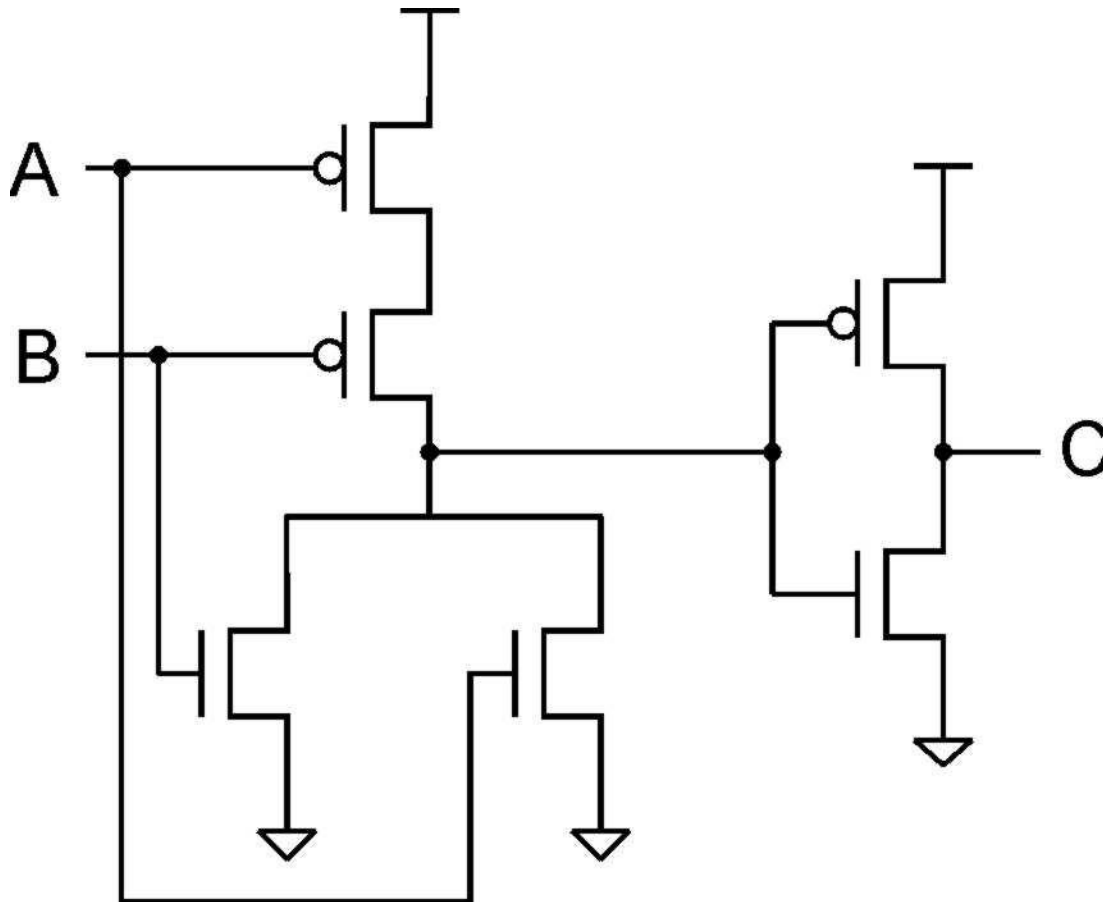

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Add inverter to NOR.


NAND Gate (AND-NOT)

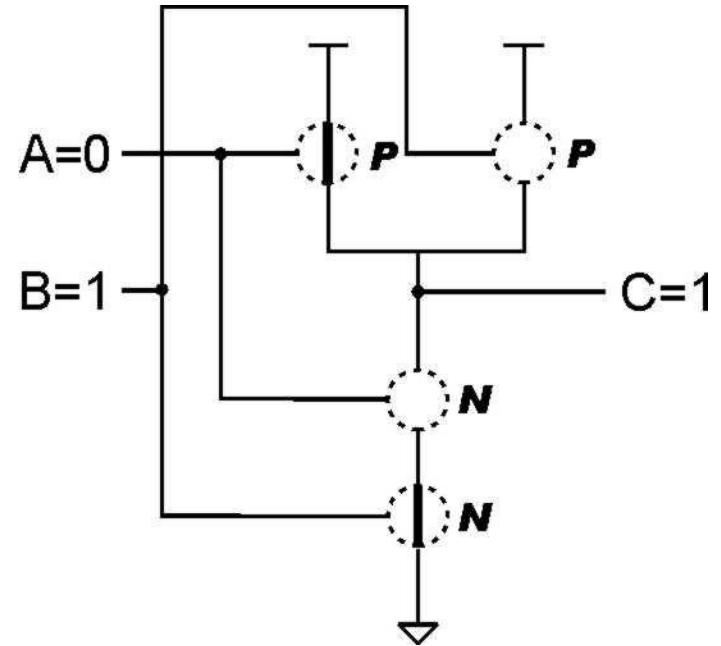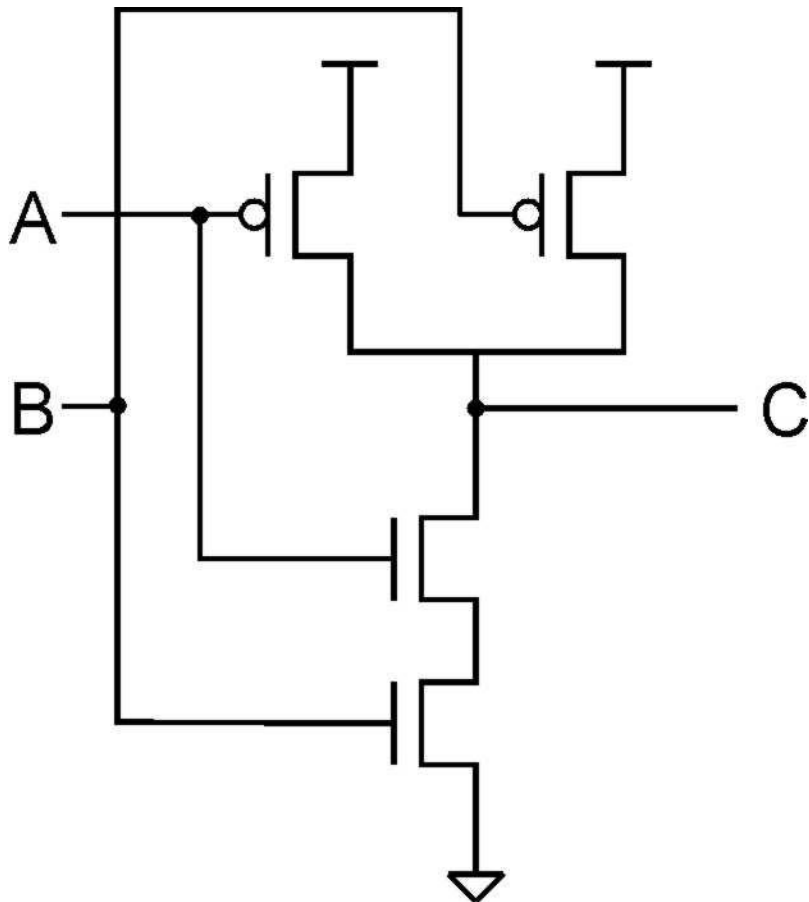

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Note: Parallel structure on top, serial on bottom.


AND Gate

 


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Add inverter to NAND.


Basic Logic Gates

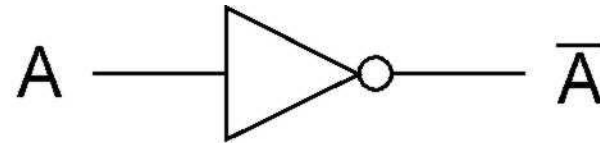


NOT

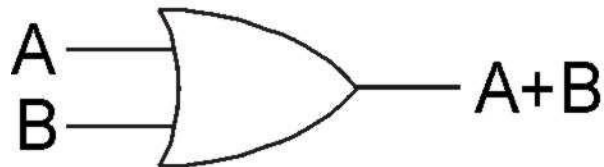


OR

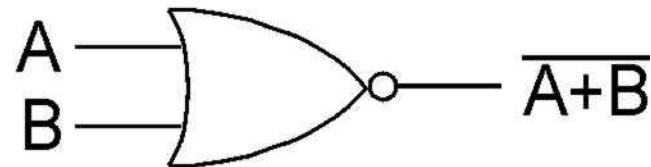

NOR

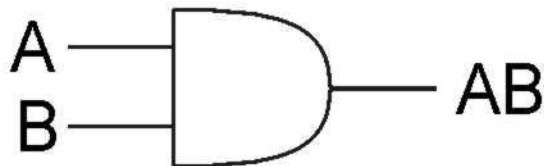

AND

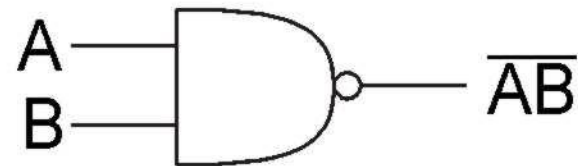


NAND

More than 2 Inputs?

AND/OR can take any number of inputs.

- **AND = 1 if all inputs are 1.**
- **OR = 1 if any input is 1.**
- **Similar for NAND/NOR.**

 Can implement with multiple two-input gates, or with single CMOS circuit.




Practice

Implement a 3-input NOR gate with CMOS.

Logical Completeness

Can implement ANY truth table with AND, OR, NOT.

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

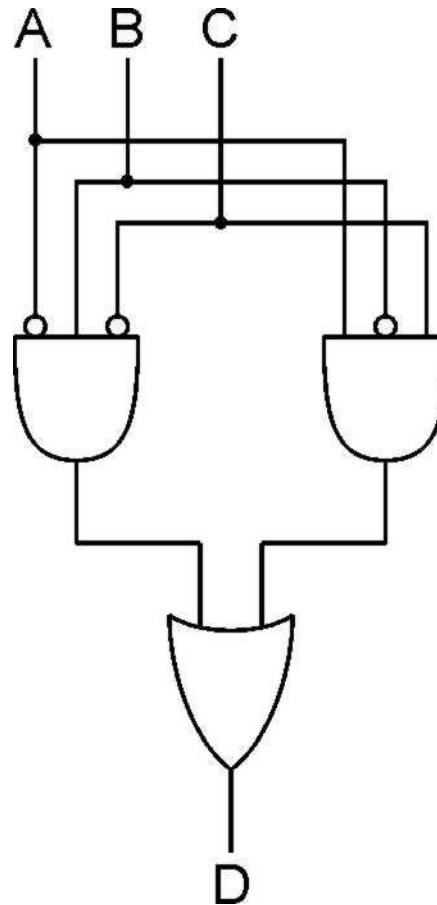

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

Practice


Implement the following truth table.

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

DeMorgan's Law

Converting AND to OR (with some help from NOT)

Consider the following gate:

 

A	B	\overline{A}	\overline{B}	$\overline{A \cdot B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as $A+B$!

*To convert AND to OR
(or vice versa),
invert inputs and output.*

Summary

MOS transistors are used as switches to implement logic functions.

- **N-type: connect to GND, turn on (with 1) to pull down to 0**
- **P-type: connect to +2.9V, turn on (with 0) to pull up to 1**

Basic gates: NOT, NOR, NAND

- **Logic functions are usually expressed with AND, OR, and NOT**

Properties of logic gates

- **Completeness**
 - **can implement any truth table with AND, OR, NOT**
- **DeMorgan's Law**
 - **convert AND to OR by inverting inputs and output**

Building Functions from Logic Gates

We've already seen how to implement truth tables using AND, OR, and NOT -- an example of *combinational logic*.

Combinational Logic Circuit

- **output depends only on the current inputs**
- **stateless**

Sequential Logic Circuit


- **output depends on the sequence of inputs (past and present)**
- **stores information (state) from past inputs**

We'll first look at some useful combinational circuits, then show how to use sequential circuits to store information.

Decoder

n inputs, 2^n outputs


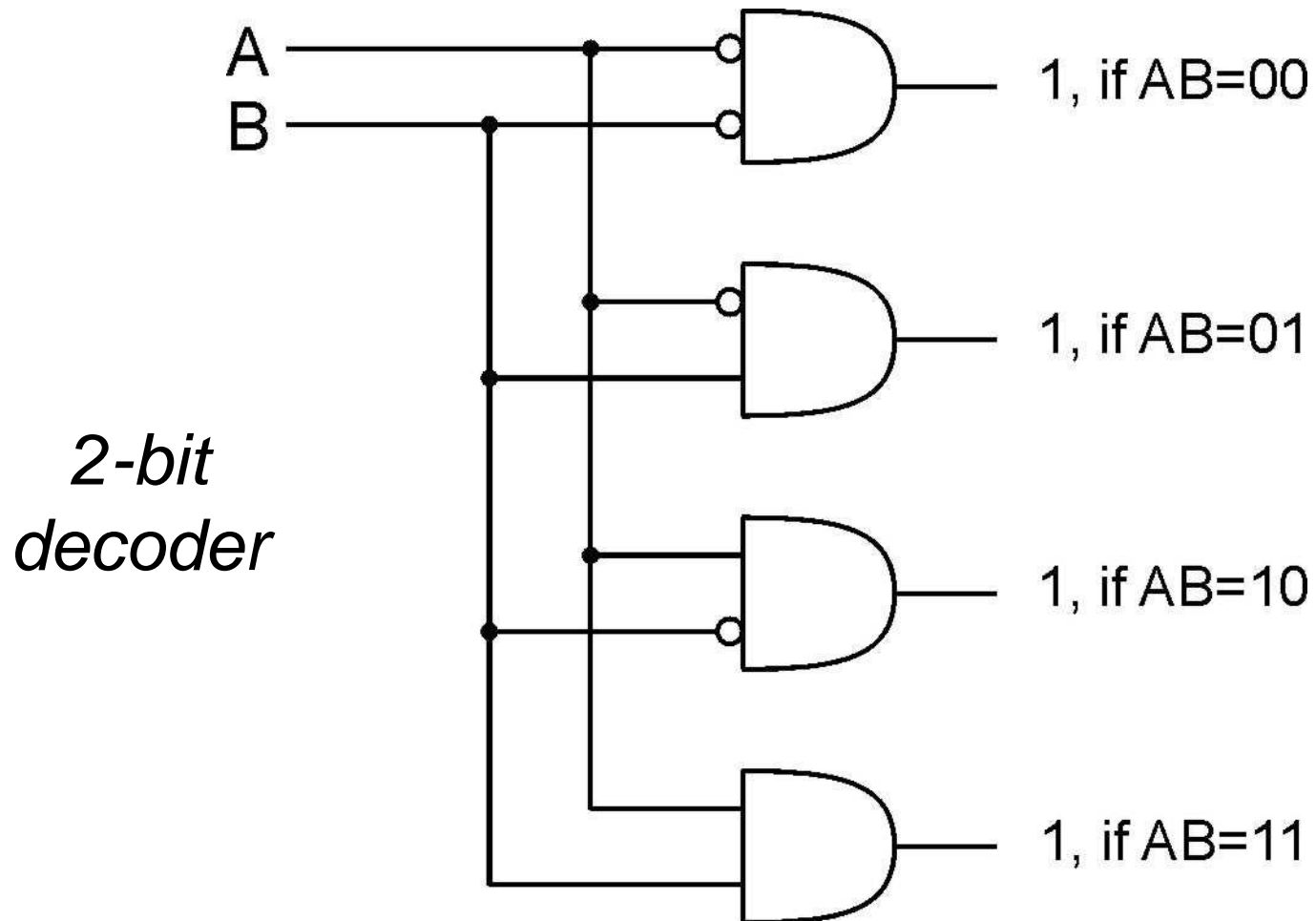
- exactly one output is 1 for each possible input pattern



Multiplexer (MUX)

n -bit selector and 2^n inputs, one output

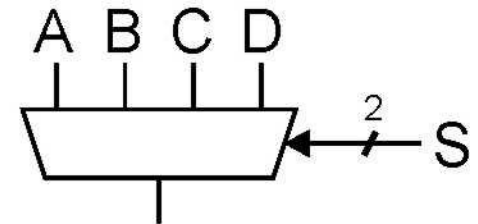 
- output equals one of the inputs, depending on selector



4-to-1 MUX


Full Adder

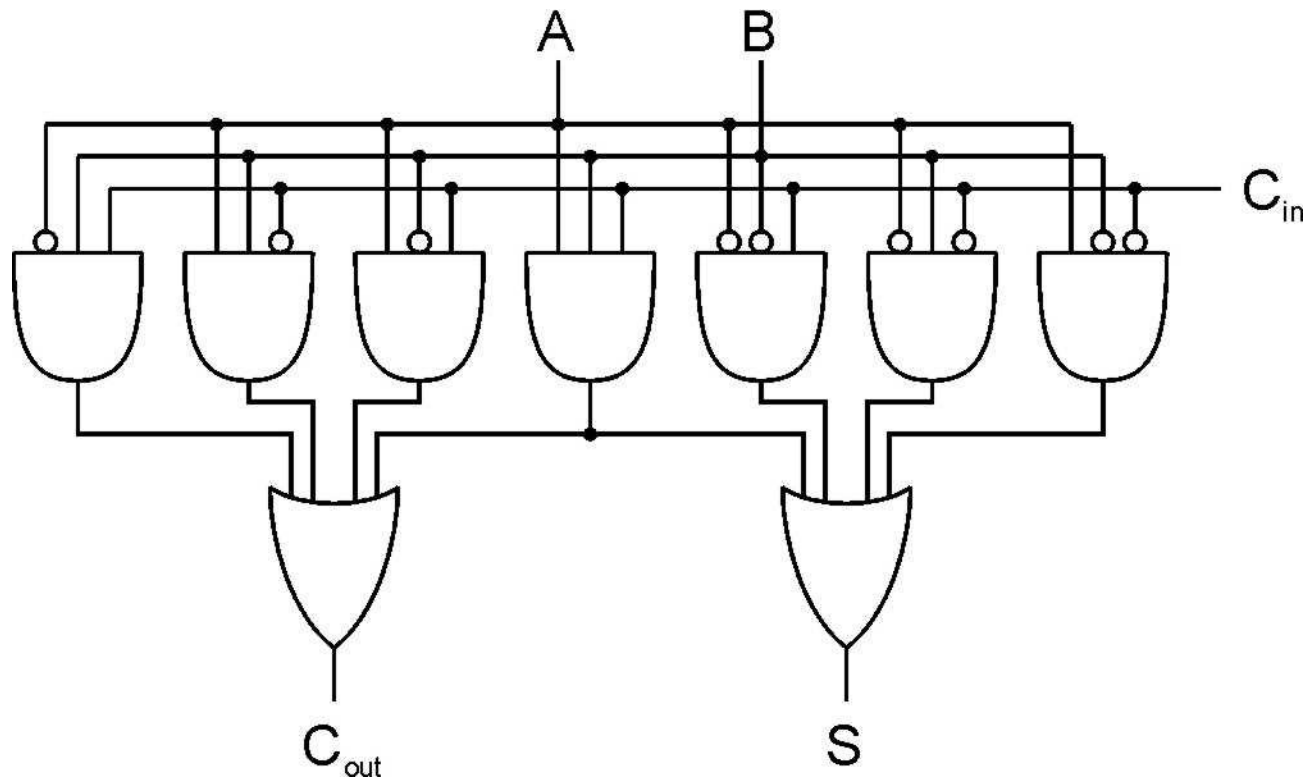Add two bits and carry-in,
produce one-bit sum and carry-out.



A	B	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Four-bit Adder

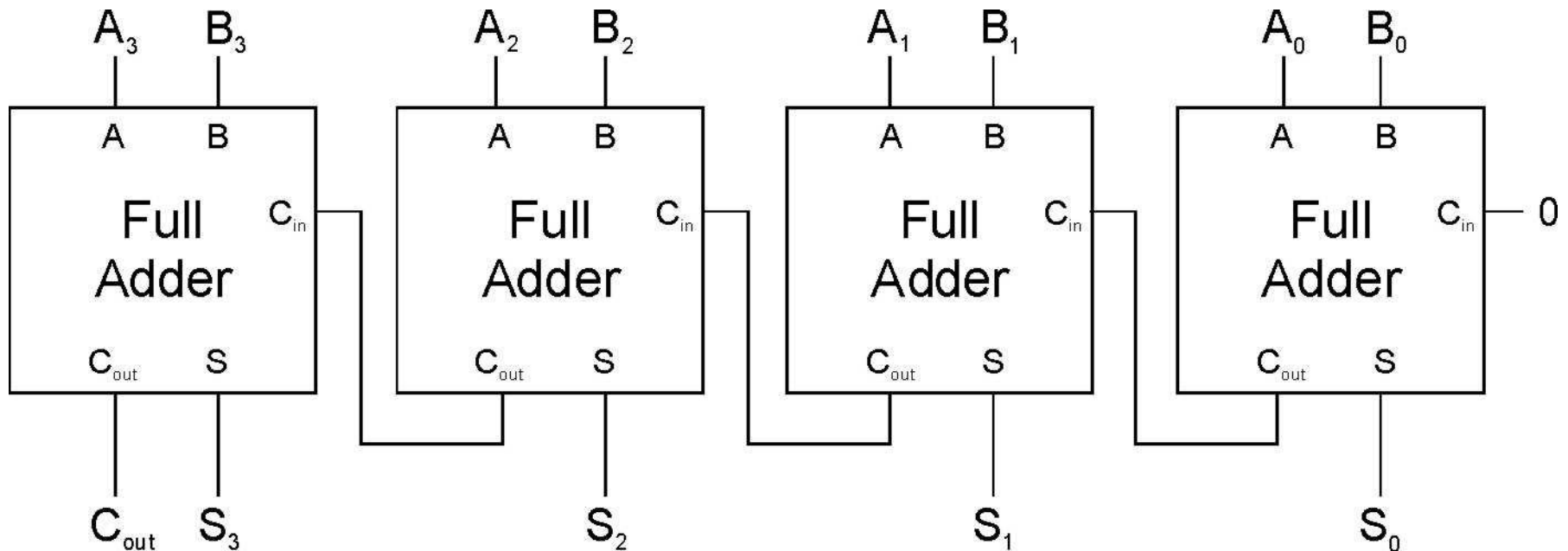

Combinational vs. Sequential

Combinational Circuit

- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs



Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
- *example:* ticket counter
 - advances when you push the button
 - output depends on previous state
- useful for building “memory” elements and “state machines”

R-S Latch: Simple Storage Element

R is used to “reset” or “clear” the element – set it to zero.

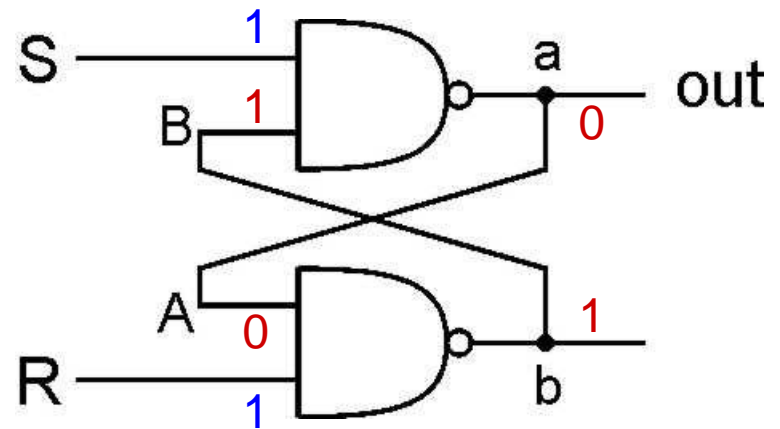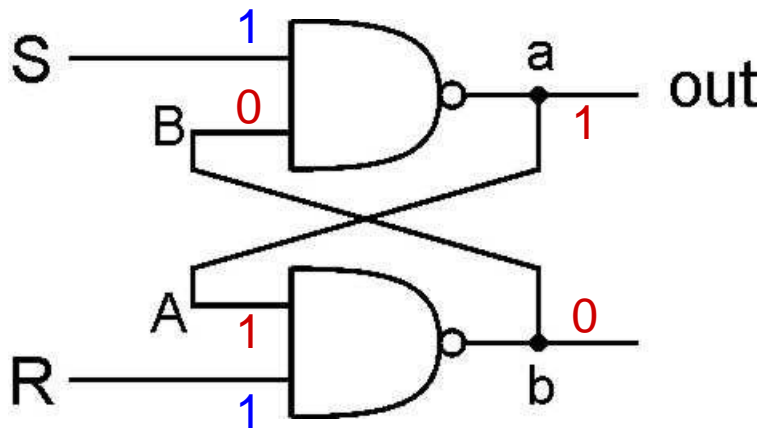S is used to “set” the element – set it to one.




If both R and S are one, out could be either zero or one.


- “quiescent” state -- holds its previous value
- note: if a is 1, b is 0, and vice versa

Clearing the R-S latch

 Suppose we start with output = 1, then change R to zero.




Output changes to zero.

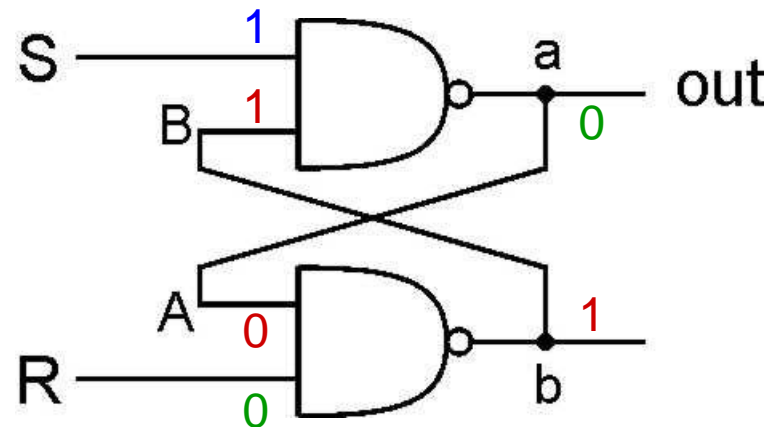


Then set R=1 to “store” value in quiescent state.

Setting the R-S Latch

 Suppose we start with output = 0, then change S to zero.



Output changes to one.

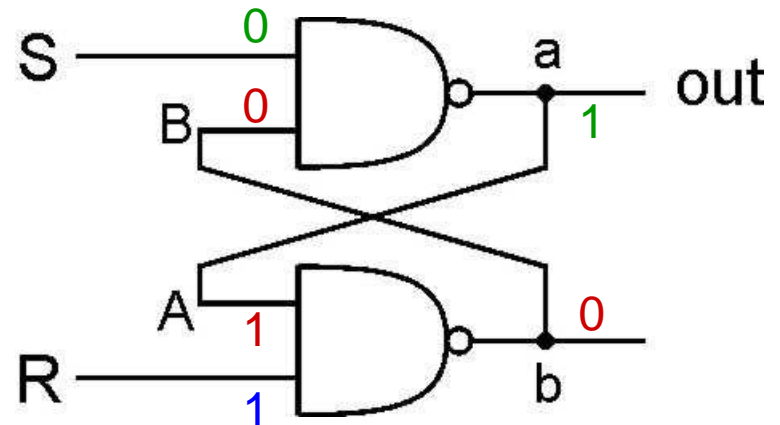

Then set S=1 to “store” value in quiescent state.

R-S Latch Summary

$R = S = 1$

- **hold current value in latch**

$S = 0, R = 1$

- **set value to 1**

$R = 0, S = 1$

- **set value to 0**


$R = S = 0$

- **both outputs equal one**
- **final state determined by electrical properties of gates**
- *Don't do it!*

Gated D-Latch

Two inputs: D (data) and WE (write enable)

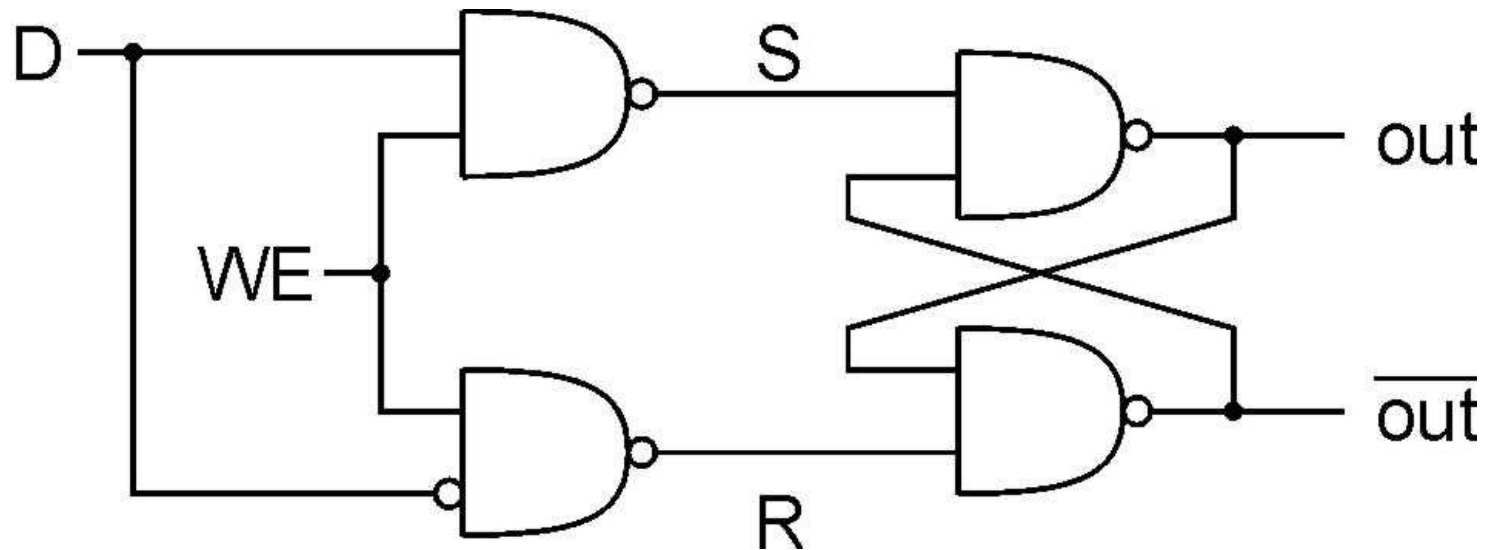
- when **WE = 1**, latch is set to **value of D**
 - $S = \text{NOT}(D)$, $R = D$
- when **WE = 0**, latch holds **previous value**
 - $S = R = 1$



Register

A register stores a multi-bit value.

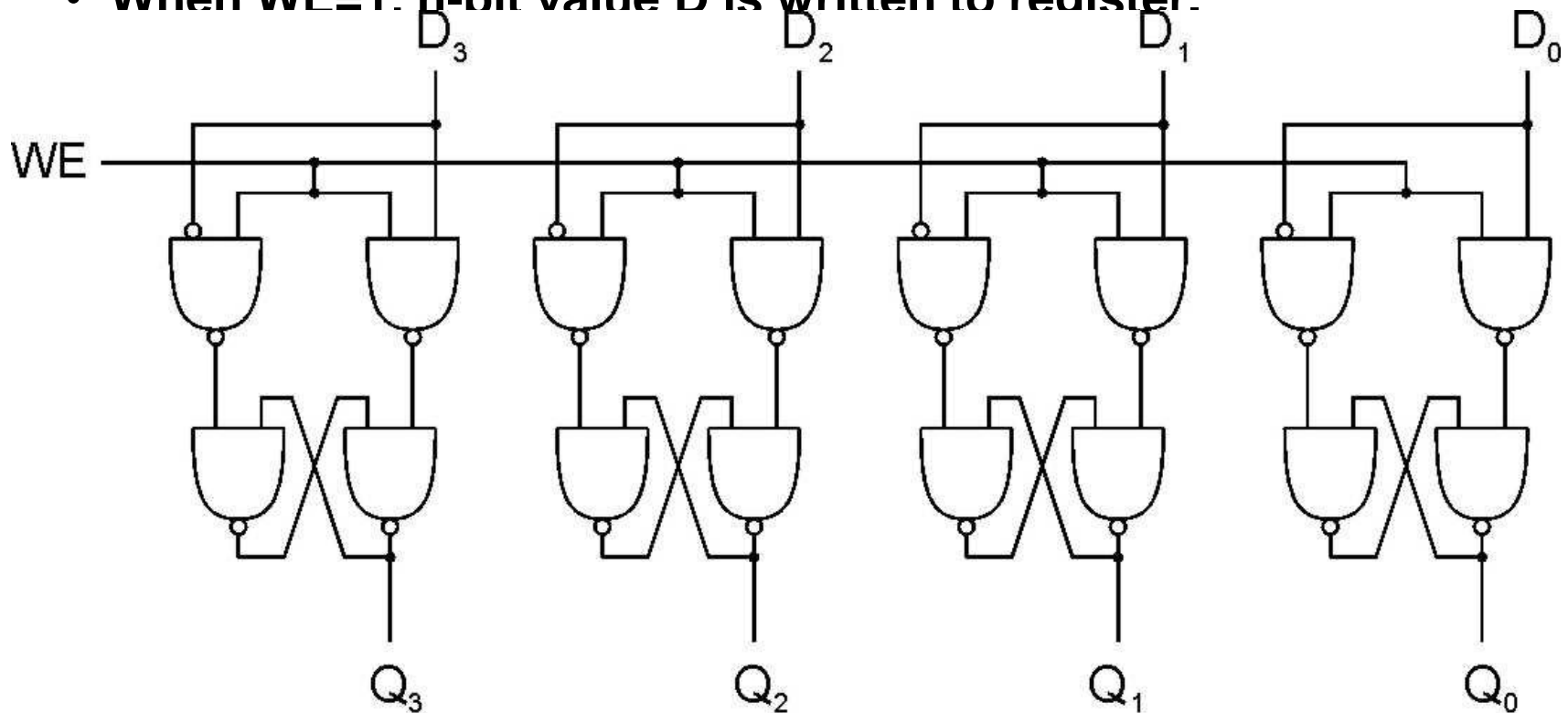- We use a collection of D-latches, all controlled by a common WE.
- When $WE=1$, n-bit value D is written to register.




Representing Multi-bit Values

Number bits from right (0) to left (n-1)

- just a convention -- could be left to right, but must be consistent

Use brackets to denote range:

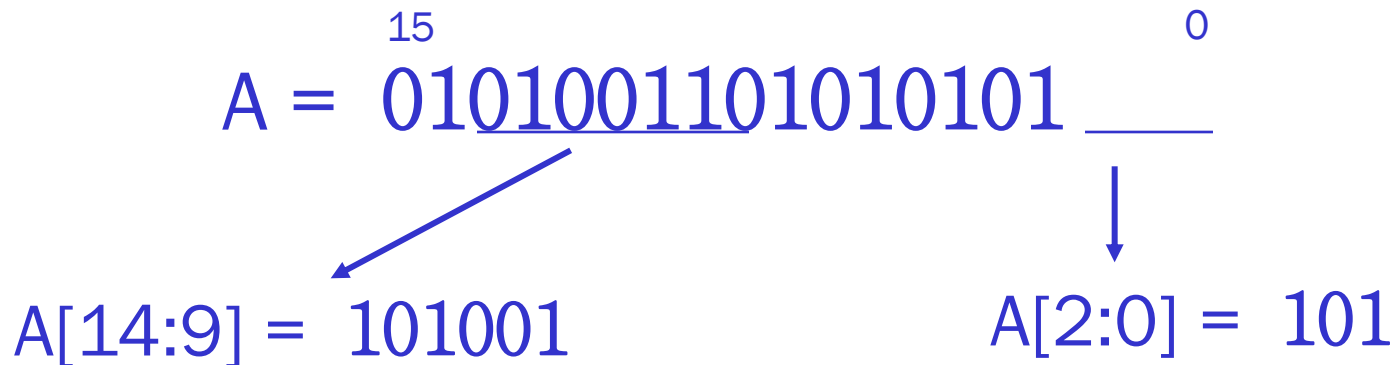$D[l:r]$ denotes bit l to bit r , from *left to right*



May also see $A\langle 14:9 \rangle$,
especially in hardware block diagrams.


Memory

Now that we know how to store bits,
we can build a memory – a logical $k \times m$ array of
stored bits.


Address Space:
number of locations
(usually a power of 2)

$k = 2^n$
locations

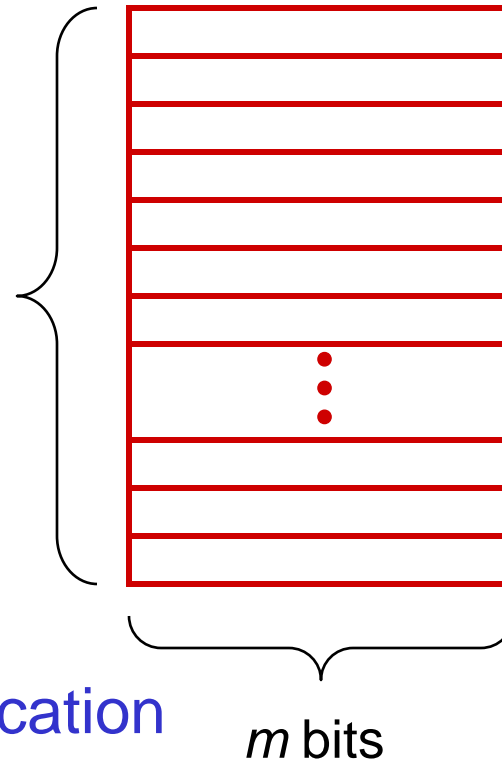Addressability:
number of bits per location
(e.g., byte-addressable)



$2^2 \times 3$ Memory

 

More Memory Details

This is a not the way actual memory is implemented.

- fewer transistors, much more dense, relies on electrical properties

But the logical structure is very similar.

- address decoder
- word select line
- word write enable

Two basic kinds of RAM (Random Access Memory)

Static RAM (SRAM)

- fast, maintains data without power

Dynamic RAM (DRAM)


- slower but denser, bit storage must be periodically refreshed

Also, non-volatile memories: ROM, PROM, flash, ...

State Machine



Another type of sequential circuit

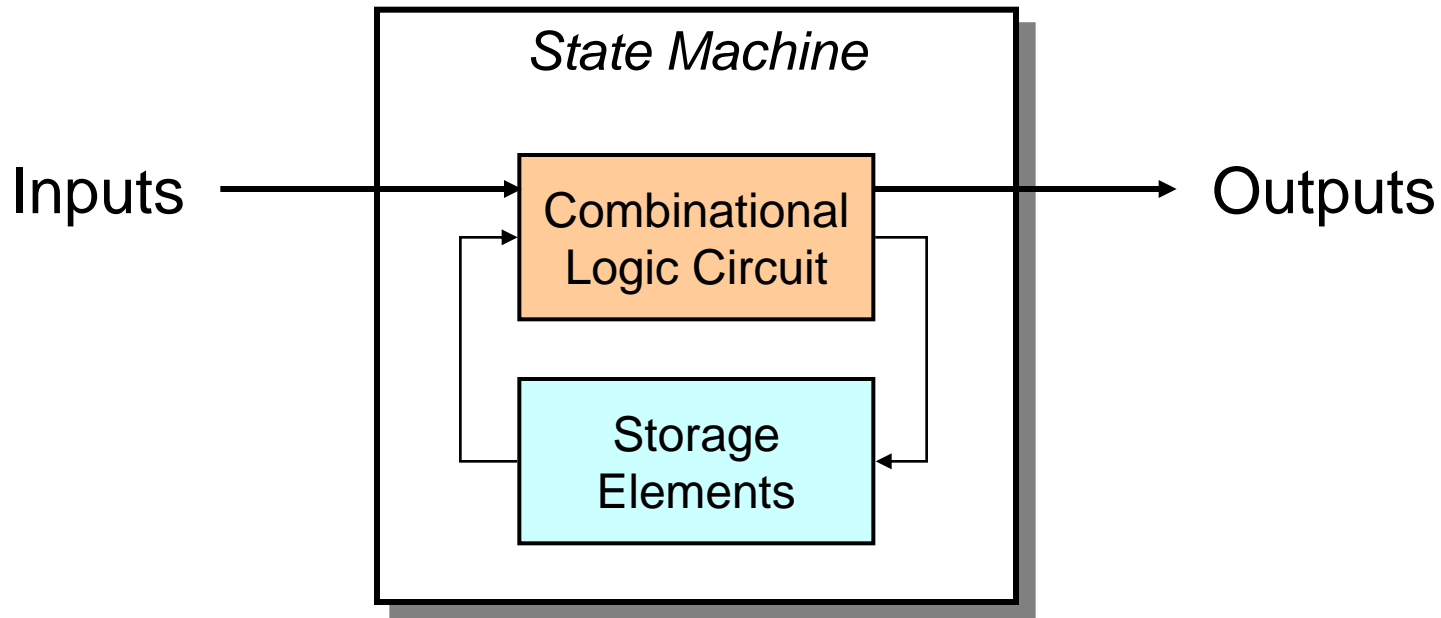- Combines combinational logic with storage
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**



Combinational vs. Sequential

Two types of “combination” locks

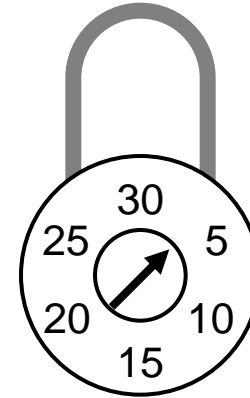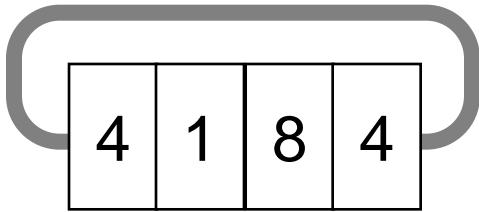

Combinational

Success depends only on the **values**, not the order in which they are set.

Sequential

Success depends on the **sequence** of values (e.g, R-13, L-22, R-3).

State

The **state** of a system is a **snapshot** of **all the relevant elements** of the system at the moment the snapshot is taken.

Examples:

- The state of a basketball game can be represented by the scoreboard.
 - Number of points, time remaining, possession, etc.
- The state of a tic-tac-toe game can be represented by the placement of X's and O's on the board.


State of Sequential Lock

Our lock example has four different states, labelled A-D:

- A:** The lock is **not open**,
and no relevant operations have been performed.
- B:** The lock is **not open**,
and the user has completed the **R-13** operation.
- C:** The lock is **not open**,
and the user has completed **R-13**, followed by **L-22**.
- D:** The lock is **open**.

State Diagram

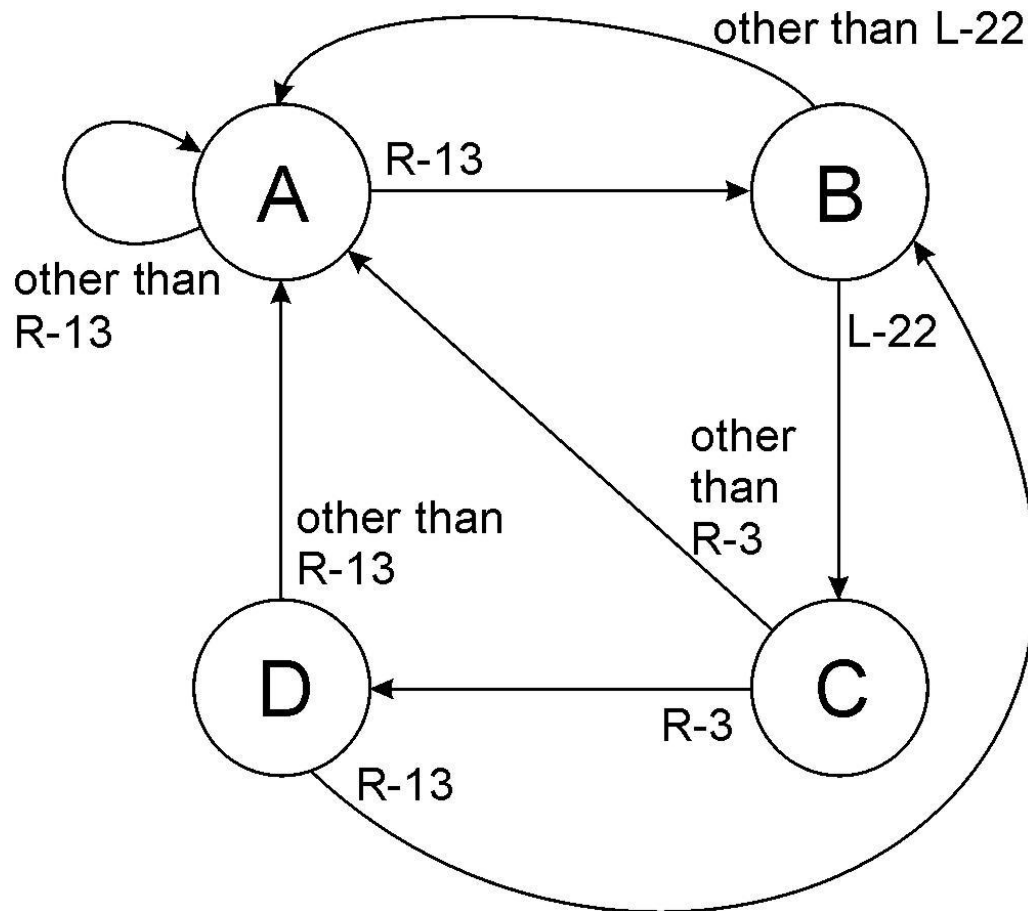Shows **states** and **actions** that cause a **transition** between states.



Finite State Machine

A description of a system with the following components:


- 1. A finite number of **states****
- 2. A finite number of external **inputs****
- 3. A finite number of external **outputs****
- 4. An explicit specification of all **state transitions****
- 5. An explicit specification of what causes each external **output value**.**

Often described by a state diagram.

- Inputs may cause state transitions.**
- Outputs are associated with each state (or with each transition).**

The Clock

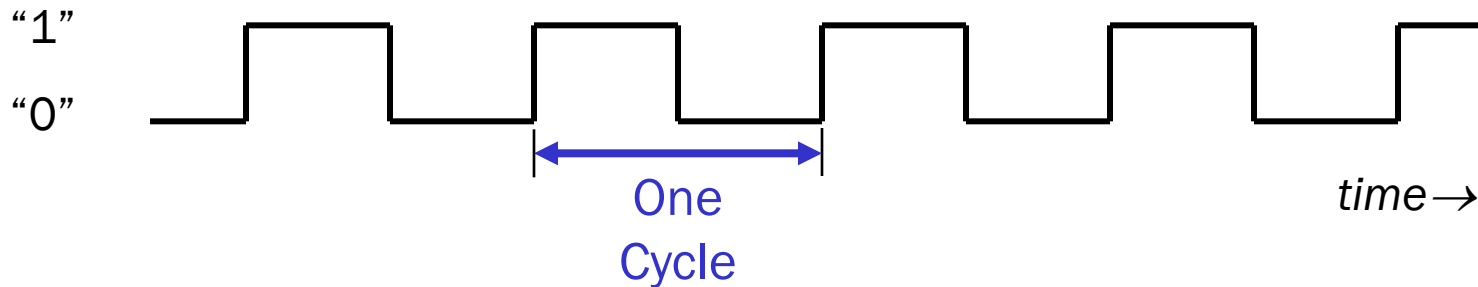Frequently, a **clock circuit** triggers transition from one state to the next.



At the beginning of each clock cycle, state machine makes a transition, based on the current state and the external inputs.

- Not always required. In lock example, the input itself triggers a transition.


Implementing a Finite State Machine

Combinational logic

- Determine outputs and next state.


Storage elements

- Maintain state representation.

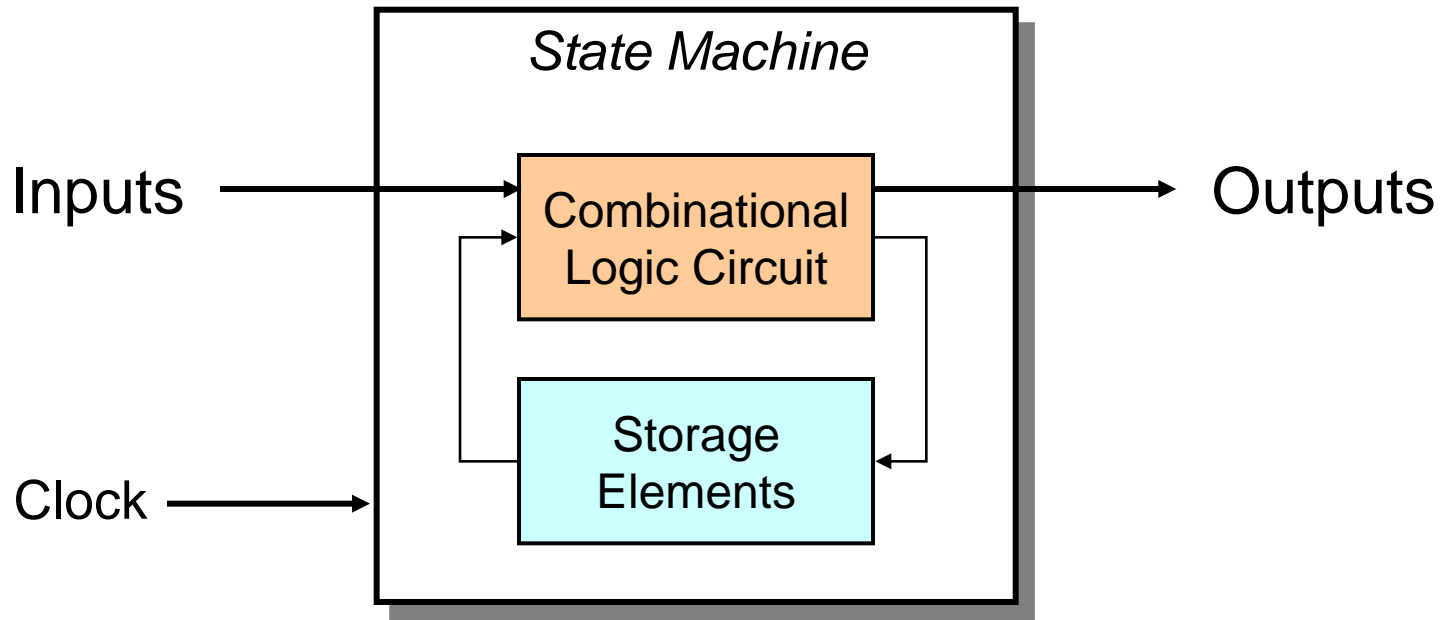

Storage: Master-Slave Flipflop

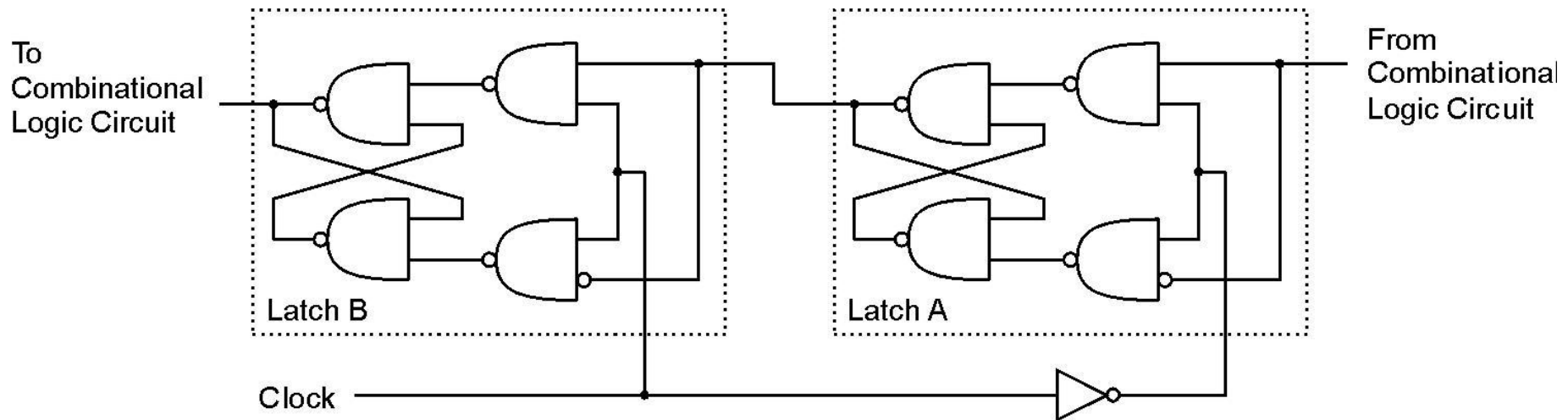A pair of gated D-latches,
to isolate *next* state from *current* state.



During 1st phase (clock=1), previously-computed state becomes *current* state and is sent to the logic circuit.

During 2nd phase (clock=0), *next* state, computed by logic circuit, is stored in Latch A.

Storage

Each master-slave flipflop stores one state bit.

The number of storage elements (flipflops) needed is determined by the number of states (and the representation of each state).


Examples:

- **Sequential lock**
 - **Four states – two bits**
- **Basketball scoreboard**
 - **7 bits for each score, 5 bits for minutes, 6 bits for seconds, 1 bit for possession arrow, 1 bit for half, ...**


Complete Example

A blinking traffic sign

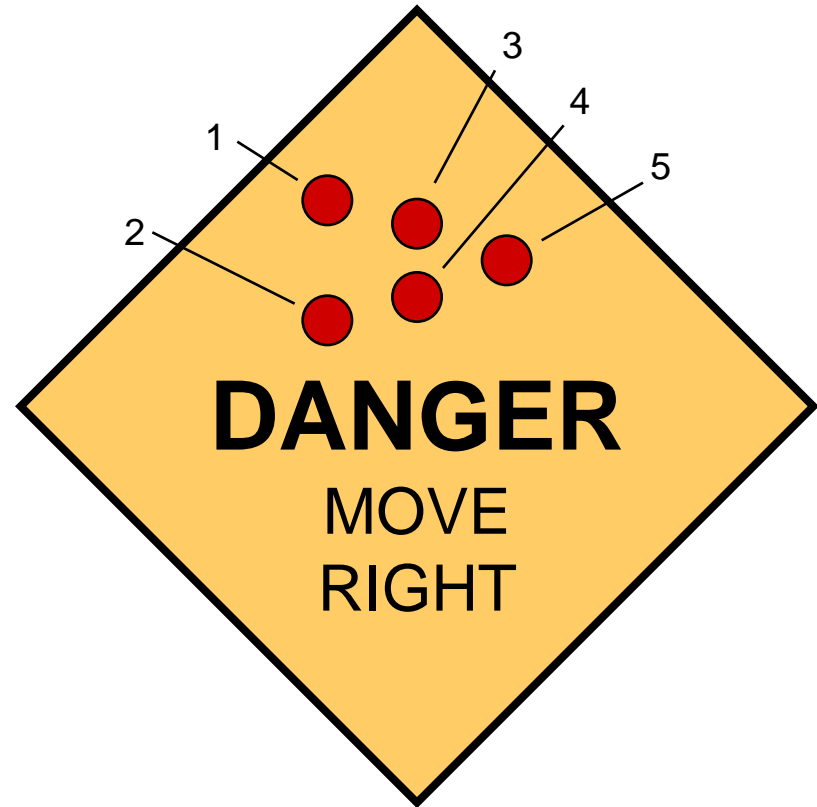- No lights on
- 1 & 2 on
- 1, 2, 3, & 4 on
- 1, 2, 3, 4, & 5 on
- (repeat as long as switch is turned on)



Traffic Sign State Diagram

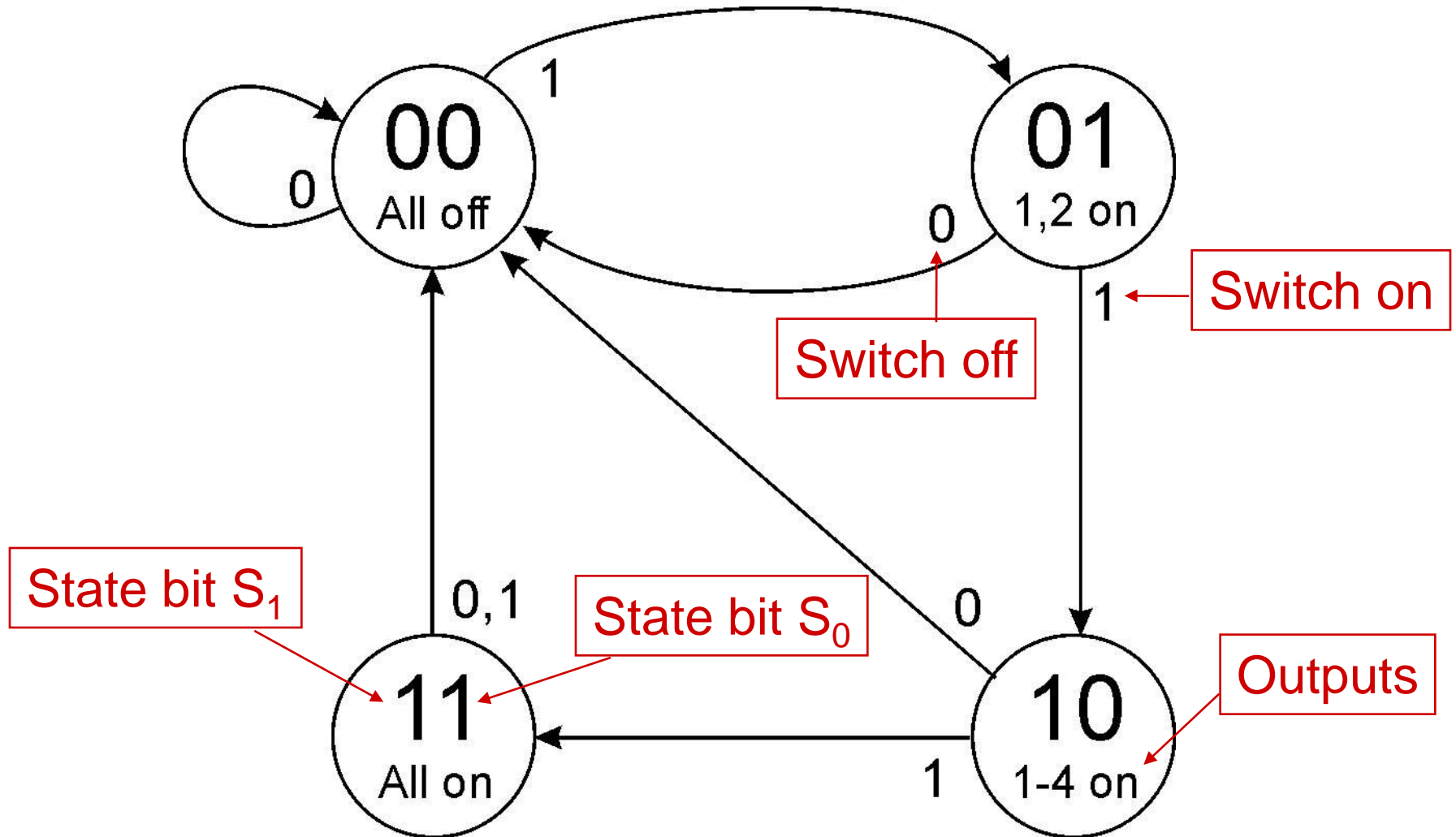

Transition on each clock cycle.

Traffic Sign Truth Tables

Outputs
(depend only on state: $S_1 S_0$)

S_1	S_0	Z	Y	X
0	0	0	0	0
0	1	1	0	0
1	0	1	1	0
1	1	1	1	1


Lights 1 and 2 → Z
 Lights 3 and 4 → Y
 Light 5 → X

Next State: $S_1' S_0'$
(depend on state and input)

In	S_1	S_0	S_1'	S_0'
0	X	X	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

Switch → In
 Whenever In=0, next state is 00.

Traffic Sign Logic

 

From Logic to Data Path

The data path of a computer is all the logic used to process information.

- See the data path of the LC-2 on next slide.

Combinational Logic

- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

LC-2/LC-3 Data Path

